

SEPT 1982

\$2.15* NZ \$2.50




ELECTRONICS
TODAY
INTERNATIONAL

WIN A
Microprofessor
Microcomputer

SPEECH SYNTHESISER

to build

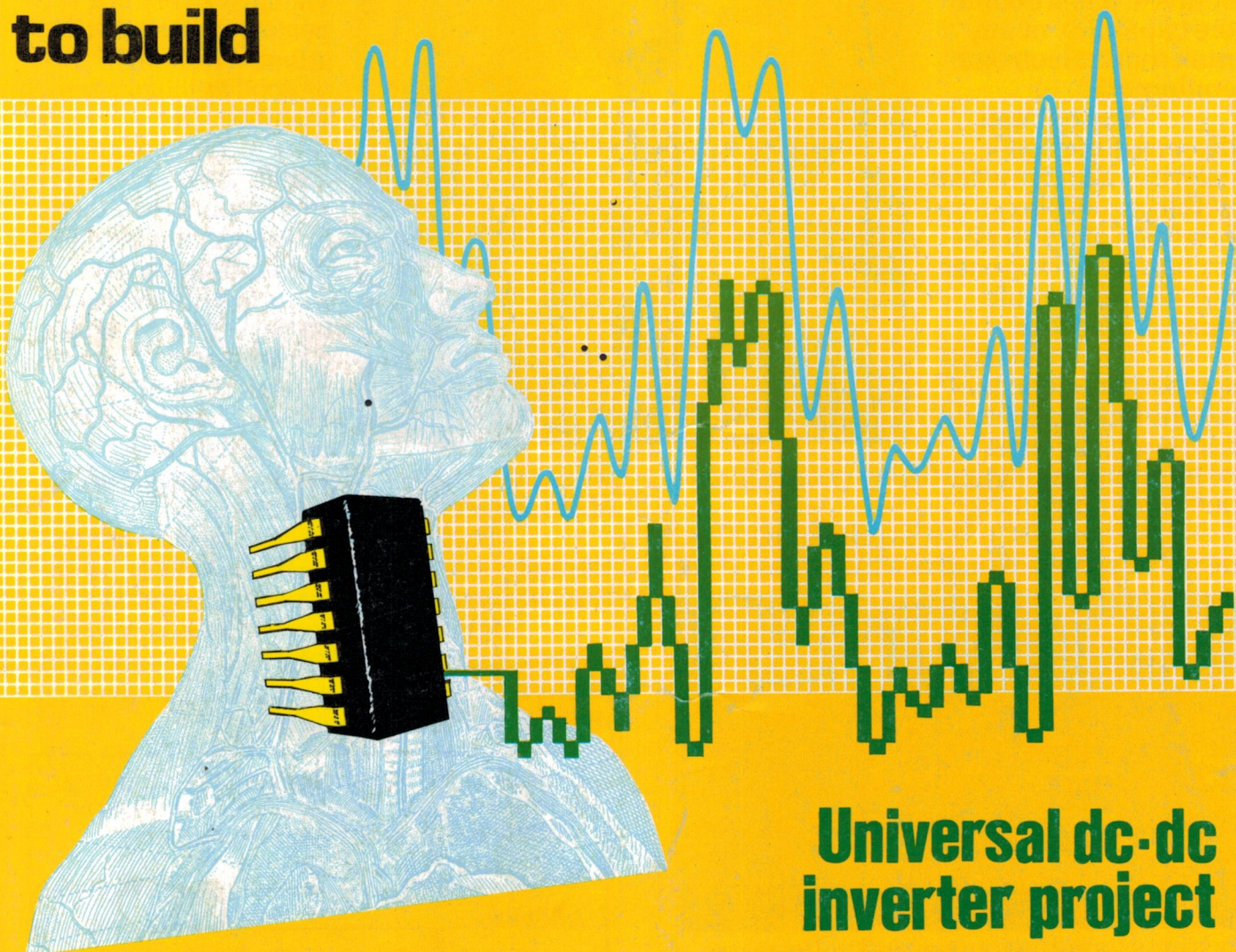

Universal dc-dc
inverter project

Build a
'Photophone' light
beam transciever

Nakamichi High-Com II
noise reduction system
reviewed

The average hi-fi designer versus the human ear.


The human ear forms part of a sound receiving system that outperforms the best audio equipment known to science.

Capable of interpreting a dynamic range of 120db or 10 octaves, it has double the capability of any man made electronic equipment.

The ear can discern direction, coloration and musical within a complex detail rendition of a 50 piece orchestra in a manner no electronic equipment is able to do.

It is, in short, a sophisticated piece of equipment that should represent the most stimulating challenge to any designer of audio equipment.

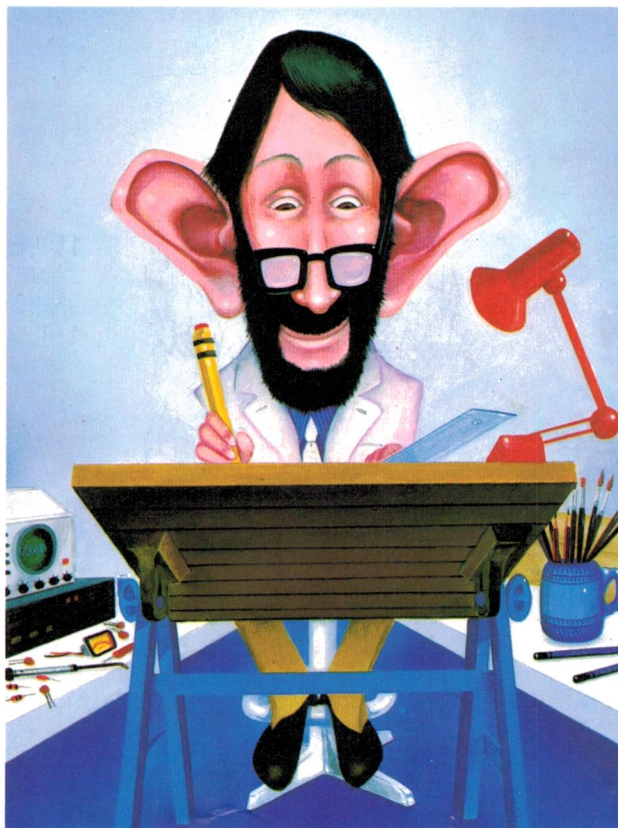Unfortunately it's a challenge that's largely ignored. Which is why in most stereo



were tired of compromise, Vector Research represents a new standard in high fidelity excellence.

Discussing the Vector VRX 9000, *Stereo Review* states "The receiver surpassed virtually every one of its performance specific ations... it sounds as good as it looks, which is saying a lot..."

High Fidelity states "a receiver with such sophisticated performance and functions demands attention." *Popular Electronics* on the Vector VCX 600 cassette deck, "Lower Flutter readings than those of the VCX 600 are hard to find..."

while not cheap, it affords excellent value." *Hi-Fi Buyer's Review* sums up.

"Vector Research is a newcomer to the audio scene, but if the VCX 600 is any guide, this company should be very successful."

If then you are an audiophile whose interest goes beyond famous names and shiny knobs then you owe it to yourself to learn more about Vector Research.



systems handling power and volume are substituted for subtlety and frequency response. Vector Research however is one of the few exceptions. Developed by a team of highly experienced audio engineers who

Dear V.R., In my book, beauty is in the ear of the beholder. Send me the test reports and the name of my nearest stockist.

Name _____

Address _____

Postcode _____

Keio International Pty. Ltd.
198 Normanby Road, South Melbourne 3205.
Telephone: (03) 64 3546.

KO 404 ETI

Vector Research. A fraction better than excellent.



Roger Harrison

Roger Harrison
Editor

COPYRIGHT: The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Murray Publishers Pty Ltd, or from the copyright holders.

LIABILITY: Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any components parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid. The Publisher accepts no responsibility for unsolicited manuscripts, illustrations or photographic material.

QUICK INDEX

FEATURES

- 8 Apple sours Oranges
- 14 Inertial Navigation
- 38 Tektronix CRO offer!
- 95 Turtle Robot Offer
- 130 Dregs

PROJECTS & TECHNICAL

- 25 918: 'Photophone' light beam transceiver
- 34 1509: Universal dc-dc inverter
- 81 647: Versatile Speech Synthesiser
- 46 Short Ccts: Exposure analyser
- 42 Mail Order Hobbyist Books
- 54 Ideas for Experimenters
- 57 'Idea of the Month' Contest
- 61 Shoparound

COMPUTING TODAY

- 69 Zilog Release 'Virtual Memory' Processors
- 72 Printout — News & Views
- 81 647: Versatile Speech Synthesiser
- 88 '660 Software
- 90 Mail Order Computer Books
- 93 The Refined Turtle
- 95 Turtle Robot Offer
- 98 RS232 Troubleshooter
- 104 'Prey' — Apple Game
- 110 D2 Kit EPROM Burner

ELECTRONIC LIFESTYLE

- 115 Sonab is Back!
- 116 Lifestyle News
- 124 High-Com II Noise Reduction System

GENERAL


- 8 News Digest
- 42 Mail Order Hobbyist Books
- 50 Babani Books — Mail Order
- 59 Letters
- 65 Communications News
- 90 Mail Order Computer Books
- 128 Mini-Mart — Readers' Adverts
- 129 Credits & Services

advertisers

Australian School of Electronics	61
Applied Technology	74,75,78,79
Altronics	12-13
Adaptive	103
Audio Engineers	119
A & R Soanar	105
Barson	109
Butterworths	73
Computer City	103
Comquip	27
Cooper Tools	45
Collingwood College	71
Convoy	118
C & K Electronics	32
Dick Smith	52-53
David Reid	11
Digitec	80
Daneva Control	97
Delta Communications	64
Deisound	89
Electronic Agencies	24
ECQ Technics	103
Emtronics	20,89
Energy Control	76
Electrocraft	56
Fairchild	108
General Electronic Services	22
G.F.S.	56
Hewlett-Packard	6
Hitachi	32
Imagineering	105
Imark	97
Intern. Correspondence School	117
Informative Systems	76
Jaycar	30-31, 44,48,49,58,62,63,66
John F. Rose	OBC
K-Nar Computer Cards	92
Kalex	47
Mail Order Centre	56
Moss	47
Melbourne Machinery	80
Magraths	33
Magnetic Media	70,71
Marantz	114
Nicholas Kiwi	113
Patons	94
Philtronics	76
Pre-Pak	55
Rod Irving	21,23,60,87,96
Radio Despatch	77
Rose Music	121
Sanyo	122,123
Scientific Devices	45
Silvertone	103
Software Source	76
Sheridan	40
Sony	131
Subscription	11
Truscotts	47
Top Projects Vol. 8	11
United Sound	120
Vanfi	IFC
Vendale	80
Wiser-Microsoft	68

eti

ELECTRONICS TODAY INTERNATIONAL

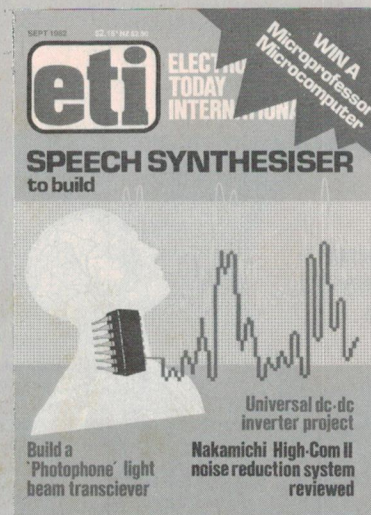

COVER

Feature project this month is the Speech Synthesiser, which starts on page 81. This project produces 'electronic speech' by the 'waveform digitisation' method — which the cover abstract is meant to represent.

Cover design by Ali White

news

NEWS DIGEST

Apple Computer Inc. in legal battle with imitators; New look at the Milky Way; CSIRO research; Mini-tools contest winners; Zinc diecast optical fibre connector; etc.

COMMUNICATION NEWS

Iskra 2 satellite in trouble; SSB above 300 MHz out of the Question?; SINADDER from Vicom; RTTY Terminal; etc.


PRINTOUT

The Graphics Magician; 16-bit microcomputer; Apple II 'Logo' language; Single chip containing a 16-bit CPU; Book review; and more.

LIFESTYLE NEWS


Sanyo's mini stereo; Technics chief discusses slump in hi-fi sales; Concept Audio expands record-range; etc.

features

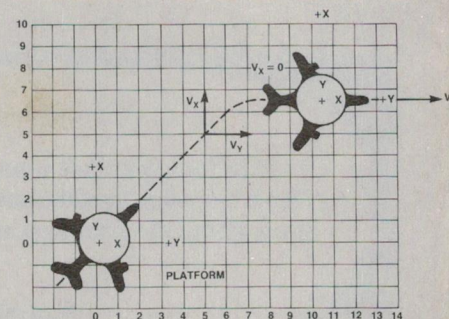

INERTIAL NAVIGATION SYSTEM 14

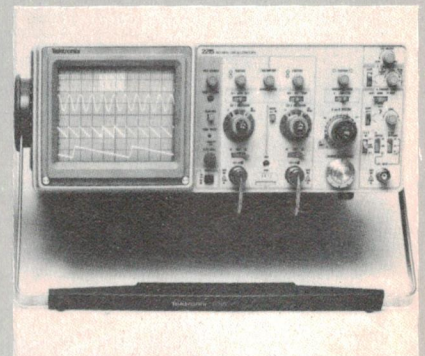Gyros, accelerometers and a computer make up a basic inertial navigation system. This article tells you how it all goes together and what it can do.




TEKTRONIX CRO OFFER 38

Get in quickly for this great opportunity to buy one (or both) of the Model 2213 or 2215 CROs at a special reduced price.

CONTEST — WIN A MICROPROFESSOR! 67

Here's a great chance to learn about micro-computing for free! Simple contest, easy to enter.

projects

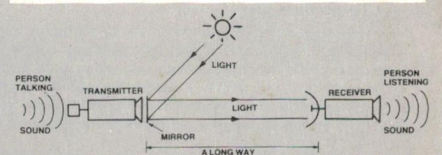


918: 'PHOTOPHONE' LIGHT BEAM TRANSCEIVER 25

An updated version of an obscure invention enables you to send voice signals along a light beam.

1509: UNIVERSAL DC-DC INVERTER

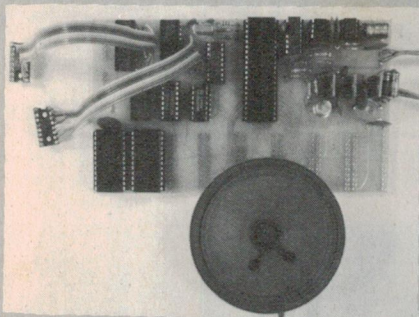Designed so that you can derive almost any dc output voltage(s) you want, simply by winding the appropriate secondary, or secondaries, on the output transformer.



647: SPEECH SYNTHESISER

This versatile programmable speech synthesiser has many unique features which enable it to be mounted in your 'Tasman Turtle Robot', interfaced to almost any computer or used as a Chinese speaking doorbell.

TASMAN TURTLE KIT — STILL AVAILABLE

This offer won't last for ever. Our special price is \$349.

computing

COMPUTING TODAY

Virtual memory processor units; Alternate-source bubble memory technology; X.25 test and development system; etc.

'660 SOFTWARE

The greeblie catchers are after you so watch your step. This is a games program where a 'catcher' and two 'greeblies' pit their skills against each other. In the other program 'Dice', you can throw any number of dice and they won't roll off the screen.

THE REFINED TURTLE

Mechanical and electronic modifications make it a better pet.

RS232 SERIAL INTERFACE TROUBLESHOOTER

This test unit enables you to patch together any wiring arrangement and monitor what's happening on each wire. Now you can find out why your RS232 serial interface won't work.

34 'PREY' — A SIMULATION FOR THE APPLE II

This program builds a 'model' of a piece of territory on which two species of animals live. One eats the other and there are some interesting results when you change the variables.

D2 KIT EPROM BURNER

2716 EPROMs can be programmed using a simple interface and a Motorola 6800 D2 kit.

lifestyle

ELECTRONIC LIFESTYLE

Sonab is Back!; New National Stereo Cassette Player; B & W Leisure Monitors; etc.

NAKAMICHI HIGH-COM II NOISE REDUCTION SYSTEM

The High-Com II really works, providing 20 dB of noise reduction and improved dynamic range for tape recorders of all sorts.

general

MAIL ORDER BOOKS

A library of information on everything you ever wanted to know about electronics. Plus books on topics you may not have even thought about. You need look no further than ETI's book sales department.

SHORT CIRCUITS

Exposure analyser for black and white prints.

ELECTRONICS BOOKS FROM ETI

Beginners' books, circuit books, data books, etc.

IDEAS FOR EXPERIMENTERS

Programmable wiper controller; Thumbwheel power supply and Idea of the Month contest.

LETTERS

SHOPAROUND

MINI-MART

ETI SERVICES

DREGS

104

110

115

124

42, 90

46

50

54

59


61

128

129

130

next month

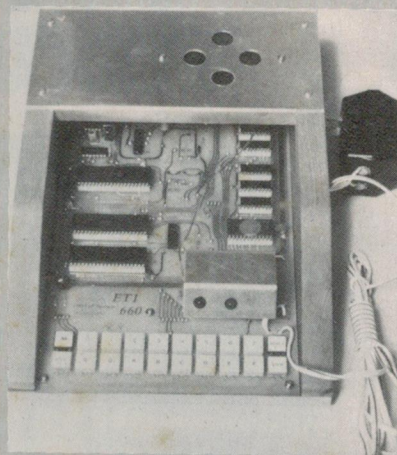

'660 PROGRAM POTPOURRI

A grand assemblage of programs for our popular ETI-660 Learners' Microcomputer! Now you can try a host of great programs like Dot Destroyer, Meteor Storm, Block Puzzle, Black Jack, Noughts & Crosses etc. An issue not to be missed by the '660 owner or CHIP-8 enthusiast!

EPROM PROGRAMMER FOR THE 2650 S100 BOARD

The ETI-685 2650 S100 computer board (Dec. '81) features three programmable ports run by an 8255 PPI. This EPROM programmer makes use of this facility, although it can be used with any microcomputer which has three 8-bit ports available. The unit is self-contained and construction is straightforward. A full program listing for use with the ETI-685 is included.

LOUDSPEAKER PROTECTOR

When we described the ETI-499 General Purpose MOSFET Amp module (March issue), we made mention of a loudspeaker protector project. This is it. This simple module can be used with very high power amplifiers, or even low power amplifiers. It requires no power supply yet provides complete protection.

XR2240 SUPER TIMER


We've had to hold this one over due to lack of space. This Lab Notes describes characteristics and applications of the recently released XR2240 timer chip that can produce accurate timing periods ranging from seconds to . . . years!

VECTOR RESEARCH VR5000 FM-AM RECEIVER

Vector Research Products are new to Australia, and this 'no frill', top-line American-made product has a number of interesting and unusual features. Full report from Louis Challis.

Although these articles are in an advanced state of preparation, circumstances may affect the final content. However, we will make every attempt to include all features mentioned here.

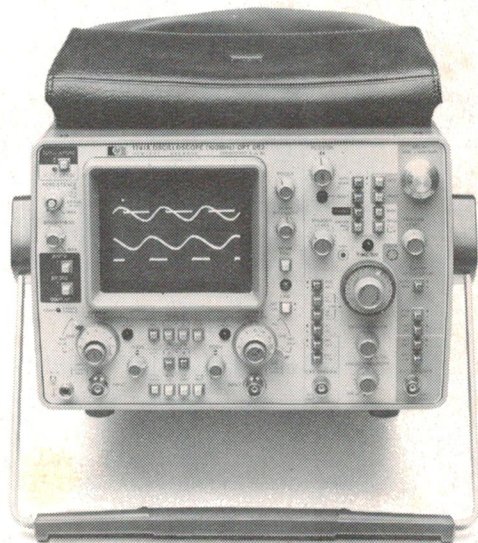Three ways of measuring a fast pulse without visiting your doctor.




High Frequency Scopes.

At Hewlett-Packard we've always had our fingers on the pulse of innovative technology. Our HP 1700 range of oscilloscopes are no exception. Bandwidths of 100, 200 or 275 MHz offered by our models 1740/1742/1743/1715/1725/1722, coupled with excellent trace quality means reproduction of pulses or wavetrains with fidelity. The Dual delayed timebase (or delta time) feature found on some models incorporates two intensified trace markers and allows more accurate measurement of pulse characteristics such as risetimes, period and phasing.

Automated Scope Set Up and Operation.


The Auto Scope feature of our model 1980 gives it the ability to auto range and display any input signal. This makes display of a repetitive pulse a breeze. Single shot applications can be handled by using the 19860 digitizing plug in while 4 channel operation is obtained by plugging in the 1950A input module.

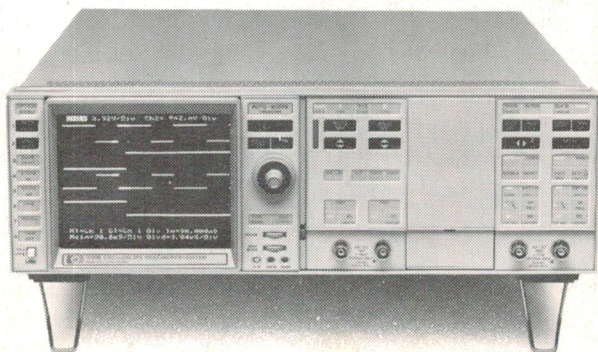The 1980 system offers the user greatly improved productivity in the fields of Production Test (manual or automated), Calibration labs and Research and Development.



Variable Persistence Storage.

Model-1741A, is the best selling 100MHz general purpose storage scope on the market. It combines 200 cm/ μ sec writing speed with features such as the babysit mode, auto erase, and auto store. These features mean its ease of use is unequalled. Models 1744A, 1727A are optimized for capture of super fast single shot or low rep rate pulses. Writing speeds of 1800 and 2000 cm/ μ sec respectively are guaranteed.

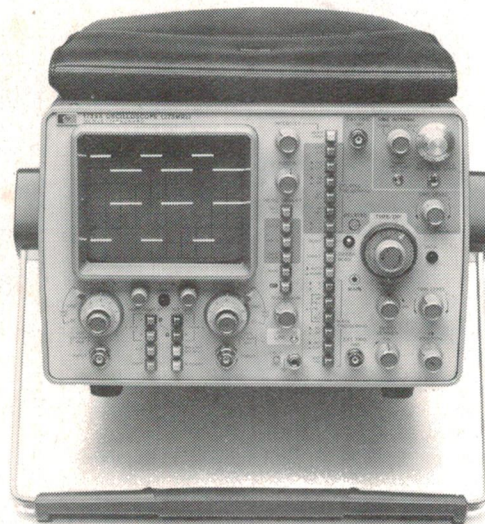

Service and Calibration.

All HP's current generation oscilloscopes have been designed with ease of access and repair in mind. We will carry out most scope repairs for a fixed fee, so you avoid the uncertainties of waiting for a quote. Annual service or calibration contracts can be arranged so that you can budget for your support needs a year ahead.

If you elect to perform your own repair work you can be confident you have good documentation to work with. The quality of our operating and service manuals is well known throughout the electronics industry; and we maintain in Australia, a large supply of scope spares.

Contact your nearest HP office for data on any of our oscilloscopes or for details of our fixed price/contract repair program.



**HEWLETT
PACKARD**

Melbourne 89 6351, Sydney 887 1611, Adelaide 272 5911, Brisbane 229 1544, Canberra 804 244, Perth 383 2188, Wellington 877 199, Auckland 687 159.

HP69

**MASSIVE
BREAKTHROUGH!**

MADE
IN ENGLAND!
— QUALITY!!

CAR COMPUTER BELOW \$200

COMPLETELY BUILT
AND TESTED —
NOT A KIT!!



CONTAINS EQUIVALENT OF
THOUSANDS OF TRANSISTORS
— USES MASSIVE CUSTOM
LSI CHIP TO ACHIEVE
LOW PRICE

**only
\$199
complete**

Never before has such a comprehensive car performance computer been offered at such a low price!! Once again miracle microprocessor technology has enabled us to pass enormous savings on to you!! But don't let the low cost fool you. The "Voyager" car computer IS THE MOST COMPREHENSIVE PRODUCT THAT WE HAVE SEEN. No other car computer matches this one AT EVEN TWICE THE PRICE! You could buy a \$20,000 Holden and not get a better car computer!! Just check the features. We are sure that you will calculate that the "Voyager" represents outstanding value!

FEATURES


- INSTANT FUEL CONSUMPTION IN LITRES/100KM AND MPG!! (MOST OTHERS HAVE ONLY ONE OF THE ABOVE) JUST SWITCH FROM ONE TO THE OTHER AS YOU DRIVE ALONG.
- INSTANT SPEED, TIME AND OTHER FUEL DATA.
- VISUAL AND AUDIBLE EXCESS SPEED ALARM.

INSTALLATION

The "Voyager" comes complete with an unbelievable array of mounting configurations, on dash, under dash or stalk mount. ALL installation hardware is supplied (even a roll of insulation tape!) as well, of course, as the speed and fuel sensors. A lavishly illustrated installation manual is provided as well as a comprehensive operators manual. If you do not want to install the unit yourself we can do this for you for a guaranteed \$39.50*. (A few exotic cars excluded!). A typically competent EA/ETI reader would do the job in 3-4 hours.

* Sydney metropolitan area only.

VOYAGER OPERATING FEATURES

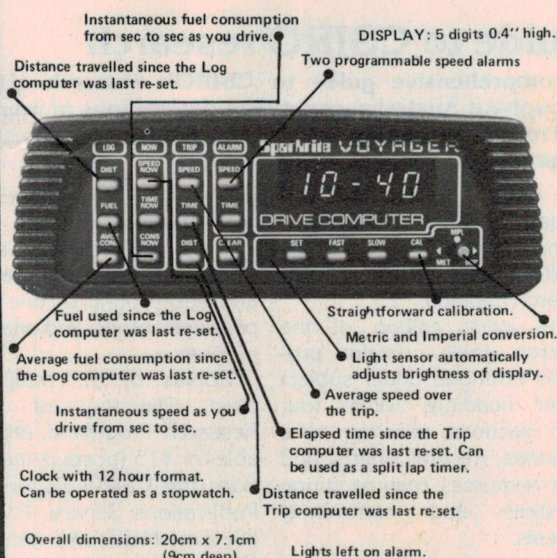

JAYCAR

125 YORK ST SYDNEY 2000
Ph. 2646688 Telex: 72293
Mail Orders To:
Box K-39 Haymarket 2000

POST AND PACKING CHARGES
\$10-\$19.99 (\$1.20) \$20-\$29.99 (\$2.40)
\$30-\$39.99 (\$3.50) \$40-\$49.99 (\$4.60)
\$50 up (\$6.20)

NEW SHOP HOURS
Mon-Fri 8.30 to 5.30pm
Sat 8.30 to 12.00pm
Thurs night to 8.30pm

Apple sours Oranges

Apple Computer Inc. has filed a number of lawsuits overseas, notably in Taiwan, Hong Kong and New Zealand, in an effort to stop the manufacture and export of Apple II personal computer 'imitations'.

In New Zealand, Apple obtained an injunction against Orbit Electronics which Apple claimed was passing off "Orange" computers from an unknown Taiwanese manufacturer as Apple II computers.

It is also common knowledge that Apple II imitations are available in Australia and investigations are continuing, as is the case in Japan and Singapore.

In Taipei, early in July, Apple brought a civil action under Taiwan's copyright laws against 'Sunrise' computer, maker of the "Apolo II" computer.

As a first step in this action, in accordance with Taiwanese law, Apple seized as evidence several Apolo computers during a surprise raid on a 'Sunrise' facility in Taipei.

Apple also plans to take simi-

lar action against another manufacturer in Taiwan. The government of Taiwan has helped prevent the export of Apple II copies, according to the company.

In Hong Kong, Apple filed a civil action under local patent laws against a small manufacturer selling Apple II copies, a number of which were seized as evidence in a surprise raid similar to the one in Taiwan. Sales and purchase records of the company were also seized.

Because patents and copyrights are enforceable in Hong Kong, Apple expects to halt all manufacturing and selling of copies there.

Apple has registered its trademarks and copyrights with US customs authorities and expects that 'bogus' Apple products will be confiscated by the US government at the port of entry.

Guide to CSIRO research

A comprehensive guide to CSIRO's research activities throughout Australia, containing descriptions of more than 700 research programs and sub-programs, was released late in June.

In clear, non-technical language, it outlines research programs being tackled by the CSIRO and the implications of research findings.

The latest edition of the research guide contains programs arranged under subject matter headings within four main sections covering rural industries, mineral, energy and water resources, manufacturing industries and community interests.

The names, addresses and telephone numbers of the people to contact for further

information about any research topic are also included.

Three index listings are included: one which lists programs and sub-programs, one listing personal names, and one listing subjects.

Copies of the publication, titled 'Directory of CSIRO Research Programs', are available for \$15 (postage included) from the CSIRO Editorial and Publications Service, P.O. Box 89, East Melbourne Vic. 3002. Cheques accompanying orders should be made out to 'Collector of Moneys, CSIRO'.



New look at the milky way

CSIRO radio astronomers in Sydney have used a new technique to discover that the Milky Way was part of a grand spiral galaxy with four catherine wheel arms trailing over a distance of more than 100 000 light years.

The research, carried out using the four-metre radio telescope at Epping (NSW), had uncovered previously unknown facts about the galaxy in which we live. The Milky Way, as normally seen, is an edge-on view of our galaxy.

"The new technique has allowed astronomers to observe the massive clouds of molecules between the stars from which new stars are born," the Minister for Science and Technology Mr. Thomson said when releasing the announcement.

"Using the four-metre radio telescope, researchers have penetrated the interstellar dust which normally obscures the light from distant stars."

"Radio waves, penetrating the dust, can probe every part of our galaxy and have enabled radio astronomers to 'piece together' the grand design of the Milky Way."

Since the 1950s, radio astronomers at CSIRO's Division of Radiophysics have played a leading role in this quest.

The team of CSIRO scientists

comprised Dr. Brian Robinson, Dr. Jim Caswell, Dr. Raymond Haynes, Dr. Dick Manchester and Dr. John Whiteoak. Collaborating in the project have been Professor Bill McCutcheon from Vancouver and Chris Rennie from the ANU's Mount Stromlo Observatory.

The researchers have taken radio measurements of the molecular clouds in our galaxy which delineate the spiral arms. These are normally highlighted optically by hot, young stars and surrounding ionized gas.

"These measurements have been convincingly made since 1980, with supporting observations made at Columbia University in the United States," Mr. Thomson said.

"Complementary radio observations of ionized gas, made over the past 10 years at Parkes in New South Wales, have been vital in understanding these observations," he said.

The scientists presented their research to international conferences in Holland and Greece last month.

New Fluke 4½-digit handheld

Fluke's 8060A, the newest in their range of DMMs, is a handheld, microcomputer-based 4½-digit multimeter that includes true RMS measurements for ac signals to 100 kHz, frequency measurements to 200 kHz and resistance measurements to 300 M.

It also has the ability to store any measurement as an offset (a positive or negative relative reference value).


Voltage measurements can be directly displayed in dBm referenced to 600 ohms, or in relative dB.

Continuity testing (with selectable visual/audible indication), conductance and constant current source diode testing are also included.

A multiplexed LCD display provides special function annunciation, low battery (20%) warning and a power-up self-diagnostic indication.

The Fluke 8060A is powered by a standard 9-volt alkaline battery (170 hour continuous operation) or optional ac battery eliminator. The Fluke 8062A, a companion model, comes without the Hz, dB and conductance functions.

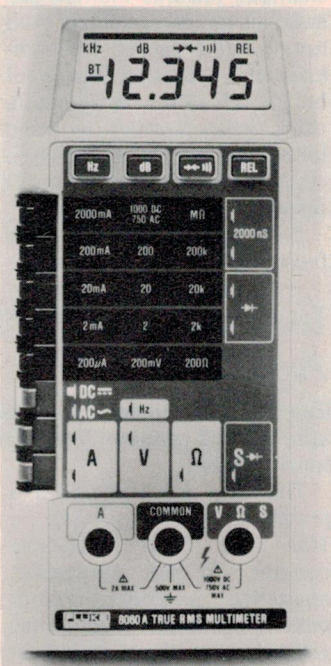Availability is from stock mainland states, or through Elmeasco offices in all major electronic retail outlets.



RIFA get Precision Monolithic Inc.

During a recent visit, Mr. Steve Pass, Vice President, Sales, of Precision Monolithics Incorporated, announced the appointment of Rifa as sole Australian distributor for the P.M.I. range.

P.M.I. manufactures a wide range of high quality, high performance linear integrated circuits including operational amplifiers, comparators, matched transistors, voltage references, D/A converters, multiplexers/analogue switches, sample-and-hold circuits as well as telecommunications circuits.


P.M.I. was established by Bourns Inc. in 1969 and since that time has become recognised, world-wide, as a leader in high performance IC's. For further information contact Peter Duddy, RIFA Pty Ltd, 202 Bell Street, Preston Vic. 3072. (03)480-1300.

NOTES & ERRATA

ETI-499 Mosfet amp, March '82. Some people have had trouble with the output offset voltage adjustment, being unable to reduce it to 10 mV or less. This can be fixed by changing R2 from 100k to 33k. The input high-pass pole only rises to just under 20 Hz, which is OK.

Circuit File: power supplies, April '82.

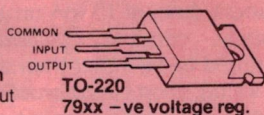On page 20 the pinout of the TO-220 79xx voltage regulator shows the common and output pins reversed. The correct pinout is shown here.



MINITOOLS CONTEST WINNERS

The contest featured in our April issue (page 13) offered a complete Minitools toolkit as first prize plus a selection of tools for second and third prizes. We had a hard time choosing three winners from the huge number of entries, but after some deliberation, we managed.

Contestants had to answer four questions and tell us in 50 words or less what features of Minitools attracted them and how this applied to their intended application.

Here are the correct answers to the four questions:

1. When drilling holes in a pc board, stability is essential to avoid breaking the very small drill bit. Thus, it would be best to hold the pistol drill in —

- ☐ your hand.
- ☐ a vice.
- ☒ the drill stand clamped to a bench.
- ☐ the dog's mouth.

2. When cutting a large hole in a panel to fit a meter, the hole is quickly and neatly cut by —

- ☐ drilling a circle of holes and filing around them.
- ☒ using a jig saw.
- ☐ using a 'nibbling' tool.
- ☐ getting the dog to chew it out.

3. Power tools for hobbyist use are most safely powered from —

- ☐ a 1500 V dc supply.
- ☐ a 240 V ac supply.
- ☐ a 415 V ac supply.
- ☒ a 12 V dc supply.

4. A flexible shaft unit for a drill is most useful for —

- ☐ doing dental work on the dog.
- ☒ drilling in awkward places where a pistol drill won't reach.
- ☐ drilling around corners.
- ☐ drilling something you're too lazy to hold in a vice.

First prize of a Minitools Workshop Kit went to:

Peter Mann of Robinvale, Victoria.

Here's what he said:

"I am a hobbyist and I make my own cases and pcbs for projects. All the features of Minitool tools would make the task of drilling and deburring holes, shaping and smoothing hardware, drilling pcbs — even cutting the pcb from blank material, a lot easier, faster and more accurate."

Second prize of a pistol drill, drill stand, flexible shaft and power pack went to:

I. Bernsteins of Mount Pleasant, West Australia.

He had this to say:

"Minitools' features are useful to me in robotics. Their small size allows them to be used where other tools can't fit and to make parts too delicate for normal power tools. The 12 V supply allows work to be done safely, even 'in-flight' using the robot's battery."

Third prize of a pistol drill, orbital sander and power pack went to:

Peter Furnell of Woollahra, NSW

for his ingenious audacity! Read this:

"I am in the business of making hand-crafted electric harps for Leprechauns. Minitool tools are ideal for these instruments because of their small scale...!"

"(The Leprechauns use the harps to play a new kind of Irish rock music called Sham Rock.)"

Thanks to the many, many readers who so enthusiastically entered this contest. It's a pity we don't have the space to print more of the ingenious, humorous and interesting replies entrants sent in.



New zinc diecast optical fibre connector

Rifa, distributors of the Amphenol range of connectors, recently released details of Amphenol's zinc diecast optical fibre connector, which can be used in place of plastic counterparts.

Optical fibres in use today are either of quartz or plastic fibre. Quartz fibre is expensive, but displays excellent performance in long-distance optical fibre telecommunications. Plastic fibre costs much less and is ideal for short-distance transmission.

The newly-developed Amphenol zinc diecast connector is designed for use with plastic fibre, and since it is metal

instead of the generally used plastic, the fibre elements can be hermetically sealed, eliminating RF and electromagnetic interference.

Evaluation kits including one receiver, one transmitter and two metres of cable are available from Rifa at \$26.50.

For further information contact Rifa Pty Ltd, 202 Bell Street, Preston Vic. (03)480-1300.

Scopex LCD CRO, local agent

The Scopex liquid crystal display oscilloscope featured in News Digest in the July issue is available in Australia through local instrument manufacturer, BWD.

The Scopex 'Voyager' is a dual-trace, digital storage instrument having very low power consumption and weighing only 2.5 kg.

The display is a dye phase-change type with a 125 x 256 matrix giving an active area of 64 x 102 mm, larger than many portable oscilloscopes.

Enquiries to BWD Instruments Pty Ltd, Miles St, Mulgrave Vic. 3170. (03)561-2888.

Digital thermostats and thermometers

The Victorian-based Twite Instrument Company has developed a range of thermostats and thermometers featuring digital operation.

The Model F1000, for example, features thumbwheel switches for easy setting of both turn-on and turn-off temperatures in 0.1°C steps, alarms for under and over temperature using delayed action to avoid false triggering, and alarm outputs for remoting. A LED display shows temperature.

Sensor and all functions may be remoted over long distances

using three-pair telephone cable and a power module, claimed to greatly reduce installation costs. The F1000 comes in a standard 430 mm (19") rack cabinet. In inside or outside mounting the sensor is supplied with the unit.

For more details on this and other units in the range, contact Twite Instrument Company, P.O. Box 176, Shepparton Vic. (058)25-2042.

Instruments for Electronic Agencies

Electronic Agencies now stock Trio CROs, and have available the full range of Trio products as well as B&K Precision Instruments.

The Trio range includes a portable 15 MHz CRO, a 100 MHz CRO, frequency counter, function generator, resistance generator, colour pattern generator, electronic voltmeters, probes, dc power supplies and an acoustic measuring system.

The B&K range includes

analogue and digital multimeters, semiconductor testers, frequency counters, logic equipment, capacitance meters, valve testers, probes, etc.

For details contact Electronic Agencies at 115 Parramatta Rd, Concord NSW.

Ceramic humidity sensor

Macron Electronic Ltd has developed a new ceramic humidity sensor with an element made of porous oxide ceramic sinter at high temperatures.

The fine crystalline surface of the element is highly absorbent to water molecules, and its resistance varies exponentially to the relative humidity of the atmosphere.

The element is packaged in a

plastic case with a plastic mesh filter window and lead termination.

Full details from Associated Controls, P.O. Box 21, Padstow NSW 2211.

Joystick control units

Technico is now stocking joystick control units claimed to provide superior operation with quality construction, made by Flight Link Control Ltd of the UK.

The Model JS4 features a contactless inductive sensing system, a life claimed to be in excess of 10 million cycles, infinite resolution and zero noise, current drain of 15 mA on 10 V supply, centring consistency claimed to be better than $\pm 1\%$ of swing, short circuit proof outputs and 10 ms response time.

The JS1, 2 and 3 models are

potentiometer types: the JS1 is a single-axis type, the JS2 a dual-axis type and the JS3 a triple-axis type. They feature all-metal construction, will accept most standard pots and wafer switches, spring or friction modes and a wide variety of levers and knobs.

Contact Technico for full details.

eti

\$4.95*

TOP PROJECTS Vol. 8

THE VERY LATEST

THIS GREAT NEW BOOK FROM ETI IS SO 'HOT OFF THE PRESS' THAT THE COVER LITERALLY GLOWS RED!

TOP PROJECTS VOL. 8

Our 'Top Projects' series have always been very popular with hobbyists, containing as they do a collection of the best projects from the past year or so's issues of ETI Magazine. Here we have 25 projects, ranging from the ETI-1501 Negative Ion Generator, to the ETI-499 General Purpose 150 W MOSFET Power Amp Module, from the ETI-574 Disco Strobe to the ETI-469 Percussion Synthesiser, from the ETI-735 UHF TV Converter to the ETI-563 NiCad Fast Charger.

Top Projects Vol. 8 is available at newsagents, selected electronic suppliers or directly, by mail order, from ETI Book Sales, 15 Boundary St, Rushcutters Bay NSW 2011, for \$4.95 plus 90¢ post and handling.



DAVID REID ELECTRONICS

IF YOU'RE INTO ELECTRONICS COME IN AND SEE US!


WE'RE A POSITIVE FORCE IN SYDNEY AND THE LARGEST ELECTRONICS DISTRIBUTOR IN NEW ZEALAND — WITH THOUSANDS OF ELECTRONIC PRODUCTS, COMPONENTS AND ACCESSORIES

YOU'LL SEE THE SIGN

DAVID REID ELECTRONICS LIMITED

Takapuna • Auckland City • Te Papapa
Hamilton • Palmerston North • Lower Hutt
Wellington • Christchurch • Dunedin.

NORRIE 1478

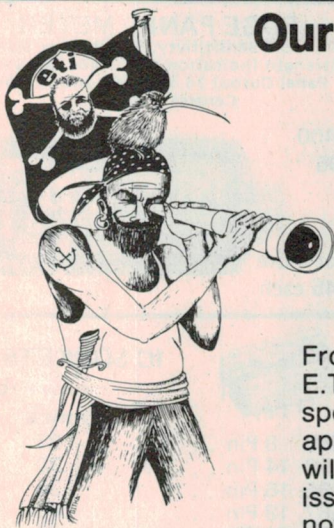

Our Subscriptions Department Discovers ...

... New Zealand

New Zealand readers are continually asking if we can arrange for subscriptions to Electronics Today International to be paid in New Zealand currency to a New Zealand address so as to avoid the hassle and expense of obtaining bank drafts.

Well we have finally done it!

From now on New Zealand readers will be able to pay for subscriptions to E.T.I. in New Zealand currency and at a New Zealand address! Also as a special offer the New Zealand subscription rate will be identical to that applicable in Australia — no surcharge to allow for exchange rate! Not only will you pay less and have fewer hassles — but you should also receive your issues much earlier. This offer ends March 1983, order your subscription now!

☐ Subscriptions: \$25.75 (NZ) per year.

I enclose \$..... for my subscription to Electronics Today International

Send orders to: Murray Publishers N.Z. Ltd.

Attention: Frank Hargreaves

ACP, 4th floor, Sun Alliance House

42-44 Shortland Street, Auckland


Name.....Address.....

Special offer lasts only till March 1983. Order now.



WILL YOUR BUDGET PROBABLY WON'T STRETCH TO AFFORD OUR PROFESSIONAL SERIES ALL ALUMINIUM RACK CABINETS

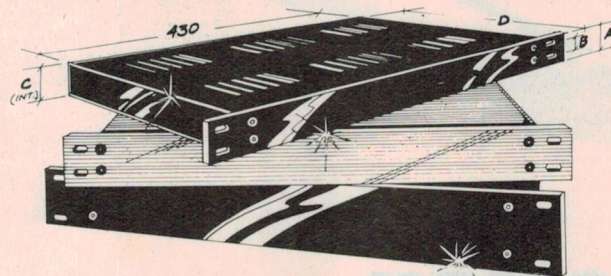NOW YOUR PREAMPS, AMPS, CONTROL MODULES MONITOR PANELS ETC. CAN LOOK EVERY
BIT AS GOOD AS TECHNICS, NAKAMICHI AND OTHER TOP MANUFACTURERS



INTRODUCTORY PRICES

Cat No.	Finish	A	B	C	PRICE	5 or More
H 0401	Natural	44	34	38	\$39.50	\$38.00
H 0402	Natural	88	57	82	45.00	42.50
H 0403	Natural	132	89	126	49.50	45.00
H 0411	Black	44	34	38	39.50	38.00
H 0412	Black	88	57	82	45.00	42.50
H 0413	Black	132	89	126	49.50	45.00

Beware of other rack boxes that do not conform to
international rack sizing.

DIODES, Small Signal


Z 0101	IN914/IN4148	.05
Z 0047	OA47	.50
Z 0090	OA90 GER	.30
Z 0091	OA91 (Equiv) GER	.20
Z 0095	OA95 GER	.25
Z 0096	OA202	.80
Z 0097	BA102 S1 Vari Cap	.80
Z 0048	AA119 GER	.40
Z 0100	HP5082 Hot Carrier	2.95

DIODES RECTIFIER

Z 0105	IN4002	100V 1A	.06	.05
Z 0109	IN4000	400V 1A	.08	.06
Z 0112	IN4007	1000V 1A	.12	.10
Z 0115	IN5404	400V 3A	.35	.28
Z 0118	IN5408	1000V 3A	.40	.34
Z 0120	R250A	400V 6A	.80	.70
Z 0125	BYX21L/200	200V/25A	2.95	2.80
Z 0126	BYX21L/200R	200V/25A	2.95	2.80

LEDs

		10	100
		Ea.	Up
Z 0140	3mm Red	.14	.10
Z 0141	3mm Green	.20	.18
Z 0143	3mm Yellow	.22	.20
Z 0150	5mm Red	.14	.10
Z 0151	5mm Green	.20	.18
Z 0152	5mm Yellow	.22	.20
Z 1054	5mm Orange	.25	.22
Z 0160	Rect. Red	.22	.19
Z 1062	Rect. Green	.25	.22
Z 1064	Rect. Yellow	.25	.22

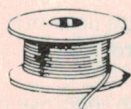

TINNED WIRE

22 gauge
100 gram Reel

W 0420 ONLY \$2.50


HOOK UP WIRE BARGAINS

Quality tinned 13/.12mm H/U wire available
in 8 colours. On 100m reels.

- W 0250 Red
- W 0251 Black
- W 0252 Brown
- W 0253 Orange
- W 0254 Yellow
- W 0255 Green
- W 0256 Blue
- W 0257 White


ALL JUST \$3.95 ea.
or eight reels for \$30.00

Fantastic Value!

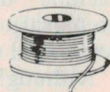

CRYSTALS

Parallel Resonant

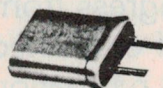


Frequencies
Quoted
in MHZ

Y 1000	1-000	5mm Pinout	11.50
Y 1003	1-8432		9.50
Y 1006	2-000		7.50
Y 1010	3-57945		3.00
	Solder		
Y 1012	4-000	12-3mm Pinout	5.00
Y 1015	4-194		5.00
Y 1017	5-000		5.00
Y 1018	6-000		5.00
Y 1019	8-000		5.00
Y 1020	10-000		5.00
Y 1025	12-000		5.00
Y 1030	16-000		5.00

VELOSTAT

Non-static sheeting for storing
CMOS IC's, LSI's etc. 1000
times better than aluminium
foil. Will store up to 150 IC's
on one 225 x 150mm sheet.

H 0500 \$3.50
per sheet

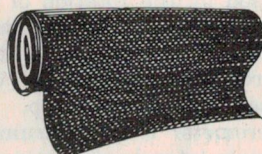

BLACK SPEAKER CLOTH

Quality German "easyfit" acoustic
cloth. Very pliable, one way
stretch. Allows neat and easy
application to speaker box front.
Extra wide 1.5m. One metre
length does a pair of average
Hi-Fi boxes.

H 9200 \$7.50
per metre

ALTRONICS RESELLERS

Please note that resellers may not have all the items
advertised in stock, and as resellers have to bear the
cost of freight, prices may be slightly higher than
advertised. ALTRONICS reseller prices should how-
ever represent a considerable saving over our com-
petitors' prices.

NEW SOUTH WALES

CITY
Radio Despatch 211 0191
Electronic Agencies 29 2098
Jaycar 264 6688

SUBURBAN

LEWISHAM
PrePak Electronics 569 9770

CONCORD

Electronic Agencies 745 3077

DEE WHY

David Ryall Electronics 982 7500

WAITARA

Applied Technology 487 2711

MATRAVILLE

Creative Electronics 666 4000

COUNTRY

BROKEN HILL
Crystal TV 4803

COFFS HARBOUR

Coffs Harbour Electronics 52 5684

PENRITH

Acorn Electronics 21 2409

NEWCASTLE

D.G.E. Systems 69 1625

WINDANG

Madjenk Electronics 96 5066

GOSFORD

Tomorrow Electronics 24 7246

KURRI KURRI

Kurri Electronics 37 2141

SOUTH AUSTRALIA

CITY
ADN Electronics 212 5505

SUBURBAN

PROSPECT
Jensen Electronics 269 4744

ELIZABETH GROVE

A.E. Cooling 255 2249

CHRISTIES BEACH

Force Electronics 382 3366

KESWICK

Freeway Electric Wholesalers 297 2033

VICTORIA

CITY
All Electronic Components 662 3506

ELLISTON

Ellistronics 602 3499

SUBURBAN

HUNTINGDALE
Stewart Electronics 543 3733

SOUTH CROYDON

Truscott Electronics 723 3860

COUNTRY

SHEPPARTON
GV Electronics 21 8866

MILDURA

Electronic and Digital Services 23 3380

QUEENSLAND

CITY
Delsound 229 6155

SUBURBAN

SALISBURY
Colourview Wholesale 275 3188

FORTITUDE VALLEY

St. Lucia Electronics 52 3547

BIRKDALE

Wholesale Sound Accessories 207 2502

COUNTRY

CAIRNS
Thompson Instrument Services 51 2404

TOWNSVILLE

Solex 72 2015

ROCKHAMPTON

Purely Electronics 21058

GLADSTONE

Purely Electronics 72 4321

GYMPIE

TV and Appliance Services 82 1671

IPSWICH

P & P Electronics 281 8001

TOOWOOMBA

Hunts Electronics 32 9677

DOWN'S RADIO AND TV

Down's Radio and TV 32 1044

NAMBOUR

Nambour Electronics 41 1604

NT

DARWIN
Radio Parts Darwin 81 8508

Kent Electronics 81 4749

Ventrionics 81 3491

ALICE SPRINGS

Farmer Electronics 52 2967

Ascom Electronics 52 1713

TASMANIA

HOBART
Beta Electronics 34 8232

KINGSTON

Kingston Electronics 29 6802

AVOCA

Freemans TV 84 2166

WEST AUSTRALIA

ALBANY
BP Electronics 41 2681

GERALDTON

Geraldton TV and Radio 21 2777

WYALKATCHEM

D & J Pease 81 1132

MANDURAH

Kentronics 35 3227

ACT

Scientronics 54 8334

Electronic Components 80 4654

RESELLERS WANTED IN ALL AREAS

(including WA)

Phone: STEVE WROBLEWSKI (09) 381 7233
for details

NEW 24 HOUR 7 DAYS P/WEEK PHONE ORDER SERVICE FOR BANKCARD HOLDERS

Take advantage of "off peak" low STD phone rates and
phone your order to our new recorded 24 hour order
service. Give your name, address with postcode, phone
number, bankcard number and expiry date then your
order—and presto your order will be processed and back
to you in a flash—Please nominate Jetservice if you
want overnight delivery.

\$2 DELIVERY AUSTRALIA WIDE We process your
order the day received and despatch via Australia Post.
Allow approx. 7 days from day you post order to when
your receive goods. Weight limited 10kgs.

\$4 DELIVERY AUSTRALIA WIDE We process your
order day received and despatch via Jetservice for delivery
next day.

BANKCARD HOLDERS CAN PHONE ORDER UP TO 8PM (EST) FOR NEXT DAY DELIVERY — SOUNDS INCREDIBLE DOESN'T IT? Alright you cynics just try us! Weight limit 3.3kgs. Jetservice cannot deliver to P.O. box numbers (Australia Post would have a fit).

\$10.00 HEAVY HEAVY SERVICE — AUSTRALIA-WIDE All orders over 10kgs must travel on the heavy service, that is — road express. Delivery time 7 days average.

ALTRONICS

105 STIRLING ST., PERTH
FOR INSTANT SERVICE

(09) 328 1599

All Mail Orders:

Box 8280 Stirling St.,
Perth WA 6000



Inertial navigation systems

Christopher G. Heath

It took the human race over 900 years to progress from the primitive lodestone compass to a self-contained navigation system dubbed INS — the inertial navigation system. Here's a rundown on how it works.

THE EARTH'S rotation was discovered by Heraclides of Pontus in the 4th Century BC. During the next century, Erathosthenes of Cyrene calculated the circumference of the Earth to be approximately 38 500 km (24 000 miles), a figure undisputed for another 20 centuries.

Early writings suggest that the first lodestone compass was discovered by the Arabs or Chinese around 100 BC. The first reference to its use by Europeans is dated 1178. Also, the astrolabe was discovered about this period, the predecessor of the sextant, which was used to measure the angular elevation of stars and planets with respect to the horizon. This information was used in conjunction with elementary astronomical tables and time to plot a rudimentary navigational fix. Using this type of instrument, Columbus sailed to the New World.

The following inventions, together with Newton's Laws of gravitation, and Faraday's rules of electricity and magnetism, made INS a reality:

- an accurate marine chronometer (1766)
- the Foucault pendulum (1800)
- the marine gyro compass (1909).

The basics of INS


A basic inertial navigation system comprises the following subsystems:

- gyros
- accelerometers
- a computer.

A gyro is a device which, when spinning, points to a fixed position in space. To move the gyro from this position, pressure must be applied to the mounting frame (gimbals). If the gyro is moved up or down, it moves to the left or right. This action is called 'precession'.

An INS employs two gyro subsystems, one fitted in each horizontal plane or axis (X and Y). However, gyros are themselves subject to natural precession (errors) caused by the rotation of the earth (coriolis error) and the movement of the vehicle in which the gyro is fitted (attitude error). These errors are corrected by a servo or follow-up loop.

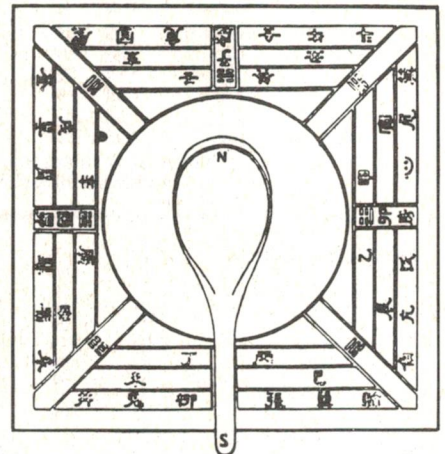An accelerometer is an instrument which measures lateral movement and converts it to an electrical signal. To reduce errors in the accelerometers they are usually mounted to the gyro assembly. The electrical outputs from the instruments are converted to a suitable form and applied to the associated computer. Usually three accelerometers are



Primitive Chinese compass consisting of a magnetic spoon resting on a polished copper plate.

fitted in a system, one in each axis (X, Y and Z).



The computer associated with an INS provides the following functions:

- coriolis correction
- latitude information
- attitude correction
- longitude information
- altitude or depth information
- distance travelled
- vehicle speed
- true or magnetic course data
- Earth's radius.


However, other systems are used in conjunction with INS to provide all the stated functions.

The computer runs an operational program automatically at system switch-on, or manually via the associated control unit. The program employs algorithms to solve various forms of mathematical equations, using detected variable and fixed quantities generated within the system or externally. These include distance travelled, vehicle acceleration, and the Earth's radius and rotational rate.

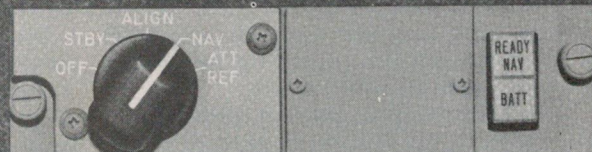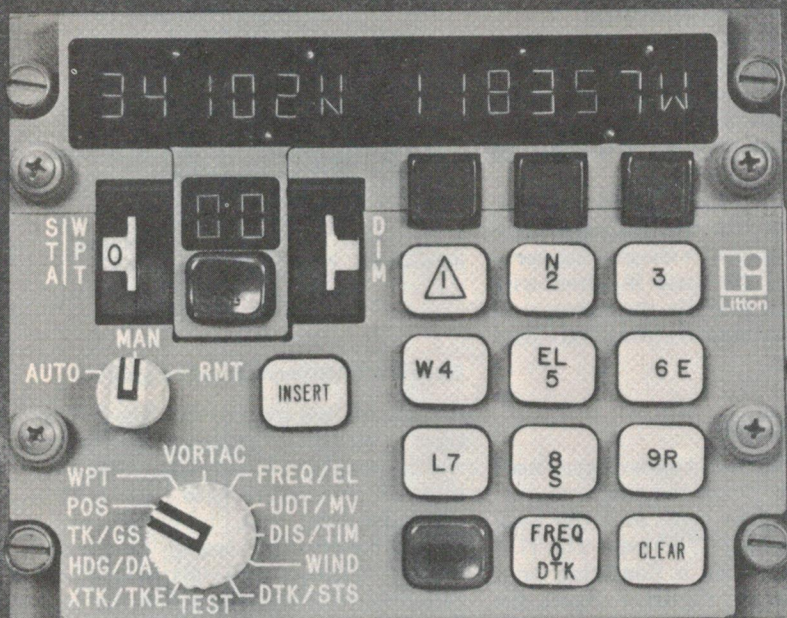Although a self-contained system, its accuracy deteriorates with running time. This requires some form of external positional updating every 24 hours. ►



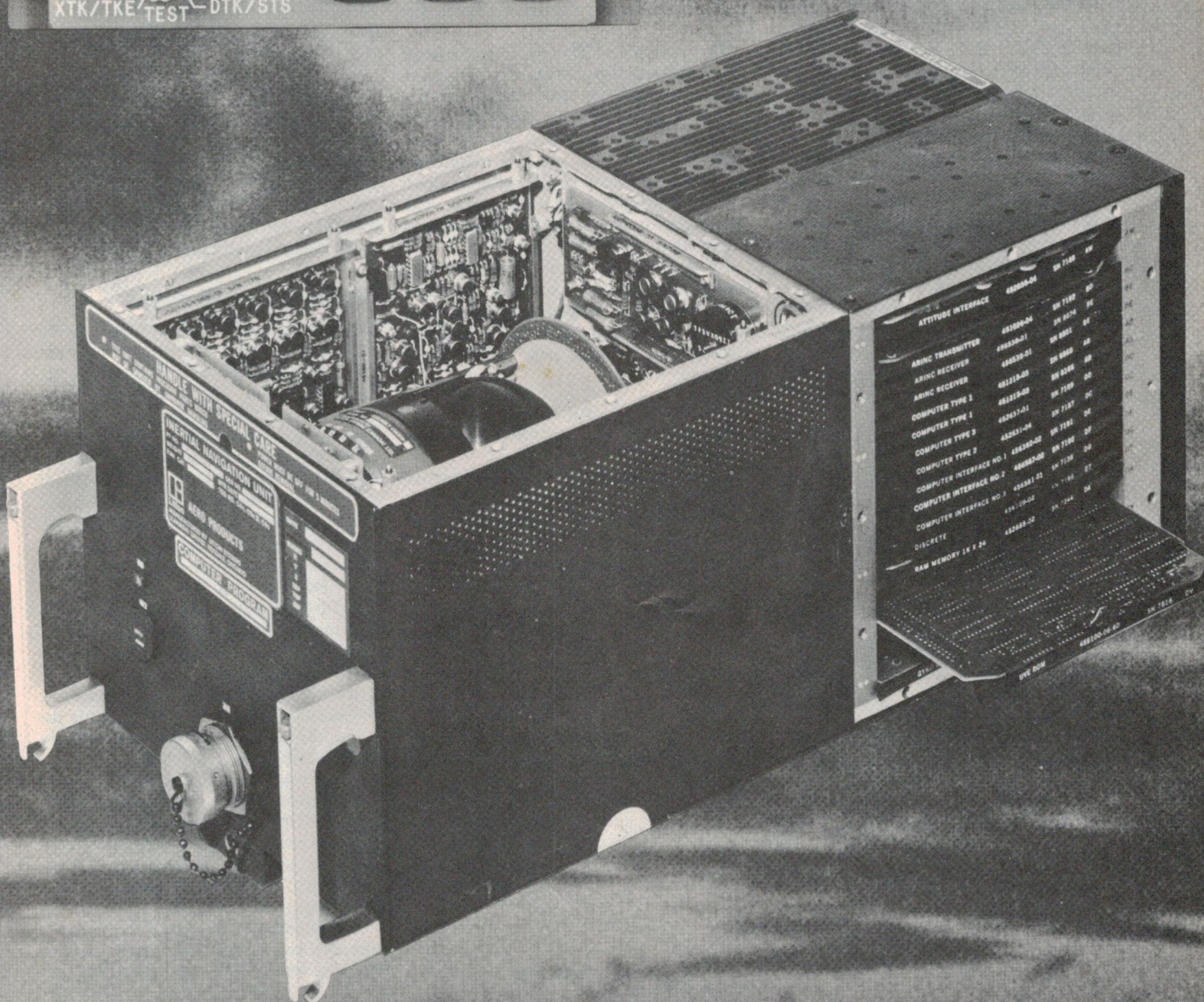A complete inertial navigation system, from Litton Aero Products. The large box contains the gimbal and inertial platform, plus servo and computer electronics, etc. At top left is the control display unit used to enter present position and waypoint co-ordinates, select track steering and display navigation data generated by the system. At top right is the mode selector unit.



usually helium or hydrogen. This reduces wear to nil while the gyro is rotating, and provides an unlimited life expectancy, determined by the number of system stop-start cycles.

The gyro float elements provide support for the spin bearings, gyro wheel, torque elements, and pickoffs, as well as forming a sealed enclosure around the rotating components. Floatation comprises suspension of the gyro sensing elements in liquid, in a similar manner to the slug of an accelerometer. However, gimballed (two-axis stabilised) rotor assemblies do not require floatation and are called 'dry gyros'.

The signal pickoff units monitor the angular displacement of the rotating components with respect to the gyro case and produce an electrical output proportional to this displacement. The pickoff elements are either inductive or capacitive devices which are highly sensitive electrical transducers, excited by an ac supply. Their characteristics ensure that they produce negligible heat and are capable of resolving the smallest increments of motion inherent in a gyro system.

The torque elements, which reposition the gyro assembly, are either synchro devices or dc force motors. These elements are manufactured to precision tolerances as they are required to produce high, variable precession velocities associated with components of Earth-rate varying with latitude.

The lead-in wires or ribbons connect the ac supply to the gyro motor, provide a signal path for the pickoffs, and apply input signals to the torquing elements.

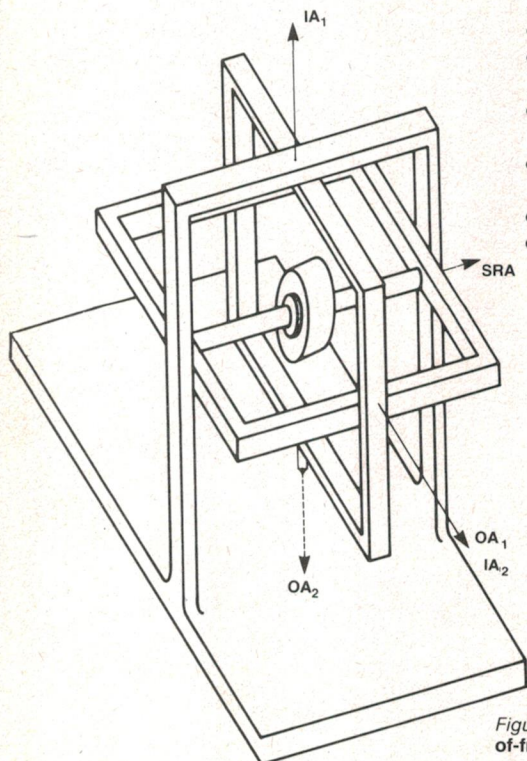


Figure 8. A gimballed two-degrees-of-freedom (TDF) gyro.

Mechanical errors produced by the lead-in wires are reduced by design.

Magnetic shields, which are made of steel alloys, are placed around the gyro assembly to reduce the effects of stray magnetic fields. These fields could produce unwanted torque on the moving parts.

The case provides a protective, gas-tight enclosure for the gyro assembly, and acts as a frame for the moving parts. The inside of the case is fitted with sensors which indicate the presence of moisture, high temperatures and excessive pressure.

Types of Gyro

There are two main types of gyro used for INS applications, the single-degree-of-freedom (SDF) type and the two-degree-of-freedom (TDF) type. The TDF gyro can be either a floatation or a gimballed device; Figure 8 shows the latter.

The gimballed TDF gyro can accept two different input torques, 90° apart. The input axis for one torque (IA_1) is also the output for one pickoff (OA_2); the converse (IA_2 and OA_1) is also true. Therefore two TDF gyros provide four sensing axes, three (X, Y and Z) of which can be controlled by two gyros. The redundant axis is caged or pegged in a closed loop servo condition.

By driving the rotor at the natural frequency of the support gimbals (tuned rotor) a rugged, unfloated gyro system is produced which has the following advantages over other gyro systems:

- reduction in components by 50%
- simplification of test and calibration procedures
- reduced manufacturing and repair costs
- improvement in reliability and mechanical performance
- increased system accuracy
- considerable reduction in size and weight.

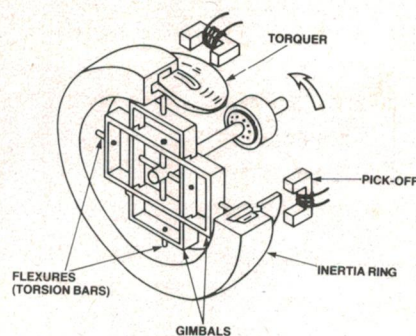


Figure 9. A 'tuned rotor' operational gyro.

An operational gyro of the tuned rotor type is shown in Figure 9. The rotor, which consists of a ring magnet encased in a soft iron return path fitted with a circumferential slot, is driven by a 400 Hz supply. The torquer (torque elements) comprises four coils, wound on a cylindrical former attached to the case. The coils in turn fit into a slot in the inertial ring where they can influence its magnetic field. The pickoffs are also magnetic devices consisting of differential transformers, which are influenced by the flux in the inertial ring. This method of pickoff can detect angular displacements in the order of 0.1 seconds of arc. To reduce non-magnetic, unwanted torques, the gyro operates in a low pressure hydrogen atmosphere.

Platform stabilisation

The gyros, accelerometers and associated equipment are known as the 'inertial platform' or 'platform' to distinguish them from the electronic, electrical and fixed components which form the rest of an INS installation.

The rotating gyro assembly possesses angular stability; the accelerometers do not, and therefore must be stabilised. This is achieved by mounting the gyros and accelerometers to a common platform. As the gyro case is attached to the same assembly as the accelerometers, their angular movement reflects the displacement between the gyro case and the rotor. These changes in movement are detected and held to a tolerable level, which in turn stabilises the platform. The application of this technique is detailed in Figure 10; however, the circuit shown is for one axis (X) only.

As the signal detected by the pickoff varies, the demodulator provides a drive signal of the opposite polarity to the platform drive motor, which adjusts the platform attitude accordingly. Over-correction is prevented by secondary servo loops.

Stabilisation in three axes (X, Y and Z) requires two gyros and three accelerometers, one in each axis. However, the Z-axis is generally used to generate

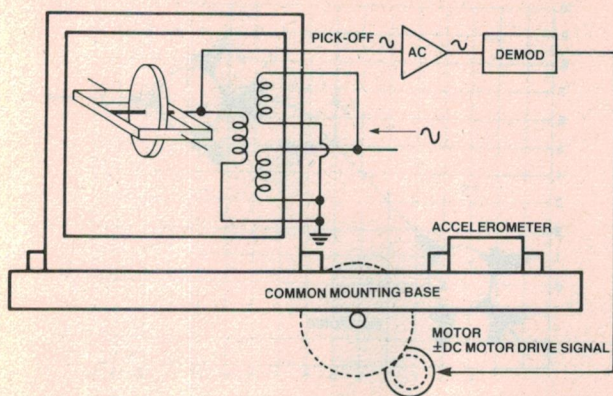


Figure 10. Gyro-to-platform stabilisation loop, general arrangement.

platform correction terms and in airborne systems to provide altitude information, whereas the X and Y axes are used to generate navigational information.

Platform corrections

When used for terrestrial navigation, an INS is subject to two major forms of error, coriolis error and centripetal error. Coriolis error is due to the rotation of the Earth, which acts upon the gyros, and centripetal error is brought about when the platform moves over the surface of the Earth between poles.

Compensation for coriolis error is achieved by the application of the Earth's rotation rate (approximately 15 degrees of arc per hour at the equator) to the platform. However, the rate varies with respect to latitude angle and is produced from a resolution of vectors, as shown in Figure 11. These vectors are calculated from the following equation:

$$\begin{aligned}\text{Horizontal vector} &= \Omega \cos \phi \\ \text{Vertical vector} &= \Omega \sin \phi\end{aligned}$$

where omega Ω is full Earth rate (15 degrees) and phi ϕ is latitude angle.

Centripetal correction is only applied to the horizontal (X and Y) axes of the platform, as the vertical (Z) axis is insensitive to centripetal accelerations.

If the platform is held tangential to the curvature of the Earth, moves at a constant velocity, shares the Earth's centre of gravity, and moves over a great circle path (one whose axis passes through the centre of the earth), then the X and Y axes will sense the path of travel as a straight line and not require centripetal correction. However, any other path requires correction, which takes the form of a constant southward acceleration applied to the X and Y axis accelerometers. This correction is required, as the system, which is north-seeking, possesses an inherent northward drift when moving. The net result of the drift and correction is a zero velocity component applied to the accelerometers. The correction is generated within the system computer.

A servo system in conjunction with

the system computer simulates the effect of the platform sharing the Earth's centre of gravity. This is called the Schuler pendulum effect, after the scientist who demonstrated the effect of Earth rotation.

To allow for radial accelerations in the Z-axis, the accelerometer is corrected for ground velocity over a curved surface given by the following equation:

$$\text{radial acceleration} = \frac{\text{velocity}^2 \times \text{gravity}}{\text{Earth's radius}}$$

The necessary functions are generated within the system computer.

System alignment

The operation of an inertial navigation system uses the mathematical integration of acceleration to obtain velocity and positional information. To implement any integration process, an accurate initial reference must be established, in this case velocity and position. The establishment of these references is called system alignment.

The alignment procedures entail the matching of platform and computer axes to external or internal known references. External references can be terrestrial, celestial or inertial. Terrestrial reference systems employ surveyed lines, benchmarks, plumb-bobs and

bubble gauges. These devices can provide level accuracies in the order of ten seconds of arc and heading accuracies to three minutes of arc.

Celestial reference systems obtain information from star trackers and radio sextants. Accuracies are similar to those for terrestrial devices.

Inertial references comprise some form of portable inertial platform. However, accuracies are only as good as the last equipment calibration, which could have been months previous to their use.

An external reference system uses some form of interface unit to connect to the INS under test. These interfaces take the form of optical couplers, synchro devices, electrical transducers, digital-to-analogue or analogue-to-digital converters, or some form of logic conversion circuit.

Internal or self-alignment systems use the sensors on the platform to sense the physical deviation from a fixed position to align the platform using its servo systems.

To determine the orientation of a three-axis, right-angled co-ordinate system (INS), at least two reference vectors are required. The Earth's spin and gravitational vectors are used for this purpose when implementing a self-alignment procedure. Using these vectors reduces computer requirements because the accelerometer outputs do not require resolution into gravity and vehicle acceleration components. Also, as the accelerometers and gyros share the same platform, their relative positions do not require computing.

A self-alignment is divided into three inter-related modes. The first is coarse alignment, or caging, followed by fine alignment, or levelling, culminating in an operation called gyro-compassing.

Coarse alignment involves slaving the gyro gimbals to their own servo output signals, or to some external source ▶

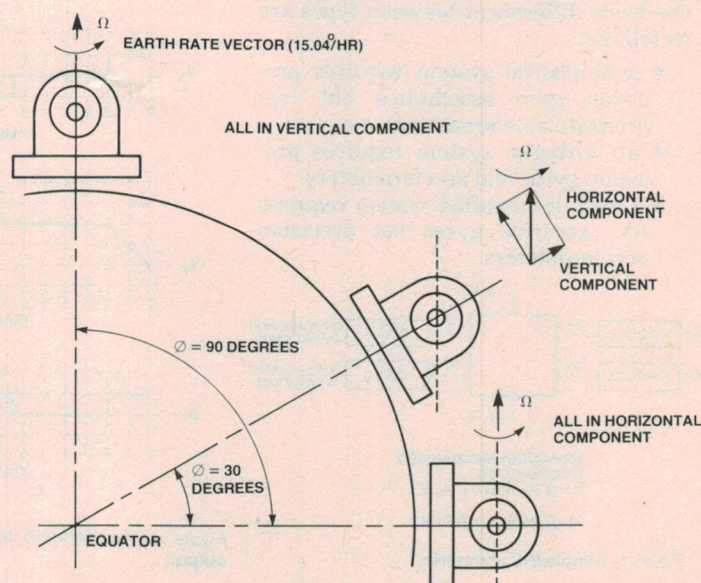


Figure 11. Resolution of vectors in coriolis correction.

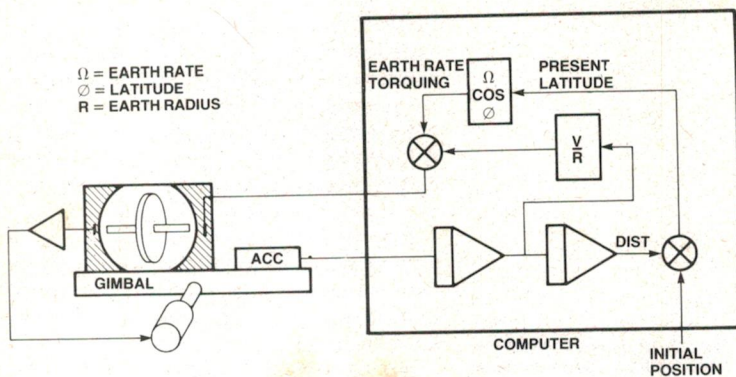


Figure 1. Basic INS diagram.

Radio navigation aids are normally used for this purpose. These include Omega, Decca, LORAN and distance measuring equipment (DME).

A basic inertial navigation system is shown in Figure 1 and operates as follows.

The accelerometer output (1) is integrated to a velocity function (2). A second integral produces distance travelled (3). This is added to initial position (4) and updates the present latitude (7). Present latitude is processed to provide Earth-rate torque (8). The velocity function (5) is processed to give transport torque rate (6). This and Earth-rate torque are added to generate gyro correction (9). This quantity causes the gyro rotor (10) to tilt with respect to the case and generate an output signal (11), which in turn is amplified to drive the gimbal motor (12). The gimbal motor moves the gimbal (13) in proportion to the Earth-rate and transport-rate terms, providing platform corrections.

Inertial navigation systems are fitted to military and commercial aircraft, surface ships of all types, submarines, hovercraft and space vehicles. To cater for this variety of system applications, the basic differences between types are as follows:

- a shipborne system requires precision gyro assemblies but less accurate accelerometers.
- an airborne system requires precision gyros and accelerometers.
- a missile-installed system requires less accurate gyros but precision accelerometers.

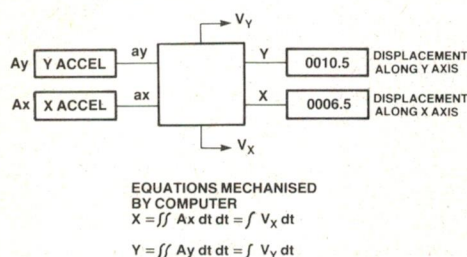


Figure 3. Simple INS computer.

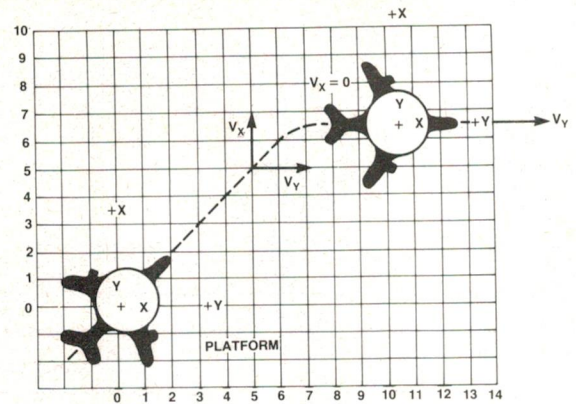


Figure 2. Two-axis navigation grid.

System description

An inertial navigation system can be divided into the following sections for the purposes of description:

- simplified INS operation
- accelerometers
- gyros
- types of gyro
- platform stabilisation
- platform corrections
- system alignment
- system computer.

Simplified INS operation

The objective of all forms of navigation is to guide a vehicle from one point to another, relative to a reference system. Figure 2 shows a grid reference system upon which the course of an aircraft has been placed, and provides vector representation of the movement of the X and Y-axis accelerometers.

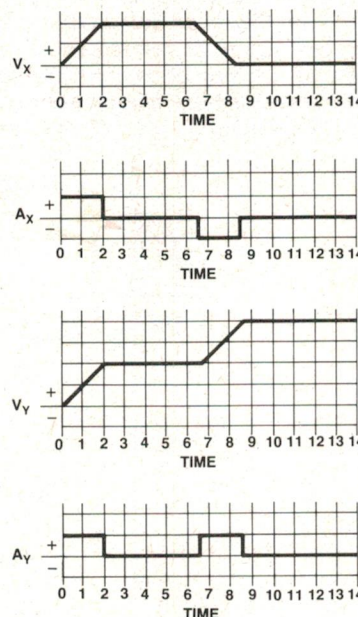


Figure 4. Acceleration input and displacement output.

Figure 3 illustrates a simple form of computer capable of resolving equations relating to vehicle displacement. Figure 4 presents a graphical indication of acceleration input and displacement output.

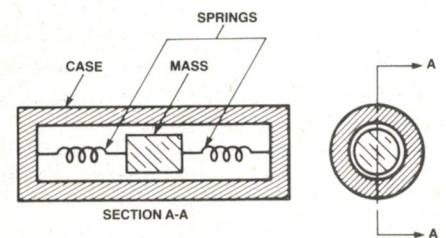


Figure 5. General arrangement of a slug-type accelerometer.

Accelerometers

A basic accelerometer, shown in Figure 5, comprises a precision-machine slug, or 'proof mass', which slides in a frictionless tube when lateral movement is detected. The slug is retained in the 'null' or zero position by springs. The magnitude of slug movement is a measure of acceleration, which is converted to an electrical signal by a 'pickoff unit'.

An alternative type of accelerometer, which operates on the pendulum principle, is detailed in Figure 6. This device provides displacement data in angular rather than linear form.

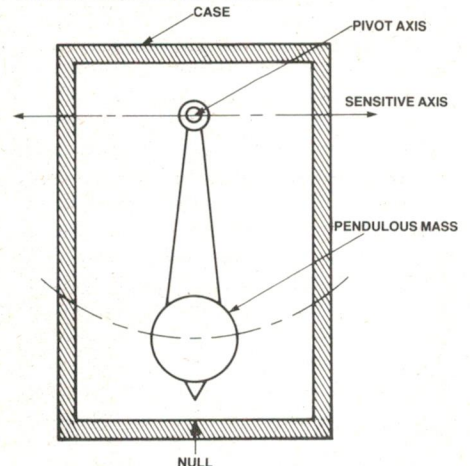


Figure 6. General details of a pendulum-type accelerometer.

The relative movement of the mass in most accelerometers is restrained and therefore small, so small that it can only be detected by electrical measurement (via the pickoff). The pickoffs comprise a pair of primary coils, mounted to the instrument case. A secondary coil, attached to the mass, sits between the primary coils in the null position.

An excitation supply, applied to the primary and secondary coils, is arranged to provide zero output at the null. Under acceleration, the secondary coil moves towards one or the other primary coils and changes the phase and voltage output. The phase relationship between primary and secondary coils determines the sense of the acceleration (plus or minus) while the amplitude is proportional to acceleration magnitude.

In a typical application, the accelerometer output is amplified and used to drive a phase sensitive demodulator. The dc output signal is used to reset the mass to null, while generating a sense and magnitude input signal to the system computer.

This action is called torque rebalancing, which instead of measuring mass displacement, measures the current required to return the mass to the null position. A torque rebalancing arrangement is shown in Figure 7.


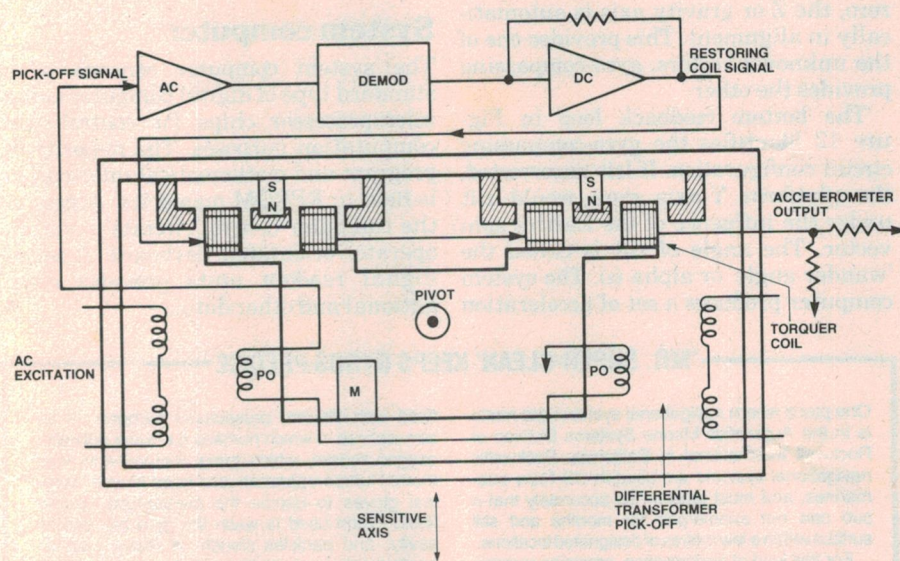


Figure 7. Schematic arrangement of a torque rebalancing servo.

Both types of accelerometer exhibit natural oscillatory characteristics, which are neutralised by immersion in damping fluid, carefully matched to the density of the mass to achieve neutral buoyancy. Other mechanical components reduce vibration and component instability to provide accuracies down to $10^{-6}g$.

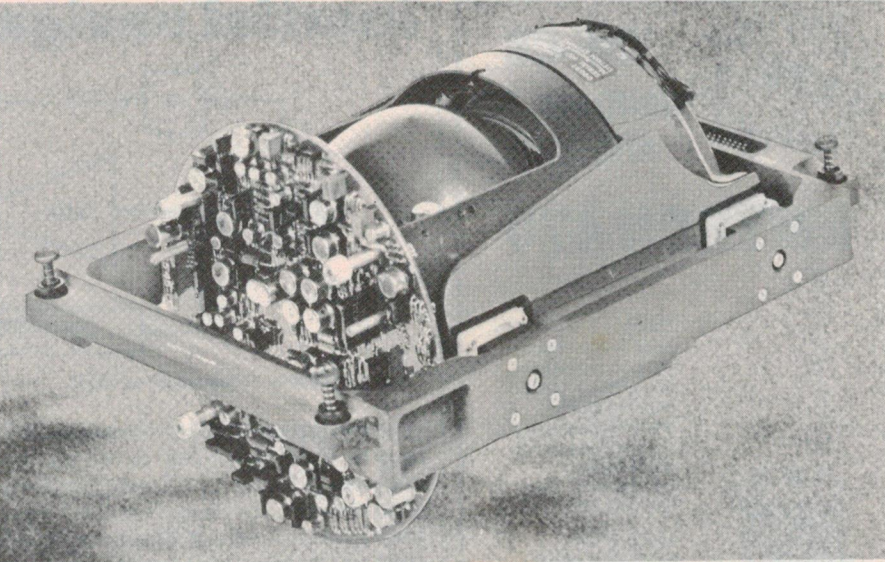The latest types of accelerometer employ ceramic discs and capacitive pickoffs incorporated in a bridge circuit



A gimbal system, from Litton. This unit contains a cantilevered gimbal set comprising two non-floated, two-axis, precession-tuned rotor gyroscopes and three flexure-supported, non-floated, torque-to-balance accelerometers.

to detect acceleration displacement, the amount of electrical imbalance indicating the magnitude of the sensed acceleration. This signal is then used to operate a coil, called a force motor, to reset the ceramic discs. The reset current required by the force motor, or 'torquer', provides a computer input in a similar manner to the inductive type of accelerometer.

turn) and skopios (to see or view). A German, Dr. Kaempfe, produced the first marine gyro compass, followed three years later by Elmer Sperry, who set the standard for gyro compass design until the introduction of INS in the 1950s. A modern gyro contains the following items:

- wheel assembly
- gyro motor
- spin bearings
- float elements
- signal pickoffs
- torque elements
- lead-in wires
- magnetic shields
- case.

The majority of the angular momentum of a spinning gyro is provided by the wheel assembly, which is a compromise of design factors. These include weight, rotation speed, diameter and construction material. Gyro wheels are usually manufactured of beryllium, to take advantage of its mechanical stability. However, titanium and stainless steel are used for some applications.

A gyro wheel is driven by a polyphase synchronous hysteresis motor, which is excited by a high frequency supply in order to achieve the required operating speed. The relative inefficiency of the motor is overcome by saturating the rotor to produce a virtual permanent magnet motor. However, the hysteresis motor has the ability to maintain, at synchronous speed, any load that it can accelerate from a dead stop.

The spin bearings are either long-life conventional ball bearing assemblies or gas-lubricated bearings. The latter eliminate metal-to-metal contact between surfaces once the device is operating. To achieve this state, the bearings run in a bath of gaseous lubricant, ▶

However, the capacitive device uses fewer components and is much smaller.


Gyros

In 1750, a Swiss mathematician called Euler studied the behaviour of spinning rotors and documented his findings. A century later, a Frenchman, Foucault, constructed a device to demonstrate the Earth's rotation. He called it a gyroscope, from two Greek words — gyros (to



**UHF-CB
HAND-HELDS
ARE HERE**

EMTRON 470

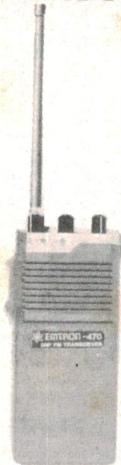

This remarkable little hand held is ideal for the man on the land, in the saddle, in a truck or on walkabout. Ideal for commercial or semi commercial as well as hobby applications. So get an EMTRON-470.

FEATURES:

- Repeater offset
- 6 Channels
- 1 Watt output
- Condenser mic
- Nicad battery
- One XTAL per Ch.

\$299

EMTRONICS

649 George St., Sydney NSW 2000
Ph: (02) 2110531 P.O. Box K21
Haymarket NSW 2000.

**Australians
are dying
younger
from heart
disease.**



National Heart Foundation.

Inertial navigation systems

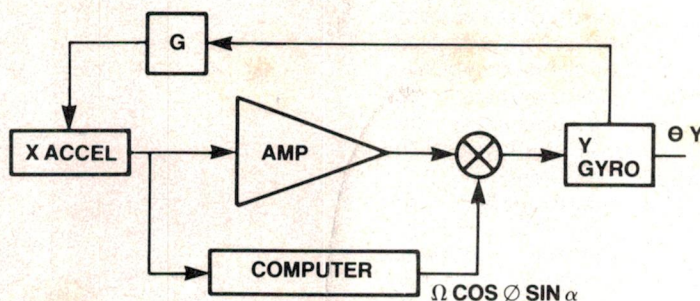


Figure 12. System alignment servo loops.

possessing a particular orientation with respect to the vehicle in which the platform is fitted. The caging sequence is automatically implemented by a timing circuit and lasts for about 30 seconds after system switch-on.

Fine alignment, together with gyro-compassing circuit configuration, is shown in Figure 12. The top feedback loop identifies levelling. This involves setting the pendulums of each accelerometer to the null position, each pendulum at 90° with respect to the other two. This is implemented by connecting the X-axis accelerometer output, via a function generator (G), to the Y-axis gyro and vice-versa. When the errors between the X and Y axes are zero, the Z or gravity axis is automatically in alignment. This provides one of the unknown vectors; gyro-compassing provides the other.

The bottom feedback loop in Figure 12 identifies the gyro-compassing circuit configuration. If left uncorrected, the platform Y-axis gyro would tilt under the influence of the Earth's spin vector. The angle of tilt is called the 'wander angle' or alpha (α). The system computer produces a set of acceleration

corrections to the Y-axis gyro for a range of values for alpha, using a modification of the coriolis correction information detailed in Figure 11. The acceleration correction is given by the following equation:

$$\text{acceleration correction} = \cos \phi \sin \alpha$$

When the output of the X-axis accelerometer is zero, the platform has been aligned in the present position and no further system alignment is required. The Y-axis gyro and X-axis accelerometer are then connected in their normal operational configurations (X-axis accelerometer with X-axis gyro).

System computer

The system computer consists of a standard type of digital computer using microprocessor chips for control and computation purposes. The majority of program and mathematical information is held in EPROM memories. Access to the computer control circuits is via an operator-orientated keyboard. A set of digital readout units provides navigational and other data.

'MR. SUPER-CLEAN' KEEPS GYROS PRECISE

One place where navigational systems are made is in the Autonetics Marine Systems Division of Rockwell International in California. Rockwell's navigational systems are used in US Navy submarines, and most function so accurately that a sub can run submerged for months and still surface within a few metres of designated locations.

For this kind of performance, precision requirements of the gyros are immense. The heart of the gyros is a rotor consisting of a ball which must be perfectly round to within four millionths of an inch — that's about the width of a sliver of human hair split lengthwise into a thousand pieces. The ball spins in a cavity whose sides it clears by one-eighth of a human hair, which means that a microscopic particle can destroy its accuracy.

According to Bill Hanebaum, division manager of advanced manufacturing technology at Rockwell, "Human cleaning, regardless of the technician's dedication and the completeness of the engineered manual procedure, had proved to be an inconsistent operation in the production of our precision navigational gyros."

The gyros have to be cleaned in a chamber


filled with filtered, pressurised nitrogen — an atmosphere in which humans can work only with oxygen masks, which bring contaminants with them. Human operators also need to wear surgical gloves to handle the pressurised, filtered liquid Freon used to wash the gyro ball and its cavity, and particles slough off these, causing contamination, regardless of the quality of the gloves.

Bill Hanebaum's answer to these difficulties was the invention of 'Mr. Super-Clean', a robot specially designed by another Rockwell division to meet the super-accurate needs of gyro production. The robot needs no oxygen mask or gloves, and its arm can move vertically and horizontally, can extend, rotate, and open and close its grippers. All movements are controlled to within thousandths of an inch, and the robot can remove particles invisible to the human eye which could nevertheless affect the accuracy of the gyro.

An AIM 65 microcomputer, manufactured by another Rockwell organisation, controls the robot, providing a control system for under \$1000 while still meeting designers' specifications.

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. (03) 489-8131

ETI-918 PHOTOPHONE

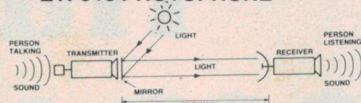

A simple, effective, easy to build light beam transceiver. You can use any light source, a torch, the sun or a laser.

Now you can put your Series 5000 amp in your vehicle! Or run the ETI-498/499 PA amp from a 12 V battery. Endless uses for this handy inverter. Will provide up to 200 W or more.


This phenomenal project has features found on no other speech synthesiser available! It comes complete with basic vocabulary chips and interface circuitry so you can hook it up to any computer — or even drive it from switches. Just add 12 V and a speaker. Speech clarity is best available.

[illegible]

TO ORDER: Heavy items sent Comet Freight on. Mail Order phone 481-1436. Wholesale Customers phone: RITRONICS WHOLESALE 489-7095

Mail Orders to P.O. 235 Northcote 3070 Minimum P&P \$2. Add extra for heavy items, registration and certified mail

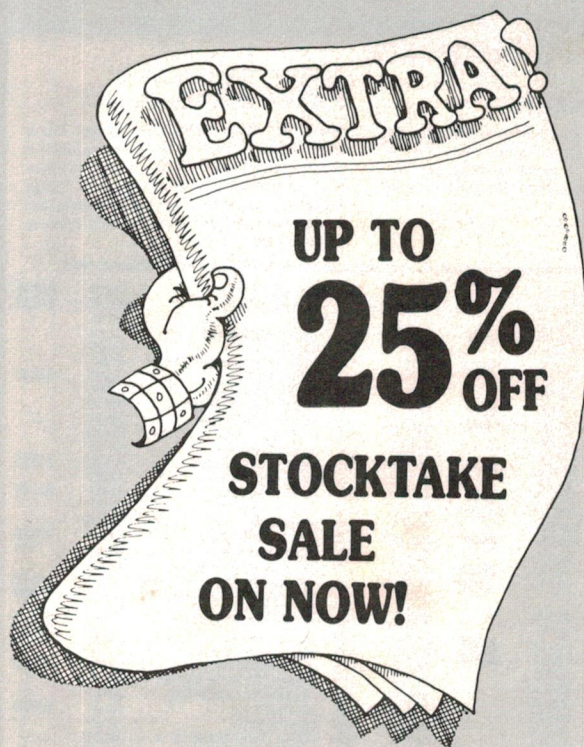Prices spec. subject to change without notice.



THE GOOD NEWS FROM



O.K. WIRE WRAPPING
TOOLS
PROTOBOARD KITS
LOGIC KITS
EXPERIMENTER
SYSTEMS
QUICK TEST KITS
TEST EQUIPMENT

CABLE PLUG ASSORTED 14 PIN 16 PIN
WIRE WRAP PINS, I.C. SOCKETS,
CABLE, CABLE PLUGS, SOCKETS
HEADERS ETC

G.I.M. I.C.'s,
MULTIMETERS, DTMF,
CLOCK, TONE, P.B.
DIALER, PLUS MORE.

CRYSTALS

18.432 MHz
2.000 MHz
3.579545 MHz
4.000 MHz
5.06880 MHz
6.000 MHz

ELECTROLUBE
SPRAYS
DIL SWITCHES
RATED 30K M/B
SPST 6 POS
SPST 10 POS
E-Z HOOK TEST
ACCESSORIES &
TEST LEADS
EDGE CONNECTORS
(VARIOUS)
12 KEY KEYPADS,
LEDS, HEATSINKS.

SPACERS, TERMINALS, LUGS, TERMINAL
BOARDS, STAND OFF INSULATION, FEED
THRU INSULATION.

There will be many other items on display, some
could even be classified as antique, but they
could be just what you've been looking for.

No reasonable offer will be refused while stock
lasts.

COME AND SEE US NOW!



GES P/L

99 Alexander St., Crows Nest NSW 2065
Phone: (02) 439 2488

MON-FRI: 8.30-5.30 SAT: 9.30-1.30
Interstate readers send for detailed list.

ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELB, VIC PH (03) 4898131 TELEX-38897


RACK MOUNTING BOXES

19 X 5 1/2 X 12"	- \$45.00
19 X 6 X 10"	- \$39.95
19 X 5 1/2 X 12"	- \$55.00
19 X 7 1/2 X 12"	- \$79.00
19 X 10 X 12"	- \$89.00
SERIES 5000	- \$55.00

CABINET OF 16 DRAWERS


PUT ALL YOUR BITS & PIECES AWAY IN THESE INCREDIBLY CHEAP CABINET OF DRAWERS.

12⁰⁰

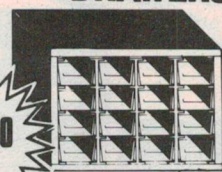

JIFFY BOXES

UB1 - 150 X 90 X 50	- \$1.80
UB2 - 196 X 113 X 60	- \$2.75
UB3 - 130 X 68 X 41	- \$1.50
UB5 - 83 X 54 X 28	- \$.90

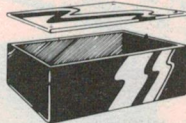

ROD CUTS PRICES ON CANNON CONNECTORS



	1-9	10 UP
LINE SOCKET -	\$2.70	\$2.60
PANEL PLUG -	\$1.70	\$1.60
LINE PLUG -	\$1.60	\$1.50
PANEL SOCKET -	\$2.90	\$2.80
XLR - LNE - 11C -	\$4.20	\$3.90
XLR - LNE - 32 -	\$2.90	\$2.50

ALSO AC POWER CONNECTORS AVAILABLE

HORN SPEAKERS

NOW ONLY 6⁷⁵



PANELMETERS

	1-9	10 +
MUS 0-30V	\$10.00	\$9.00
MUS 0-20V	\$10.00	\$9.00
MUS 0-100uA	\$10.00	\$9.00
MUS 0-10A	\$10.00	\$9.00
MUS 0-50uA	\$6.50	\$5.50
MUS 0-100uA	\$6.50	\$5.50
MUS 0-50uA	\$6.50	\$5.50
MUS VU	\$6.50	\$5.50
MUS 0-20V	\$6.50	\$5.50
MUS 0-1A	\$6.50	\$5.50
MUS 0-1mA	\$6.50	\$5.50
MUS 0-10A	\$6.50	\$5.50



CONNECTORS DB 25

DB25P - PLUG -	
DB25S - SOCKET -	
DB25C - COVER -	
	1-9 10 +
	\$3.90 \$3.50
	\$4.90 \$4.50
	\$2.20 \$1.80

SAVE

ALIGNMENT TOOL SET

2⁹⁵ This month only 1⁹⁵




SOLDERING IRON STAND

5⁵⁰




WELLER SOLDERING STATION

62.50

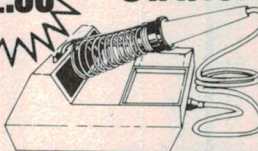

TRANSFORMERS

	1-9	10-19	20+
2851	\$2.90	\$2.50	\$1.90
2155	\$4.50	\$3.90	\$3.30
6672	\$5.50	\$5.40	\$5.10

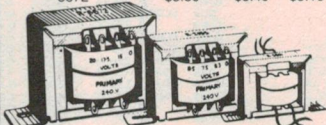

HOOK UP WIRE

3⁷⁵ a roll



MULTITESTERS

YF 370	28 ⁵⁰
YF 303	17 ⁵⁰
YF 10	34 ⁵⁰
	21 ⁵⁰




UNIVERSAL TEST LEAD KITS

4⁹⁵ This month only 3⁹⁵




COMPUTER COOLING FANS

16⁹⁰ This month only 115V 240V 4%

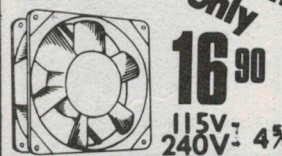

RELAYS

6 AMP CONTACTS PCB MOUNTING	
12V SP	\$4.50
12V DP	\$5.50
24V SP	\$4.90
24V DP	\$5.90

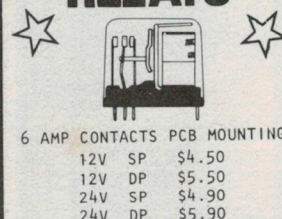

COMPONENT SPECIALS

BF469	- \$.90	
BF470	- \$.90	
2114	- \$1.95	BD 139 - .45c
4116	- \$1.95	10 FOR \$4.00
2703	- \$4.50	BD 140 - .45c
2716	- \$5.50	10 FOR \$4.00
2732	- \$9.50	4MHZ XTAL \$2.00
TP50	- \$1.10	

BATTERY SNAPS A STEAL AT 10c EACH

3AG FUSE HOLDER 50c
2AG FUSE HOLDER 50c

	1-9	10-99	100-999	1000
IN4148	.06c	.05c	.04c	.03c
IN4001	.06c	.05c	.05c	.05c
IN4002	.06c	.05c	.05c	.05c
IN4003	.06c	.05c	.05c	.05c
IN4004	.07c	.06c	.05c	.04c
IN4005	.09c	.08c	.07c	.06c
IN4006	.10c	.09c	.08c	.06c
IN4007	.12c	.09c	.08c	.07c

2.2 MF POLY	
400V CAPS	- .90c
555	- .25c

10 For \$ 2.20	
74C926	\$ 5.00
BC547	100 For \$ 9.00
BC558	100 For \$10.00
BC559	100 For \$10.00
BC548	100 For \$ 9.00



COMPUTERS OF THE DECADE Sorcerer Mk II - Dick Smith System 80 'Ask Rod for a price' ?



We have the cheapest price on Philips speakers

Please debit my Bankcard ET19/82/1

Bankcard No. _____

Expiry Date _____

Name _____

Signature _____

MAIL ORDERS: P.O. BOX 235 NORTHCOTE, VIC. 3070
Min. P&P \$2.00. Mail Order Enquiries (03) 481 1436.

Bill Edge's

ELECTRONIC AGENCIES

115-117 Parramatta Rd. Concord 2137
(Corner Parramatta Rd & Lloyd George Ave)
Telephone (02) 745 3077 (two lines)
117 York St. Sydney Phone 29 2098

bankcard
welcome here

TRADING HOURS
BOTH STORES
Mon-Fri 9am-5.30pm
Saturday 9am-12pm

COMPONENTS

Mail Orders:
PO Box 188
Concord
2137

MAIL CHARGES
\$5.99
\$10.24
\$20.49
\$50.99
\$100 or more

what else do we carry? HI-FI ★ KITS ★ TEST EQUIPMENT ★
All prices correct and goods in stock at time of going to press. Please phone to check current availability

SEPTEMBER SPECIALS

CAPACITORS

Strictly limited quantities. Trade not supplied.

CAT. No.	Normal Price	Special Price
RE268 2uf Greenpac 100V	\$1.25	30c
RE505 10uf 16V Electrolytic	30c	5c
RE507 10uf 16V Electrolytic	30c	5c
RE515 47uf 16V Electrolytic	25c	8c
RE520 47uf 25V Electrolytic	30c	10c
RE525 10uf 16V Electrolytic	35c	10c
RE535 22uf 16V Electrolytic	40c	20c
RE540 22uf 25V Electrolytic	60c	25c
RE545 100uf 16V Electrolytic	80c	25c
RE550 22uf 16V Electrolytic	\$1.00	40c
RE552 1uf 63V Electrolytic	20c	5c
RE555 47uf 25V Electrolytic	30c	15c
RE558 22uf 25V Electrolytic	\$1.50	30c
SE100 DPT on/off Rotary switch	\$3.00	50c
CE2002 Turntable Hinges (pair)	85c	45c
RE123 20K Linear Pot		45c

6 HOUR TURNAROUND ON MAIL ORDERS

2 STORES

CONCORD AND SYDNEY

WE ARE THE KIT SPECIALISTS

OPEN THURSDAY TILL 8 pm

SPEAKERS

CE2003 Tweeter Foster CN C050N08	4.50
CE2005 Tweeter Phil DME AD01A078	13.95
CE2010 Tweeter Phil DME AD01A078	13.95
CE2012 Tweeter Phil DM AD01A0578	16.95
CE2013 Tweeter Phil DM AD01A078	15.95
CE2014 Tweeter Phil DM AD01A078	15.95
CE2015 Tweeter Phil DM AD01A078	15.95
CE2024 Tweeter Plesio HFI KSN1005	16.00
CE2026 Tweeter Plesio HFI KSN1016	18.50
CE2028 Tweeter Plesio HFI KSN1016	18.50
CE2042 Tweeter Foster RIBN ELI0708	18.50
CE2065 Mid-range Phil CN AD50605Q8	25.95
CE2070 Mid-range 45 in Pioneer 102	6.50
CE2072 Mid-range Phil C050M06	4.50
CE2078 Mid-range Phil C050M06	4.50
CE2079 Mid-range Phil C050M06	4.50
CE2082 Mid-range Phil DM AD01A0578	16.95
CE2085 Mid-range Phil DM AD01A0578	16.95
CE2100 Woofer 4 in Magnavox 4W	17.50
CE2105 Woofer Phil 5 in AD5060W8	17.50
CE2108 Woofer Phil 5 in AD5060W8	17.50
CE2110 Woofer 4 in Phil C200L09	10.50
CE2111 Woofer 4 in Phil C200L09	10.50
CE2113 Woofer 4 in Phil C200L09	10.50
CE2115 Woofer 4 in Phil C200L09	10.50
CE2117 Woofer 4 in Phil C200L09	10.50
CE2119 Woofer 4 in Phil C200L09	10.50
CE2120 Woofer 4 in Phil C200L09	10.50
CE2121 Woofer 4 in Phil C200L09	10.50
CE2128 Woofer 4 in Phil C200L09	10.50
CE2135 Woofer 4 in Phil C200L09	10.50
CE2300 W/range 4 in Phil C100K03	8.95
CE2307 W/range 10 in Phil C100K03	9.50
CE2315 W/range 10 in Phil C100K03	9.50
CE2325 W/range 8 in Economy Speaker	7.50
CE2335 W/range 8 in Magnavox 3W	20.95
CE2345 W/range 10 in Magnavox 10W	21.95
CE2355 W/range 12 in Magnavox 12W	27.00
CE2400 Kit Coral 85A1 3 Way Speaker	75.00
CE2410 Kit Coral 125A1 3 Way Speaker	125.00
CE2420 Kit Coral 125A1 3 Way Speaker	125.00
CE2422 Kit PAS100 P/Less 3/12	379.00
CE2424 Kit PAS50 P/Less 3/10	225.00
CE2426 Kit PAS50 P/Less 2/8	199.00
CE2430 Kit ETIA000/14 Way Speaker	499.00
CE2440 Kit ETIA000/23 Way Speaker	380.00
CE2445 Bookshelf Speakers	24.95
CE2450 Cabinets Suit 12A1 Pair	109.00
CE2455 Cabinets Suit P/Less 12"	259.00
CE2470 Cabinets Suit 4000/1 Pair	280.00
CE2480 Cabinets Suit 4000/2 Pair	310.00
CE2494 X/over 2 Way 2K/4K XOI	5.50
CE2515 X/over 3 Way 2K/4K XOI	9.50
CE2516 X/over 3 Way 2K/4K XOI	9.50
CE2520 X/over 3 Way 2K/4K XOI	9.50
CE2521 X/over 3 Way 2K/4K XOI	9.50
CE2522 X/over 3 Way 2K/4K XOI	9.50
CE2609 X/over 3 Way 2K/4K XOI	9.50

KITS

Don't just sit there, build something!
When you purchase a kit from Electronic Agencies you are assured that:

- All components are top quality, prime spec
- Instructions are included in ALL kits
- Free with kits over \$20. Bill's Kit Constructor Guide
- Kits are ex stock, not made up to order
- All parts will be IN the kit it is extremely rare that parts are missing
- Electronic Agencies' kits are the best
- We are the kit specialists!

KE0110 KIT ET048 Buzz Board	4.90
KE0120 KIT ET048 Basic Amplifier	5.90
KE0150 KIT ET048 Electron Siren	5.90
KE0180 KIT ET048 Led Dice	7.50
KE0190 KIT ET048 Led Dice	7.50
KE0195 KIT EA 12/81 Flashing Leds	15.50
KE0199 KIT EA 5/82 Touch Switch	12.00
KE0200 KIT ET1607A Bomb & Explon.	11.95
KE0210 KIT ET1607B Siren & Whistl	10.95
KE0220 KIT ET1607C Phaser & Alarm	9.95
KE0230 KIT ET1607D Phaser & Explon.	10.95
KE0240 KIT ET1607E Gun Shot	11.95
KE0250 KIT ET1607F Propeller	22.95
KE0260 KIT EA 12/80 Selectator	22.95
KE0270 KIT EA 11/81 Photon Torped	26.50
KE0280 KIT ET1492 Sound Blaster	22.95
KE0290 KIT EA 7/81 Lonty Pools	19.95
KE0300 KIT EA 11/81 Sandglaz	26.50
KE0310 KIT EA 5/81 PC Birds	14.95
KE0320 KIT EA 7/81 Steam T Whistl	15.00
KE0330 KIT EA 1/82 Metronome	17.50
KE0340 KIT ET1608 Tuning Fork	23.00
KE0350 KIT ET1608 Light/Sound Flash	25.00

NEW KITS

D.C. Inverter.


KE1700 \$30.00 see ETI Sept 82

KE1075 KIT ETI 469 Drum Machine	10.95
KE1076 KIT ETI 469 Sequencer	10.95
KE1080 KIT EA 2/81 Fuzz Box	9.95
KE1085 KIT HEI21 Scratch Hiss Flash	5.95
KE1090 KIT ETI225V Flasher	12.00
KE1095 KIT EA 5/81 Speed Sentry	15.00
KE1100 KIT ETI724 U/W Wave Oven DT	14.95
KE1110 KIT EA 2/82 Cten Voice	18.95
KE1120 KIT EA 3/81 La Gong D/Bell	15.00
KE1125 KIT ETI259 Versatile Timer	44.50
KE1130 KIT EA 4/82 Voice Op Relay	15.50
KE1140 KIT HEI26 FM W/Less Mic	7.50
KE1155 KIT EA 4/82 Voice Cancellor	20.00
KE1400 KIT ETI467 Mixer Preamp	29.50
KE1410 KIT EA 5/80 TV CRO Adapter	39.00
KE1420 KIT EA 2/82 Cten Voice	45.00
KE1450 KIT ETI449A Metal Detector	35.00
KE1460 KIT ETI500 Metal Detector	199.00
KE1470 KIT EA 5/81 Intra Red P. CR	39.00
KE1485 KIT EA 8/79 M/Head AMP MK2	35.00
KE1500 KIT EA 10/81 Windspeed MTR	44.50
KE1510 KIT EA 1/82 Wind Rain Ind	12.95
KE1520 KIT ETI524 Led Voltmeter	12.95
KE1530 KIT ETI084 Car Alarm	12.50
KE1700 KIT ETI330 Car Alarm Del	29.50
KE1770 KIT EA 5/81 Engin Analys	53.00
KE1810 KIT EA12/81 Frequency Mit	119.00
KE1825 KIT EA 12/81 Pre Scaler	29.50
KE1875 KIT EA 11/79 Trans Attn Ign	35.00
KE1880 KIT EA 10/81 Buss Amp	45.00
KE1895 KIT EA 6/81 Benchmate	45.00
KE1877 KIT EA 11/81 Low OHMS Metr	45.00
KE1880 KIT EA 1/82 Epm Program	52.50
KE1900 KIT ETI438 Led Level Mtr	19.95
KE1950 KIT EA 4/80 Vol Regulator	9.95
KE1975 KIT ETI471 P/Amp Control	47.90
KE2050 KIT EA 10/80 Status Timer	45.00

AUDAX SPEAKER KIT

As reviewed in EA this month.
Speaker kit includes 2 200 mm bextrene coned woofers and 2 25 mm dome tweeters and crossovers.
Cabinet kit includes 2 enclosures with input panels, grills and badges.
Other manufacturers who have Audax speakers include: Monitor Audio, Mission, Meridian, IMF, Borda, KFF and AMW.
CE2450 Speaker Kit \$199.00 pair.
CE2490 Cabinet Kit \$99.50 pair.
Comet freight \$10 anywhere

KE2075 KIT ETI455 Ldspk Protect	26.00
KE2080 KIT ETI445 Gen Pur Preamp	8.50
KE3000 KIT EA 7/81 Electric Organ	68.00
KE3005 KIT EA 8/81 Color Chaser	89.00
KE3010 KIT ETI499 Guit Amp 150W	99.00
KE3015 KIT ETI498 P.A. Preamp Amp	109.00
KE3020 KIT ETI480 P/Supply	19.50
KE3030 KIT ETI480 50W Module	19.50
KE3040 KIT ETI480 100W Module	25.00
KE3050 KIT ETI480 300W Module	69.50
KE4010 KIT Panel Mtr 3.5 Dig Led	29.90
KE4020 KIT ETI572 Meter	12.50
KE4030 KIT EA 9/80 Die Capac Mtr	59.90
KE4040 KIT EA 3/82 Dig Cap Mtr	59.90
KE4050 KIT EA 3/82 Dual Pwr Suppl	89.50
KE4060 KIT EA 6/80 Inverter	195.00
KE4070 KIT EA 9/81 Audio Oscillat	68.00
KE4080 KIT EA 4/82 Function Gener	85.00
KE4090 KIT EA 11/80 Wideband Rn	75.00
KE4100 KIT EA 11/80 Wideband Rn	64.80
KE4110 KIT EA 2/81 Graphic Amp	119.00
KE4120 KIT EA 1/81 Mosfet AMP 50W	169.00
KE4300 KIT ETI477 Mosfet Module	59.90
KE4310 KIT ETI480 50W Module	19.50
KE4320 KIT ETI480 100W Module	25.00
KE4330 KIT ETI480 300W Module	69.50
KE4340 KIT ETI478 Movcoil Preamp	19.50
KE4400 KIT ETI478 Movement Preamp	18.50
KE4500 KIT ETI480 50W Module	19.50
KE4510 KIT ETI480 100W Module	25.00
KE4520 KIT ETI480 300W Module	69.50
KE4530 KIT ETI480 50W Module	19.50
KE4540 KIT ETI480 100W Module	25.00
KE4550 KIT ETI480 300W Module	69.50
KE4560 KIT ETI480 50W Module	19.50
KE4570 KIT ETI480 100W Module	25.00
KE4580 KIT ETI480 300W Module	69.50
KE4590 KIT ETI480 50W Module	19.50

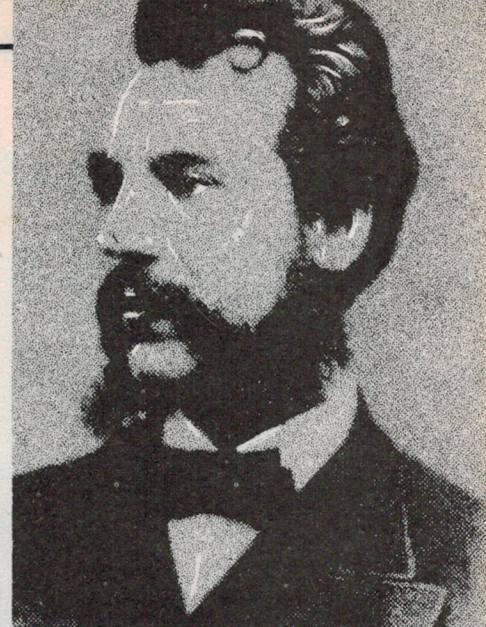

Bell, inventor of the photophone, pictured in 1876, the year he patented the telephone.

Build a 'photophone' light beam transceiver

Unlike the telephone, the photophone is probably Alexander Graham Bell's most obscure invention. Instead of wires, you can talk on a beam of light. This modern — solid state! — version is simple to build and remarkably effective.

Phil Wait
William Fisher


A **PHOTOPHONE** is a device for sending voice signals along a light beam. The word 'photophone' dates from 1880, when Alexander Graham Bell coined it to describe his own light-beam communication system. At his death in 1922, Bell was still convinced that the photophone was his most important invention, more important even than the telephone, which by that time had spread into a worldwide network.

However, the world in general disagreed with Bell and went ahead with communication systems using wires or radio waves as carriers, in preference to light waves. (The development of fibre optics may reverse this trend, but that's another story.) The photophone was forgotten by everyone except a few historians of science.

In the interests of nostalgia and entertainment we have revived this ancient invention, using some modern electronics instead of the cumbersome and unreliable modulation and detection equipment that Bell was forced to use. (He was working in the pre-electronic age, nearly thirty years before triode valves were invented and seventy years before transistors.)

The principle

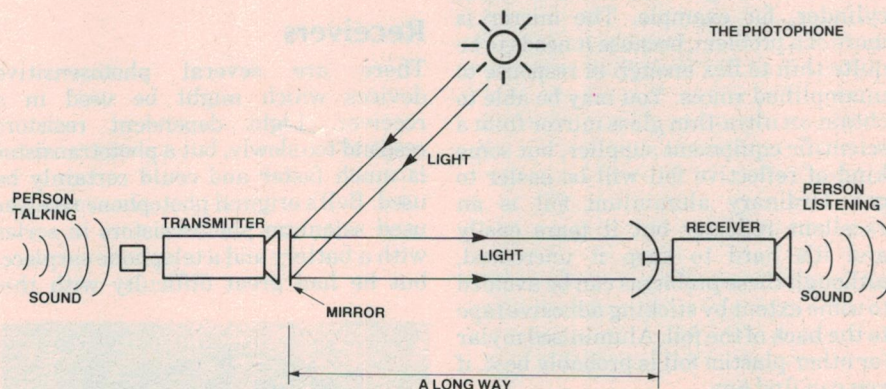The basic principle of the photophone is that a normally flat mirror is made to



Illustrating the basic principle of the photophone.


flex slightly by sound waves impinging on it. A light beam is reflected off the mirror and aimed at a photosensitive receiver. As the mirror is flexed by the sound waves it becomes alternately convex and concave, which means that the beam reflected onto the receiver becomes alternately wider and narrower, in time with the sound wave. The total number of photons in the light beam is not altered by these changes in its width, but the fraction of that energy which falls on the receiving surface does vary (providing the beam is always wider than the receiver). So the intensity of the light received varies with the width of the light beam, which in turn varies with the curvature of the mirror,

which is caused by the pattern of sound waves hitting it.

The variations in light intensity at the receiver can be converted into an electrical signal which drives a loudspeaker via an amplifier to reproduce the sounds originally produced at the transmitting end. The whole arrangement is a kind of amplitude modulation of the light beam, with the mirror acting as the modulator and the photosensitive surface acting as the demodulator.

Transmitters

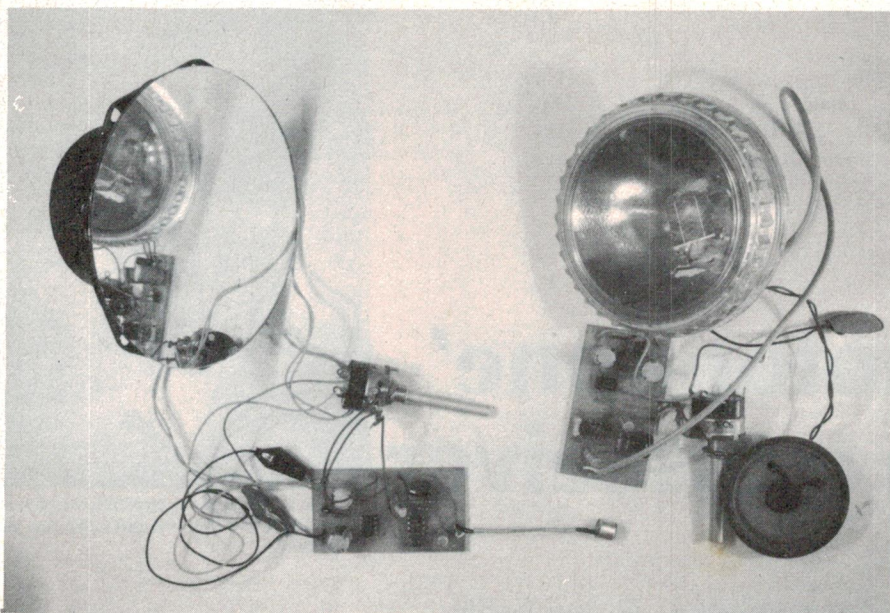The first problem is to make the mirror flex in time with the sound wave. Bell's original mechanism for doing this was very simple. He used a thin mirror ►



The assembled prototype transmitter and receiver. The transmitter was powered by a 6 V lantern battery, the receiver by a 9 V transistor radio battery. We used a solar cell mounted in a lantern reflector, as described below.


firmly glued over the end of a flexible tube. When he spoke into the other end, sound waves travelled down the tube to make the mirror vibrate. This method is quite effective and you can use any kind of tube — a rigid cardboard or metal cylinder, for example. The mirror is more of a problem, because it needs to be quite thin to flex enough in response to unamplified voices. You may be able to obtain an ultra-thin glass mirror from a scientific equipment supplier, but some kind of reflective foil will be easier to get. Ordinary aluminium foil is an excellent reflector but it tears easily and it's hard to keep it uncreased, although these problems can be avoided to some extent by sticking adhesive tape to the back of the foil. Aluminised mylar (or other plastic) foil is probably best, if you can find any.

For our own transmitter we opted to use a circular glass mirror of normal thickness, such as you might buy in any chain store as a shaving mirror (the flat variety — not concave). We mounted this on the frame of a 150 mm diameter circular loudspeaker and made an amplifier to drive the speaker with sufficient power to flex the mirror. If you want to use this method, buy the speaker first, then look around for a shaving mirror the same diameter or slightly larger. Remove the metal or plastic rim and you will usually find two mirrors, one flat and one concave. Discard the concave mirror and glue the flat one to the metal rim (NOT the cone) of the speaker, using epoxy resin. Don't use a silicone compound like Silastic, because the joint must be rigid. The wider the

speaker and mirror you use, the better the range and the lower the distortion, because a wider mirror can flex more. The amplifier and microphone are described under 'Electronics'.

Receivers

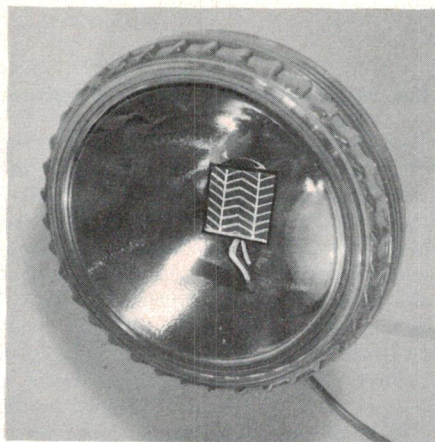There are several photosensitive devices which might be used in a receiver. Light dependent resistors respond too slowly, but a phototransistor is much faster and could certainly be used. Bell's original photophone receiver used selenium photoresistors in series with a battery and a telephone earpiece, but he had great difficulty with this



Close up of our receiver input device. This consists of a small solar cell piece mounted in a reflector taken from a 'Dolphin' lantern. To mount the cell, we cut a slot in one side of the reflector, put Silastic on the rear of the solar cell (leads already attached) and inserted it in place. It proved very effective.

system. (Bell deserves credit for any success with this astonishingly crude arrangement. As Dr. Johnson remarked about a dog walking on its hind legs — it was not done well, but it is astonishing that it was done at all!)


For our receiver we opted to use a 'solar cell', which is a kind of silicon photodiode. The large area and easy availability of solar cells make them the best choice overall. The effective area of the cell was made even larger by mounting it near the focus of a parabolic reflector taken from a hand lantern and an even larger effective area could be obtained by using a car headlamp reflector. Bell's original photophone used a reflector nearly a metre in diameter to gather the light, but anyone thinking of using very large reflectors should remember that the reflector must not be wider than the beam it is collecting, otherwise the modulation cannot be detected.

Light sources

In principle any light source will work. At night, with no other lights nearby, a pocket flashlight has been reported to work by some experimenters, but we haven't tried this ourselves. In daylight you need an intense and collimated (i.e: parallel) beam to get any reasonable range. A gas laser (such as a helium-neon type) is an ideal source, which in principle could give you a range of several kilometres in open country or over water, but some precautions are necessary. A low power laser is safest, preferably one having an output of one milliwatt. If possible, a 'beam expanding telescope' should be fitted to it. This increases the diameter of the beam making it easier to aim and reducing possible harmful effects to the eyes of any person who may accidentally look into the beam. The person setting up the receiver should not look toward the laser. Note that the beam at the receiver must be larger than the receiving device. This is where a beam expanding telescope helps.

This project makes a good 'science demonstration' project if your school science department has a suitable laser.

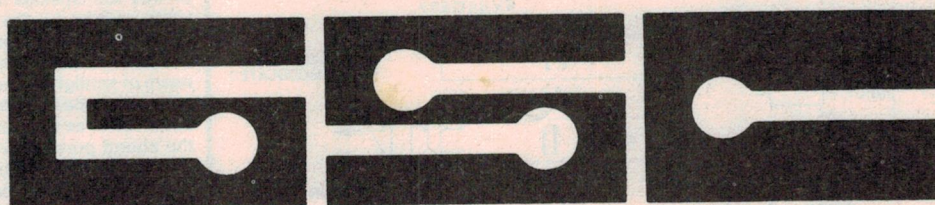However, a much more readily-available light source is the Sun whose light output is quite intense and has reasonably parallel rays. Using reflected sunlight, we found that we could communicate intelligibly by photophone over distances of a few hundred metres. With more efficient transducers (ours were deliberately simple) this distance could probably be extended. ►



for bread-boarding and test equipment

Recently, an extensive study was conducted by an independent research organization on what product qualities most influence professionals in their choice of electronic instruments. Know what they said?

Lower price. Small more compact packages. Simpler operation. Which is exactly what our product philosophy has always been. But that's no co-incidence!

GSC products are not just designed for the task, they are designed for the market, and engineered to be innovative in approach, technology and value.

More than a half million customers worldwide have chosen GSC products over any other. We have gone to a lot of trouble to build our reputation, and we are proud of our success.

That is why we think it is worth your time to take a closer look at the GSC products now available in Australia. They have proven our philosophy time and again.

Send for a free catalogue on the following product groups.

- GSC solderless bread boards
- GSC Proto-Board® solderless bread boards
- The Logical Force™ digital troubleshooters
- GSC pulse and function generators
- GSC MAX frequency Counters

You will see the features, the prices and the benefits that have made these products so popular.

For further information and free catalogue please contact — Australian Distributor



COMMQUIP PTY. LTD.


The Electronics and Communications Professionals.

PO Box 74, Leederville, WA 6007

9 Douglas St, West Perth, Western Australia

Telephone (09) 328 9451 Telex AA94918

Project 918

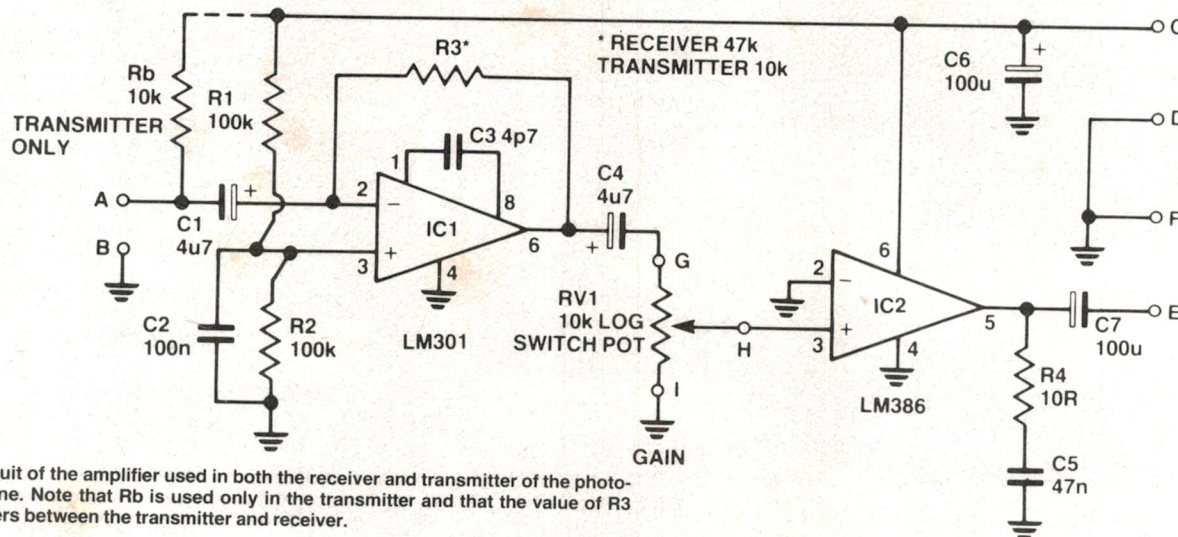

Circuit of the amplifier used in both the receiver and transmitter of the photophone. Note that Rb is used only in the transmitter and that the value of R3 differs between the transmitter and receiver.

Electronics

To amplify speech to drive the loudspeaker of the transmitter, we designed a simple amplifier around two ICs — an LM301 voltage amplifier and an LM386 power amplifier. There was no point in making a low noise, low distortion amplifier because the transmitting and receiving transducers are relatively noisy and non-linear. However, performance is quite acceptable. Speech

signals from an electret microphone insert are amplified by the LM301, then attenuated by a gain-control potentiometer before being fed to the LM386, whose output drives the loudspeaker. The large speaker needs a lot of current to drive it, so a six volt lantern battery is the best kind of power supply.

The receiver uses a very similar amplifier to boost the tiny signal derived from the solar cell, the dc component of this signal being blocked by a capacitor.


The receiver amplifier is so similar to the transmitter amplifier that it uses the same pc board design. The only differences are that the feedback resistor (R3) around the LM301 op-amp has a larger value in the receiver to give

HOW IT WORKS — ETI-918


Sound received by an electret condenser microphone is amplified by the transmitter amplifier and used to drive a loudspeaker. A plane (i.e. flat) mirror attached to the housing of this loudspeaker is flexed by the sound wave emitted by the speaker, so that it becomes alternately convex and concave as the sound pressure increases and decreases. A beam of sunlight reflected by the mirror onto a solar cell at the receiving end becomes broader or narrower as the mirror flexes, in phase with the sound pressure variations. Providing the beam always completely covers the collecting surface, a broader beam means that fewer photons are collected by the solar cell and a narrower beam means that more photons are collected.

The variation in the number of photons collected causes a proportional variation in the current generated by the solar cell. These current variations cause variations in the voltage across resistor Ra, and these voltage variations are amplified by the receiver amplifier, which drives a small loudspeaker to reproduce the sounds spoken into the transmitter microphone.


The transmitter and receiver amplifiers are essentially similar, each using an LM301 op-amp (IC1) for voltage multiplication and an LM386 power amplifier (IC2) with a switch potentiometer (RV1) between these two ICs for manual gain control. Resistor Rb (in the transmitter amplifier only) provides bias for the electret microphone. Capacitor C1 blocks dc signals. The gain of IC1 is set by the ratio of the resistance of R3 to the impedance of C1 at audio frequencies. The potential divider formed by R1 and R2 biases the non-inverting input of IC1 up to half the supply voltage, so that IC1 can be used with a single ended supply. C4 blocks any dc offset of IC1's output, R4 and C5 prevent instability around the output stage and C8 prevents any dc offset from being applied to the speaker. C4 and the internal resistance of the battery form a low-pass filter that removes battery noise from the supply line.

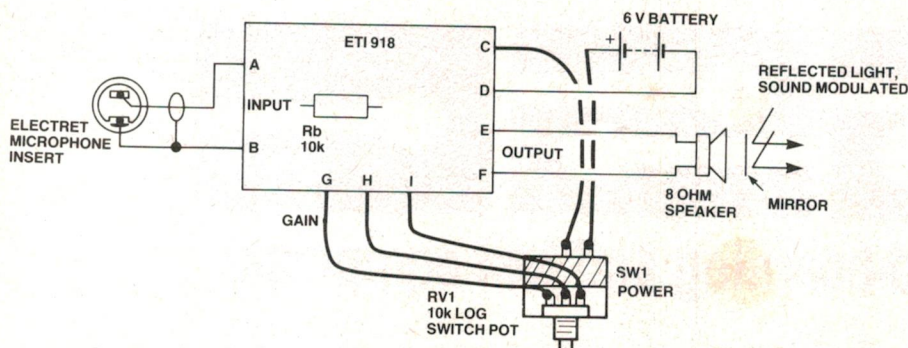

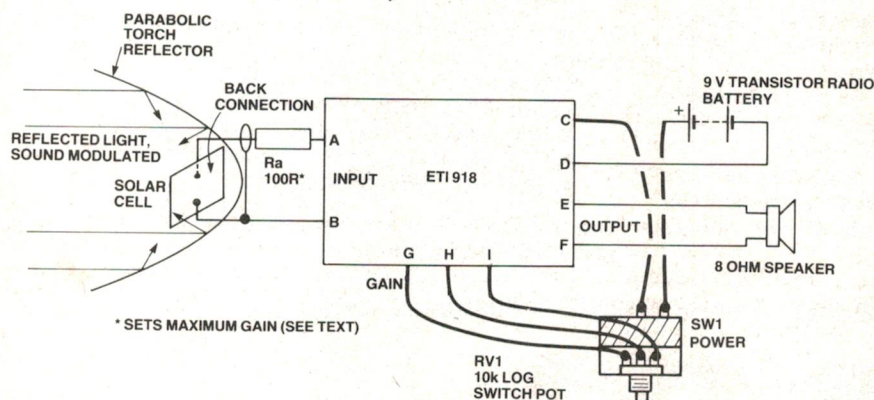
Wiring diagram of the photophone transmitter. Note the wiring to the rear of the electret microphone insert. You'll find one connection attaches to the mic case. This is the 'common' and goes to B on the pc board. Some inserts have leads already attached. Usually the common lead will be black. Use a shielded lead between the mic and the input to the amp.



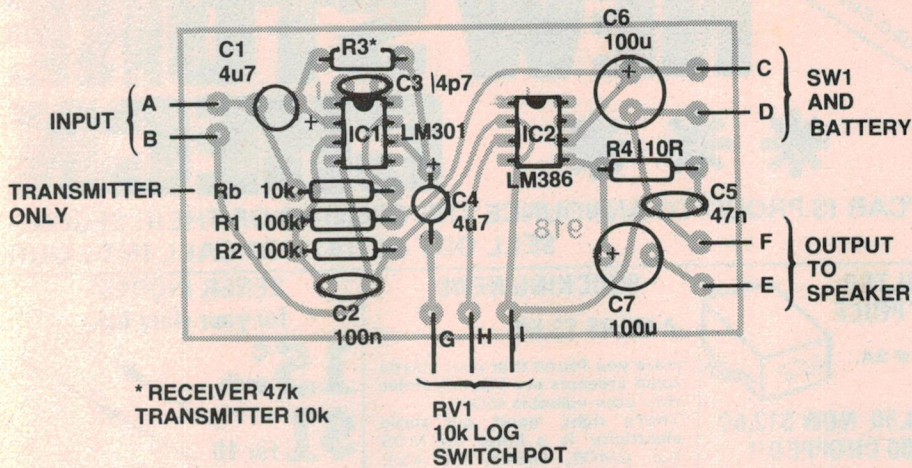Photophone receiver wiring diagram. Use a shielded lead between the solar cell and the amplifier input. Don't forget to connect a 100 ohm resistor in series with the lead to terminal A on the amp.



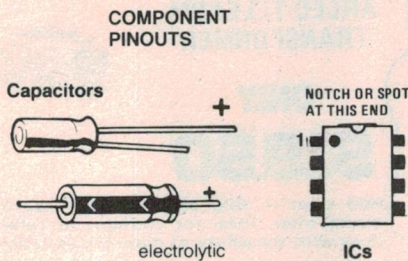Component overlay for the amplifier. Note that Rb is not needed in the receiver amplifier and that the value of R3 differs between the transmitter and receiver.



See 'Shoparound' page in this issue for where to buy components

higher gain, and the transmitter has an extra resistor (Rb) to bias the microphone. Only a small speaker is necessary for the receiver, so that a nine volt transistor radio battery can be used as power source.

Construction

We haven't designed any kind of box for this project. Obviously permanent housings for the transmitter and receiver will make the photophone much easier to use, but you can't make them until you've done some experimenting and finally decided what shape and size of reflectors you are going to use. In any case, this is a magazine about electronics, not carpentry or metalwork!

The two amplifiers should present no difficulties in assembly, providing you remember the usual precautions — check the orientation of capacitors, diodes and transistors, use a smallish bit when soldering the IC pins and let the ICs cool down for a few seconds between soldering each pin.

The electret microphone insert is polarised, so it can only go one way round. Make sure you solder the negative lead (usually black) to point B on the pc board and the positive lead

(usually red) to point A. Glue the flat mirror to the metal rim of the transmitter loudspeaker (not to the cone), using epoxy resin (not any other adhesive).

Some solar cell pieces come with leads attached, some do not. If you have to attach your own leads, do it very carefully, using a low wattage iron and thin flexible wire. Most cells have electrodes on the front and back surfaces: solder to the back electrode first, by forming a small pool of solder near the edge of the cell and holding the end of the wire in the pool until it cools. The front electrode is usually in the form of a thin strip and needs more care. Apply enough solder to form a bump or ridge, reheat the solder and position the second wire. The leads must be protected from strain and can be glued to the reflector if one is used. Connection to the amplifier should be made through shielded cable. Don't forget to insert the 100 ohm resistor (Ra) in series with the lead that connects to point A on the pc board (see the overlay diagram). The solar cell can be held in position with plasticene while you are

experimenting, or with silicone compound (such as Silastic) for a more permanent bond.

Operation

Leave the receiver with a friend and walk in the direction of your shadow, then point the transmitter so that the sun's reflection is directed at the receiver. It helps to put the receiver in the shade, so that you can see the spot of light from the transmitter mirror more easily.

You'll find that only a very small movement of the transmitter is enough to move the spot off the receiver, so it's easier if, once you've got the direction approximately right, you keep the transmitter steady on the ground or on a table and move the receiver to make the fine adjustments. Alternatively, you could keep the receiver fixed and mount the transmitter on a tripod.

A word of warning — don't point the light beam at your assistant's eyes (or anyone else's) if you're using the sun as the light source. To be safe, wear sunglasses (half-silvered types cut out most light) and never look directly at the mirror.

PARTS LIST — ETI-918

The following is a list of parts needed to build an electronically amplified transmitter and receiver to our specifications. The numbers in brackets represent the total number of components required of that value or type. If you are not using an amplifier in your transmitter, you will only need one of each component listed (i.e.: one of R1, one of R2, etc.)

Resistors all ½ W, 5%
R1, R2 100k (4)
R3 (2) see text
R4 10R (2)
Ra 100R (1)
Rb 10k (2)

Potentiometers
RV1 10k log. switch pot

Capacitors
C1, C4 4u7/16 V RB electro. (4)
C2 100n greencap (2)
C3 4p7 ceramic (2)
C5 47n greencap (2)
C7, C8 100u/16 V RB electro. (4)

Semiconductors
IC1 301 op-amp (2)
IC2 386 power amp (2)

Miscellaneous
One or two ETI-918 pc boards, one electret microphone insert, small solar cell piece, parabolic torch reflector, small 8 ohm speaker, 150 mm 8 ohm speaker, 150 mm or larger diameter round mirror to match diameter of speaker, 6 V lantern battery, 9 V transistor radio battery, short length of shielded cable, insulated hookup wire.

Price estimate

\$35 — \$40
(complete)

\$22 — \$25
(electronics only)

**NEW STORE
opening October
in Carlingford**

AT CARLINGFORD COURT NEXT TO KENTUCKY FRIED CHICKEN

NEW STORE CHECK



JAYCAR IS PROUD TO ANNOUNCE THE OPENING OF THEIR SECOND
SELL OUT IN DAYS SO CALL INTO OUR

FLASHING LED's

**NEW
LOW
PRICE**

**2 for
79¢**


Flashing LED's - NEW LOW
PRICE.

— Will they ever be this cheap
again?

Thousands went at 49c (for one)
now you can have 2 for 79c!!

MAINS FILTER NEW LOW PRICE

250V AC @ 3A.

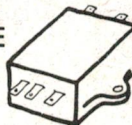

**WERE \$14.50 NOW \$12.50
\$2.00 CHOPPED!!**

This month only \$2.00 chopped
from our normal price.
Includes data sheet. The most
economical mains filter avail-
able!!

SHOCKING NEWS

A MERE \$3.50

Have you found that your plastic
soled creepers are blasting holes
thru your valuable MOS?

That's right, good old static
electricity is a killer for MOS
(i.e. CMOS, RAMs, LSI etc).
Don't despair we have conductive
foam sheets to protect them.

A whopping 6"x9" sheet -
(150 x 228mm).

Holds 00's of devices!!!

ZENER DIODES

for your glory box

**15¢
each
\$1 for 10**



Improve your Dowry with these!
The following values only (5%
1 watt).

9V1, 10V, 13V, 16V, 20V, 22V
24V, 30V, 39V & 56V.

MUFFS SCARCE - GRAB NOW!!



**ONLY \$5.95 for a set of two
(One for each ear)**

The Sennheiser HD414 Earmuffs are now
back in stock. Who needs a pair of mangy
muffs around the ears?
Spruce up your Headphones with these
bright Blue earmuffs.

OHMS LAW BREAKTHROUGH

ONLY \$36 each (Paint extra)

Programmable resistors. We have exclusive
rights to a totally new concept in resistance.
Just imagine you are slaving over the sold-
ering iron. It's 2.00am on Sunday morning
and you need a 39.7K ¼ watt. What do you
do? You break out the Jaycar programmable
resistor!! Each resistor is supplied blank &
you just paint the colours on yourself!!
What could be more simple?? Once paint
is applied the resistor conforms to the value
required.

ARLEC TELECOM TRANSFORMER



**ONLY
\$19.50**

600 ohm - 600 ohm Telecom approved
transformer. Ideal for coupling to Telecom
lines with the safety of dielectric isolation.

WILL POTS EVER BE THIS CHEAP AGAIN????

PACK 1

This pack contains over 50 assorted potentiometers (see note below). We have
deliberately kept the weight of this pack down to 500 grams so that postage is
not too bad.

P & P \$1.20

THAT'S JUST UNDER 20 CENTS EACH!!

\$9.95

PACK 2

This pack contains over 120 assorted potentiometers. Whilst weighing in at over a
kilo it's fantastic value despite the extra postage.

P & P \$4.00

(Note the higher than normal postage)

THAT'S JUST OVER 16 CENTS EACH!!

\$19.50

PACK 3

This is the big daddy of them all.

Over 250 pots in all!! Enough to last most people a lifetime. The advantage of this
pack is that you usually get a fair quantity of each value which can be handy.
We send this one out by road because postage would kill us!!

\$6.00 Freight

THAT'S JUST UNDER 14 CENTS EACH!!

\$34.50



NOTE: Each pack contains the same style of pot which includes:- single gang and dual gang. Switched and unswitched in
log and linear. All pots have plain shafts, most with a flat and have either PCB type terminals or solder eyelet terminals. Up
until June this year they sold for 50 cents each (single gang) in 100+ quantities. THEY ARE BRAND NEW STOCK

JOSEPH'S COAT BINDING POSTS

38¢ each



We keep standard binding posts in
the following colours: RED, BLUE
BLACK, WHITE, YELLOW &
GREEN. If you want any other
colours buy yourself a can of
spray paint. Japanese made quality

CHASSIS/PCB INSULATED FUSEHOLDER

Only 95¢

Ideal if you cannot avoid having mains
on the PCB and there is no room for
bulkhead-type fuseholders.
3AG type only. Japanese quality.



SPECIALS- US OUT! ***

STORE - RIGHT AT CARLINGFORD COURT. MOST OF OUR SPECIALS
YORK ST OR CARLINGFORD STORE AND SAVE!!!

INSULATED 6.5mm STEREO JACKS

ONLY
\$1 each



Body moulded in glass-filled nylon. Ideal where earth loops are a problem. We have been selling them for years but forgot to tell you about them. Isolates front panel from signal.

NEW!! NEW!! NEW!! NEW!! METAL RCA PLUG RANGE

We stock high quality metal RCA line plugs - both Nickel plated and Gold plated. Both plugs have spring cord relief grommets for long wear and tear.



	1-9	10+
Nickel plated plug	60c	50c
Gold plated plug	\$2.50	\$1.95
Gold plated chassis socket	\$2.95	\$2.25
Metal line socket	50c	45c

AT LAST!!!



\$6.95 each

Double-Pole Double Throw Footswitches. We had to import these ourselves to get the quality at a reasonable price. Heavy duty. Ideal for any musical effects-pedal application.

wireless guitar link

MASSIVE PRICE
BREAKTHROUGH!

- NOT A TOY -
- NOT A KIT -

\$149.50



Send SAE for further details

As reviewed in
September EA

Free yourself from the lead to the amp. This unit gives a ROCK SOLID SIGNAL over a 50 metre (YES!) range. Specially designed to take electric guitar signal levels. This small 9V battery powered unit clips to the strap. You won't notice it when playing! Transmits to any FM tuner in the little-used 88-100 MHz band. You can even practice at home on your Hi Fi. This is a professional unit at a budget price. Bring your guitar in for a demo or send SAE for more information. This unit is 100's of dollars cheaper than inferior units.

Smoke Detector

CONSUMER FLOP - CONSUMER FLOP
CLUB, HOTEL, HOSTEL & MOTEL MANAGERS

PLEASE NOTE

One of the greatest consumer flops of the last decade was the Ionization Chamber Smoke Detector. Even though it is a brilliant product (reliable compact, easy installation, fail-safe etc) it just did not sell. Human nature being what it is finds safety-oriented products just not worth the investment. We all know that accidents and fires never happen to US!! As smoke is the greatest killer in a fire, the market research gurus thought that such a product would have wide appeal. When they were \$49.50 no-one wanted them. The price fell to a very reasonable \$29.50 and still they stayed on the suppliers shelves. We have now been instructed to clear them for less than 1/2 of \$29.50

- Contains Americium 241 Ionization Chamber
- 9V Mallory Duracell included
- Contains very loud solid state buzzer
- 12 month factory warranty




GENERAL ELECTRIC

Grab One NOW **\$14.50**

* FAMOUS * GENERAL ELECTRIC
BURGLAR ALARM SLASHED!!!
HUGE SCOOP PURCHASE - ONCE SOLD FOR OVER \$100

* Slashed to
\$29.50

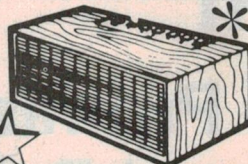

Amazingly low price for a full feature ultrasonic proximity/burglar alarm. + Completely self contained + 12 month manufacturer guarantee + Instant or delayed alarm + Handsome imitation woodgrain + Cabinet measures 180Wx85Hx100D + Programmable multi-code disable switch + Single 9V Alkaline battery* lasts one year + Unit beeps when battery gets low + Contains receiver element designed for greater sensitivity without false triggering + Uses State-of-the-art LSI circuitry + Worth the money in parts alone + Comprehensive 24 page manual included + Comes complete with 4 window deterrent stickers + Absolutely no installation needed. * Battery extra
SAVE A FORTUNE - COMPARES WITH UNITS OVER \$100
Below cost distress stock - Factory orders to sell.


LAMP/CdS CELL ARRAYS

ONLY
1.95 each



Extremely useful component. At one end of an enclosed tube a filament (long life) lamp. At the other end a Cadmium Sulphide cell. As the current through the lamp increases, the resistance of the CdS cell decreases.

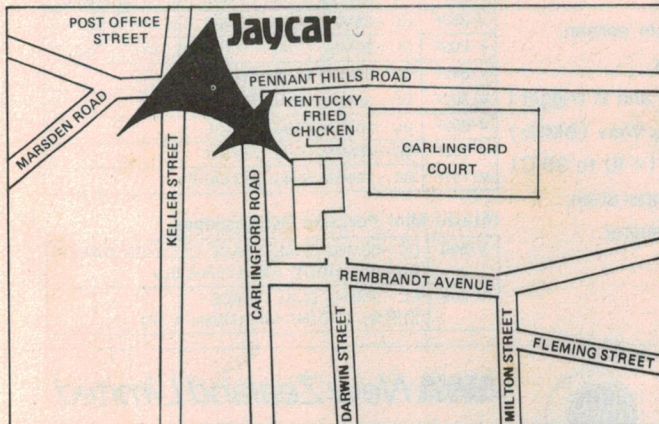- Provides dielectric isolation between circuits.
- Ideal as 'noiseless' volume controls.
- Can be used in volume compressors etc.
- Many other uses.
- Globe voltage 6-24V.
- Very compact dimensions.




give your projects a touch of Glass...

High Quality Phenolic Standoffs. Most with brass threaded inserts. Metric 3mm x 5mm ISO screws. We have the largest range in Australia of these hard-to-get components.

Size	Pack Qty.	Price	Price Bulk (100 mixed)
*10	6	\$1.50	0.19 ea
+15	5	\$1.65	0.25 ea
+20	4	\$1.75	0.30 ea
+25	4	\$1.85	0.32 ea
+30	4	\$1.95	0.35 ea

Sizes in mm

* Bakelite thread + Brass thread

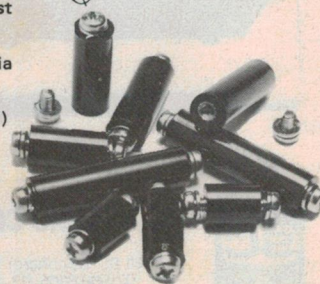

JAYCAR

125 YORK ST SYDNEY 2000
Ph. 2646688 Telex: 72293
Mail Orders To:
Box K-39 Haymarket 2000

POST AND PACKING CHARGES
\$5-\$9.99 (\$1.20) \$10-\$24.99 (\$2.40)
\$25-\$49.99 (\$3.50) \$50-\$99.99 (\$4.60)
\$100 up (\$6.20)

NEW SHOP HOURS
Mon-Fri 8.30 to 5.30pm
Sat 8.30 to 12.00pm
Thurs night to 8.30pm

... and now we have

Collet Knobs*

and caps and pointers
and figure dials and nut
covers ... and they all
fit together to
form competitively
priced, vibration-proof
and very satisfying
knob
assemblies

Call us NOW!
to talk about your requirements ...
from single to O.E.M. custom made quantities.



C&K Electronics (Aust.) Pty Limited

15 Cowper Street Parramatta NSW 2150
PO Box 229 Parramatta NSW 2150 Telephone (02) 635 0799 Telex 23404
Agents Melb. 598 2333/Adel. 277 3288/Bris. 36 1277/Perth 458 7111/Hobart 34 2233/
Laun. 31 6533.


Bringing you the excellence of International Professional components

* Manufactured by
SIFAM LTD England



HITACHI

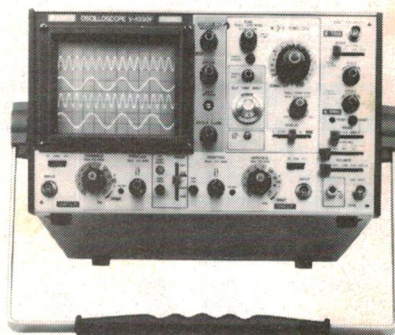Hitachi Promise You Quality and Reliability



Hitachi Oscilloscope
V-1050F/100MHz

1. Large Bright 8 × 10cm screen.
2. Quad trace operation.
(CH1, CH2, A trigger and B trigger)
3. High sensitivity 500 μV/div (5MHz)
4. High accuracy ±2% (+10 to 35°C)
5. Alternate time base operation.
6. 20 MHz bandwidth limiter.
7. Full TV triggering.

Hitachi Portable Oscilloscopes

V-650F	DC~65MHz DUAL-TRACE DELAYED SWEEP
V-353F	DC~35MHz DUAL-TRACE DELAYED SWEEP
V-203F	DC~20MHz DUAL-TRACE DELAYED SWEEP
V-352F	DC~35MHz DUAL-TRACE
V-302F	DC~30MHz DUAL-TRACE
V-202F	DC~20MHz DUAL-TRACE
V-152F	DC~15MHz DUAL-TRACE
V-151F	DC~15MHz SINGLE-TRACE

Hitachi Mini Portable Oscilloscopes

V-509	DC~50MHz DUAL-TRACE DELAYED SWEEP 215(W) × 110(H) × 350(D) mm 5kg
V-209	DC~20MHz DUAL-TRACE 215(W) × 110(H) × 350(D) mm 4.5kg



STANDARD COMPONENTS PTY. LTD.

10 Hill St., Leichhardt N.S.W. 2040
PH. (02)660.6066 (13 lines)



AWA New Zealand Limited

Wi-neera Drive, Porirua, N.Z. P.O. Box 50-248.
Telephone: PRO 75-069

MAGRATH'S 6-PACK SPECIALS

6 for the price of 5

DIGITAL & LINEAR

6x4016B	\$1.50
6x4066B	\$2.40
6x4511B	\$3.45
6x74LS00	\$1.00
6x74LS04	\$1.00
6x74LS14	\$2.00
6x74LS90	\$2.10
6xLM324	\$2.10
6xLM340KC.12	\$6.00
6xLM340T.5	\$2.55
6xUA317UC Regulator	\$6.00
6xUA348PC Op Amp	\$4.25
6x74C00	\$1.00
6x74C107	\$1.50
6x74C04	\$1.00
6x74C02	\$1.00

LEDs

6xMV505S	35c
----------	-----

BRIDGES

6xKBPC602 6A 200V	\$5.00
-------------------	--------

SCRs

6x6006L 6A 600V	\$4.00
-----------------	--------

DIODES

IN4002 100 per pack	\$4.50
IN4148 100 per pack	\$3.50

TRANSISTORS

6xPN2222A	25c
-----------	-----

CAPACITORS

	Normal Price	Special Price Per Each Pack of 6
STETTNER 3.12 pf CERAMIC TRIMCAPS	50c	\$2.50

ELECTROLYTICS

2.2Mfd 25V RB's	16c	80c
10Mfd 16V RB's	16c	80c
10Mfd 25V RB's	16c	80c
25Mfd 25V RB's	17c	85c
47Mfd 16V	20c	\$1.00
47Mfd 25V RB's	22c	\$1.10
100Mfd 10V RB's	20c	\$1.00
100Mfd 25V RB's	26c	\$1.30
220Mfd 25V RB's	36c	\$1.80

POLYESTERS

.001Mfd 100V Greencaps	8c	40c
.0047Mfd 100V Greencaps	8c	40c
.01Mfd 100V Greencaps	14c	70c
.012Mfd 100V Greencaps	14c	70c
.022Mfd 100V Greencaps	14c	70c
.033Mfd 100V Greencaps	14c	70c
.039Mfd 100V Greencaps	14c	70c
.056Mfd 100V Greencaps	14c	70c
.068Mfd 100V Greencaps	14c	70c
.1Mfd 100V Greencaps	14c	70c

HARDWARE

RCA Plugs	20c	\$1.00
RCA Chassis sockets	35c	\$1.75
3.5mm Plugs mono	20c	\$1.00
3.5mm Chassis sockets	35c	\$1.75
MS102 Push to make switch	35c	\$1.75

Philips Carbon Resistors


1/4W 50 per pack	\$1.00
1/2W 50 per pack	\$1.00

Ask about other 6-Pack Specials
There's lots more

AUDIO POWER AMPLIFIERS

from Sanken

UNBEATABLE VALUE

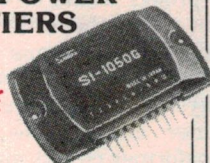

Multi-purpose Linear Amps
0.5% harmonic distortion
1/2db response
20 to 100 Khz
Built-in current limiting
SI-1010G 10W output \$10.40
SI-1050G 50W output \$37.60

HIRSCHMANN CONNECTORS

Screened Multipole Connectors
Top quality German made




5 Pin Plug	\$0.45
6 Pin Plug	\$0.45
7 Pin Plug	\$0.55
8 Pin Plug	\$1.20
5 Pin Socket	\$0.45
6 Pin Socket	\$0.45
7 Pin Socket	\$0.50
8 Pin Socket	\$0.83

SUPER VALUE

Horwood Instrument Cases

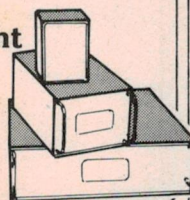
Light & strong
3"x4" high
Various sizes.
from \$2.04
to \$14.90



HILLS TV ANTENNAE

Designed to provide the best possible reception in your area. Built to highest electrical standards. Simple, lightweight, strong and easy to install.

EFC2 Metro Antenna	\$39.77
EFC3 Fringe area Antenna	\$66.81
FM3 Outdoor FM Antenna	\$23.35

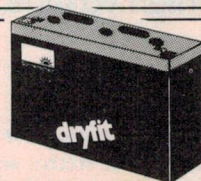

SONNENSCHN DRY FIT BATTERIES

Ideal for starting glow plugs in model aeroplanes. 2 volt 9.5AH
\$25.56 - RECHARGEABLE

HI-FI HEAD- PHONES

True Sennheiser sound
Top quality with economy
The most successful Hi Fi stereo headphones in the world.
HD 400 \$28.00
HD 410 \$40.50
HD 414X \$70.38
TAX PAID



FERGUSON TRANSFORMERS


Low profile, high quality, general purpose.

5VA 6 VOLT TO 40V	\$6.50
20VA 6 VOLT TO 40V	\$12.00
40VA 6 VOLT TO 40V	\$13.50
60VA 12 VOLT TO 40V	\$17.50

VALUE PLUS

Photo sensitive Riston Board for the home enthusiast.

6x9"	\$3.30
12"x12"	\$7.50
Developer	\$1.05

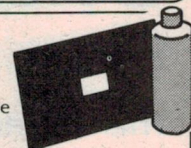

MEMORY BARGAINS

HM6116P-3 2K x 8 CMOSRAM	\$7.50
MB2716 2K x 8 EPROM	\$3.00
MB2764 64K EPROM	\$12.00
MB8118 16K DYNAMIC RAM (Intel 2118) 120ns	\$4.00

ELECTRONICS TOOLS

High quality Cushion grip

HT12 Electronic Snippers \$8.15

HT13 Micro Shears \$5.16

HT16 Mini Pliers \$5.45

QUALITY & VALUE

MAGRATH'S SEPTEMBER MONEY SAVERS SEMICONDUCTORS


See 6 pack Specials for super prices, on asterisked products.

4011B	19c	7406	20c	*74LS14	40c	LM301A DIP	35c
*4016B	30c	7414	33c	74LS47	72c	LM308 DIP	49c
4023B	19c	74164	48c	*74LS90	42c	*LM324	42c
4028B	55c	74365	37c	74LS161	53c	LM339 DIP	42c
*4066B	44c	*74LS00	20c	81LS95	87c	*LM340KC.12	\$1.20
*4511B	69c	*74LS04	20c	81LS98	88c	*LM340T.5	51c
4520B	74c					LM340T.15	60c
						LM386N	60c
						LM555	25c
						LM741N DIP	23c
						LM741 DIP	36c
						*74C02	20c
						74C89	\$1.50
						*74C107	30c
						*UA317UC REG.	\$1.20
						*KBPC602 6A 200V BR.	\$1.00
						*S6006L 6A 600V SCR	80c

UNBEATABLE PRINTER VALUE FOR YOUR TRS80™ or APPLE® MICROLINE 82A.

120CPS Serial Dot Matrix Printer.

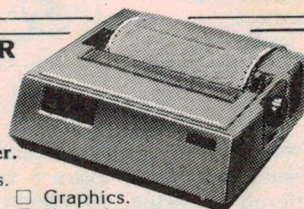- ☐ Head life 200 million characters.
- ☐ Dual interfaces — Serial & Parallel.
- ☐ 80 column standard characters.
- ☐ 132 column with condensed characters.
- ☐ Graphics.
- ☐ Uses plain paper.



Unbeatable value \$825
Also Microline 80 \$495.00

Add Sales Tax if applicable
Prices valid until stock sold
Prices subject to alteration

J.H. MAGRATH,
208 Little Lonsdale Street,
Melbourne, Vic. 3000.
Telephone: (03) 663 3731



SEAL OF SATISFACTION
MAGRATH'S
WORLD OF ELECTRONICS

24 Pin Socket

Zero Insertion Force
Only \$7.50

Universal dc-dc inverter

This inverter can be configured to suit a wide variety of applications — powering our audio amplifier modules from a 12 V battery, powering 12 V equipment from a 24 V or 32 V battery, deriving a high voltage supply from a low voltage dc source etc, etc.

**David Tilbrook
Roger Harrison**

WE'VE CALLED this a 'universal' dc-dc inverter as it has been designed so that, simply by winding the appropriate secondary, or secondaries, on the output transformer you can derive almost any dc output voltage(s) you want. Thus, this project can be used to power any of our audio power amplifier modules (ETI-470, ETI-477, ETI-480, ETI-499), with perhaps the exception of the ETI-466 300 W amp. You can power the ETI-565 HeNe laser and the ETI-452 Guitar Practice Amp, or any other project or device you desire, providing it falls within the power rating of the inverter.

We described a dc-dc inverter power supply to power a PA/guitar amp employing one of our 100 W '480 modules way back in May 1977. This was the ETI-481PS which provided ± 40 V rails from a 12 V battery. It ran at 20 kHz and required special rectifier diodes, a pot-core and a ferrite transformer assembly — all of which are now very difficult, if not impossible, to obtain. Since we described the Series 5000 stereo power amplifier in the January-February-March '81 issues, many readers have sought to adapt it for use in their vehicles (car/truck/sin bin...). Some managed to chase up the parts for the ETI-481PS, but they have now virtually 'dried up' and we have been pressed to do a 'replacement'. Well, this is it, albeit with some refinements.

We decided to make this inverter a 'universal' project as it struck us there are wider applications than was first envisaged. Besides, we've had a number of requests for a 12 V inverter to power the ETI-565 HeNe laser, both to provide portability and to free it from mains

operation for improved safety. It seems that many schools have built the laser for use in their science labs.

Design considerations

A number of factors were considered of prime importance when we tackled the design of this inverter. First came the frequency of oscillation. Would we have a low frequency design, which eases component selection and ensures their availability, or set the oscillation frequency above the audio band? A third option was to do something between those two extremes. Cost, size and component availability were also important.

The problem with a low frequency inverter, operating at — say — 2 kHz or less, is suppressing the switching 'spikes' that appear on the power supply rails. This can be difficult and these spikes almost inevitably create interference in low-level input stages. As the spikes contain predominantly odd harmonics the result is a cacophony of buzzes that is constantly present. Rectifier filter capacitors at the lower frequencies are, by necessity, large and we didn't want a bulky project.

Setting the inverter oscillation frequency above the audio band, at 20 kHz for example, gets rid of the above problem but introduces several others. Circuit techniques that work at low frequencies require specialised components at 20 kHz. Hence, a different inverter technique is necessary, and this inevitably increases costs and specialised components often prove hard to get — which became the major problem with the ETI-481PS which ran at about 25 kHz.

We chose the median course. Setting the oscillation frequency at around 6-7 kHz puts the odd harmonics where they (mostly) won't be heard. Filtering is easy and suitable capacitors are compact.

We wanted a design that used a minimum number of components, so that the project would be compact, but consistent with the other restraints. There are three common techniques employed in transistor dc-dc inverters these days — the self-excited single transformer circuit, the self-excited dual transformer circuit and the driver inverter.

The self-excited single transformer inverter is by far the simplest. The general form of this inverter is shown in Figure 1. The transistors operate in push-pull and feedback is taken from a winding on the output transformer. It

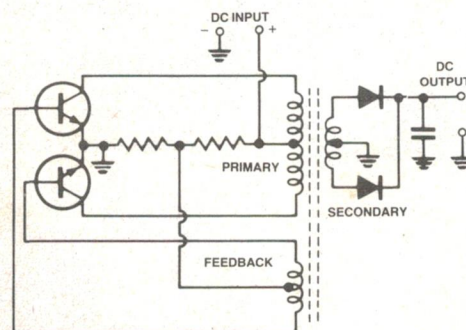


Figure 1. Typical circuit of a self-excited single transformer dc-dc inverter. Efficiency of this type of circuit often exceeds 90%, with correct choice of transistors.

has two great advantages — simplicity and high efficiency. With proper choice of transistors, efficiency can be in excess of 90%. However, at the sort of powers

we envisaged the inverter would have to deliver — around 200 W or so — switching transistors with suitable current ratings and low saturation voltages (for that's where you lose efficiency) are not cheap, or readily available. Germanium switching transistors are the best. Tried to buy a 20 A germanium switching transistor lately? Some MOS switching devices are also suitable, but still hard to get. You could parallel transistors of lower current rating but the traditional method of using emitter 'ballast' resistors severely affects efficiency. By using a special primary winding on the transformer, as shown in Figure 2, the devices are essentially in parallel but collector-emitter current sharing is done in the transformer primary. Base current sharing is effected by the series base resistors.

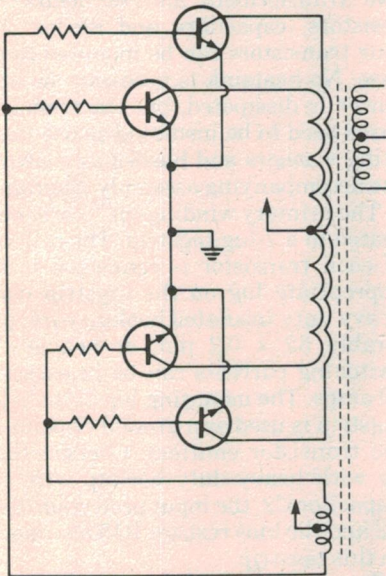


Figure 2. Obtaining more power output from the simple self-excited inverter by means of 'paralleling' transistors with a special, quadrifilar-wound, primary. For high power use, lower cost transistors can be used.

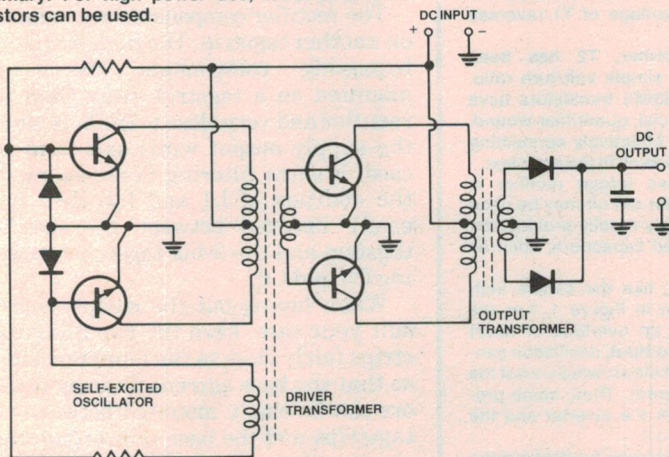


Figure 3. Typical circuit of a driven dc-dc inverter where a low power self-excited oscillator drives a set of transistor switches which drive the output transformer. Of the three types, this technique has the poorest efficiency.

Thus, common-or-garden transistors, like 2N3055s, can be used and little power is lost here. The major drawback is attaining the required oscillation frequency. For this sort of inverter, the oscillation frequency is given by:

$$f \cong \frac{V_{\text{supply}}}{4N\delta_m}$$

where: f is frequency of oscillation


V_{supply} is dc input

N is primary turns, collector to centre tap

δ_m is magnetic properties of transformer core

Thus, for a given voltage and core properties, N must be relatively small to achieve the required frequency of oscillation. But here comes a catch. The feedback winding must develop enough voltage to drive the base such that the transistor(s) saturate properly. In practise, this means about 3 V. If the dc input is 12 V, you need a turns ratio of 4:1 between the primary and feedback windings. If you make the feedback winding (centre tap to one set of bases) one turn, then the primary has to be four turns. With available cores, the oscillation frequency did not even approach what we wanted.

A driven inverter is more complex, but it overcomes the problem just outlined. A typical arrangement is shown in Figure 3. This employs a low power, self-excited push-pull oscillator driving a set of push-pull output transistor switches which drive the output transformer. The old ETI-481PS inverter was of this type. Efficiency is the greatest drawback of this type of circuit. The driving oscillator always draws significant power. You can achieve efficiencies

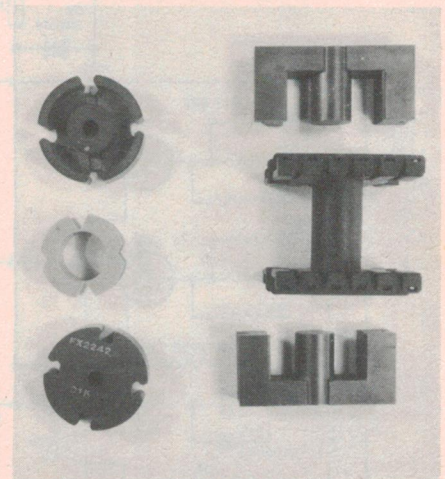

The transformer assemblies we used. At left is the FX2242 potcore assembly; right is the Philips EC52/24/12 assembly. Note the ferrite 'Es' of this assembly have round centre legs. The bobbins are shown in the middle.

of 80%, typically, but at 200 W output, you're losing 40 W and in a battery system, this is not good.

We settled on the self-excited dual transformer technique, illustrated in Figure 4. Here, a separate feedback transformer is used and it is this which controls the frequency of oscillation. This enables the choice of the right sort of core to obtain realistic turns ratios and the desired frequency of oscillation. We managed to use a common potcore for the feedback transformer (a 36 mm diameter FX2242 type) and an EC-core for the output transformer of a type we have used previously (in the ETI-1505 fluorescent light inverter). Supply rail filtering can be done quite effectively with common greencaps. Ordinary 2N3055 transistors — which cost less than a dollar these days — can be employed, thus keeping the cost down. ▶

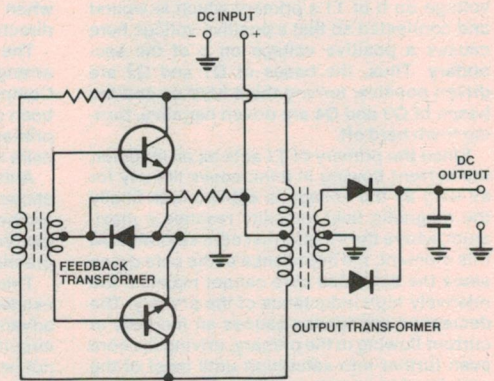


Figure 4. Circuit of a self-excited dual transformer dc-dc inverter where the feedback is separated from the output transformer. In this circuit, the oscillation frequency is determined by the feedback transformer. Efficiencies similar to the Figure 1 circuit can be achieved.

Project 1509

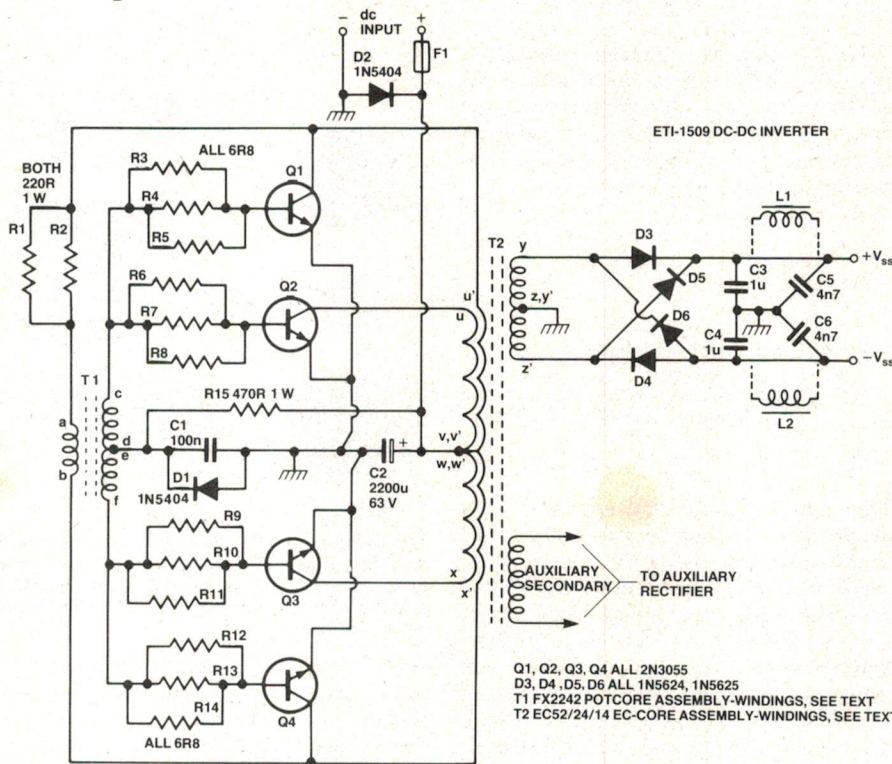


Figure 5. Circuit of the universal dc-dc inverter. The two inductors shown at the rectifier output, L1 and L2, are only necessary if extra filtering of the dc output is necessary. These can be any value between about 1 mH and 10 mH. Speaker crossover inductors are ideal for this application. Choose inductors rated to carry the dc output current. At low currents (200 mA or less, say) RF chokes will suffice.

HOW IT WORKS — ETI-1509

The circuit is a push-pull self-oscillating inverter with feedback provided by transformer T1, output being taken from T2. The moment the supply voltage is connected, current flows through the 470 ohm resistor R15, through the secondary of T1 (c-d-e-f) and the base current limiting resistors of the transistors Q1 to Q4. One of these transistors will turn on as circuit balance is not perfect and device characteristics are not matched. If, for example, Q1 commences to turn on, current will flow through the u'-v' primary of T2. This causes a magnetic field to build up in the transformer core creating a positive voltage on x' (x goes positive too). This puts a positive voltage on b of T1's primary which is wound and connected so that a positive voltage here causes a positive voltage on c of the secondary. Thus, the bases of Q1 and Q2 are driven positive, turning them hard on and the bases of Q3 and Q4 are driven negative, turning them hard off.

Since the primary of T1 acts as an inductor, the current flowing in it increases linearly for as long as the voltage is applied until finally the magnetic field intensity reaches a maximum, where the transformer core saturates. At this moment, the impedance of the core drops since the saturated core cannot maintain the relatively high inductance of the primary. The decreased impedance causes an increase in current flowing in the primary, driving the core even further into saturation until most of the coupling between the primary and secondary is lost. This causes the drive voltage to the bases to disappear. Current stops flowing in the transformer and the magnetic field starts to collapse. This causes the voltage sense of each winding to reverse. Thus, u and u' on T2

go positive and x-x' go negative. This causes b on T1 to go negative and thus c goes negative, removing charge from the bases of Q1 and Q2 which turn off. At the same time, f goes positive, turning Q3 and Q4 on. The whole sequence of events then repeats for the opposite 'side' of the oscillator, until once again, Q1 and Q2 are driven on and oscillation results.

The frequency of oscillation depends primarily on the core material of T1, the turns on its primary winding (a-b) and the applied voltage. In this case the frequency is around 6 - 7 kHz. Resistors R1 and R2 provide control of the feedback and diode D1 provides a return path for the base emitter current to the transistors when the secondary voltage of T1 reverses direction.

The output transformer, T2 has been arranged to provide a simple volt/turn ratio. Common, low cost 2N3055 transistors have been used and the special, quadrifilar-wound, primary is a means of effectively connecting pairs in parallel, as discussed in the main text.

Although a full wave bridge rectifier is shown here, any rectifier circuit may be used on the output. Filtering is readily provided by low value non-polarised capacitors, such as greencaps.

This inverter circuit, like the simple self-excited inverter shown in Figure 1, has the advantage that, when an overload or short circuit is applied to the output, oscillation cannot be maintained and it stops, which is not the case with a driven inverter. Thus, some protection is afforded both the inverter and the equipment connected to it.

Diode D2 prevents damage by blowing the fuse should the dc supply input be connected in reverse.

The circuit of the inverter is shown in Figure 5.

As it was to be a 'universal' inverter, the output transformer was designed to provide a simple volts/turn ratio for the secondary, making it easy to calculate and wind the secondary for the required output. The ratio is two volts per turn. A 'Table of Suggested Outputs' has been drawn up for a variety of applications. Note that more than one secondary can be wound on the output transformer if required.

Construction

The inverter can be housed in any convenient enclosure and we have shown only general construction as layout is not particularly critical. A suggested layout is shown in the wiring diagram. A metal case is assumed. Four tagstrips are used as tiepoints to terminate the two transformers and to mount the resistors, capacitors and diodes. The four transistors can be mounted to the case. No heatsink is necessary as little power is dissipated, but the transistor cases need to be insulated so use insulating washers and bushes as shown in the accompanying assembly diagram.

The primary windings of T1 are terminated to a 7-lug tagstrip. The collector of each transistor is connected to the appropriate lug on the tagstrip using heavy duty insulated hookup wire, preferably 32 x 0.2 mm or heavier, as switching currents can be in excess of 20 amps. The mounting lug of the 7-lug tagstrip is used as a ground tiepoint for the transistor emitters. Connect them up with heavy duty hookup wire too. Capacitor C2, the input protection diode D2 and the bias resistor R15 also mount on this tagstrip.

Two 5-lug tagstrips are used to terminate the feedback transformer, T1, and to support the base current limiting resistors and several other components.

The rectifier components are mounted on another tagstrip. The high frequency bypassing components should be mounted on a tagstrip away from the rectifier and very close to the hole where the supply output wires exit from the case. If extra filtering is necessary (by the addition of L1 and L2) then it is easily inserted between the rectifier tagstrip and the 3-lug tagstrip containing C5 and C6.

When laying out the components to suit your case, keep the two 5-lug tagstrips fairly close to the four transistors so that the base current limiting resistors can be easily mounted between the tagstrips and the base pins of the transistors. Also, mount the 7-lug tagstrip that terminates the primaries of T1, close to the transistors so that high

PARTS LIST — ETI-1509

Resistors all ½ W, 5% unless noted
 R1, R2 220R, 1 W
 R3—R14 6R8
 R15 470R

Capacitors
 C1 100n greencap
 C2 2200u/63 V axial electro.
 (or 2500u/50 V)
 C3, C4 1u greencap
 C5, C6 4n7 ceramic

Semiconductors
 D1, D2 1N5404
 D3, 4, 5, 6 1N5624, 1N5625
 Q1, 2, 3, 4 2N3055

Miscellaneous
 T1 FX2242 potcore assembly
 (windings, see text).
 T2 Philips EC-core assembly
 (windings, see text).
 2 x EC52/24/14 cores
 (4322-020-52520)
 1 x former, no tags
 (4322-021-33020)
 clamp assembly:
 1 x 52PLATE
 1 x 55UBOLT
 2 x 632NC2A


Two 7-lug tagstrips; two 5-lug tagstrips; one 3-lug tagstrip; chassis or box as required; winding wire — 1 mm and 0.4 mm enamelled copper wire; 32 x 0.2 mm hookup wire; 10 x 0.2 mm hookup wire; nuts, bolts etc.

Price estimate \$30 — \$35

current carrying leads are kept short.

Make sure you have enough room to mount both T1 and T2. A single bolt through the centre hole of the T1 potcores will secure it but use a fibre washer under either the head of the bolt or under the nut to prevent cracking one of the potcore halves.

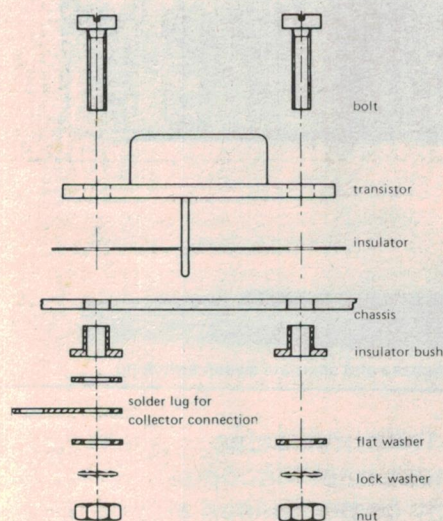If you use a chassis that comes in two halves (like we did on our prototype) mount all the tagstrips and components



Mounting the power transistors.

on the one half so that all the ground tie points are connected together whether the case is split in half or not. If you use a box with a lid (like a diecast box, for example) mount all the components and tagstrips either on the lid or in the box, for the same reason.

When you have a layout finalised for the housing you're using, it's best to assemble all the electronics first, leaving the transformers till last. Then wind the transformers. Use our Table of Suggested Outputs and the Transformer Winding Details as a guide to assemble the two transformers. When you've done these and checked that all is correct, mount the transformers and wire them up.

For the dc input leads, use heavy duty cable or hookup wire, remembering that 20 A or so may be passing through it. Don't forget the line fuse.

Firing it up


Simple. If you're confident you've wired

it up correctly (and checked it), hook a multimeter to the dc output and connect power to the dc input. You should hear the transformers 'sing' immediately at quite a high pitch (around 6 kHz if your pitch sense is that good). The output voltage should rise to what you require, also. If you don't hear the transformers sing, then switch off and reverse the primary (a-b) connections of T1. Switch on and the inverter should burst into life. If it doesn't — or worse, bursts into flames! — switch off and take a look at your wiring. Correct any faults before trying again. In particular, make sure you have D1 the right way round.

If all is working as it should, you could try and assemble a 'dummy' load for the output. A suitable set of power resistors will do. The exact resistance will depend on the supply and the load current it has to supply. We'll have to leave this to you.

Under load, the output voltage should be within a few per cent of what you require and power dissipation of the

continued on page 41 ►

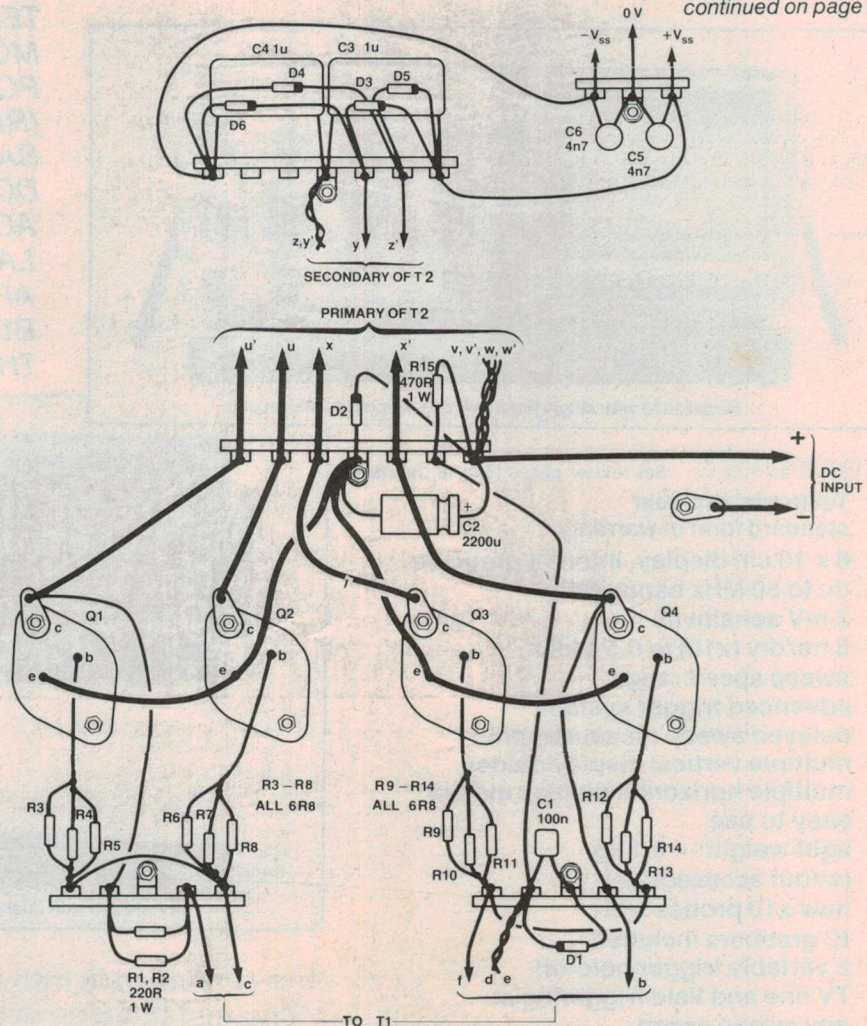

General wiring diagram of the inverter. Layout is not critical. However, use heavy duty (32 x 0.2 mm) hookup wire for the heavy leads shown here for wiring the collectors and emitters of the four power transistors. Capacitors C5 and C6 provide high frequency bypassing of the output rails. Mount them close to where the supply output leads exit the case.

R EXCLUSIVE ETI READER OF

TEKTRONIX DUAL-TRACE HIGH PERFORMANCE 60 MHz PORTABLE OSCILLOSCOPES

Here is an excellent opportunity to buy a high performance 60 MHz oscilloscope from the world's leading oscilloscope maker at a very special price — exclusive to ETI readers.




Model 2213 with single timebase and delayed sweep facility

THROUGH THIS SPECIAL DEAL TEKTRONIX IS OFFERING THE MODELS 2213 AND 2215 PORTABLE OSCILLOSCOPES (REVIEWED LAST MONTH) AT SAVINGS UP TO HUNDREDS OF DOLLARS OFF. ORDERS WILL BE ACCEPTED ONLY WHILE STOCKS LAST AND IN ANY EVENT NOT AFTER 31 OCT. '82. ORDERS MUST BE PLACED BY COMPLETING THE COUPON OPPOSITE.

FEATURES See review, pages 15 to 18, July issue.

- Tektronix' two-year standard form of warranty.*
- 8 x 10 cm display, internal graticule
- dc to 60 MHz bandwidth
- 2 mV sensitivity
- 5 ns/div (x10) to 0.5 s/div sweep speed range
- advanced trigger system
- delayed sweep measurements
- multiple vertical display modes
- multiple horizontal display modes
- easy to use
- light weight — 6.1 kg (w/out accessories)
- new x10 probes with IC grabbers included
- a variable trigger hold-off
- TV line and field triggering at any sweep speed
- enhanced auto mode
- Z-axis input (brightness modulation)

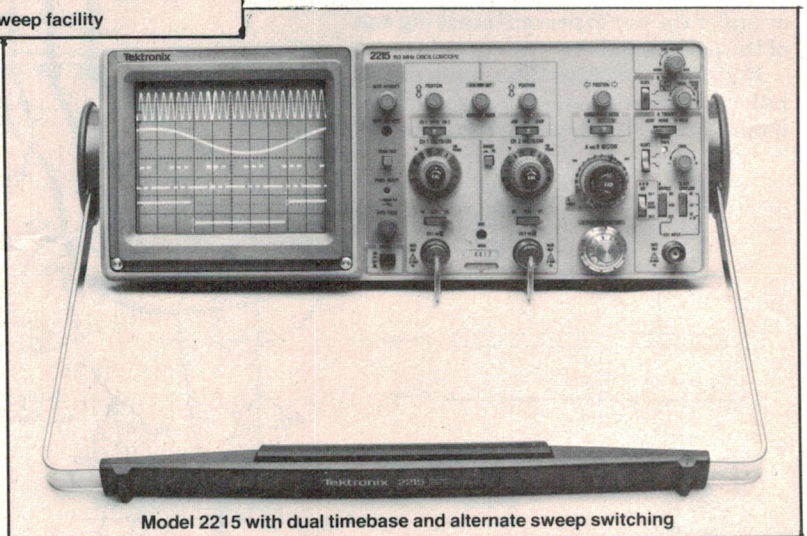

Model 2215 with dual timebase and alternate sweep switching

You cannot walk into a Tektronix sales office and buy one of these oscilloscopes at this price — it can only be purchased at this special price through ETI.

* The standard "Corporate Warranty Statement" of Tektronix Australia Pty Ltd is available for inspection at any of the offices shown opposite.

ER EXCLUSIVE ETI READER OF

SPECIAL OFFER PRICES

☆ Model 2213

\$1139 excl. sales tax
\$1348.58 inc. sales tax

☆ Model 2215

\$1422 excl. sales tax
\$1683.65 inc. sales tax

Both models are supplied as illustrated and come complete with two P6120 x10, 60 MHz probes and instruction manuals. Cover and accessory pouch not included. (Usual cost \$65.)

● Prices including sales tax have had to be increased owing to sales tax increases in the recent budget.

Tektronix currently list the 2213 at \$1392 (\$1648.13 inc. tax) and the 2215 at \$1758 (\$2081.47 inc. tax), which includes probes, manuals, cover and pouch.

Anyone purchasing a 2213 or 2215 through this offer may later obtain accessories, but only directly from Tektronix. Tektronix accessories for these oscilloscopes include: cover and accessory pouch (020-0672-00); viewing hood (016-0566-00); C-5C Opt 04 scope camera; Model 200C SCOPE-MOBILE cart; rack adaptor kit (016-0466-00).

INSPECTION

You can inspect one of these oscilloscopes during office hours at the following places:

Sydney: ETI Offices 15 Boundary St Rushcutters Bay NSW	Melbourne: Murray Publishers Offices 22nd Floor, 150 Lonsdale St Melbourne	Adelaide: Tektronix 128 Gilles St Adelaide (Phone 223-2811)	Brisbane: Tektronix 737 Logan Rd Greenslopes (Phone 394-1155)	Perth: Tektronix 66 Wellington St East Perth (Phone 325-8433)
--	--	--	--	--

HOW TO ORDER YOUR OSCILLOSCOPE

Fill out the coupon here and enclose a cheque, bank cheque or money order for the amount required made out to TEKTRONIX.

If you are not paying sales tax, please quote your sales tax number on the coupon, where indicated, or for schools, colleges or other educational institutions, enclose a sales tax declaration on your letterhead. The completed coupon, together with your cheque, bank cheque or money order should be sent to:

TEKTRONIX SCOPE OFFER
c/o ETI, 15 Boundary St
Rushcutters Bay NSW 2011

DELIVERY Tektronix will endeavour to deliver the goods inside four (4) weeks from receipt of payment. Delivery (or acknowledgement of coupon) should occur within two weeks.

Please supply, on the terms outlined in this offer and in the standard "Corporate Warranty Statement" of Tektronix Australia Pty Limited.

..... Model 2213 CRO(s) @ \$1139 each, excl. tax or @ \$1348.58 each, inc. tax.

..... Model 2215 CRO(s) @ \$1422 each, excl. tax or @ \$1683.65 each, inc. tax.

Sales Tax No (if applicable).

I enclose \$ total.

Name


Address Postcode

Cheque or Money Order No Signature

Send completed coupon with cheque or money order to:

TEKTRONIX SCOPE OFFER, c/o ETI, 15 Boundary St, Rushcutters Bay NSW 2011

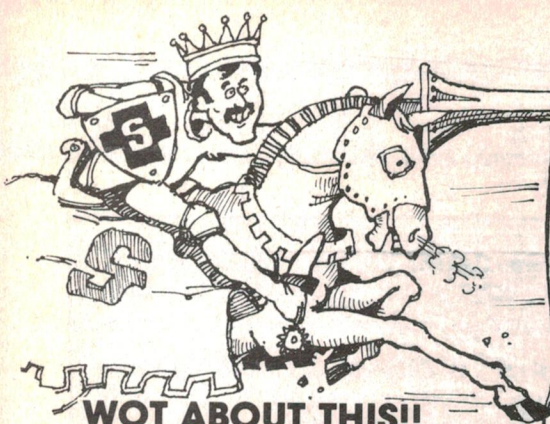
This offer is made by Tektronix Australia Pty Limited (Incorporated in ACT).



WOT ABOUT THIS!! LITRONIX DISPLAYS

1st time offer - Litronix Red Single
Digit Light Pipe Dip "Displays"
Type: DL-750 common cathode display
Character height: .630"
7 segment D.P. left light output (MCD)
Typ. 5.0 Min. 2.0 = 20ma
Fwd. volt. Typ. 3.4 Max 4.00


ONLY \$1

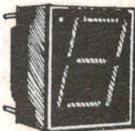

7 BANK DPDT ISOSTAT SWITCH

We're robbing ourselves!! Just take a note of
this - you'll be amazed
7 Bank DPDT 'ISOSTAT' switches (less
knobs) with on/off power. 10 for the price of
one. All new - all unused.

\$2.50 FOR 10!

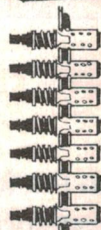

TENPACK SPECIALS

Low Profile 16 pin I.C. sockets..... 10 for \$1.10
Low Profile 14 pin I.C. sockets..... 10 for \$1.10
C106C1 SCR 4A 400V TO202 Pkg..... 10 for \$3.50
C106F1 SCR 4A 50V TO202 Pkg..... 10 for \$3.00
C122F SCR 8A 50V TO202 Pkg..... 10 for \$5.00
Beckman Resistor Arrays
16 pin package 100kΩ and 1.8kΩ..... 10 for \$5.00
10 pin SIL package 12kΩ..... 10 for \$4.00
8 pin SIL package 8.2kΩ..... 10 for \$3.75
Transistor BC547 Moulded TO18..... 10 for 80c
BC557 Moulded TO18..... 100 for \$6.00
TIP29B NPN Power Transistor TO220..... 10 for \$2.00
PUT 2N6028..... 10 for \$3.00
2 way Terminal Block Polythene..... 10 for \$1.25
Bournes 50kΩ Cermet Trimpot 3/8" SQ..... 10 for \$3.00
No Seconds — All New — All Cheap

IM6403P INTERSIL LOW POWER UARTS

From Intersil. Compatible with standard
IM6402 but with these extra features:
• Tiny power consumption less than
10mW @ 2MHz
• Programmable word length, stop bits, parity.

Data available. 7 page
Data sheet at 20c per
page


**\$4.00
each**



RIFA METALLIZED POLY- PROPYLENE CAPACITORS

Special purchase. Suitable for use as
fluorescent ballasts etc. 8 or 9 MFD.
at 250V 50Hz. Giveaway at only.

**\$1.00 each
10 for \$9.00**

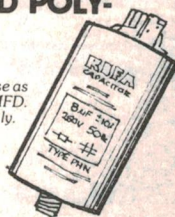


12V DIL RELAY

Specs:-
SPST, 12V DC.
Coil resistance 1100
ohms, Nominal current
11mA, Pull in voltage 8V
Contact rating 500mA

**only
\$1.00**

90c 10up,
80c 100up

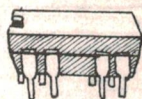

SLIDER POT

Combined 100K Slider Pot with
S.P. 3 pos. rotary switch. (Slider
Pot has windowed indicator). 10
for the price of one. All new - all
unused.

\$2 FOR 10!



THE PRICE WAR IS ON AGAIN!!! CHARGE INTO SHERIDANS - THE COMPONENT KINGS

HERE WE GO AGAIN

but only in
limited quantities

Fairchild Displays

Fairchild 7 segment common cathode
numeric displays. .5" character height-
colour red. Only \$1 ea. or 10 for
\$9.00



VERY IMPORTANT SPECIALS ON DISPLAYS AT VERY SPECIAL PRICES-

BUT IN
LIMITED QUANTITIES

TYPE	PRICE	DESCRIPTION	Type	Price	Description
DL-57	\$2.10	Red alphanumeric no drivers no memories multiplexed 5 x 7 dot matrix. Single digit .35" Fwd. V. 2. Current 10ma. Litronix.	DL-527	\$1.95	As DL-522 but common anode and 7 segment D.P. right. Litronix.
DL-750	\$1.00	Red single digit light pipe DIP. common cathode. 7 segment D.P. left. .630" height. Fwd. V. 4. Litronix.	FND-530	\$0.95	7 segment single display. Common cathode. Green. .5" height. Max. Fwd. volts 1.7 C.F.C. 25ma. Fairchild.
DL-722	\$1.95	Red two digit light pipe dip. common cathode ± polarity overflow. .510" height. Fwd. volt 2. 30ma Max. C.F.C. Litronix.	FND-560	\$0.95	Red 7 segment single display. Common cathode. .5" height. Max. Fwd. volts 1.7 C.F.C. 25ma. Fairchild.
DL-728	\$1.95	As DL-722 but 7 segment D.P. right	FND-531	\$0.95	Green single digit display. Common cathode. .5" height. ± polarity overflow. Max. Fwd. volts. 1.7 per segment. C.F.C. 25ma. Fairchild.
DL-701	\$1.00	Red single digit light pipe DIP. Common anode ± polarity overflow. .3" height. Fwd. volt. 2 Max. Litronix.			
DL-721	\$1.95	Red two digit light pipe DIP. Common anode. ± polarity overflow. .510" height. Max. Fwd. Volt. 2. C.F.C. per segment 30ma. Litronix.			
DL-522	\$1.95	Red two digit reflector dip. Common cathode ± polarity overflow. .50" height. Max. Fwd. Volt. 2. C.F.C. per segment 30ma. Litronix.			

If purchasing 10 or over of each of the
above displays take 10% off of total price.

PRICE CRASH

ELECTROS - SAVE 50%!

Huge scoop purchase of brand new computer
grade electros from Philips, Sprague and Sangamo
means you save if you get in now!!

Mounting clips
only \$1.00 each!!

CAP MFD.	WKG. VOLTS	MAKE	DIA HEIGHT MM MM	PRICE
500	250	SPRAGUE 35	80	\$5.00
590	200	SPRAGUE 35	80	\$5.00
1800	50	SNGAMO 35	60	\$3.50
2300	60	SPRAGUE 35	80	\$4.00
2400	50	SPRAGUE 35	55	\$4.00
2400	50	SNGAMO 35	60	\$4.00
3000	75	SNGAMO 35	125	\$5.00
3100	450	SPRAGUE 75	220	\$12.00
3300	75	SNGAMO 35	110	\$5.50
3600	25	SNGAMO 35	60	\$3.25
3700	30	SNGAMO 35	60	\$3.50
4300	25	SNGAMO 35	60	\$3.75
4700	63	PHILIPS 50	90	\$5.75
5400	35	SNGAMO 35	90	\$4.25
7000	35	SNGAMO 35	90	\$5.00
7500	15	SPRAGUE 35	60	\$5.00
8000	35	SNGAMO 35	110	\$6.00
8200	25	SNGAMO 35	90	\$5.75
8700	40	SPRAGUE 35	110	\$7.50
9100	60	SNGAMO 50	110	\$10.00
10000	25	SNGAMO 35	90	\$6.00
10000	40	SPRAGUE 50	90	\$6.50
12000	10	SPRAGUE 35	85	\$5.50
13000	60	SPRAGUE 65	110	\$10.00
14000	25	SPRAGUE 50	85	\$5.50
14000	40	SPRAGUE 50	110	\$9.00
15000	3	SNGAMO 35	60	\$3.50
15000	10	PHILIPS 35	85	\$4.50
15000	16			\$5.00
15000	63			\$5.00
20000	25			\$3.50
22000	6.3			\$4.00
22000	10			\$4.00
22000	75			\$5.00
26000	10			\$4.00
30000	25			\$5.00
30000	25			\$12.00
33000	16			\$3.00
36000	20			\$3.25
39000	25			\$3.50
39000	30			\$3.75
44000	35			\$5.75
47000	10			\$4.25
47000	25			\$5.00
55000	3			\$5.00
65000	35			\$6.00
67000	10			\$7.50
70000	50			\$10.00
76000	25			\$6.00
88000	10			\$6.50
100000	3			\$5.50
100000	10			\$10.00
110000	10			\$10.00
110000	20			\$9.00
120000	15			\$5.50
150000	6.3			\$3.50
200000	3			\$4.50
PHILIPS 35	115			\$5.00
PHILIPS 65	120			\$11.00
SNGAMO 45	110			\$8.75
PHILIPS 35	85			\$5.00
PHILIPS 35	117			\$6.00
SPRAGUE 75	145			\$19.00
SNGAMO 35	110			\$6.50
SNGAMO 65	85			\$13.00
SPRAGUE 50	110			\$12.00
SPRAGUE 50	120			\$12.00
SNGAMO 50	110			\$7.75
SNGAMO 50	150			\$10.00
SPRAGUE 50	145			\$13.00
SNGAMO 75	110			\$15.75
PHILIPS 50	120			\$13.00
PHILIPS 65	120			\$17.00
SNGAMO 35	135			\$6.00
SNGAMO 75	150			\$20.00
SNGAMO 50	125			\$12.50
SNGAMO 75	225			\$26.00
SNGAMO 75	125			\$22.00
SPRAGUE 50	145			\$14.50
SNGAMO 65	85			\$7.00
PHILIPS 65	115			\$13.00
SNGAMO 65	120			\$15.00
SNGAMO 75	150			\$20.50
SPRAGUE 65	145			\$18.00
PHILIPS 65	113			\$10.00
SNGAMO 65	135			\$12.00



SHERIDAN ELECTRONICS

164-166 Redfern St., Redfern NSW 2016. Phone (02)699 6912, (02)699 5922
Mail Orders to Dept EA, PO Box 229 Redfern NSW 2016

Trading Hours:-

Mon-Fri. 9am-5.30pm
Thursday 9am-7pm
Saturday 9am-12noon

Mail Charges:-

\$5.00-\$9.99 \$2.50
\$10.00-\$24.99 \$3.00
\$25.00-\$49.99 \$5.00
\$50.00-\$99.99 \$6.00
\$100.00 or more \$7.00

Heavy or bulky
items sent freight
forward by
'Overnights'

bankcard
welcome here

TRANSFORMER WINDING DETAILS

T1

- Core** FX2242, 36 mm dia. potcore, two halves with single section bobbin.
- Wire** enamelled copper wire, about one metre of 1 mm diameter wire and about 1.5 metres of 0.4 mm.
- Primary (a-b)** 20 turns of 0.4 mm wire wound evenly on the bobbin. Cover with a layer of insulation tape. Note that b is the start.
- Secondary (c-d, e-f)** 4 turns, bifilar wound (see diagram), of 1 mm wire spread over bobbin. Cover with a layer of insulation tape. Bring out the starts at one end of the bobbin, finishes at the other. Starts are c and e.
- Notes** The above refers to T1 wound for a **12 V (nominal) supply**. On a **24 V (nominal) supply**, the primary (a-b) and secondary (c-d, e-f) should be doubled (i.e. 40 turns and 8 turns, bifilar, respectively). On a **32 V (nominal) supply**, the primary turns (a-b) should be increased to 50, the secondary (c-d, e-f) to 10 turns, bifilar.
- Winding order** Wind the primary (a-b) first.

T2

- Core** Philips EC-core assembly, as per the parts list.
- Wire** enamelled copper wire, 0.4 mm dia. — length to suit application, and about two metres of 1 mm dia.
- Primaries (u-v, u'-v', w-x, w'-x')** use 1 mm wire wound **quadrifilar** (see diagram), two volts per turn. i.e. for 12 V (nominal) supply — six turns; for **24 V (nominal) supply** — 12 turns; for **32 V (nominal) supply** — 16 turns.
- Secondary (y-z, y'-z')** 0.4 mm or 1 mm wire (to suit current) bifilar wound, two volts per turn. i.e. for **±40 V supply rails** — 20 turns; for **±50 V rails** — 25 turns, etc. See table of suggested outputs.
- Winding order** Wind the quadrifilar primaries (u-v, u'-v', w-x, w'-x') first. Cover with two layers of insulation tape.

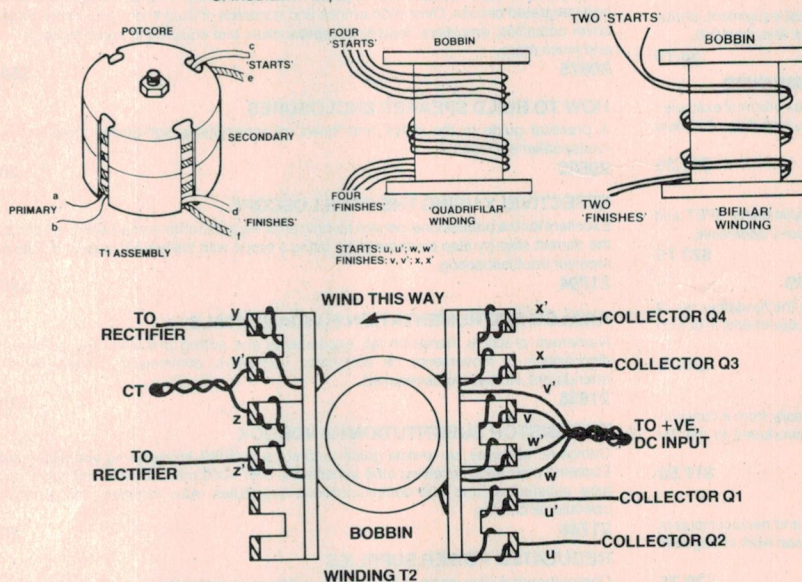


TABLE OF SUGGESTED OUTPUTS

OUTPUT	T2 SECONDARY	RECTIFIER	APPLICATION
±50 V	25 turns bifilar	2 x fullwave	Power 2 x ETI-477 (Series 5000) or 1 x ETI-498 module.
±40 V	20 turns bifilar	2 x fullwave	Power 2 x ETI-480 (50 W or 100 W versions) or 2 x ETI-470 modules.
±15 V	8 turns bifilar (Note 1)	2 x fullwave	Auxiliary secondary to power a preamp. e.g. ETI-481M guitar mixer/preamp or ETI-498 PA preamp.
1400 V	700 turns (Note 2)	voltage doubler (Note 2)	Power ETI-565 laser
12 V (from 24 V or higher dc input)	7 turns (Note 1)	fullwave bridge	Power 12 Vdc equipment from 24 V or higher dc input.

Note 1. This takes rectifier voltage drop into account.

Note 2. The secondary can drive the ETI-565 laser power supply directly, replacing the original power transformer.

► from page 37

transistors should be quite low. They should only get warm to the touch. (But don't touch them while the inverter's operating — you can get a 'belt'!) You will notice that the operating pitch of the inverter drops when a load is applied.

If all tests out well, hook up the inverter to the unit it is intended to power and try it out. With audio amp modules the 6 kHz oscillation frequency of the inverter should not be audible in the loudspeakers or should be a very, very long way 'down'. Where it is used in conjunction with a sensitive preamp, earthing loops and supply line induction into input leads and earths can cause 'break through' of the 6 kHz oscillation frequency. Take care with the routing of supply leads from the inverter. Keep them away from input leads and make sure the audio equipment is earthed at a single point, either at the power supply chassis or at the dc input common (negative).

Avoid radiation from the inverter inducing 6 kHz breakthrough into any equipment by keeping the inverter physically separate from such equipment. Both transformers have very little external field, but the wiring of the inverter carries considerable switching currents and can induce small, but significant, signals into sensitive audio or RF input leads. If you intend mounting it inside the equipment case, build it in a separate, shielded (i.e. all metal) enclosure and mount that inside the equipment but away from input circuitry.


Performance

This project was hastily built up one Saturday, from a 'lash-up' prototype, to power the ETI-498/499 PA amp for a function the following day! It worked first off. We didn't even have to reverse the primary of T1 to get the feedback phase correct!

Performance was faultless — for both the inverter and the PA.

Occasionally you win some! Breakthrough of the 6 kHz oscillation frequency was only evident with the low level mic gain and the volume pot on the PA amp set full up. Two secondaries were wound on the inverter output transformer (T2), one to provide the power amp with ±50 V and the other to provide the preamp with ±15 V. The breakthrough was subsequently found to be primarily due to a double-earthing problem.

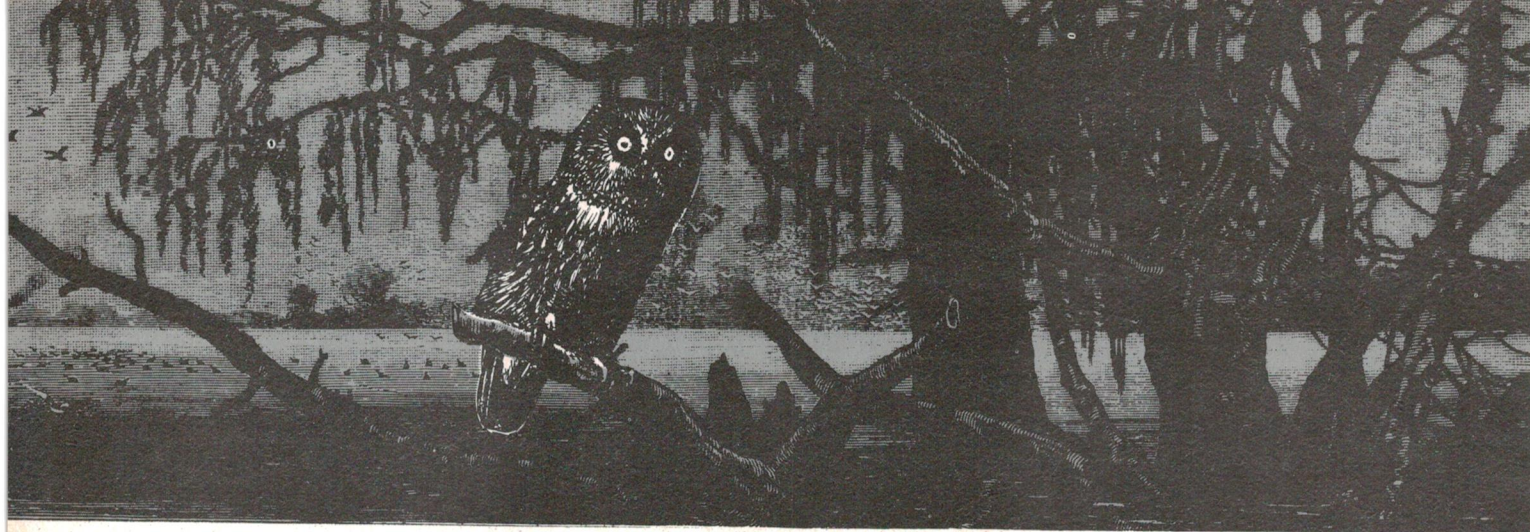The PA amp ran from a 12 V battery faultlessly for an all-day event. The inverter ran cool — admittedly, it was midwinter and quite cold, but efficiency approaches or exceeds 90% and in this sort of application, average dissipation is very low.



Getting swamped in high technology?

REFERENCE DATA FOR RADIO ENGINEERS

The largest and most comprehensive collection of equations, graphs, tables, and other reference data needed in general radio engineering and design. Contains hundreds of charts, monographs, diagrams, curves, tables and illustrations.

21218 \$51.00

99 PRACTICAL ELECTRONIC PROJECTS

Sixteen different groups of projects for the beginner — audio amps, test equipment, photography, devices for your car. Many of the projects can be constructed for less than \$10.

21635 \$8.75

555 TIMER APPLICATIONS SOURCE BOOK, WITH EXPERIMENTS

This book describes the construction of the 555 timer and gives numerous practical examples of its applications in all areas of electrical and computer engineering, including 17 simple experiments.

21538 \$11.25

IC OP-AMP COOKBOOK

Basic op-amp theory in detail, with 200 practical, illustrated circuit applications: JFET and MOSFET units are featured, plus manufacturers' data sheets and company addresses.

21695 \$23.75

DESIGN OF TRANSISTOR CIRCUITS, WITH EXPERIMENTS

A self-teaching course in transistor circuits — seven chapters explore the fundamentals of active semiconductors and their operating principles and procedures. Experiments in design and semiconductor testing provide hands-on experience.

21626 \$20.75

TV TYPEWRITER COOKBOOK

This book shows you how to project words and pictures quickly and easily from a common microprocessor-based system onto an ordinary TV set. You'll be introduced to the TV typewriter (TVT) communication medium.

21313 \$17.50

DON LANCASTER'S MICRO COOKBOOK, VOLUME 1

This 'cookbook' starts with the very fundamentals of microprocessors and microcomputers and takes you through number systems, codes, memory, etc., until you can work intelligently with micros.

21828 \$20.75

DON LANCASTER'S MICRO COOKBOOK, VOLUME 2

Carries on where Volume 1 left off.

21829 \$20.75

CHEAP VIDEO COOKBOOK

Complete discussion of a new, low-cost way to get words, pictures and opcode out of your computer and onto any ordinary TV screen, using a seven-IC easy-to-build circuit which you can build for less than \$20.

21624 \$11.75

TTL COOKBOOK

A complete look at TTL logic circuits — what TTL is, how it works, and how to use it. Many kinds of practical TTL are included, such as digital counters, electronic stopwatches, digital voltmeters, etc.

21035 \$17.50

ACTIVE-FILTER COOKBOOK

Learn how to construct filters of all kinds — highpass, lowpass, bandpass. The book is easy to understand — no advanced maths or obscure theory is used.

21168 \$21.95

PRACTICAL SOLID-STATE CIRCUIT DESIGN

An introductory course in practical solid-state circuit design for the experimenter, designer or technician who is interested in constructing 'tailor-made' circuits.

21787 \$14.95

MICROCOMPUTER INTERFACING WITH THE 8255 PPI CHIP

A self-instructional text designed to introduce you to the Intel 8255 Programmable Peripheral Interface (PPI) through discussion and practical experiments.

21614 \$14.95

AUDIO CYCLOPEDIA

A complete, in-depth look at the art of audio — from the basic principles of sound to solid-state and integrated circuits. Over 3000 entries and hundreds of illustrations and circuit diagrams cover acoustics, amplifiers, recording, reproduction, test equipment, audio measurements, and much more.

20675 \$66.00

HOW TO BUILD SPEAKER ENCLOSURES

A practical guide to the 'whys' and 'hows' of constructing high-quality top-performance loudspeaker enclosures.

20520 \$8.75

EFFECTIVELY USING THE OSCILLOSCOPE

Excellent for the professional service technician or the serious do-it-yourselfer, as it combines the correct step-by-step procedures for using a scope with the specific nuts and bolts of TV receiver troubleshooting.

21794 \$14.95

ANALOG INSTRUMENTATION FUNDAMENTALS

Numerous practical, hands-on lab experiments and solved problems are included, plus discussions of movements, dc ammeters, voltmeters, ohmmeters, bridges, filters and attenuators. No calculus is required.

21835 \$29.75

TRANSISTOR SUBSTITUTION HANDBOOK

Complete, accurate, up-to-date guide to direct substitutes for receiving and picture tubes. Contains over 6000 receiving tube substitutes, over 4000 monochrome and colour picture tube substitutes, and 600 communications substitutes. Also includes pinouts for quick operational checks.

21746 \$8.75

REGULATED POWER SUPPLIES

Comprehensive discussion of the internal architecture and operation of the latest solid-state regulators. Explains when regulated supplies are needed and how to incorporate them in your projects, and discusses modern circuitry including linear and switching circuits and late ICs.

21808 \$29.75

IC TIMER COOKBOOK

Gives you a look at the hundreds of ways IC timers are used in electronic instrumentation.

21416 \$15.95

AUDIO IC OP-AMP APPLICATIONS

This book discusses IC op-amps and their application in audio systems, and describes the numerous advantages of using op-amps, including small spatial needs, low power consumption, reliable performance and low cost. Assumes a basic understanding of op-amp theory.

21558 \$13.25

DESIGN OF OP-AMP CIRCUITS, WITH EXPERIMENTS

The design of the fundamental circuits that are the basic building blocks of more sophisticated systems. A series of 35 experiments illustrates the design and operation of linear amps, differentiators and integrators, voltage and current converters, active filters, and lots more.

21537 \$16.50

VIDEO TAPE RECORDERS

In this completely revised second edition, the author tells in simple language how helical VTRs work and how to operate and service them. Includes numerous examples of circuits and mechanical systems.

21521 \$17.50



Here's 39 new ways out of the maze!

RF CIRCUIT DESIGN

A practical approach to the design of RF amplifiers, impedance-matching networks and filters. Uses a minimum of complex maths.

21868 \$29.75

PRACTICAL TRANSFORMER DESIGN HANDBOOK

An easy to understand, illustration-filled guide to designing and constructing transformers. Reviews the fundamentals of electricity, magnetism and algebra needed to understand transformer theory, and covers general design considerations, transformer types, power losses and transformer use in converters and inverters.

21657 \$36.25

UNDERSTANDING CMOS INTEGRATED CIRCUITS

This book tells you what CMOS ICs are, how they work, and how they can be used in electronic circuit designs. Many practical circuits, complete with parts values, are included.

21598 \$9.95

GUIDE TO CMOS BASICS, CIRCUITS, AND EXPERIMENTS

If you are already familiar with TTL devices and are ready to examine the benefits of CMOS, this book is your complete source. It tells you what CMOS devices are, their characteristics and design rules. 22 experiments demonstrate the concepts discussed.

21654 \$14.95

SCRS AND RELATED THYRISTOR DEVICES

Written for experimenters, technicians and engineers, this book is a practical and comprehensive guide to theory, operation, specifications and applications of silicon-controlled rectifiers (SCRs) and related thyristor devices.

21806 \$19.25

CMOS COOKBOOK

This book explains CMOS technology and its application to 'real-world' circuitry. A mini-catalogue is included, which lists over 100 devices, giving their pinouts and application notes.

21398 \$19.25

MODERN RECORDING TECHNIQUES

Explains the equipment, controls and techniques found in a modern recording studio and how to use them creatively and correctly to produce a desired result. Numerous photographs, diagrams and charts.

21037 \$19.25

UNIQUE ELECTRONIC WEATHER PROJECTS

Fun and easy-to-build projects include an IC barometer to serve as a tornado warning and a 'thermostat with a brain' to help conserve energy.

21484 \$13.25

TROUBLESHOOTING WITH THE OSCILLOSCOPE

Excellent for the professional service technician or the serious hobbyist, as it combines step-by-step procedures for using the scope with the specific nuts and bolts of TV receiver troubleshooting.

21738 \$15.95

AUTOMOTIVE TUNE-UP AND EMISSION CONTROL SERVICE

Car owners who wish to save money and maintain their cars at peak performance will learn from this book how to adjust, repair and maintain the systems that ensure best operation.

21712 \$20.75

ELECTRONIC CIRCUITBOOK 1: PROJECT CONSTRUCTION

Your basic guide to project construction, covering component identification, power supplies, proper tool selection, troubleshooting techniques, oscilloscope use, custom-made enclosures, and more.

21241 \$7.50

DESIGN OF VMOS CIRCUITS, WITH EXPERIMENTS

The authors look at the technology which makes dramatic advancements possible with VMOS, and show how these components can easily and effectively be integrated into common circuit designs to enhance their responses.

21686 \$17.50

IC OP-AMP COOKBOOK

Guide covering basic op-amp theory in detail, with over 200 illustrated circuit applications to reflect the latest technology. JFET and MOSFET units are featured, and manufacturers' data sheets and addresses are included.

21695 \$23.75

IC CONVERTER COOKBOOK

Written for the practising engineer, technician, hobbyist or student, this book will be an invaluable working guide to the understanding and use of IC analogue/digital and digital/analogue converters.

21527 \$20.75

DESIGN OF PHASE-LOCKED LOOP CIRCUITS, WITH EXPERIMENTS


An excellent introduction to the theory, design and implementation of phase-locked loop circuits using various TTL and CMOS devices. Includes manufacturers' data sheets and describes the use of breadboarding aids in the wide range of laboratory-type experiments.

21545 \$15.95

INTRODUCTION TO AUTOMOTIVE SOLID-STATE ELECTRONICS

For the professional as well as the home mechanic — explains the functions of most on-board automotive black boxes and logic systems, including anti-skid braking, electronic spark control, diagnostic systems and trip computers.

21825 \$14.95

 **ORDER FORM**

Send to ETI Book Sales, 4th Floor, 15 Boundary St, Rushcutters Bay NSW 2011.

Please allow 4-5 weeks for delivery. Post & Handling: \$2.20 per book.

Please debit my ☐ Bankcard ☐ American Express card Expiry Date

Number:

Signature

Please supply

No.	Qty.	21035	21168	21416	21558	21835	21868	21974	21979
21218	21168	21558	21484	21738
21635	21787	21537	21712	21241
21538	21614	21521	21686	21695
21695	20675	21868	21527	21545
21626	20520	21657	21806	21825
21313	21794	21598	21398		
21828	21835	21654				
21829	21746	21806				
21624	21808	21398				

I enclose \$ inc. p&h

Name

Address

Postcode

NEW STORE
opening October
in Carlingford
AT CARLINGFORD COURT NEXT TO KENTUCKY FRIED CHICKEN

JAYCAR- for hard to get Semiconductors

WE NOW STOCK HUNDREDS MORE IC's THAN MOST OF OUR COMPETITORS AT
THE BEST PRICES AROUND

CMOS

4000	Dual 3 Input NOR Gate	
4001	Quad 2 Input NOR Gate	
4002	Dual 4 Input NOR Gate	
4006	18 Stage Static Shift Register	
4007	Dual Complimentary Pair Plus Inverter	
4008	4-Bit Full Adder	
4009	Hex Buffer (Inverting)	
4010	Hex Buffer (Non-Inverting)	
4011	Quad 2 Input NAND Gate	
4012	Dual 4 Input NAND Gate	
4013	Dual D Flip Flop	
4014	8-Stage Static Shift Register	
4015	Dual 4-Bit Static Register	
4016	Quad Analog Switch	
4017	Decade Counter/Divider	
4018	Resettable Divide-by-N	
4019	Quad AND OR Select Gate	
4020	14-Stage Binary Counter/Divider	
4022	Divide-by-8 Counter/Divider	
4023	Triple 3-Input NAND Gate	
4024	7 Stage Binary Counter/Divider	
4025	Triple 3-Input NOR Gate	
4026	Decade Counter-7-Seg Output	
4027	Dual JK Flip Flop	
4028	BOD-to-Decimal Decoder	
4029	Presentable Up-Down Counter	
4030	Quad 2 Input EXCLUSIVE OR Gate	
4031	64 Stage Static Shift Register	
4032	Triple Serial Adder	
4034	8 Stage TRI STATE Universal BUS Register	
4035	4 Bit Shift Register	
4038	Triple Serial Adder (Negative Logic)	
4040	12 Stage Binary Counter	
4042	Quad Clockable D Latch	
4046	Micropower Phase-Lock Loop	
4047	Low Power Mono/Astable Multi	
4049	Hex Inverting Buffer	
4050	Hex Buffer (Non-Inverting)	
4051	8 Channel Analog Multiplexer	
4053	Triple 2 Channel Analog Multiplexer	
4055	Dual Analog Switch	
4066	1-of-16 Analog Switch	
4068	8 Input NAND Gate	
4069	Hex Inverter	
4070	Quad 2 Input EXCLUSIVE OR Gate	
4071	Quad 2 Input OR Gate	
4073	Triple 3 Input AND Gate	
4075	Triple 3 Input OR Gate	
4076	Quad D Flip Flop	
4077	Quad EXCLUSIVE NOR Gate	
4078	8-Input NOR Gate	
4081	2-Input NAND Gate	
4093	Quad 2-Input NAND Schmitt Trigger	
4411	Decade Counter 7 Seg Output	
4500	Triple Gate	
4502	Strobed Hex Inverter	
4503	Hex 3 Stage Buffer (Non Inverting)	
4508	Dual 4-Bit Latch	
4512	BCD to 7 Seg Decoder/Driver	
4514	4 to 16 Line Decoder/4 Bit Latched	
4517	Dual 64 Bit Static Shift Register	
4518	BCD Up Counter	
4520	Dual Binary Up Counter	
4526	Programmable 4-Bit Binary Counter	
4528	Dual Mono Multi	
4538	Dual Mono/Precision Multi	
4543	BCD to 7 Seg Latch/Decoder/Driver/LCD	
4553	3 Digit BCD Counter	
4557	1 to 64 Bit Variable-Length Shift Register	
4581	4 Bit	
4582	Look Ahead Carry Block	
4584	Hex Schmitt Trigger	
74C02	Quad 2 Input NOR Gate	
74C04	Hex Inverter	
74C14	Hex Schmitt Trigger	
74C22	16 Keyboard Encoder	

SUPPORT

8255	PPI	\$9.95
5303	UART	\$12.95
1771	Floppy Disk Controller	\$19.95
1488	RS232 Quad Line Driver	\$1.50
1489	RS232 Quad Receiver	\$1.50
8131	6-Bit Comparator (Negative Out)	\$4.95
81LS97	Octal Buffer	\$2.35
81LS98	Octal Buffer (Inverting)	\$2.35

74LS TTL

40	74LS00	Quad 2 Input NAND Gate	
35	74LS01	Quad 2 Input NOR Gate	
48	74LS02	Quad 2 Input NOR Gate	
40	74LS03	Quad 2 Input NAND Gate (oc)	
38	74LS04	Hex Inverter	
95	74LS05	Hex Inverter (oc)	
\$1.10	74LS08	Quad 2 Input AND Gate	
90	74LS09	Quad 2 Input AND Gate (oc)	
20	74LS10	Triple 3 Input AND Gate	
90	74LS12	Triple 3 Input NAND Gate (oc)	
\$1.00	74LS13	Dual NAND Schmitt Trigger	
95	74LS14	Hex Schmitt Trigger	
50	74LS20	Dual 4 Input AND Gate	
\$1.20	74LS21	Dual 4 Input AND Gate	
50	74LS27	Triple 3 Input NOR Gate	
75	74LS30	8 Input NAND Gate	
\$1.45	74LS32	Quad 2 Input OR Gate	
\$1.25	74LS33	Quad 2 Input NOR Gate (oc)	
28	74LS42	1 of 10 Decoder	
\$1.18	74LS47	BCD to 7 Seg Decoder/Driver (oc)	
35	74LS48	BCD to 7 Seg Decoder/Driver	
\$2.20	74LS49	BCD to 7 Seg Decoder/Driver	
90	74LS73	Dual JK Flip Flop with Clear	
\$1.18	74LS74	Dual D Flip Flop with Preset & Clear	
\$1.25	74LS75	4 Bit Bistable Latch	
80	74LS76	Dual JK Flip Flop	
\$2.20	74LS78	Dual JK Flip Flop	
\$1.95	74LS83	4 Bit Full Adder	
\$2.95	74LS85	4 Bit Magnitude Comparator	
50	74LS86	Quad 2 Input EXCLUSIVE OR Gate	
\$1.95	74LS90	Decade Counter	
\$1.65	74LS92	Divide by 12 Counter	
70	74LS93	4 Bit Binary Counter	
\$1.75	74LS101	4 Bit Shift Register	
75	74LS109	Dual JK Flip Flop	
60	74LS112	Dual JK Edge-Triggered Flip Flop	
95	74LS122	Retrig Monostable with Clear	
\$1.75	74LS123	Dual Retrig Mono with Clear	
50	74LS125	Quad BUS Buffer Tri-State (lo enable)	
\$2.95	74LS126	Quad BUS Buffer Tri-State (hi enable)	
48	74LS138	1-of-8 Bit Decoder/Multiplexer	
70	74LS147	10 Line dec to 4 Line Priority Encoder	
48	74LS148	8 Line to 3 Line Priority Encoder	
60	74LS151	1 of 8 Selector/Multiplexer	
65	74LS153	Dual 4 Line to 1 Line Selector/Mplexer	
\$1.25	74LS155	Dual 1 of 4 Decoder	
60	74LS156	Dual 1 of 4 Decoder (oc)	
65	74LS157	Quad 2 Input Multiplexer (Non-Inverting)	
\$1.50	74LS158	Quad 2 Input Multiplexer (Inverting)	
60	74LS160	BCD Decade Counter Asynch. Reset	
80	74LS161	4-Bit Binary Counter Asynch. Reset	
\$1.75	74LS162	BCD Decade Counter Synchron. Reset	
\$2.20	74LS163	4-Bit Binary Counter Synchron. Reset	
\$2.50	74LS164	8-Bit Shift Register	
\$1.95	74LS165	Parallel Load 8-Bit Shift Register	
\$1.95	74LS166	8-Bit PISO Shift Register	
\$5.00	74LS173	4-Bit D Type Register	
\$1.50	74LS175	Up/Down Decade Counter	
\$1.25	74LS191	Up/Down Binary Counter	
\$2.50	74LS192	Up/Down Decade Counter Dual Clock	
\$1.95	74LS193	Up/Down Binary Counter Dual Clock	
\$1.50	74LS194	4-Bit Left-Right Shift Register	
\$1.50	74LS195	4-Bit Parallel Access Shift Register	
\$1.50	74LS221	Dual Monostable Multivibrator	
\$1.25	74LS240	Octal Tri-State Driver	
\$2.65	74LS241	Octal Tri-State Driver	
\$1.95	74LS244	Octal Buffer/Driver	
\$6.50	74LS245	Octal Bus Transceiver	
\$3.50	74LS257	Quad 2 Input Multiplexer Tri-State	
\$2.50	74LS258	Quad 2 Input Multiplexer Tri-State	
\$2.50	74LS273	Dual D Type Flip Flop	
\$1.65	74LS276	Quad EXCLUSIVE NOR Gate (oc)	
50	74LS273	Octal D Type Flip Flop	
55	74LS365	Hex Buffer with Common Enable	
55	74LS366	Hex Inverter with Common Enable	
\$1.50	74LS367	Hex Buffer 4 Bit and 2 Bit	
\$9.50	74LS368	Hex Inverter 4 Bit and 2 Bit	
	74LS373	Octal Transparent Latch	
	74LS374	Octal D Type Flip Flop	
	74LS393	Dual L593	

SPEECH SYNTHESISER

DT1050	National Digitaltalker Processor & ROM Set	\$95.00
DT1057	National Digitaltalker Second ROM Set	\$69.00
Send SAE for more details. NOTE new low price. Data sheets included in chip sets.		

LINEAR DEVICES

35	ZN414	\$2.50	LM381N	\$3.95
40	TL061	\$2.45	LM381AN	\$5.95
40	TL062	\$2.45	LM382	\$2.60
60	TL064	\$4.75	LM394CH	\$5.95
40	TL071	98	NE555	35
60	TL072	\$1.45	LM7555	\$1.95
40	TL074	\$3.50	LM556	\$1.10
50	TL075	\$3.50	LM567	\$1.95
40	TL081	65	LM570	\$7.50
40	TL082	95	NE571	\$6.50
40	TL084	\$2.95	LM723	\$1.45
60	TL085	\$3.50	M741	40
85	LM234	\$3.50	LM747	\$1.95
40	LM301	60	LM1496	\$1.98
35	LM307	90	LM3046	\$1.45
60	LM308	\$1.25	LM3080	\$1.30
50	LM311	95	LM3130	\$1.80
45	LM319	\$3.50	LM3140	\$1.45
40	LM324	\$1.20	LM3900	95
50	LM334	\$2.50	LM3914	\$6.50
\$1.45	LM339	95	LM3195	\$4.50
\$2.95	LF347N	\$3.50	LM39152	\$12.50
\$1.95	LM348	\$2.25	LM4136	\$1.85
95	OM350	\$9.50	LM558	\$1.50
75	LM361	\$3.75	LM5534N	\$1.55
65	LM380	\$1.48	LM5534AN	\$2.00

DISCRETE DEVICES

\$1.25	VN88AF	\$3.00	BC547	15
50	BCY71	95	BC548	15
75	JD79203	\$1.95	BC549	15
\$1.25	40411	\$5.00	BC550	65
85	MJ15003	\$4.75	BC556	65
75	MJ15004	\$4.75	BC557	18
55	ZS49(P)	\$6.50	BC558	18
60	BDV648	\$5.95	BC559	18
60	BUX80	\$9.50	BC639	34
75	ZSK134(N)	\$6.50	BC640	34
\$1.10	BU105	\$12.50	BD266AD	\$1.50
55	MPSA05	95	BD139	53
75	TP131A/B	90	BD140	53
92	TP132A	90	MJ2955	\$1.50
\$1.45	TP12955	\$1.20	2N3055	\$1.50
\$2.95	TP13055	\$1.20	2N3442	\$2.50
\$3.95	MPF102	95	2N3569	45
75	MPF105/2N5459	95	2N3638	35
75	MPF106/2N5495	95	2N3643	45
\$1.00	MPSA11	95	2N3645	45
\$1.00	MFE133	\$1.98	2N3773	\$5.00
\$1.50	BF115	75	2N4258	35
79	BF200	95	2N4584	85
95	BF469	\$1.65	2N5087	65
95	BF470	\$1.65	2N5589	\$8.50
\$1.20	MJE340	\$1.98	2N5590	\$9.50
\$1.20	MJE350	\$1.98	2N5591	\$12.50
\$1.20	2TX501	45	2N5245	90
60	BC337	25	2N6027/D13T1	58
\$2.95	BC546	65	TT800	85
95	BF469	\$1.65	2N3566	45
75	BF470	\$1.65		

SPECIAL FUNCTION

\$1.65	SA80600	Door Chime	\$9.95
95	AY-15050		\$9.50
\$5.00	TEA-1002	PAL Colour Encoder	\$17.50
\$2.25	TD-1022	Bucket Brigade	\$29.50
\$3.50	EXAR 2206	Function Generator	\$5.95
\$3.50	MOC-3020	TRIAC Opto Coupler	\$3.90
\$2.95	MM 5837	Noise Generator	\$4.50
\$2.95	TA 7205P	Audic Amp	\$47.50
85	ZN16A	Frequency Control Display Driver	\$5.95
75	SN 76488NF	Sound Effects Generator	\$19.50
\$1.25	AY-0212	Tot Octave Synthesiser	

Z-80A/6800

Z-80A	CPU 4MHz	\$8.50	Z-80A	DART 4MHz	\$32.95
Z-80A	PID 4MHz	\$8.50	Z-80A	DMA 4MHz	\$20.95
Z-80A	CTC 4MHz	\$8.50	6802	CPU	\$11.00
Z-80A	SIO/0.4MHz	\$20.95	6810	RAM	\$4.95
Z-80A	SIO/1.4MHz	\$20.95	6821	PIA	\$4.95
Z-80A	SIO/2.4MHz	\$20.95			

ZENER DIODES

From 3.3V to 33V 35

JAYCAR DEALER: G&J Electric,
Forresters Beach NSW 2260
Ph: (043) 845787

125 YORK ST SYDNEY 2000
Ph. 2646688 Telex: 72293
Mail Orders To:
Box K-39 Haymarket 2000

MEMORIES

	1-7	8 up
2102	1K x 1 RAM	\$1.95 \$1.65
2114-3	1K x 4 RAM 350ns	\$2.45 \$2.00
4116	16K x 1 Dynamic RAM 250ns	\$2.50 \$2.00
6116	2K x 8 CMOS RAM	\$12.50 \$9.90
2708	1K x 8 EPROM	\$7.95
2716	2K x 8 EPROM (Single +5V)	\$6.50
2532	4K x 8 EPROM (Single +5V)	\$14.95
2564	8K x 8 EPROM (Single +5V)	\$35.00

VOLTAGE REGULATORS

7805	5V+ Regulator TO-220/amp	\$1.05
7805	5V- Regulator TO-220/amp	\$1.65
7812	12V+ Regulator TO-220/amp	\$1.05
7912	12V- Regulator TO-220/amp	\$1.65
7815	15V+ Regulator TO-220/amp	\$1.05
7915	15V- Regulator TO-220/amp	\$1.65
7812	12V+ Regulator 100mA	\$1.00
7815	15V+ Regulator 100mA	\$1.00
7915	15V- Regulator 100mA	\$1.00
LM323	3amp 5V TO-3	\$7.50
LM309	1.5amp 5V TO-3	\$1.50
LM317T	2-30V adjustable 1amp TO-220	\$2.80
LM317KC	2-30V adjustable 3amp TO-3	\$6.50
LM337K	3amp variable 2-30V TO3	\$3.50
LM396K	10amp variable 1.25-15V TO3	\$9.50

LED's

5mm Red	15 3mm Yellow	28
5mm Green	26 Rectangular Red	40
5mm Yellow	30 Rectangular Green	40
5mm Orange	28 Rectangular Yellow	40
3mm Red	18 Flashing Red	49
3mm Green	28 Flashing Red 10+ each	45

BRIDGE RECTIFIERS

W04	68
PD4	\$2.95
MOA3504	\$4.50

OPTO

COY89	Infr Red LED	\$1.25	FND500	"	\$1.35
BPW50	Infr Red Diode	\$2.95	FND507	"	\$1.75
LT332	7 seg Display	\$1.45	LT547	"	\$2.95
LT303	7 seg Display	\$1.45			

DIODES

IN4002	8 BA102	25 BYX21L/200R	\$1.90
IN4006	20 BA114	25 OA91	12
IN5404	35 BA215/219	25 OA202	50
IN5414	5 BR100	95 OA97	20
BAW62	29 BYX21L/200	\$1.90 5082-2800	\$2.75


IC SOCKETS - SOLDER

8 Pin	25	18 Pin	35	24 Pin	50
14 Pin	30	20 Pin	38	28 Pin	60
16 Pin	35	22 Pin	40	40 Pin	70



National

A NEW WAVE IS ON THE HORIZON

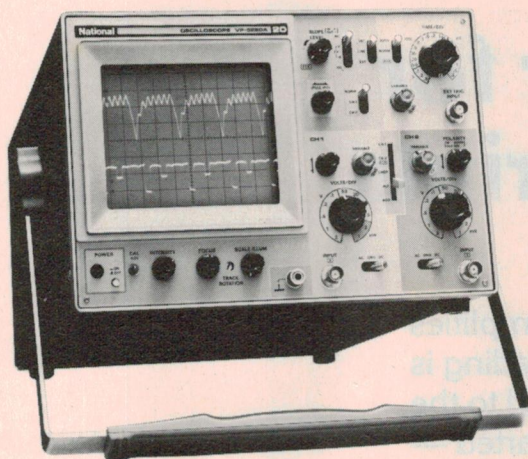

Available in four models these low cost oscilloscopes feature:

- 15-20-30 MHz.
- 1mV/Div sensitivity
- Stable automatic trigger 'AUTO FIX'
- Full range of triggering mode
- Bright and sharp CRT with Auto Fix
- TV(V) and TV(H) sync separator circuit
- Rectangular tube, illuminated internal graticule (VP-5220A and VP-5231A)
- Built-in delay line for observation of pulse transient (VP-5231A only)
- High reliability—MTBF 15,000 hours


National have a wide range of scopes—to 300 MHz. Please call or write for further information

...FROM \$389.00 (NOT INC. S.T.)

Probes supplied as standard accessory



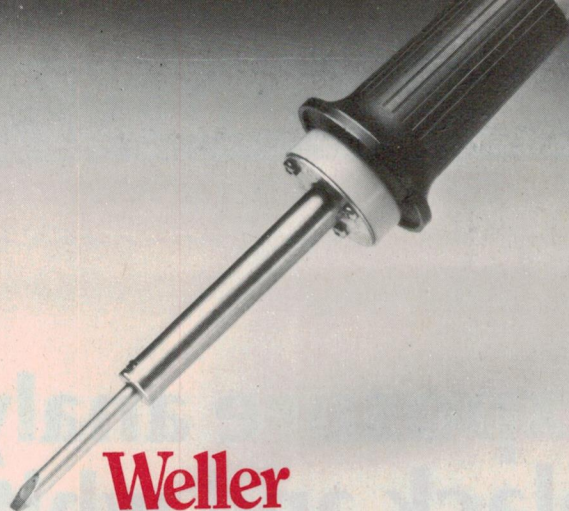SCIENTIFIC DEVICES AUSTRALIA PTY. LTD.
 2 JACKS ROAD, SOUTH OAKLEIGH, VICTORIA, 3167.
 TELEPHONE: 579 3622
 P.O. BOX 63, SOUTH OAKLEIGH, VICTORIA, 3167. TELEX: AA32742
 CABLES: DEVICES MELBOURNE
 31 HALSEY ROAD, ELIZABETH EAST, S.A., 5112.
 TELEPHONE: (08) 255 6575
 35-37 HUME STREET, CROWS NEST, N.S.W., 2065.
 TELEPHONE: (02) 43 5015



Weller



Weller

The Tools. from Cooper The Toolmaker.

Weller industrial SPI non-temperature controlled line voltage soldering irons, with iron plated copper tips, stainless steel barrels. Impact and heat resistant handles are lightweight.

Available as SPI25D 25 watt or SPI40D 40 watt irons.

The Weller WTCNP soldering station is temperature controlled and combines high volume capability with precision performance. The low voltage TC201 soldering pencil employs the exclusive "closed" loop method to control maximum temperature and protect sensitive components.



Lufkin

Official Supplier of
Measuring Tapes to the
XII Commonwealth Games
in Australia 1982.



The Cooper Group
 CRESCENT LUFKIN NICHOLSON PLUMB
 WELLER WISS XCELITE

The Cooper Tool Group Limited
 P.O. Box 366, Nungong Street
 Albury NSW 2640, Australia
 Tel. 215511 Telex: 56995

Exposure analyser for black and white prints

This exposure analyser, coupled to a timer, simplifies making black and white prints. A light intensity reading is taken from the image, the 'time' control is adjusted to the balance point and lights two LEDs, the timer is started — and your enlarger is turned on for the correct time.

Peter Cox


THE REASON for building an exposure analyser such as this was to avoid making test strips for different negatives or for different degrees of enlargement. Commercially available analysers are often either fiddly to use or comparatively expensive. Some operate by adjusting the aperture of the enlarger and keeping a constant exposure time, which is less satisfactory than varying the exposure time as most enlarger lenses give better performance when stopped down from maximum aperture.

There have also been several analyser circuits in electronics magazines, but I found these to be either too full of drafting errors to be practicable or, in one case, going into technical overkill — using 23 ICs, digital exposure readout to tenths of a second, and requiring an IC (CA3140) to perform better than its published specifications. So I decided to design and build my own exposure analyser.

Circuit operation

The circuit is in two parts, excluding the power supply: the light-measuring comparator has an LDR in one leg of a resistive bridge.

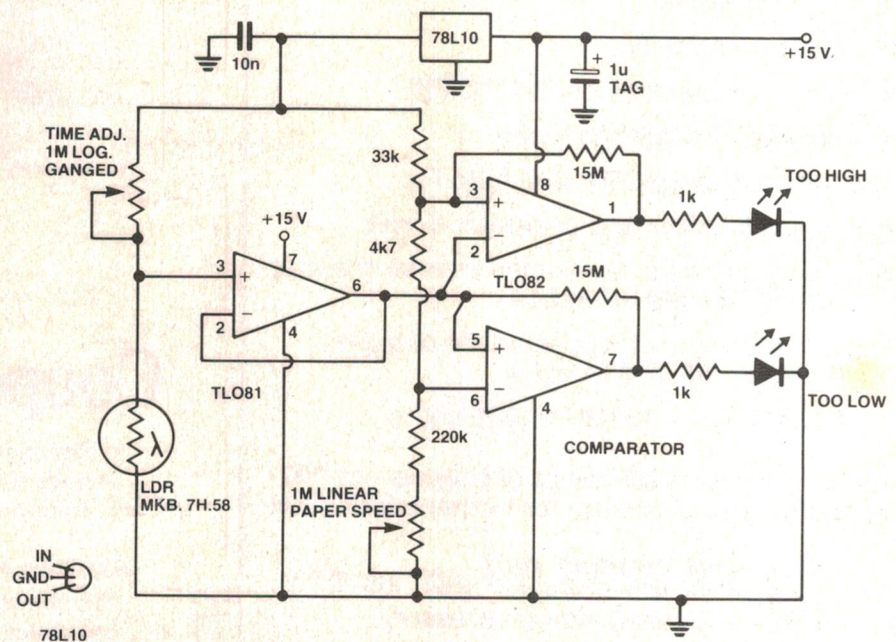As the LDR resistance can be up to 20-30k, the voltage is buffered by a TLO81 BiFET op-amp. Voltages from the bridge are applied to a window voltage comparator made from a dual BiFET IC. A small amount of hysteresis



78L10

NOTES:

1. TLO81, TLO82 ARE BIFET OP-AMPS, VERY HIGH INPUT IMPEDANCE: 10^{12} OHMS TYPICAL.

2. BYPASS 78L10 REGULATOR WITH CAPACITORS SHOWN: MAKE SURE THEY'RE CLOSE TO THE IC.

3. SET 1M LOG. (GANGED) POT TO 50% ROTATION: RESISTANCE SHOULD BE CLOSE TO 100k. WITH 2k 'CALIBRATE' POT NEAR MIDDLE, PICK CAPACITOR TO GIVE PULSE DURATION OF 10 SECONDS. TRIMPOT HAS ADJUSTMENT RANGE OF +40%, -20%.

USE:

1. SET TIME ADJUST POT TO 10 SECONDS. MAKE A PRINT THAT REQUIRES 10 SECONDS EXPOSURE: WITH LDR MEASURE MID-GREY OR HIGHLIGHTS (NOT BOTH) AND ADJUST PAPER SPEED POT FOR BRIDGE BALANCE: BOTH LEDS LIGHT.

2. PUSH START BUTTON TO BEGIN TIMING CYCLE.

is provided by the 15M resistors. I didn't worry about using buffering on the other side of the bridge because of lower resistances.


The bridge is fed from a 10 V voltage regulator, as otherwise the IC output voltages may be restricted, the inputs working within 0.75 V or so of the posi-

tive rail. The time adjust pot, a 1M log unit, is ganged, and the other section determines the output duration of a 555 monostable. A timer calibrate pot is included to simplify setting up the timer.

The capacitor used in the 555 RC network should be very low-leakage, but ordinary tag tantalums seem to give consistent timings despite leakage currents of 50 nA/uFV (maximum quoted on ITT tag data sheet).

Parts

BiFET op-amps are freely available — singles, duals or quads; the TLO84 quad costs \$3 or less. The LDR is made in Japan by Moririca, and is sold by Plessey Professional Components of Villawood NSW, costing \$1 each in small quantities (when I bought some a while ago). There are many Moririca types available, so others may be more suitable than the ones I used; I bought the LDRs originally for use in an AGC amplifier, as an LDR-LED gain reduction element.

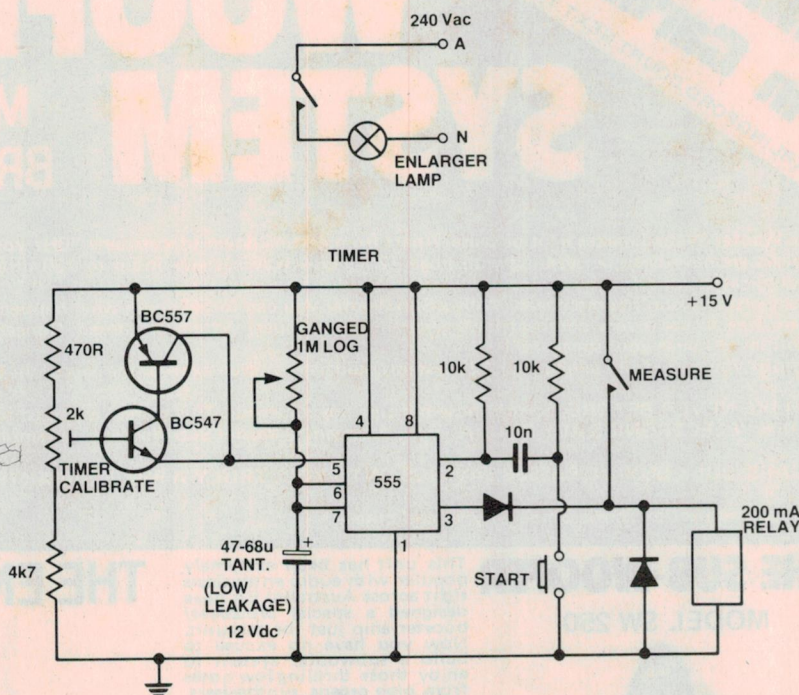

ELECTRONIC HOBBYIST!

DO YOU LIVE IN ...

Ringwood Lilydale
Boronia Wantirna
Bayswater Croydon
Moorebank etc....

We carry a comprehensive range of electronic components at very keen prices.

Ian J. TRUSCOTT ELECTRONICS

CNR EASTFIELD
& BAYSWATER ROADS,
SOUTH CROYDON, VIC.
TELEPHONE (03) 723 3860

Sensitized P.C. Board Riston 3000 Coated

(Fibreglass Base)

	SINGLE	DOUBLE
36x24	\$45.00	\$57.00
24x18	\$22.00	\$30.00
18x12	\$12.50	\$16.00
12x12	\$ 7.90	\$10.75
12x 6	\$ 4.50	\$ 5.85

Quantity Discounts

\$100+	10%
\$250+	12½%
\$1000+	15%

All plus sales tax if applicable.

RISTON DEVELOPER PROMOTION SPECIAL

Concentrate (1 = 4) \$4.25 litre
—5 litre \$19.50—

3M SCOTCHCAL
Image 'N' Transfer
MAJOR STOCKISTS

KALEX

101 Burgundy St,
Heidelberg 3084
(03) 458 2976
Telex AA 37678
MELTON
(03) 743 1011

MOSS COMPONENTS

PO BOX 324, FAIRFIELD, NSW 2165.

Capacitors & Resistors
Integrated Circuits
Wires & Cables
Semiconductors
Hirose Connectors
Ribbon Cable
Plugs & Sockets

MAIL ORDER SUPPLY SPECIALISTS

FOR YOUR ELECTRONIC NEEDS

**NEW STORE
opening October
in Carlingford**

AT CARLINGFORD COURT NEXT TO KENTUCKY FRIED CHICKEN

SUB- WOOFER SYSTEM



**MASSIVE PRICE
BREAKTHROUGH!!!**

A Sub-Woofers System makes a lot of sense. Apart from getting down to a genuine 30Hz you could actually save money over all. For years we have been persevering with huge 12" 3 or 4 way systems in up to 120 litre cabinets to try to get down to—at best 45Hz. We have even duplicated our effort by having a stereo pair for this frequency!!!

Big 12" systems don't come cheap. With a Sub-Woofers you can forget about what happens below the non-stereo <100Hz region. Once that's done you are free to use a very compact (and generally far cheaper) system for stereo. Concert hall sounds in your lounge room without needing an auditorium to house your speakers.!!!

The profit you make from selling your 12" system could pay (or even exceed) the cost of the Sub-Woofers system. — AND you can get down to 30Hz!!!

1812 LIKE NEVER BEFORE. So too those big pipe organ records. This system is a must for the direct or digital disk enthusiast. Now that "ELECTRONICS AUSTRALIA" have designed *a Mosfet Sub-Woofers, filter/amplifier and speaker system you have no excuse.

JAYCARS' BULK BUYING PASSES SAVINGS ONTO YOU. TRULY A PRICE BREAKTHROUGH FOR SUB-WOOFERS SYSTEMS.

*(With due respect to Thiele, Small, Snyder and others!)

THE SUB-WOOFER

MODEL SW 250



ONLY \$79.50

This unit has been extremely popular with audio enthusiasts right across Australia! EA have designed a special crossover/booster amp just for this unit. Now you have no excuse to build a subwoofer system to enjoy those thrilling low notes from pipe organs, synthesizers, 1812 cannons etc!!

SPECS:

Diameter 10" (250mm) Cast Frame. QT=0.39. VAS=631
Power Handling = 100WRMS.
Free-air Resonance 32Hz ±1Hz
Voice Coil = 2" (51mm). Dia.
Magnet Assy = 3kg (6.6lbs).

A FREE SUB-WOOFER
CABINET DESIGN IS
PROVIDED WITH EACH
UNIT!!

THE ENCLOSURE




ONLY \$79⁵⁰

This compact 63 litre vented enclosure was specifically designed around the parameters of the SW250 Sub-Woofers. It follows the theory pioneered by the work of Thiele, Small and Snyder. The Jaycar enclosure is easy to build and is made of high quality durable materials. The heavy walled cabinet is covered with an attractive black vinyl veneer. All timber is pre-cut and the black grille is already made. Assembly takes less than one hour.

NB. The photo shows the prototype which was finished in white. The production units are only available in black. Freight anywhere in Australia only \$10.00.

AMPLIFIER/FILTER UNIT

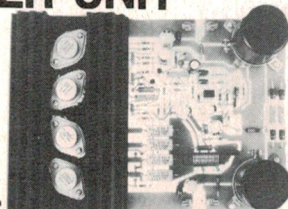

REF. EA JULY 1982

State-of-the-art power Mosfet technology combined with an active low pass filter results in a sub-woofer amp without equal anywhere!!

FEATURES: Around 100WRMS Drive capability.
Low pass (sub-woofer) filters on board.
Can hook-up to pre-amp out or power-amp out.
Power supply on board.
(Transformer needed. ONLY \$39.50)

ONLY \$79

AMPLIFIER/FILTER
UNIT:
Amplifier Module \$79
Transformer to suit \$39.50

Metal case specially made to suit including front panel, hardware etc. (not a twin 25 case). Only \$29.50 \$148.00

Buy the lot for only \$125.00 If you purchase the enclosure and woofer at the same time.

VOICE OPERATED RELAY KIT

Ref: EA July '82
Extremely useful circuit, has dozens of applications.


\$14.50

technical

- Signal-to-noise Microphone Input — 75dB with ref to +4dBm
- Signal-to-noise line input — 90dB with ref to +4dBm
- Line out level +4dBm (0VU)
- Distortion less than 0.005%
- Power requirements 240VAC 50Hz 25 watts

dimensions

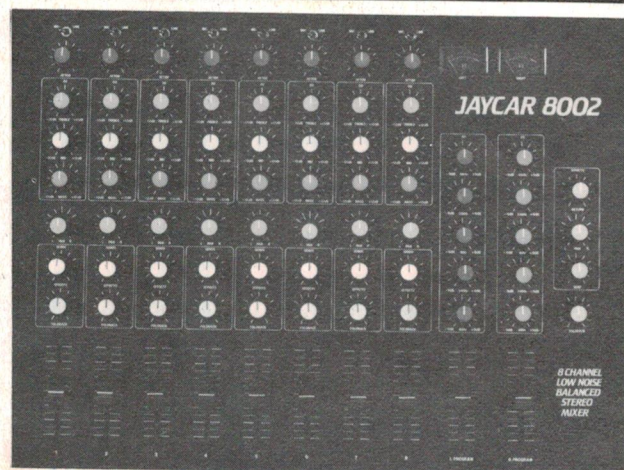Width 483mm
Height 355mm
Depth (console mount) 150mm



- Balanced (600 Ohm) Mic. Inputs/Line Inputs.
- Cannon Connectors included in the price.
- Bass, Mid & Treble Equalization on each Input.
- "Effects" (i.e. Echo etc.) capability.
- Foldback and Stereo Pan on ALL 8 Inputs.
- 60mm Slide Faders used throughout.
- 19" Rack Mount capability (or Console Mount).
- Professional Black Front Panel with Format borders & multi-coloured knobs to assist function identification.
- VU Metering.

SEND SAE FOR FULL DATA ON 5000 SERIES &/OR MIXER

JAYCAR DEALER: G&J Electric, Forresters Beach NSW 2260 Ph: (043) 845787

MOSFET MAGNIFICENCE

THE 5000 SERIES AMPLIFIERS FROM ETI
HAVE NO EQUAL

POWER AMP. REF: ETI JAN. MAR. 81

"BLACK MONOLITH"

SPECIFICATIONS

POWER OUTPUT FREQUENCY RESPONSE

Around 100W RMS into 8 ohms
8Hz to 20kHz, +0 - 0.4dB
20Hz to 65kHz, +0 - 3dB
Note: these figures are determined solely by passive filters

INPUT SENSITIVITY

HUM

NOISE

2nd HARMONIC

DISTORTION

3rd HARMONIC

DISTORTION

TOTAL HARMONIC


DISTORTION

INTERMODULATION

DISTORTION

STABILITY

1V RMS for 100W output
- 100dB below full output (flat)
- 16dB below full output (flat, 20kHz bandwidth)
<0.001% at 1kHz (0.0007% on prototypes) at 100W output using a 56V supply rated at 4A continuous
<0.003% at 10kHz and 100W
<0.0003% for all frequencies less than 10kHz and all powers below clipping
Determined by 2nd harmonic distortion (see above)
<0.003% at 100W (50Hz and 7kHz mixed 4:1)
Unconditional

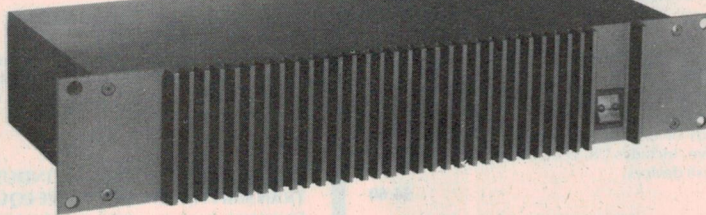

In "2001" Arthur C. Clarke's Black Monolith symbolised awesome power - intelligence. So too do the 5000 "BLACK MONOLITH" Power Mosfet amp kits from Jaycar. Why would you choose a Jaycar "BLACK MONOLITH" 5000 Power amp over conventional kits? Because you, too are intelligent. You have seen the specs, and you know that this amp IS the best. You want the best because (whether you know it or not) you are a perfectionist. You won't be conned by cheap and nasty compromises to David Tillbrook's brilliant design. You will want to know if there have been mods to the original design. (There have - and only Jaycar kits reflect them). But let's be specific about the improvements.
- Completely redesigned flag heatsinks for the Driver Transistors. Thoroughly endorsed by David Tillbrook. (The original ones were too small for the bias current was set high for low distortion).
- Ventilation grilles in the covers. These were not included in the original design.
- Blind tapped holes in the exclusive 'Superfinish' front panel. Heavy gauge screws used for stronger connection of the heatsink bracket to the panel.
- Jig drilled, EXTRUDED, deburred and black anodised heatsink bracket in heavy gauge. All other kits we have seen, a flimsy punched out piece of sheet metal is supplied. Not even anodised!! This is one of the most critical components in the kit.

- Beryllium Oxide heatsink washers supplied. A tube of heatsink compound is also supplied - with enough left over to use elsewhere.
- 'Superfinish's Front Panel. Despite what others may claim ours is still the best.
- Dual 3 Pin DIN 30V Power Outlets. This extra power outlet enables you to power extra 5000 series components as they arrive on the scene.
- And all of the extra features of our normal Superfinish 5000 amp, like: Metal 1% film resistors, Pre-wound Chokes, Fibreglass PCB's, Heavy Duty Earth Braid, Quality Capacitors, Original Chassis - bar design, Flux shorting straps on transformers etc., etc.
The Jaycar "BLACK MONOLITH" is worth far more than the inferior kits around the market today. That goes without saying.

BUT IT COSTS NO MORE!

That's right. FOR THE MOMENT we are holding our price on this kit to a staggering low \$299. We probably won't be able to keep this quality kit below \$300 for long. We all enjoyed '2001' for the first time a long time ago now. You can enjoy your 5000 "BLACK MONOLITH" forever!

ONLY \$299—
PAY NO MORE!!!

"BLUEPRINT" 5000 PREAMPLIFIER



BLUEPRINT \$275

The refinement continues. The silk screen stencil for the front panel is renewed after every run of 25 panels. This ensures the crispest possible lettering. Note that ONLY JAYCAR use the ORIGINAL ETI front panel design. Don't get caught with something you may not like the look of! We use the extra high quality LM394H in the M.C. preamp, and now AT NO EXTRA CHARGE supply gold plated RCA sockets on all inputs, not just the M.C. input.
Despite what others may say, their's is not as good as the original BLUEPRINT Preamp. They do not, for example, get special low capacitance screened cable made to Jaycar specs. just for the pre-amp. (It's made in Australia, not Taiwan).

AMONG OTHER FEATURES OF THE BLUEPRINT :-
- EXTREMELY CLOSE TRACKING TO
- RIAA EQUALISATION.
- ENGLISH 'LORLIN' LOW NOISE
- SELECTOR SWITCHES USED
- LOW NOISE 1% METAL FILM
- RESISTORS USED
- TINNED F/GLASS PCB'S
- QUALITY IC SOCKETS PROVIDED
- SPECIAL REAR PANEL
- MULTICOLOURED LED
- DISPLAY (EASIER TO READ
& BETTER LOOKING)
- THERMALLOY HEASINK USED
ON REGULATOR

We still have the standard \$245 version of this kit which is better than the other \$245 kits. We don't sell many though - the BLUEPRINT is better value. 'BLUEPRINT' ONLY \$275.

SPECIFICATIONS

Frequency Response

High level input: 15Hz-150kHz, 0-1dB
Low level input-conforms to RIAA equalisation
0.001% (see detail on Phono spec.)
1kHz 0.003% on all inputs (limit of resolution on measuring equipment due to noise limitation)
High level input, master full, with respect to 300mV input signal at full output (1.2V)
92dB flat, 100dB A-weighted

Distortion

MM input, master full, with respect to full output (1.2V) at 5mV input, 500 ohm source resistance connected 86dB flat
92dB A-weighted

S/N noise

MC input, master full, with respect to full output (1.2V) and 280mV input signal
71dB flat 75dB A-weighted

ETI-478MM Moving Magnet input stage

Gain

Frequency Response

Disorder

Noise

S/N ratio

ETI-478MC Moving coil input stage

Gain

Frequency Response

Disorder

Noise

S/N ratio

Total Harmonic Distortion

Gain

Frequency Response

Disorder

Noise

S/N ratio

Total equivalent input noise

Gain

Frequency Response

Disorder

Noise

S/N ratio

15, 1kHz
Conforms to RIAA Equalisation = 0.2dB

0.001%, 1kHz, 10mV RMS input

28dB with respect to 5mV RMS input signal, i.e. 130mV RMS

Total equivalent input noise, 122mV 'A', input shorted, 216mV flat, input shorted

Flat 1mV 5mV 10mV

73dB 87dB 93dB

A-weighted 78dB 92dB 98dB

24

7Hz-15kHz 0-1dB

0.003%, 1kHz, 30mV input

Total equivalent input noise

83mV flat, input shorted

42mV 'A', input shorted

56mV flat, after RIAA Eq. input shorted

34mV 'A', after RIAA Eq. input shorted

FROM \$245

8 CHANNEL MIXER 8002

PRICE
BREAKTHROUGH!!!

The Jaycar 8002 Mixer was originally conceived to be the successor to the very popular ETI414 Master Mixer. The 414 was basically configured as a 'stage' mixer and suffered from a number of severe technical limitations - notably poor signal-to-noise figures. Enormous advances in Audio IC's have occurred since the 414 was designed. Jaycar engineers have taken advantage of this. The incredibly low noise and distortion figures of the 8002 are a testimony to the sound basic design of the mixer coupled with the performance capability of these IC's. Whilst the 8002 is the ideal 8 channel compact stage mixer, other applications have been kept in mind. AS A 'STUDIO' MIXER. The prime requirement of a studio mixer is that it must be quiet - i.e. have good S/N. Due to the fact that the 'miracle' 5534 IC's are used in the 8002 studio applications are entirely feasible. In addition to this, metal film resistors are used in critical signal areas. AS A DISCO MIXER. The balanced input feature of the 8002 is not really necessary for disco use. This section can easily be bypassed with either a moving magnet (Dynamic Cartridge) preamp, or a moving coil preamp. The sensible format of the 8002 and tremendous equalization facilities should make this mixer popular for disco use.

AS A STAGE MIXER

This is where the 8002 really excels. The 8002 front panel measures 19" wide x 14" high (8 rack units). This enables the 8002 to be mounted into PA equipment racks if necessary. Strickly speaking, the chassis is not needed in this configuration although the chassis is also rack mountable. The 8002 can also console mount with attractive heavy timber end-pieces adding to the appearance of the unit. Powerful "Sends" capability is built into this mixer. Both special effects ('cho' for example) and foldback for the stage performers can be sent FROM ANY ONE OR ALL of the 8 input channels. Fully variable calibrated sends attenuators are provided on each channel. Sends can be panned across the stereo image to create spectacular sonic effects. You could, for example, pan a pre-recorded tape of a steam train rushing from the right hand side of the stage - across - and exit stage left with this facility. Balancing sorts the real mixers out from the toys. With the 8002 you can take either a microphone level input or a line level input into any of the 8 channels. An input selector switch is provided at the top of the mixer panel. Another attenuator is provided at this point to prevent over-load of the input circuitry should the incoming signal prove to be higher than normal microphone or line levels. Each input channel has 3 band equalization capability with a massive 12dB boost or cut. A pan control enables each input channel to be positioned left thru right across a stereo image. Inputs out of stereo position on a stage can be positioned in the mixer. Finally a quality 60mm slide fade control is provided. We felt that in keeping with the professional nature of this instrument that the extra resolution that the larger control offers is warranted. METERING. The left and right monitor channels have VU metering. Also provided is a 5-band Graphic Equaliser (+/-9dB). An optional LED peak-metering circuit will be available shortly. Master foldback send is also provided.

JAYCAR

125 YORK ST SYDNEY 2000
Ph. 2646688 Telex: 72293
Mail Orders To:
Box K-39 Haymarket 2000

POST AND PACKING CHARGES
\$5-\$9.99 (\$1.20) \$10-\$24.99 (\$2.40)
\$25-\$49.99 (\$3.50) \$50-\$99.99 (\$4.60)
\$100 up (\$6.20)

NEW SHOP HOURS
Mon-Fri 8.30 to 5.30pm
Sat 8.30 to 12.00pm
Thurs night to 8.30pm

More **BABANI BOOKS** to you by post

REACTANCE/FREQUENCY CHART FOR AUDIO AND RF.

Enables the reactance of any capacitor or resistor to be read off immediately — from 10 Hz to 100 MHz. Resonant frequencies of LC networks ditto.

196 75¢

PRACTICAL TRANSISTORISED NOVELTIES FOR HI-FI

Circuits for audio power meter, stereo phone adaptor, multi-channel mixers, gain control, contour network etc. etc.

201 \$1.30

HI-FI LOUDSPEAKER ENCLOSURES

Data for building corner reflex, bass reflex, exponential horn, folded horn, tuned port, Klipschorn labyrinth, tuned column, loaded port and multi speaker panoramics. Clear dimensioned diagrams included.

205 \$3.50

DIODE CHARACTERISTICS, EQUIVALENTS & SUBSTITUTES

Includes signal, zener, rectifier diodes etc. Full interchangeability data and characteristics of thousands of diodes of all types with every possible alternative. Includes UK, USA, European, Russian, and Far Eastern devices.

211 \$4.60

AUDIO ENTHUSIASTS' HANDBOOK

Discusses audio and hi-fi topics including record/playback curves, stylus compliance, disc recordings — then and now, evaluating loudness, equipment compatibility, acoustic feedback, equipment performance figures and standards etc. etc.

214 \$4.05

BUILD YOUR OWN ELECTRONIC EXPERIMENTERS' LAB USING ICs.

Includes many circuits and designs for constructing test and measuring instruments mostly using modern ICs. Includes AF osc, ITL pulse detector, hi-impedance Vm, square-wave osc/pulse gen, logic probe, lo-range ohmmeter, bridge, signal tracer etc.

218 \$3.10

SOLID STATE NOVELTY PROJECTS

A number of novelty projects using modern ICs and transistors. Includes 'Optomin' — a musical instrument played by reflecting a light beam with your hand, water warbler for pot plants, music tone generator, LEDs and ladders game, touch switch, electronic roulette wheel etc.

219 \$3.10

BUILD YOUR OWN HI-FI & AUDIO ACCESSORIES

Essential for keen hi-fi and audio enthusiasts. Projects include stereo decoder, three-channel mixer, FET preamp for ceramic pick-ups, mic preamp with adj. bass, stereo dynamic noise limiter, loudspeaker protector, voice-operated relay, etc.

220 \$3.10

28 TESTED TRANSISTOR PROJECTS

Some circuits are new, others are familiar designs. Projects can be split and/or combined for specialised needs.

221 \$4.60

SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS

Design and construction of several solid-state short-wave receivers giving high level of performance yet utilising relatively few inexpensive components. See also 226.

222 \$4.60

50 PROJECTS USING CA 3130 ICs.

The CA3130 is an advanced operational amplifier capable of higher performance than many others: circuits often need fewer ancillary components. Interesting and useful projects in five groups. Audio projects. RF projects. Test equipment. Household projects. Misc. projects.

223 \$4.60

50 CMOS PROJECTS

Many interesting and useful projects — multivibrators, amplifiers and oscillators; trigger devices; special devices.

224 \$4.60

PRACTICAL INTRO TO DIGITAL ICs

Introduction to digital ICs (mainly TTL 7400). Besides simple projects, includes logic test set to identify and test digital ICs. Also includes digital counter-timer.

225 \$4.60

HOW TO BUILD ADVANCED SHORT WAVE RECEIVERS

Full practical constructional details of receivers with performance equal to commercial units. Also 'add-on' circuits of Q meter, S meter, noise limiter etc.

226 \$4.60

BEGINNERS' GUIDE TO BUILDING ELECTRONIC PROJECTS

Enables total beginners to tackle electronic projects. Includes component identification, tools, soldering, building methods, cases, legends etc. etc. Practical basic projects are included.

227 \$4.60

HANDBOOK OF RADIO, TV, INDUSTRIAL & TRANSMITTING TUBE & VALVE EQUIVALENTS

Equivalents book for amateurs and servicemen. More than 18 000 old and new valves from UK, USA, Europe, Japan et al. CV (military) listings with commercial equivalents included.

BP2 \$2.25

FIRST BOOK OF PRACTICAL ELECTRONIC PROJECTS

Full constructional data, circuits, components lists for many practical projects including audio distortion meter, super FET receiver, guitar amp, metronome, etc.

BP23 \$2.55

GIANT CHART — RADIO, ELECTRONICS, SEMI-CONDUCTOR & LOGIC SYMBOLS

Identify those symbols at a glance. A must for beginners and advanced enthusiasts alike. Professionals can always hide it in their desks! A steal at only . . .

BP27 \$2.20

50 FET PROJECTS

Projects include amplifiers and converters, test equipment, tuners, receivers and receiver aids, mixers and tone controls etc etc. The FET used is not critical. This book is of interest and value to SW listeners, radio amateurs, hi-fi enthusiasts and general experimenters.

BP39 \$6.10

IC555 PROJECTS

One wonders how life went on before the 555! Included are basic and general circuits, motor car and model railway circuits, alarms and noise makers plus section on subsequent 556, 558 and 559s.

BP44 \$6.45

MOBILE DISCO HANDBOOK

Most people who start mobile discos know little about equipment or what to buy. This book assumes no preliminary knowledge and gives enough info to enable you to have a reasonable understanding of disco gear.

BP47 \$4.60

ELECTRONIC PROJECTS FOR BEGINNERS

This book gives the newcomer to electronics a wide range of easily built projects. Actual components and wiring layouts aid the beginner. Some of the projects may be built without using soldering techniques.

BP48 \$4.60

LM 3900 IC PROJECTS

Unlike conventional op-amps, the LM 3900 can be used for all the usual applications as well as many new ones. It's one of the most versatile, freely obtainable and inexpensive devices around. This book provides the groundwork for simple and advanced uses — it's much more than a collection of projects. Very thoroughly recommended.

BP50 \$4.95

LONG DISTANCE TV RECEPTION (TV-DX)

Written by UK authority, the book includes many units and devices made by active enthusiasts. A practical and authoritative intro to this unusual aspect of electronics.

BP52 \$6.60

PRACTICAL ELECTRONIC CALCULATIONS & FORMULAE

For the practical person's workbench. Bridges gap between technical theory and cut-and-dried methods which work but leave the experimenter unfulfilled. There's a strong practical bias. Tedious and higher maths avoided where possible. Many tables included. This one's a beauty!

BP53 \$8.25

HOW TO BUILD YOUR OWN SOLID-STATE OSCILLOSCOPE

Project divided into sections for builder individually to construct and test — then assemble into complete instrument. Includes short section on scope usage.

BP57 \$5.50

SECOND BOOK OF CMOS IC PROJECTS

Leading on from book number 224 '50 CMOS IC PROJECTS', this second book provides a further selection of useful circuits mainly of a fairly simple nature. Contents have been selected to ensure minimum overlap between the two books.

BP59 \$5.10

BEGINNER'S GUIDE TO DIGITAL ELECTRONICS

Covers all essential areas including number systems, codes, constructional and sequential logic, analog/digital/analog conversion.

BP61 \$3.50

ELEMENTS OF ELECTRONICS

This series provides an inexpensive intro to modern electronics. Although written for readers with no more than basic arithmetic skills, maths is not avoided — all the maths is taught as the reader progresses.

The course concentrates on the understanding of concepts central to electronics, rather than continually digressing over the whole field. Once the fundamentals are learned the workings of most other things are soon revealed. The author anticipates where difficulties lie and guides the reader through them.

BOOK 1 (BP62): All fundamental theory necessary to full understanding of simple electronic circuits and components.

BOOK 2 (BP63): Alternating current theory.

BOOK 3 (BP64): Semiconductor technology leading to transistors and ICs.

BOOK 4 (BP77): Microprocessing systems and circuits.

BOOK 5 (BP89): Communications.

This series constitutes a complete inexpensive electronics course of inestimable value in hobby or career.

Books 1/2/3 \$8.25 (each)

Book 4 \$10.80

Book 5 \$9.95

SINGLE IC PROJECTS

Simple to build projects based on a single IC. A few projects use one or two transistors as well. A strip board layout is given for each project plus special constructional and setting up info. Contents include low level audio circuits, audio power amps, timers, op-amps and miscellaneous circuits.

BP65 \$5.10

BEGINNER'S GUIDE TO MICROPROCESSORS & COMPUTING

Introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. Only prior knowledge assumed is very basic arithmetic and an understanding of indices.

BP66 \$6.40

COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS

Well-known author F.G. Rayer features applications and projects using various types of numerical displays, popular counter and driver ICs, etc.

BP67 \$6.40

52 PROJECTS USING IC741

This book of projects using the inexpensive 741 integrated circuit is translated from the original highly popular German version, with copious notes, data and circuitry.

BP24 \$3.50

POPULAR ELECTRONIC PROJECTS

A collection of the most popular types of circuits and projects to interest most electronics constructors. The projects cover a wide range and are divided into four basic types: radio, audio, household and test equipment.

BP49 \$4.95

ELECTRONIC SECURITY DEVICES

Besides including both simple and more sophisticated burglar alarm circuits using light, infrared and ultrasonics, this book also gives circuits for gas and smoke detectors, flood alarms, fire alarms, doorphones, baby alarms, etc.

BP56 \$5.35

PRACTICAL CONSTRUCTION OF PREAMPS, TONE CONTROLS, FILTERS ATTENUATORS

This book shows the enthusiast how to construct a variety of magnetic tape recording, microphone and disc preamplifiers, and also a number of tone control circuits, rumble and scratch filters, attenuators and pads.

BP60 \$5.30

CHOOSING AND USING YOUR HI-FI

Provides fundamental info invaluable when buying hi-fi. Explains tech. specs, advice on minimum acceptable standards and specs for adequate sound. Also invaluable advice on how to buy and install and maximise your equipment's potential. Includes glossary of terms.

BP68 \$6.10

ELECTRONIC GAMES

How to build many interesting electronic games using modern ICs. Covers both simple and complex circuits for beginner and advanced builder alike. Good one!

BP69 \$6.40

ELECTRONIC HOUSEHOLD PROJECTS

Most useful and popular projects for use around the home. Includes two-tone buzzer, intercom, smoke and gas detectors, baby alarm, freezer alarm etc. etc.

BP71 \$6.10

A MICROPROCESSOR PRIMER

This small book takes the mystery out of microprocessors. It starts with a design for a simple computer described in language easy to learn and follow. The shortcomings of this basic machine are then discussed and the reader is shown how these are overcome by changes to the instruction set. Relative addressing, index registers follow as logical progressions. An interesting and unusual approach.

BP72 \$6.40

REMOTE CONTROL PROJECTS

Covers radio, infra-red, visible light, ultrasonic controls. Full explanations are provided so that the reader can adapt the projects for domestic and industrial as well as model use.

BP73 \$7.15

ELECTRONIC MUSIC PROJECTS

Provides constructors with practical circuits for the less complex music equipment including fuzz box, waa-waa pedal, sustain unit, reverb and phaser, tremolo generator etc. Text covers guitar effects, general effects, sound generators, accessories.

BP74 \$6.40

ELECTRONIC TEST EQUIPMENT CONSTRUCTION

Describes construction of wide range of test gear including FET amplified voltmeter, resistance bridge, field strength indicator, heterodyne frequency meter etc.

BP75 \$6.40

TRANSISTOR RADIO FAULT-FINDING CHART

Used properly, this chart should enable the reader to trace most common faults quickly. Across the top of the chart are four rectangles containing brief descriptions of these faults: sound weak but undistorted; set dead; sound low and distorted; background noises. Selecting the appropriate fault, the reader simply follows the arrows and carries out the suggested checks in sequence until the fault is cleared.

BP70 \$1.85

ELECTRONIC CALCULATOR USERS' HANDBOOK

Presents formulae, data, methods of calculation, conversion factors, etc. for use with the simplest or most sophisticated calculators. Includes the way to calculate using only a simple four-function calculator: trigonometric functions (sin, cos, tan); hyperbolic functions (sinh, cosh, tanh); logarithms, square roots and powers.

BP33 \$4.60

LINEAR IC EQUIVALENTS AND PIN CONNECTIONS

Shows equivalents and pin connections of a selection of popular linear ICs, with details of families, functions, country of origin and manufacture. Includes devices from Analog Devices, Advance Micro Devices, Fairchild, Harris, ITT, Motorola, Philips, RCA, Raytheon, Signetics, Sescocem, SGS-ATES, Siemens, AEG-Telefunken, Teledyne, Texas Instruments.

BP41 \$10.00

ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST

Knowledge of a subject considerably increases the enjoyment and satisfaction derived from its practice, and the object of this book is to supply the electronics hobbyist with a background knowledge tailor-made for his or her specific requirements. Minimum maths!

228 \$4.60

PRACTICAL COMPUTER EXPERIMENTS

How to build typical computer circuits using discrete logic. This book is useful intro to devices such as adders and storers as well as a general source book of logic circuits.

BP78 \$6.50

RADIO CONTROL FOR BEGINNERS

How complete systems work with constructional details of solid state transmitters and receivers. Also included — antennas, field strength meter, crystal controlled superhet, electro-mechanical controls. Ideal for beginners. Section dealing with licensing etc. not applicable to Australia.

BP79 \$6.40

POPULAR ELECTRONIC CIRCUITS — BOOK 1

Yet more circuits from Mr Penfold! Includes audio, radio, test gear, music projects, household projects and many more. An extremely useful book for all hobbyists, offering remarkable value for the designs it contains.

BP80 \$7.15

ELECTRONIC SYNTHESIZER PROJECTS

For the electronic music enthusiast, an invaluable reference. This book is full of circuits and information on how to build analogue delay lines, sequencers, VCOs, envelope shapers, etc. etc. The author takes a clear and logical approach to the subject that should enable the average enthusiast to understand and build up what appears to be a quite complex instrument.

BP81 \$6.45

ELECTRONIC PROJECTS USING SOLAR CELLS

Well-known author Owen Bishop has designed a number of projects that benefit from solar power and obviate the problems encountered with batteries, such as weight and bulk, frequency of replacement, and failure when batteries are exhausted.

BP82 \$7.15

VMOS PROJECTS

A book to suit the dyed-in-the-wool experimenter. Though primarily concerned with VMOS power FETs and their applications, power MOSFETs are dealt with, too, in a chapter on audio circuits. A number of varied and interesting projects is covered under the headings: Audio Circuits, Sound Generator Circuits, DC Control Circuits and Signal Circuits. Learn while you build.

BP83 \$7.20

DIGITAL IC PROJECTS

Companion to No. 225 Practical Introduction to Digital ICs and BP61 Beginner's Guide to Digital Electronics. The projects included in this book range from simple to more advanced projects — some board layouts and wiring diagrams are included. The more ambitious projects have been designed to be built and tested section by section to help the constructor avoid or correct any faults that may occur.

BP84 \$7.20

INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

Companion to BP1 and BP14 equivalents books, but contains a huge amount of information on modern transistors produced by over 100 manufacturers. Wherever possible, equivalents are subdivided into European, American and Japanese types. Also shown are the material type, polarity, manufacturer and indication of use or application.

BP85 \$10.85

AN INTRO TO BASIC PROGRAMMING TECHNIQUES

Ideal for beginners seeking to understand and program in BASIC. Book includes program library for biorhythms, graphing Y against X, standard deviations, regressions, generating musical note sequences, and a card game.

BP86 \$6.60

SIMPLE LED CIRCUITS — BOOK 2

Sequel to BP42. Further light-emitting diode circuits. If you liked BP42 you'll love this one. If you don't know either it's well worth buying both!

BP87 \$5.05

ELECTRONIC CIRCUITS FOR MODEL RAILWAYS

Constructional details of a simple model train controller, a controller with simulated inertia, a high-power controller, an electronic steam whistle and a 'chuff generator'. Signal systems and train lighting and RF suppression also covered.

BP95 (was 213) \$6.60

ORDER FORM

Send to ETI Book Sales, 4th Floor, 15 Boundary St, Rushcutters Bay NSW 2011.

Please allow 4-5 weeks for delivery. Trade enquiries welcomed.

Please forward:

Book Qty.

196 224

201 225

205 226

211 227

214 BP2

218 BP23

219 BP27

220 BP39

221 BP44

222 BP47

223 BP48

BP50

BP52

BP53

BP57

BP59

BP61

BP62

BP63

BP64

BP65

BP66

BP67

BP68

BP69

BP71

BP72

BP73

BP74

BP75

BP76

BP77

BP78

BP79

BP80

BP81

BP67

BP68

BP69

BP71

BP72

BP73

BP74

BP75

BP77

BP78

BP79

BP80

BP81

BP82

BP83

BP84

BP85

BP86

BP87

BP88

BP89

BP90

BP91

BP92

BP93

Post & Handling:

1 — 4 books: \$1.35

5 — 10 books: \$2.70

11 — 20 books: \$3.50

Over 20 books: \$5.00

I enclose \$ (inc. p & h.)

Name

Address

Postcode

SAVE A FORTUNE ON A SCANNER!

The new DICK SMITH PRO 40 SCANNER

Compare with similar performance elsewhere at nearly twice the price! The new PRO 40 Scanner from Dick Smith represents the state-of-the-art in computerised scanning receivers!

★ Completely solid state computer-controlled circuitry — no expensive crystals to buy — complete with backup battery for stored frequencies.

★ Specially prepared Australian instruction manual (written and produced by our own engineers). Other scanners often have hard-to-understand foreign instruction manuals.

★ Touch-type splashproof keypad for direct entry of all operational commands, frequencies etc.

★ Ideal as either a base or mobile scanner (operates from 12V — beware of others that don't operate from 12V!) with its own self-contained whip antenna or external plug-in antenna.

★ Complete with mobile mounting bracket and DC power cable.

LOOK AT THESE SPECIFICATIONS:

Frequencies covered	68 to 88MHz — 136 to 174MHz — 360 to 512MHz.
Scanning steps	5, 10, 12.5, & 25kHz (depending on band)
No. of channels	40
Power supply	12 to 16 volts DC (battery memory backup 9V)
Scan rate	Approx 18/sec
Cat D-2805	

AND LOOK AT OUR LOW, LOW PRICE

\$395⁰⁰ VALUE!!

**FIRST SHIPMENT
ARRIVE EARLY SEPT.**

FAMOUS BEARCAT 20/20 SCANNER

Catch all the action with this incredible receiver! It covers most of the VHF and UHF bands.

Listen to ...

Aircraft, amateurs, pagers, business radio, marine and harbour, UHF CB, taxis and more. Cat D-2810.

WHY PAY MORE? ONLY

\$475

★ **COMING SOON** ★

DICK SMITH'S Australian Radio Frequency Handbook

Enter the exciting world of scanning with this superb book. Covers everything you could possibly want to know about scanning. Watch our ads for further details.

AUSTRALIA'S MOST POPULAR KIT COMPUTER!

OVER 2,000 SOLD!!

Cat. K-3600

The Electronics Aust./ Dick Smith SUPER 80 A FULL SIZE COMPUTER

You are supplied with a full board including power-on EPROM monitor, 16K of RAM, cassette interface (relay activated) for universal control of any tape recorder, TV modulator and direct video output PLUS full size professional keyboard — not a 'feel less' toy!

\$239⁵⁰ was \$295⁰⁰

SUPER 80 Options

Transformer (M-2325)	\$23.00
BASIC Interpreter (tape) (K-3602)	\$12.50
IC Socket Set (K-3603)	\$12.50
Lower Case Generator Option (K-3607)	\$49.00
BASIC in EPROM (K-3604)	\$49.50
S-100 Expansion Unit (K-3606)	\$19.50
Metal Case (H-3200)	\$44.95
SUPER 80 Technical Manual (B-3600)	\$9.50
SUPER 80 BASIC Handbook (B-3602)	\$9.50

DEMO & STORE STOCK SPECIALS — YOU SAVE!!

Making room for new stock - Full 12 mth warranty

Item	Description	Cat No	Was	Now
FT207R	2m hand held - not many left	D-2888	\$358	\$235
PA2	Mobile charger for FT207R	D-2884	29.95	19.95
SPECIAL OFFER: BOTH OF THE ABOVE FOR ONLY \$246.50				
FT107M	HF TX all solid state	D-2883	ONLY	8.50
FT207RVH	2m-25 watt TX scanning	D-2890	449.95	369.95
FT1012D	Digital readout 101 WARC TX	D-2859	910.00	850.00
FT227RB	2m with scanning 10 watt	D-2891	379.00	319.00
FV707DM	Digital VFO for FT707	D-2896	299.50	265.00
MMB2	Mobile bracket for FT707	D-2897	36.00	25.95
	Gaibraith paddle	D-7103	only	14.95
FT902D	HF WARC TX 180 watt	D-2853	1195	995
FT901D	HF 180 watt TX	D-2854	1075	950
SPECIAL PACKAGE with FT 901D or FT 902D Bonus DC converter (D-2856) while they last				
SPECIAL DEAL: FT 902D (D-2853) plus FC 902 (D-2855) plus DC conv. (D-2856) for \$1195 - while they last!				
SPECIAL DEAL: FT 901D (D-2854) plus memory (D-2858) included for only \$1025 (\$1283 value!)				
	DC-DC Converter for FT901/902	D-2856	69.00	49.00
	Memory for FT901/902	D-2858	139.50	99.00
FT101Z(fm)	HF ★ WARC ★ FM ★ TX	D-2872	only	885.00
FT101Z	HF ★ WARC ★ TX	D-2862	849.00	795.00
HOT PACKAGE: FTV707 (D-2876) plus 2 mtr module (D-2877) for only \$244 (that's \$294 value!)				
SPECIAL DEAL: with FT101Z (fm) (D-2872) or FT101Z (D-2862) — 101 counter unit (D-2861) FOR ONLY \$101!!				

THAT'S AN UNBELIEVABLE \$142.50 VALUE — CRAZY DICK!!

LIMITED STOCKS ON ALL THESE ITEMS — RING JIM POWELL (02)888 3200 — HE KNOWS WHERE ALL THESE CRAZY SPECIALS ARE FROM CRAZY DICK !!!

FT 102 HF ALL MODE TRANSCEIVER



New from Yaesu and Dick Smith. Look at these great features: Unique recessible controls for VOX GAIN, DELAY, MIC GAIN, processor COMP, NB LEVEL, and FM SQL; dual meter allowing much more all around operating convenience; novel chassis design and rugged cabinet construction AND MUCH MORE. Come in and check it out! Cat D-2880

value! only \$1195

Introducing ... The DICK SMITH WIZZARD

The Video Entertainment system with computer capability*

- Great range of games — Sonic Invaders, Auto Chase, Planet Defender and many more!
- 'Nasa' type hand controllers with 16 positions and qwerty keyboard.
- High Resolution graphics — lighter matrix gives much better picture quality — you'll appreciate the difference.
- Latest technology — other TV consoles were designed 2 or even 3 years ago — a lifetime in electronics.



Cat. Y-1600

at only **\$295⁰⁰**

you'd be crazy not to check out the Dick Smith WIZZARD!

*available soon: BASIC cartridge, simply plug in and your Wizzard is now your own personal computer.

WOT'S THIS?

It could be part of a space shuttle ... or even an Exo-cet missile. We're pretty sure they could find a use for it if they tried. The truth is, it's a double eyelet assembly, as used in CDI and TAI systems. Because of the insulation, they can be used in literally hundreds of applications. At our price, you can get a lot of them for the junk box — just in case!

30c each

Cat. K-6001

Short wave Antenna Kit

ONLY \$9.95

Get the best reception from your receiver with this high quality shortwave antenna. Complete and ready to assemble and needs no soldering. Cat K-3490.




SAVE \$96

**COMPUTER OWNERS —
BUY A PRINTER
NOW AND
SAVE!**

SAVE \$170


OUR TOP
SELLING
PRINTER!

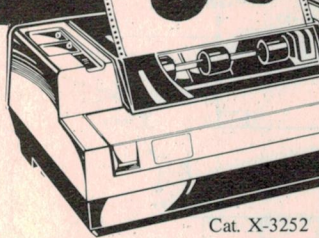

Cat. X-3252

DOT MATRIX PRINTER

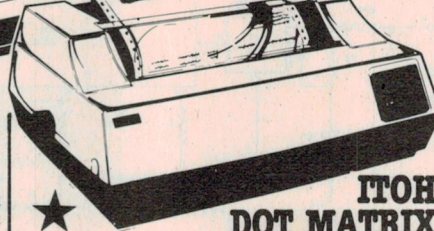How's this for value! A tractor-fed impact type dot matrix printer for under the cost of most thermal printers! You have to see the high resolution graphics to believe them! This amazing printer is fitted with a standard Centronics-type parallel data interface, making it compatible with most current computers! Unbelievable value!



ITOH DOT MATRIX

The Itoh 8300P features high speed, bidirectional printing with a full upper and lower case character set and accepts standard fan form sprinkled paper up to 240mm wide. Why not come in and check out one of these top selling printers for yourself? But be quick, stocks are limited!

Cat. X-3255

NOW \$799

~~WAS \$970~~

**WORD
PROCESSOR
QUALITY
UNDER
\$2000**

Why Pay More?



**DON'T PAY
OVER \$2,900!**

The
Dick Smith

DAISY WHEEL PRINTER

Improve the appearance of your correspondence with this quality printer! It delivers ultra-sharp, clean copy at THREE TIMES the speed of a golf ball typewriter (40 c.p.s.) with fewer moving parts than other daisy wheel printers to improve reliability. If you buy a daisy wheel anywhere else, you're wasting money! Cat X-3265.

**AMAZING \$1995
VALUE AT**

**WAS \$495
NOW \$399**



**TOP
QUALITY
AMPEX
CASSETTES**

Yes, we've made a huge scoop purchase of these famous, top quality Ampeg tapes at BELOW MANUFACTURER'S COST! It's high grade tape with rugged construction that will last for years to come. Look at the value you get:

Cat:	Type:	WAS	NOW	10 UP
C-3078	C-45 ELN	\$2.16	\$1.50	\$1.35
C-3080	C-60 ELN	\$2.40	\$1.99	\$1.79
C-3082	C-90 ELN	\$3.15	\$2.49	\$2.24
C-3086	C-60 EDR	\$3.49	\$2.25	\$2.00
C-3088	C-90 EDR	\$4.15	\$2.99	\$2.69



**CAR
COMPUTER
KIT**

At last! The kit you've been waiting for! This new Car Computer Kit is the ideal way to find out how your car is performing — and how much it is costing you to run it! It gives you 12 different readings — distance, consumption, time, etc. The kit is housed in an attractive case with special silk-screened front panel. Cat. K-3400

\$89.50

SEE EA
JULY '82

**\$21.00 WORTH OF
METAL FILM 1% FOR
ONLY \$12.90**



Yes! Save a fortune on this one — a specially selected pack (no rubbish) of 300 precision metal film resistors, worth \$21.00 at normal 1 off prices! 1% tolerance, high stability, low temperature coefficient. A must for all serious uses (test equipment, etc.) Cat. R-7105

LITTLE TRIMMER



Hard-to-get 7-60pF compression trimmer. Our price only

\$2.50

Compare elsewhere!
Cat. R-2905

PUSH BUTTON

High quality, precise micro switch type action. Ideal for computer program switches Cat. S-1220

was \$2.30

**now
\$1.90
each**


**YOU REAP
THE BENEFIT!**

SAVE \$40!

HORNET II 40 ch AM/SSB

The latest in 40 channel CB technology. The quality of this unit is even better than the high standard set by its predecessor, the Hornet I, our most popular CB ever!

**ONLY \$199.00
WAS \$239.50**

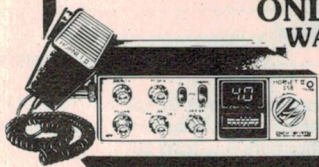

Cat D-1710
DOC APP.
NO. 249A006

DICK SMITH Electronics

**31 STORES
AUSTRALIA WIDE**



Terms available to
approved applicants
through...



**MAIL ORDER CENTRE:
PO BOX 321, NORTH RYDE NSW 2113
Telephone Orders: (02) 888 3200**

**bankcard
welcome here**

POST & PACKING CHARGES

ORDER VALUE	CHARGE	ORDER VALUE	CHARGE
\$5.00-\$9.99	\$1.40	\$50.00-\$99.00	\$4.60
\$10.00-\$24.99	\$2.40	\$100.00 or more	\$6.20
\$25.00-\$49.99	\$3.50		

Charges are for goods sent by post in Australia only — not airmail, overseas or road freight.

SPEEDY PHONE/BANKCARD ORDER SERVICE

Just phone through your order and
Bankcard details — it's so simple!
(02) 888 3200



- NSW** 145 Parramatta Rd AUBURN 648 0558 — T55 Terrace Level BANKSTOWN SQ. 707 4888 — 613 Princes Hwy BLAKEHURST 546 7744 — 552 Oxford St BOND JUNCTION 387 1444 — 818 George St BROADWAY 211 3777 — 531 Pittwater Rd BROOKVALE 93 0441 — 147 Hume Hwy CHULLORA 642 8922 — 162 Pacific Hwy GORE HILL 439 5311 — 396 Lane Cove Rd NORTH RYDE 888 3200 — 30 Grose St PARRAMATTA 683 1133 — 6 Bridge St SYDNEY 27 5051 — 125 York St SYDNEY 290 3377 — 173 Maitland Rd NEWCASTLE 61 1896 — 263 Keira St WOLLONGONG 28 3800 — Tamworth Acde & Kable Ave TAMWORTH 66 1961
- ACT** 96 Gladstone St Fyshwick 80 4944
- VIC** 399 Lonsdale St MELBOURNE 67 9834 — 260 Sydney Rd COBURG 383 4455 — 656 Bridge Rd RICHMOND 428 1614 — Springvale & Dandenong Rds SPRINGVALE 547 0522 — Ross Smith Ave & Nepean Hwy FRANKSTON 783 9144 — 205 Melbourne Rd GEELONG 78 6766
- QLD** 293 Adelaide St BRISBANE 229 9377 — 166 Logan Rd BURANDA 391 6233 — 842 Gympie Rd CHERMSIDE 59 6255
- SA** 60 Wright St ADELAIDE 212 1962 — 435 Main North Rd ENFIELD 260 6088 — Main South & Flagstaff Rds DARLINGTON 298 8977
- WA** 414 William St PERTH 328 8977 — Wharf St & Albany Hwy CANNINGTON 451 8666
- TAS** 25 Barrack St HOBART 31 0800

DSE/A334/LM

Ideas for Experimenters

Programmable wiper controller

This simple circuit uses cheap, readily-available components.


The relay contact is wired in parallel with the standard windscreen wiper switch. A single push of the WIPE button activates the relay for about one second, giving one wipe of the screen. Another push of the WIPE button within 40 seconds of the first will operate the wiper again, which then continues at the interval set by the time between the first and second presses of the WIPE button. The interval is therefore easily programmed by pressing the WIPE button twice, when the screen needs wiping at intervals. If the rainfall increases, the WIPE button is pressed again to set a shorter interval between wipes.

The STOP button may be pressed at any time to stop the wiping. However, if the WIPE button is again pressed within 40 seconds after the last wipe, an interval is again programmed. The last wipe is always remembered as long as it was less than 40 seconds ago. Programming becomes second nature once you've done it once or twice and requires no fiddling.

The circuit operation is as follows: If a wipe has not occurred within the last 40 seconds, pins 6 and 2 of IC3 are below their threshold level, so pin 3 of IC3 is high. When the WIPE button is pressed, pin 2 of IC5 momentarily goes low, allowing the one-second monostable, IC5, to work, activating the relay and the wiper. At the same time, the 33uF capacitor is charged up. This discharges slowly after the relay has again turned

IDEA OF THE MONTH

J.D.W. Herston Qld.

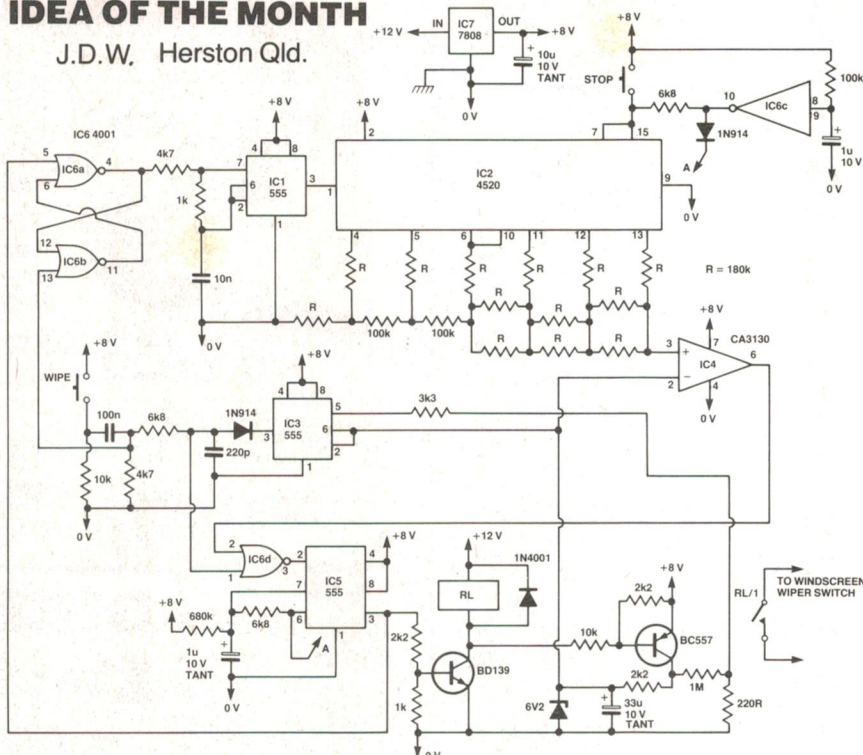

off. When the WIPE button is again pressed, within 40 seconds of the first press, pin 3 of IC3 is now low (pins 2 and 6 are above the threshold) so IC6d cannot operate. The flip-flop formed by IC6a/IC6b is switched so that the oscillator formed by IC1 is enabled, thereby causing IC2 to count up, ramping up pin 3 of IC4 until the voltage on it rises to that on pin 2, thereby operating the monostable, IC5, via IC6d. IC6a is also

switched, stopping the counter. A count is thus stored in IC2, corresponding to the interval time.

The STOP button resets the counter. IC6 forms a power-on reset circuit.

The circuit was built on a 60 x 67 mm pc board and mounted in a cigarette box-sized case under the dashboard, with the two buttons on the front. The relay was mounted in the engine compartment so it could not be heard.

'IDEA OF THE MONTH' CONTEST

Scope Laboratories, who manufacture and distribute soldering irons and accessory tools, have offered to sponsor a contest with a prize to be given away every month for the best item submitted for publication in the 'Ideas for Experimenters' column — one of the most consistently popular features in ETI. Each month we will be giving away a Scope Panavise pc board holder, model 333 — as described in News Digest, p.8, October '81 issue. Selections will be made at the sole discretion of the editorial staff of ETI Magazine. Apart from the prize, worth about \$70, each winner will be paid \$10 for the item published. You must submit original ideas of circuits which have not previously been published. You may send as many entries as you wish.

RULES

This contest is open to all persons normally resident in Australia with the exception of members of the staff of Scope Laboratories, Murray Publishing, Offset Alpine, Australian Consolidated Press and/or associated companies.

Closing date for each issue is the last day of the month. Entries received within seven days of that date will be accepted if postmarked prior to and including the date of the last day of the month.

The winning entry will be judged by the Editor of ETI, whose decision will be final. No correspondence can be entered into regarding the decision.



Winner will be advised by telegram the same day the result is declared. The name of the winner, together with the winning idea, will be published in the next possible issue of ETI.

Contestants must enter their names and address where indicated on each entry form. Photostats or clearly written copies will be accepted but if sending copies you must cut out and include with each entry the month and page number from the bottom of the page of the contest. In other words you can send in multiple entries but you will need extra copies of the magazine so that you send an original page number with each entry.

This contest is invalid in states where local laws prohibit entries.

Entrants must sign the declaration on the coupon that they have read the above rules and agree to abide by their conditions.

COUPON

"I agree to the above terms and grant Electronics Today International all rights to publish my idea in ETI Magazine or other publications produced by them. I declare that the attached idea is my own original material, that it has not previously been published and that its publication does not violate any other copyright."


* Breach of copyright is now a criminal offence.

Title of idea
Signature
Name
Date
Address
Postcode

Cut out and send to: Scope/ETI 'Idea of the Month' Contest, ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011.

PRE-AMP KITS

\$21.99

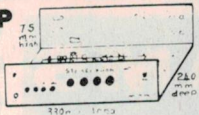

BUILD YOUR OWN STEREO AMP AT "NEXT-TO-NOTHING" PRICES. We still have a limited quantity of these new SINCLAIR pre-amps with pre-punched chassis and lettered front panels. Featured are VOL/BASS/TREBLE/BAL controls, and ON-OFF SWITCH and PHONO/TUNER/AUX. inputs and it operates on 9-40V DC at about 20mA. You can build your own power amp with power supply, use it as a 3 input Disco Mixer or to improve an existing sound system.

NEW TOROIDAL TRANSFORMERS

40V 1.2AMPS

PLUS 15V 200mA

Made in Sweden by TRANSDUKTOR

\$21



These high-efficiency Toroidal Transformers are only 80mm diam.x33mm high. Regular price \$42.00

12V DC ROTARY SOLENOID STEPPING SWITCH
U.S.A. Made!
12 POSITION, SINGLE POLE, SHORTING.
\$19.99

ALL STOCK MUST CLEAR

SALE 20% OFF!

OUR USUAL PRICES

THE COOLERS




SQUIRREL-CAGE FANS
SINGLE OUTLET

115V OR 220V AC

\$14 \$20

Very rugged, powerful, ex-computer blowers.

DUAL BLOWERS

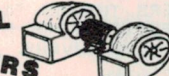

"BLOW-ME-DOWN" These high-volume coolers are for really heavy-duty use!

\$24 115v OR 230v

PARTY STROBE



BRAND NEW FACTORY WARRANTY

NORMAL PRICE \$29.95 SAVE NEARLY \$5

\$25


"Freeze" the action at your next party or theatrical show! Mains operated with a continually variable flash rate, housed in an attractive black vinyl box 150mm

POWER TRANSFORMERS

DOUBLE BONUS OFFER!

Scoop!

12v-0-12v 500mA

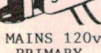

MAINS 120V PRIMARY

PRIMARY CAN BE IN SERIES (240V) SECONDARIES CAN BE SERIES/PARALLEL

Outputs of 12V, 24V, 36V, or 48V at 500mA, 12V or 24V at 1A are possible!

FOR PERSONAL SHOPPERS ONLY

FOR 2

FACTORY CLEARANCE

BY PHILLIPS

\$12.99

Parcels of good gear for hobbyists and experimenters - we bought over 2 TONS, as used in PHILLIPS RADIOS, STEREOs AND TV's etc. Each JUMBO PARCEL weighs over 2Kgs, worth approximately \$40-\$50

HEATSINKS

HUGE RANGE AVAILABLE!

3"x4" WITH 1xT03 TRANS. \$2.50
6"x4" WITH 2xT03 TRANS. \$3.00
9"x4" WITH 4xT03 TRANS. \$4.00
3"x4" 3x100PIV 35A RECT. \$2
VARIETY PACK - 10 ASSORTED HIGH-QUALITY HEATSINKS WITH SCR'S, RECTIFIERS AND TRANSISTORS. IDEAL FOR EXPERIMENTERS \$9.95 ONLY WHILE THEY LAST! WOW!

DC MOTORS

6-12V LARGE SIZE! IDEAL FOR TOYS, MODEL BOATS, CARS, HOBBY ETC. OPERATES FROM 4.5V TO 12V. POWERFUL AND RUGGED. SIZE 47MM DIAM x 60MM 10 for \$25

HEADSETS WITH MIC

from SONY \$25 Electret Condenser Microphone



Power Transformers

Bulk purchase of new, best quality MAINS TRANSFORMERS used in H and K chassis AWA-Thorn colour TV sets.
H Primary: 0,120V,125V plus 0,120, 125V for 240V, 250V operation.
H Secondary: 0,120V 1 Amp +6V 1 Amp
K Primary: 0,240V,250V
K Secondary: 0,105V 1.3 Amp plus 6V
\$9 \$2 EXTRA 0.9 Amp plus 12V 0.25 Amp. POST. LAST FEW AVAILABLE!

VALU ASSORTMENTS



\$2

EACH PACK

LUCKY-DIP PACKS \$2EA
500 1/4WATT RESISTORS
200 1/2WATT RESISTORS
50 1/4 HI-STAB RESISTORS
20 MIXED POTENTIOMETERS
25 PRESET POTS ASST.
50 POLY. GREENCAPS
100 CERAMIC CAPACITORS
45 ELECTROLYTIC CAPS
12 VARIOUS SWITCHES
40 RADIO/TV KNOBS
50 ASST TAGSTRIPS

PUSH-BUTTON SWITCHES

only 4 for \$1.00

PCB MOUNTING SINGLE POLE PUSH"ON" MOMENTARY

Ideal for alarm equipment, custom keyboards, intercoms etc. GREAT VALUE - LIMITED QUANTITY AVAIL.

BARGAIN BUYS

FANS



EX-COMPUTER

5 INCH

115v \$8

220v \$10

IC's



Approx 100 ASST.

FOR \$11.50

"SWEEPINGS OFF THE FACTORY FLOOR"

1000 for \$100

SPECIALS

CB XTALS 27.880, 27.890, 27.900, 27.910...pr\$1.50
TTL 7406.....10for\$2.00
TTL 7420.....10for\$1.50
TTL 7473.....10for\$4.00
TTL 7490.....10for\$4.50
5mm Red LEDs...10for 0.90
5mm Bezel for LED.ea.0.05
3AG Fuseholders- in-line plastic.....10for\$2.00
PCB Fuse-Clips.8for 0.50
Philips 2"8Jweeters 20W power.....2 for\$4.00
4" Mid-range 8a20W power, imported Novik ea.\$4.00
6"x4",4"sq.15a...ea.\$3.00
Record Cleaner Arm, with cleaning kit...ea.\$2.00
12V 100mA mini-globes, wire leads...10for\$1.00
Neons NE-2 90v 8for\$1.00
DPDT slide switch.ea.25
DP3T slide switch.ea.30
DPST rocker " "ea.30
3 pos 10Amp rotary sw, with white knob..ea.50
4 pos 0ak rotary switch, with On-Off.....ea.50
0.1uF 250v poly 12for \$1
0.22uF 100v " 10for \$1
0.015uF 200v " 15for \$1
0.068uF 400v " 10for \$1
0.047uF 200v " 10for \$1
0.022uF 200v " 12for \$1
0.15uF 250v " 10for \$1
0.68uF 260v " 4 for \$1
0.056uF 1KV " 3 for \$1
0.47uF 400v " 4 for \$1
0.1uF ceramic 12for \$1
0.047uF ceramic 15for \$1
1000pf ceramic 20for \$1
100pf 25v styro 20for \$1
15uF 35v tantalum ea.30

TAKE 20% OFF YOUR TOTAL ORDER

NEW PACK AND POST CHARGES: BASIC \$2.00 PLUS 5% OF ORDER VALUE. We still subsidise many of the orders, as over 500gm postal charges are \$3.60 to some states, up to \$6.60 over 10kg. We believe this is a fairer system for all

PRE-PAK electronics p/l

1a WEST ST, LEWISHAM, NSW

569-9797 24 HR. PHONE ORDER SERVICE

Phone or mail order BANKCARD accepted

JIL SX-200, A BETTER SCANNING MONITOR RECEIVER.

Covers 26-88 MHz & 108-180 MHz
& 380-514 MHz



Monitors over 33,000 frequencies from 26 to 88 MHz, 108 to 180 MHz and 380 to 514 MHz. Bands included within this range are HF and UHF CB, 27 and 155 MHz MARINE, Australian LOW BAND, AIRCRAFT band, VHF SATELLITE band, 10 Mx, 6 Mx, 2 Mx and 70CMx AMATEUR BANDS, VHF High BAND as well as UHF two-way band.

Mechanically rugged the SX-200 uses high quality double-side Epoxy-Glass printed circuit boards throughout. Some of its other outstanding features include 3 MODE SQUELCH circuitry which allows the lockout of spurious and carrier only signals, extremely low spurious count, AM and FM detection on all bands, FINE TUNING control for off channel stations, 240 VAC on 12 Volt DC operation, Accurate QUARTZ CLOCK, Squelch operated OUTPUT for switching a tape recorder etc, 16 Memory channels, MEMORY BACKUP which lasts up to two years, high SENSITIVITY and SIGNAL-TO-NOISE ratio on all bands, CRYSTAL FILTER for excellent SELECTIVITY and easy servicing due to component layout as well as a 90 day warranty.

Its high quality and performance is testified by the fact that it is in use by a large number of State government and Federal bodies including most state and federal police departments.

Contact GFS, the Australian Distributors, or our interstate outlets for full technical specifications.

We also market a range of pocket scanning receivers and transceivers. Contact us for full details.


PRICE \$512 INCL S.T.+\$8 P&P
SERVICE MANUAL \$10+\$1 P&P
SCAN-X BASE ANTENNA \$48+\$8 P&P

Interstate Dealers:
WA: (09) 387 4966
NSW: (02) 211 0531
QLD: (07) 397 0808
SA: (08) 269 4744

GFS Electronic Imports

15 McKeon Road
Mitcham, 3132 Vic
TLX 38053 GFS
(03) 873 3939

VIDEO RECORDING "BUGS"

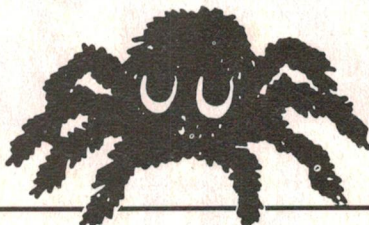

Are you plagued with BUGS in your TV-FM or Video cassette, the performance is dependant on the level & quality of the signal being fed into the equipment. Regardless of how much you spend on your TV/FM receiver or Video Cassette, your equipment will only perform as well as the *Antennae system will allow.*

You could be down in signal level & require an amplifier for more gain which would allow you extra outlets. Or ghosting problems, a change of aerial could rectify this & give you Ch. 0. Whatever your problems don't go to the super market for your advice & parts, the salesman is a nice guy, but knows little about aerial problems. We can talk of many thousands of installations in Australia since 1956.

We have the largest stocks of antenna equipment available. Sixty different types of VHF Aerials 16 types of UHF Aerials 12 types of FM aerials from 5 different manufacturers. Aerials from \$19 Amplifiers from \$56 Rotators from \$97.

**DOWN CONVERTORS UHF to
VHF \$95.**

**FIELD STRENGTH METERS
From \$350.**

Trade Supplied.

ELECTROCRAFT MANUFACTURING PTY LTD

Free verbal advice given Phone or call.
438 4308 or 438 3266
68 Whiting St ARTARMON 2066 Hours
8am to 5pm Mon: to Friday.
Off Street Parking at rear.

AMS MAIL
ORDER
CENTRE

TAPES CHEAP!

BULK TAPES DISCOUNTED

Maxell

UDXLII C90	EPITAXIAL	12 for \$58
UDXLII C90	EPITAXIAL	12 for \$49
UD C90	ULTRA DYNAMIC	12 for \$38
LN C90	LOW NOISE	12 for \$28

TDK

SA-X C90	SUPER AVILYN DUAL COATING	10 for \$49
SA C90	SUPER AVILYN	10 for \$39
AD C90	ACOUSTIC DYNAMIC	10 for \$30
D C90	DYNAMIC	10 for \$24

BASF

CRO ₂ C90	CHROMDIOXIDE	10 for \$48
FE C90	FERROCHROME	10 for \$38
LH C90	LOW NOISE	10 for \$25

VIDEO - OPEN REEL - METAL
MAXELL, TDK, BASF, AKAI

— Send for
complete Tape Price Lists — FREE

HI-FI SYSTEMS

AMPLIFIERS, TUNERS, TAPE DECKS,
TURNTABLES, SPEAKERS, HEADPHONES,
RECEIVERS.

Our range includes:

Sansui

PIONEER

marantz AKAI
SOUND DYNAMICS KSW

CAR SOUND

RECEIVERS, TAPE PLAYERS, BOOSTERS,
EQUALISERS, SPEAKERS — Including:

PIONEER VOXSON

ACCESSORIES

CARTRIDGES, STYLII, CLEANERS,
DEMAGNETISERS, DISCWASHER

CCI

— PARABOLIC STYLUS —
Complete Range

ortofon

Moving Coil and
Magnetic Cartridges

Ring or Write for Free Price Lists!

TAPE ORDERS:


Add: Pack and Post \$3.00 per Order
and send cheque/money order to:

AMS

MAIL ORDER CENTRE
135 HAWTHORN ROAD,
CAULFIELD, VIC. 3162
(03) 528 1149

Stock at prices shown available at time
of going to press.

Ideas for Experimenters

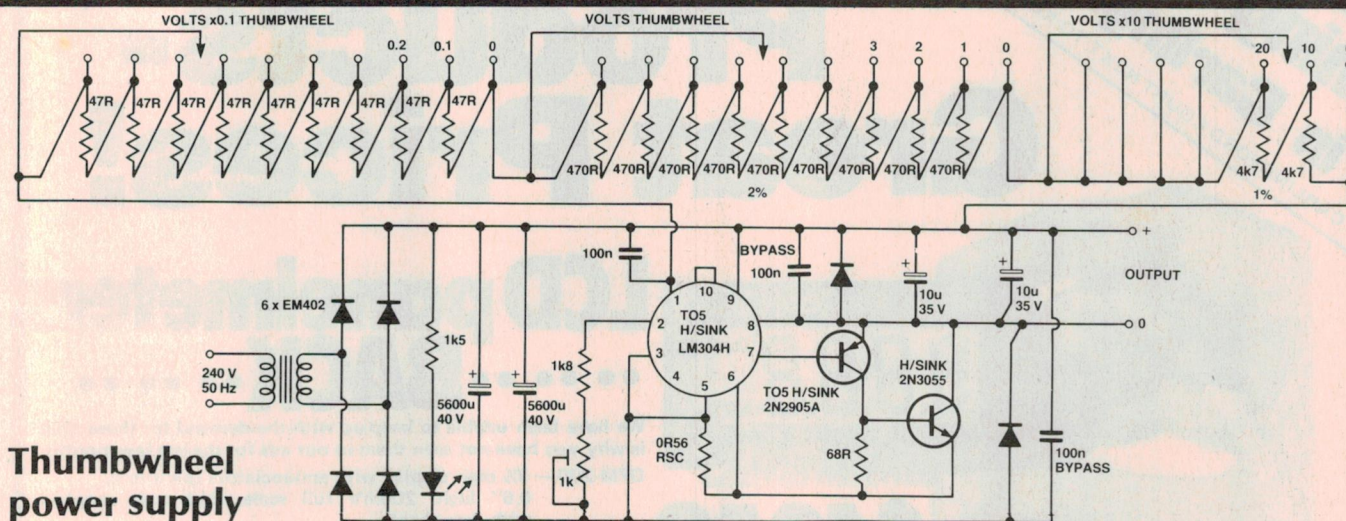

Thumbwheel power supply

Most power supplies take time to use because the voltage and current limits have to be set individually. This supply, from **L.W. Brown** of **Burwood, Victoria**, is easy to use, as the current limit is fixed and the voltage is adjusted by dialling the value on thumbwheels.

It is not necessary to have a voltmeter or ammeter on this power supply, although an ammeter could be added in series with the current limit resistor (RSC) to reduce any voltage drop problems. Almost any moving coil movement can be used for the ammeter if RSC is used as the meter shunt and a preset pot in series with the meter is used to set a useful scale value.

Two per cent resistors were used for the unit volts divider, and 1% values for the tens divider. If close tolerance resistors are difficult to obtain, it may be possible to select some from a batch of 5% types with a multimeter. The actual resistance value is not critical, but the ratio of these resistors *is* important. The final voltage adjustment should be achieved with a good multimeter and a near full-scale voltage.

If the decimal thumbwheels are not suitable, an alternative would be a clockface multiturn potentiometer — but these are expensive.

The LM304H is a negative adjustable regulator. Two external transistors increase the output current to over 2 A; output currents of 4 A are possible if transistors with a larger power dissipation and a better than average current gain are used. The maximum input voltage is 40 V, giving a usable output voltage of 0-30 V. This regulator

is unusual in that it uses resistor voltage programming. Each additional 500 ohm resistor in series between pin 1 and the positive supply (pin 9) will produce an additional 1 V at the output.

The adjustable resistor between pin 2 and the negative supply provides some trimming, so realistic values of resistors can be used. The resistor RSC sets the current limit. The LM304H has a transistor junction across RSC, and when this conducts the regulator begins to current-limit.

I have provided a table to enable personal customising of the circuit. Some people will need particular voltage ranges; others will only have certain transformers available to optimise the circuit.

My first prototype used three thumbwheels side by side, with individual wiring back to the pc board. The range of the power supply was 0-29.9 V at 3 A. The power transistor (better than a 2N3055) was mounted on a chunky heatsink, in turn mounted on the outside rear of the apparatus. A popular transformer for amplifiers, the M0148, was used, as it is rated at 26-0-26 at 2 A. As this was a centre-tapped winding the

two upper diodes were eliminated and the CT connected to the upper positive rail.

A simpler version of the power supply was then constructed, with the output range of 0-19.9 V at 1 A. The output transistor, a 2N3055, was mounted on the pc board with two sheets of 1.5 mm. aluminium folded to form a heatsink. One thumbwheel was used for the units and another for the tenths. A slide switch took the place of the tens thumbwheel. The thumbwheels were mounted vertically above each other and mounted flat on the pc board; the only wiring used was the two wires for the output and the power transformer connections.

The one critical component was the output capacitor. I finally used two 10u 35 V tag tantalum caps and a 2u2 green-cap in parallel. An unusual feature is that a TO5 top-hat type of heatsink is necessary on both the LM304H and the 2N2905. This heatsink improves power dissipation, but more importantly the reduced temperature improves both voltage and current limit stability. The current limit varies markedly with temperature because of the simple control circuit used in the LM304H.

Table of optional ranges

Voltage Range Vdc	Transformer secondary voltage — Vac	Number of thumbwheels	Actual voltage range
10	12	2	0-9.9
20	18	2+1 switch or 3	0-19.9
30	27	3	0-29.9

Current range — A	RSC ohm	Output tran- sistor type	Number of filter caps	Transformer current — Aac	Heatsink	Diode rating Adc
1	0.56	2N3055	1	1.5	On pcb	1
2	0.33	2N3055	1	3.0	Large — on pcb	1
3	0.22	2N3771	2	4.5	On case rear	3
4	0.15	MJ15003	3	6.0	Large — on case rear	6

**NEW STORE
opening October
in Carlingford**

AT CARLINGFORD COURT NEXT TO KENTUCKY FRIED CHICKEN

Great ★ Products- Great Prices!



DPM-05

\$39.50

DPM-200

\$49.50

LCD panelmetersBACK.....

We have been unable to keep up with the demand for these, that is why you have not seen them in our ads for the last few months.

DPM-200 — 3½ digit display with annunciators (pictured). 0.6" high. 200mV full scale. Each unit supplied with data sheet.

DPM-05 (Not illustrated). 3½ digit display with "plus", "minus" and "low batt". Annunciators with 0.5" readout. Both units sample at 3/second.


If you want to express any physical measurement in a bright easy to read display these are for you. They contain all analogue-to-digital electronics and LCD drive circuitry. Send SAE for more information.

RBLL CAPACITORS — NOW IN STOCK!!

The RBLL — logical and economical replacement for Tantalum capacitors.

0.1uF	32 cents each
0.15uF	32 cents each
0.22uF	32 cents each
0.33uF	32 cents each
0.47uF	32 cents each
0.68uF	32 cents each
1uF	35 cents each
1.5uF	35 cents each
2.2uF	35 cents each
3.3uF	35 cents each
4.7uF	38 cents each
6.8uF	40 cents each
10uF	45 cents each
22uF	45 cents each
33uF	45 cents each
47uF	50 cents each
100uF	60 cents each

MOVING COIL CARTRIDGE MODEL MC-100

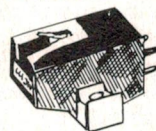

LOW COST BUT HIGH QUALITY!

- ½" standard mount
- Does not need transformer
- Samarium Cobalt magnets for high output
- Frequency Response 15Hz - 35kHz
- Whopping 2.5mVout (1kHz/50mm/s)
- Compliance 8 x 10⁻⁶ cm/dyne
- 2.0 gram tracking force
- 0.6mil Diamond stylus
- Supplied with mounting hardware

STAGGERING
VALUE

\$49.50

PLESSEY SPEAKERS 12" PA UNITS FROM \$24.50 — LESS THAN 50cents/watt!!

New low price for quantity. OEMS please note!! The 50WRMS PA C300K05 is the most popular PA speaker around and we have sold hundred's. Our last (DEFINITELY) shipment is now here.

1-9 pcs	\$39.50
10 - 24 pcs	\$29.50
25+	\$24.50

**LAST
CHANCE**



3600 & 4600 SYNTHESIZER CONSTRUCTION BOOK


The Australian edition of this very popular project book has been out of print for over 12 months. We now have the English edition of this popular book. If you missed out on the Australian edition then this is for you. (It contains the latest improvements such as the digitally scanned keyboard circuitry). Complete construction details on both synthesizers provided.

BOOK ONLY \$17.50

\$17.50

"How to play the
Synthesiser" book

\$12.50

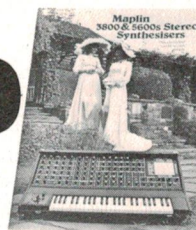

ETI 160 POWER SUPPLY 13.8V @ 10A

Oodles of regulated high current! Great for powering your high power mobile or linear at home!! Can also charge up a car battery pretty smartly too!! The Jaycar kit comes with Beryllium Oxide washers to help get the heat out of the two MJ15004 series regulator transistors. Complete kit includes box.

ONLY \$79

INNER EAR MINI PHONE

MODEL MT310

FEATURES: Samarium Cobalt magnets
102dB/mW
Weight 15 grams
Response: 50Hz-20kHz
Impedance: 32 ohms

Unit fits into the cusp of your ear. Can be worn under motorcycle helmets. Unbelievably clean sound.

ONLY \$19.50

HI-VOLTAGE HITACHI MOSFETS

V_{DD} 160V



The Hitachi complimentary Power Mosfets are very popular in Hi Fi and PA amplifiers. Up until now the very highest voltage versions have been hard to get. We now have these devices as well as the popular 2SK134 and 2SJ49 (140V) types. The 2SJ50 and 2SK135 enable you to use higher rail voltages for higher power.

2SJ49 & 2SK134	\$6.50	ea
2SJ50 & 2SK135	\$8.50	ea

POST AND PACKING CHARGES
\$5-\$9.99 (\$1.20) \$10-\$24.99 (\$2.40)
\$25-\$49.99 (\$3.50) \$50-\$99.99 (\$4.60)
\$100 up (\$6.20)

NEW SHOP HOURS
Mon-Fri 8.30 to 5.30pm
Sat 8.30 to 12.00pm
Thurs night to 8.30pm

JAYCAR 125 YORK ST SYDNEY 2000
Ph. 2646688 Telex: 72293
Mail Orders To:
Box K-39 Haymarket 2000

LETTERS

Dear Sir,

I wish to make reference to the recent article entitled 'Circuit Source Guide', as published in your February 1982 issue of ETI. On page 27 there is shown the circuit for a 'Six-bit DAC with 10-bit Precision'. This circuit is based on the well-known (?) R-2R ladder network to provide an analogue representation of the digital input data.

Regretfully, the author appears to have repeated the error which I have found elsewhere. That is, the value of the resistor from the ladder network to ground at the LSB should be '2R' and not 'R' as shown, that is of the value 200k and not 100k as shown. With the value of this resistor as 'R', the analogue output of the DAC produces a seemingly confused mixture of single and double steps, etc., as the input digital signal is varied. When this resistor is correctly valued as '2R' the expected single-bit interval step is obtained, should the output be graphed as the input is run up (or down) over its full range.

This correction to the published circuit has been verified in the practical application of a DAC, but also agrees with information gleaned from a number of sources, including 'Digital Interfacing with an Analogue World', J. Carr, TAB Books. The practical application of this problem relates to my employment, where a commercially produced data transmission system used the R-2R ladder network DAC in both the remote ADC and in the office DAC, so as to produce a control room analogue display of a slowly varying remote analogue condition. The same mistake as described above was repeated in both the ADC and the DAC, and as a consequence the output signal in the control room exhibited a seemingly random display of single and double bit steps on a graphical display as the remote analogue signal was slowly varied in magnitude. Much effort was expended in attempting to discover the cause of this fault, and when all other possibilities were expended the manufacturer's design was closely examined, so revealing the above original design flaw. One wonders how many other systems are about of similar equipment which contain the same mistake, which probably would not be recognised unless the output is displayed on a graphical recorder of sufficient resolution to display the irregular stepping.

Lastly, perhaps your article should more clearly state that the R-2R ladder network requires a BCD digital input

to function correctly, although this could probably be deduced from the description of the digital inputs.

I trust that the above information may be of interest to your readers, and should any have built this circuit, that the correction as described will improve the resolution of their system.

G. Clover
Wellington, NZ.

Thank you for pointing this out. We did miss it. As you say this is an error that is repeated in many places — with disastrous effect!

Roger Harrison
Editor, ETI

Dear Sir,

After waiting for some considerable time, I obtained from my newsagent a copy of 'Hobby Electronics Project Book'. Congratulations on an excellent job. From page 6 to 26 it is outstanding.

As an operator of soldering irons and hand tools over a period of more than 50 years, I cannot fault these 20 pages of information and instructions. All the projects are interesting and the reference section extremely handy. When's your next project book coming out?

However we can't be perfect all the time. I'm referring to the two crystal receiver projects, and in particular, to your list of suitable diodes. The OA202 is not a germanium diode, but a silicon rectifier. It will not perform as well with the low signals encountered in crystal receivers. I tried it, some time ago.

J. Ratcliffe
Southport Qld.

You are quite correct. The OA202 is a silicon diode and, if used, the crystal sets will have less sensitivity than if germanium diodes were employed. I am glad that you enjoyed our Hobby Electronics Project Book otherwise, though.

Roger Harrison
Editor, ETI

Dear Sir,

In the Letters page of the November issue last year you published a reader's letter concerning an electric fence project which you answered in the negative. I think such a project would be very popular, for a number of reasons. Commercially

available units tend to be either crude (electromechanical) and not wholly effective, or sophisticated and overpriced. It seems to me that you could design an effective electric fence energiser, perhaps using an ordinary car ignition coil and not a special transformer, that would outperform ready-made ones and cost considerably less.

P. Gosling
Seaham, NSW.

There are two approaches to designing an electric fence energiser: (a) battery-powered and (b) mains-powered. We have looked very closely into both avenues as that letter we published last November has occasioned many readers to write in a similar vein to yourself. Electric fence energisers, or controllers, are covered by Australian Standard 3129-1981, published 1 April 1981 (true!). If you care to fork out \$5.80 you will see the requirements an electric fence has to meet. Meeting the principal requirements with regard to output presents problems that are not simply solved yet still result in a device that is effective. The standard says:

12.3 Output Test No 1. The controller shall be connected as for normal operation and a measuring circuit shall be connected across the fence circuit terminals. The measuring circuit shall consist of a calibrated oscillograph, resistors, and capacitors arranged so that the load presented to the controller consists of a resistance adjustable to 500 Ω or 1 M Ω in parallel with a capacitance variable between 0 and 0.01 μ F.

Under these conditions the controller shall comply with the following requirements:

- (a) **Peak voltage.** With the resistance of the measuring circuit set to one megohm and the capacitor adjusted to a value to give the maximum voltage output, the peak output voltage shall not exceed 5000 V.
- (b) **Output current.** With the resistance of the measuring circuit set to 500 Ω , and the capacitor adjusted to give maximum output current, the output current shall not exceed 300 mA for more than 0.3 ms.
- (c) **Duration of pulse.** With the measuring circuit adjusted as for paragraph (b) above, the duration of the pulse shall not exceed 0.1 s and the time interval between pulses shall be not less than 0.75 s.
For the purpose of this test, the duration of the pulse shall be taken as the time from the beginning of the pulse until the pulse current has finally decreased to an instantaneous value of 5 mA.
- (d) **Current between pulses.** With the measuring circuit adjusted as for paragraph (b) above, the average of the r.m.s. values of current flowing between pulses shall not exceed 0.7 mA.
- (e) **Quantity of electricity.** With the measuring circuit adjusted as for paragraph (b) above, the quantity of electricity per pulse, obtained by integrating the area of the current time trace, shall not exceed 2.5 mC for the pulse duration as defined in paragraph (c) above. Where the pulse contains one or more cycles of an alternating current, the area integrated shall include the areas above and below the zero current line.

Experiments with a solid-state pulser and an ignition coil demonstrated to us that such a simple system would not comply with the standard. We could 'ignore' the standard and leave it to constructors and their consciences to see that their units complied but we regard that course as irresponsible. Development is continuing.

ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. (03) 489-8131.

ELECTRONIC COMPONENT SUPPLIERS, DESIGNERS & MANUFACTURERS.
RITRONICS WHOLESALE (03) 489-7099. MAIL ORDERS (03) 481-1436.

TELEX: AA38897

For heavier items add additional postage. Extra heavy items sent Comet freight on. Prices subject to change without notice. Send 60c and SAE for free catalogues. Minimum pack and post \$1.00. Bankcard Mail Orders welcome.

SUPER SPECIALS				BU326				\$1.90				16 Pin				1.20				1.10				15.00uf				40V				12.00				40 Way				400				3.50																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
2708		\$ 4.50		ZBOS10				\$18.00				74LS40	.50	81LS97	2.10	2N5874	1.40	TIP32C	1.00	8295	25.00																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																								</

Shoparound

THIS PAGE is to assist readers in the continual search for components, kits and printed circuit boards for ETI projects. If you are looking for a particular component or project — check with our advertisers if it is not mentioned here.


ETI-647 'Turtle Talk' speech synthesiser

This project is being distributed as a kit, wholesale, by Flexible Systems. To date,

Rod Irving Electronics, All Electronic Components and Electronic Agencies have indicated they will be stocking the kit. If you're after a kit, contact one of these firms, not Flexible Systems.

ETI-918 'Photophone'

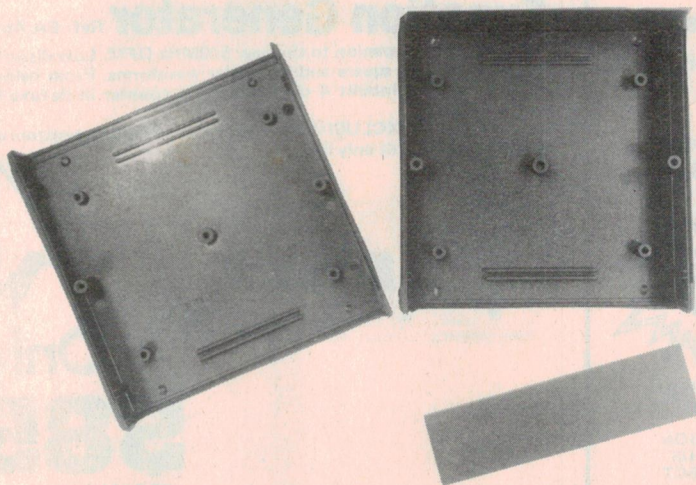This little light beam transceiver is amazingly effective — in daylight or in dark! Suppliers who have indicated they'll be stocking this as a kit are



LOCALLY-MADE INSTRUMENT CASE

A smart new instrument case, model I/C-1, moulded in ABS plastic has been released by Cadin/Cliff Electronics P/L. The case features rounded edges and has provision internally for a variety of pc board mounting positions for both the top and bottom covers. Internal slots also provide for recessed front and/or rear panels.

It comes complete with pc board mounting hardware, self-adhesive rubber feet and blank 'easy cut' styrene front and rear panels. The case measures 132 x 129 x 38 mm and is ideally suited for small instrumentation applications, housing projects, prototypes etc.

All enquiries to Cadin/Cliff Electronics, Melbourne. (03)288-6244, (03)870-0684.

— Altronics in Perth, All Electronic Components and Rod Irving Electronics in Melbourne and Dick Smith stores. If you've got most of the parts in your junk box, you'll probably be trying to hunt up a solar cell and the electret mic insert. Solar cells are stocked by: Tandy — who have two suitable types, 276-124 which is 25 x 50 mm, and the 276-125 which is 50 x 50 mm; Dick Smith stocks a circular segment type, catalogue number Z-4835, and Jaycar currently stock some small ones — two circular types, 30 and 45 mm in diameter, plus a rectangular type measuring 12 x 25 mm.

Electret microphone inserts are widely stocked. Tandy have one, catalogue number 270-092. Electronic Agencies have one, catalogue number CE0162 and Dick Smith stocks one, catalogue number C-1160. Jaycar also have a suitable insert.

Printed circuit boards will be available from the suppliers listed in last month's Shoparound. All the other components are off-the-shelf items and you should have no difficulty getting them.

ETI-1509 dc-dc inverter

The only specialised components used in this inverter are the two transformer cores. The feedback transformer uses the FX2242 potcore, which is widely available. The output transformer uses the Philips EC-core assembly, specified in last month's 12 V Fluorescent Light Inverter (ETI-1505). This assembly should be readily available this month, although you'd better get in early because both the Fluorescent Light Inverter and this project are likely to be quite popular and supplies might diminish quite rapidly.

MASTER ELECTRONICS NOW! The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical, way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

New Job? New Career? New Hobby? Get into Electronics Now!

Post coupon now:

The Australian School of Electronics Pty Ltd.
(Inc. in Victoria)
P.O. Box 108, Glen Iris,
Victoria 3146.


A Registered
Correspondence College



FREE
COLOUR BROCHURE



by SEEING

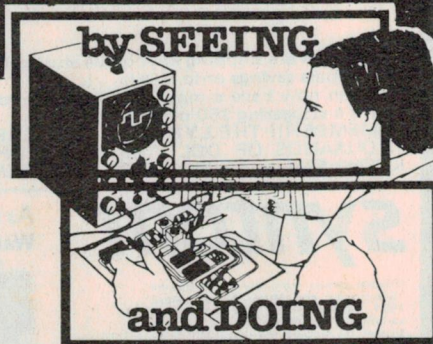

Please send your brochure without any obligation to:

Name _____

Address _____

Post Code _____

ETI 9/821

YOUR BONUS

JAYCAR QUALITY FOR NO MORE

500MHz Digital Frequency Period Meter

REF: EA Dec '81 - Feb '82

NOW BACK IN STOCK! The best version of this kit in Australia is now back in stock. Why settle for an inferior kit at the same price as ours?

500MHz option only \$26 extra
50MHz Version \$119



Tilting Bail to suit ONLY \$4.95

Other people may appear to be selling this kit for less. But you GET less!!! Exclusive Jaycar features:

- * Heavy gauge front panel. Pre-punched, and silkscreened. (NOT Scotchcal).
- * Low aging rate 10,000 MHz crystal
- * Quality IC sockets provided (A MUST)
- * All metal film resistors used (1% 50ppm)
- * Thermal alloy heatsink for +5V regulator

Beware of advertised units that do not conform to the original design. They may have inferior performance.

THE BEST QUALITY KIT VERSION OF THIS PROJECT IN AUSTRALIA


ONLY \$119

Function Generator

Ref: EA April 1982

"Pigeon Pair" companion to the new 500MHz DFM. Low distortion generator of sine, square and triangular waveforms. From below 20kHz to over 160kHz. Inbuilt 4 digit frequency counter in de-luxe Pac-Tec case. Only \$85

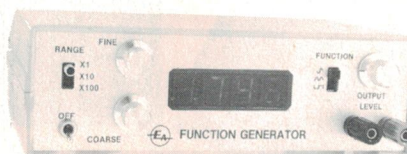JAYCAR EXCLUSIVE - 1% 50ppm metal film resistors used for stability and it's still only \$85!!!



Only \$85
SPECIAL JAYCAR PANEL SUPPLIED

Unit pictured with EA Panel

Lyrebird Piano Kit

REF: EA 11/81-1/82

NEW LOW PRICE

\$475

SAVE \$50!!!



BOTH PIANO KITS FEATURE I.C. SOCKETS PROVIDED AT NO EXTRA CHARGE!!!

7 1/4 OCTAVE (88 NOTE) VERSIONS \$589

* Stand \$75 extra

Because we are shipping keyboards and other expensive components in bulk due to high demand, we can pass savings onto YOU.

You can now have a magnificent "Lyrebird" six octave touch sensitive piano for only \$475!!! That's a staggering \$50 off the old price.

REMEMBER!! THE LYREBIRD OUTPERFORMS READY BUILT PIANOS COSTING UP TO THOUSANDS OF DOLLARS MORE. WHY PAY MORE WHEN YOUR CONSTRUCTION KNOWLEDGE CAN SAVE YOU A FORTUNE?

syntom

As used by Warren Cann of 'Ultravox'



Only \$32.50

Original design from the UK magazine "Electronics and Music Maker" April 1981. Self-contained unit produces a variety of fixed and falling pitch effects. Trigger by tapping the unit itself or by striking a drum to which the unit is attached. The Jaycar "SYNTOM" comes complete with high quality pre-drilled moulded all ABS box 152 x 80 x 47mm with professional silk-screened front panel.

FEATURES: Decay from less than 0.1 second to several seconds, pitch control, sweep control and volume on/off.

THIS MONTH ONLY!! SAVE \$4.00

GOOD-BYE 3002


This 2x300WRMS P.A. Head is a classic road amp. Ruggedly constructed, 19" rack mount makes an ideal main P.A. or foldback unit. Great for Disco use as well.

We are discontinuing this amp because it is becoming too expensive to make. The metalwork costs alone now account for well over 50% of the unit. Because of this we have reluctantly decided to discontinue the unit.

You can grab one now while they last for only \$399

\$489 \$399

SAVE \$89!!!

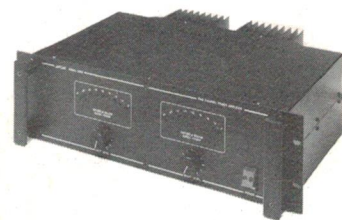

Send SAE for full spec. sheet.

"SELLOUT" EA LOW-DISTORTION AUDIO OSCILLATOR

Ref: EA June 1981.

15Hz - 150kHz 0.003% distortion. Sine and Square wave.

WAS \$64.50

NOW \$54

SAVE OVER \$10!!

CRYSTAL FILTER 10.695 MHz


We have limited stocks of what is normally a very expensive component. High quality multi-stage unit suitable for precision I.F. work.

This device enables you to produce very high selectivity receivers for many applications.

Only \$5.00 ea.

Were \$19.95 ea.

10.695 MHz Crystal to suit, only \$2.50

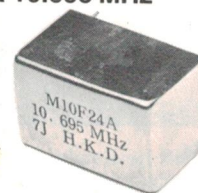

1/3 OCTAVE 28 BAND EQUALISER

The 2801 is a single channel graphic equaliser that divides the audio spectrum into twenty eight one third octave bands. Each frequency segment is controlled by a slider that provides up to -10dB of adjustment in standard ISO steps. The 2801 was designed primarily to compensate for any deficiencies in the linearity of speaker systems, acoustic peculiarities of the hall or listening room, and inadequacies of program source quality.

In P.A. application the equaliser may be used to improve sound quality and increase intelligibility by attenuating problem frequencies that cause ringing, boominess or other disruptive resonances that occur in acoustically difficult rooms. The 2801 allows sound systems to be "tuned" according to the special acoustics of a room, to maximize output and minimize feedback.

As a creative tool in sound recording or re-recording the 2801 allows complete freedom in contouring response over the complete audio spectrum from 31.5Hz to 16KHz.

TOTALLY REFURBISHED MODEL-2801 MKII A


This model is distinct from the 2801, 2801 MK II. It features quality I.C. sockets for all I.C.'s as well as several component changes. ie: We are using 4136 op amps again because they draw less current than the TLO75/85. This results in less hum radiation from the transformer. We are also using higher value slide pots, and a 5534 op amp for the line driver. Using the 5534 renders the output short circuit proof-handly when on the road.

You get all these great new features at no extra cost!

NEW MkII model A

SPECIFICATIONS


DISTORTION (@ 2 volts out)	Less than .04% 20Hz-20kHz
FREQUENCY RESPONSE	Flat
-EQ. IN	20Hz-20kHz ±.5dB
SIGNAL TO NOISE RATIO (@ 2 volts out, controls flat)	Greater than 85dB
OUTPUT IMPEDANCE	50k to 100k depending on the input configuration
MAXIMUM INPUT VOLTAGE	10 volts
EQ centre frequencies	31.5, 40, 50, 63, 80, 100, 120, 160, 200, 250, 315, 400, 500, 630, 800, 1K, 1.25K, 1.6K, 2K, 2.5K, 3.15K, 4K, 5K, 6.3K, 8K, 10K, 12.5K, 16K, Hz
Range of controls	+10dB
Individual Filters	+15dB
LEVEL MATCH	28 Vertical potentiometers continuously variable
EQUALISATION	Rotary potentiometer variable +15dB
LEVEL	Toggle switch
EQ BYPASS	Toggle switch
POWER	Rear panel RCA sockets and 6.5mm sockets for input and output
TERMINATIONS	19" x 3 1/2" x 8" (standard rack mount size)
PHYSICAL	4kg
Size	Front panel brushed and anodised black with lettering, black Marvplate cover.
Weight	
Finish	

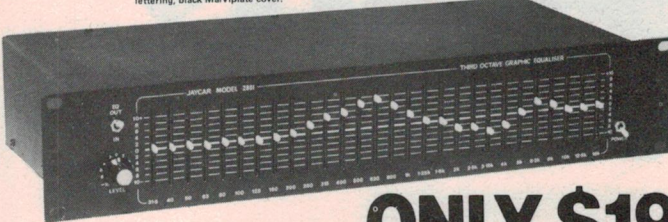

ONLY \$198

JAYCAR 2010 EQUALISER

The 2010 is a two channel graphic equaliser featuring ten adjustable controls on octave centre frequencies (independent for each channel). Each control provides up to = 14dB of adjustment. Each channel is also equipped with a level match control giving an overall gain of adjustment of = 14dB. The functional versatility of the 2010 equaliser is unsurpassed. Eight modes of operation are available from the push button switches on the front panel. Included amongst these are the ability to equalise both recording and playback when dubbing tapes. The 2010 has been designed to be compatible with all commercially available equipment and is ideal for use in a Hi Fi system or PA system

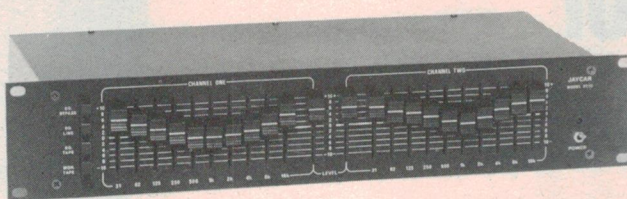

ONLY \$129

SPECIFICATIONS

ELECTRICAL (EACH CHANNEL)	+0.5dB 10Hz to 20kHz, Controls flat
FREQUENCY RESPONSE	Flat
F.O. LINE OR TAPE	Greater than 87dB
EQ BYPASS	Less than .04% 20Hz to 20kHz
SIGNAL TO NOISE RATIO	100ohms
2 VOLTS OUT CONTROLS FLAT	2 Volts RMS into 10K load
TOTAL HARMONIC DISTORTION	10 volts RMS
1 VOLTS OUT CONTROLS FLAT	50K nominal
OUTPUT IMPEDANCE	10 volts RMS
RATED OUTPUT	31, 62, 125, 500, 1K, 2K, 4K, 8K, Hz ±10%
INPUT IMPEDANCE	+12 dB at Centre Frequency
MAXIMUM INPUT VOLTAGE	+10dB
EQ CENTRE FREQUENCIES	10 Vertical Slide Controls for each channel
RANGE OF CONTROLS	Vertical Slide Control each Channel
INDIVIDUAL FILTERS	Pushbutton Switch
LEVEL MATCH	Pushbutton Switch
CONTROLS	Pushbutton Switch
EQUALISATION	Pushbutton Switch with LED indicator
LEVEL	Rear panel RCA sockets for both input and output connections
EQ BYPASS	
F.O. LINE	483mm x 89mm x 152mm
MONITOR TAPE	(19" x 3 1/2" x 8")
POWER	4kg
TERMINATIONS	Front panel brushed and anodised Aluminium silk screened lettering. Black Marvplate covers.
PHYSICAL	
DIMENSIONS	
WEIGHT	
FINISH	

NEW MkII model A with QUAD-FETs

EXCLUSIVE!!! ALL JAYCAR TEST EQUIPMENT KITS ARE PROVIDED WITH QUALITY I.C. SOCKETS AT NO EXTRA CHARGE!!!

Digital EA2/82 Thermometer


Ref: EA Feb 1982
Read the temperature in your room (or outside) from 0 degrees C to 100 degrees C in fact to within 0.1 degree C. Fantastic resolution on a bright easy-to-read display.
INC CASE



\$69

DIGITAL CAPACITANCE METER

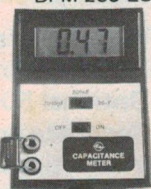Ref: EA March 1982
This kit once again uses the amazing DPM 200 LCD display/driver module. Capable of measuring capacitance from: 1pF to 19.99uF. It is a must in every workshop or lab. Kit includes case.



\$69

HEART RATE MONITOR

Ref: EA 7/82



NOW \$69

*** WAS \$79 SAVE \$10**


This unit enables you to measure your own pulse instantly and accurately. It is light enough even for joggers to carry. A must for people who may have heart problems. Complete kit including LCD Display.

EA dual tracking P/S

EXCLUSIVE!!
US-MADE
10 TURN .25%
LINEARITY POT
used for greater
accuracy

\$84.50

Ref: EA March '82

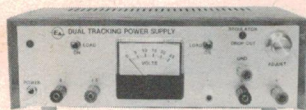


1% resistors used NOT 2%.

At last!! A dual-tracking power supply with fixed +5V reg. at a reasonable price!!

YOU PAY NO MORE FOR A QUALITY JAYCAR KIT!!

Digital Storage CRO Adaptor

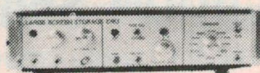Ref: Feb 1982 EA
Not only can you avoid buying an expensive CRO but you can have the features of the REALLY expensive ones!!!



\$110

- Can display very slow waveforms
- One shot triggering
- Inbuilt graticule shows on TV screen
- Crystal locked timebase
- DC-100kHz bandwidth
- capable of storage operation
- Staggering value at \$110.

NEW!!! LCD TACHO KIT!

ref: EA May 1982



\$49.50

- USES NEW DPM-05 DISPLAY
- FITS INTO YOUR DASHBOARD
- RPM, DWELL DISPLAY

JAYCAR

125 YORK ST SYDNEY 2000
Ph. 2646688 Telex: 72293
Mail Orders To:
Box K-39 Haymarket 2000

POST AND PACKING CHARGES
\$5-\$9.99 (\$1.20) \$10-\$24.99 (\$2.40)
\$25-\$49.99 (\$3.50) \$50-\$99.99 (\$4.60)
\$100 up (\$6.20)

NEW SHOP HOURS
Mon-Fri 8.30 to 5.30pm
Sat 8.30 to 12.00pm
Thurs night to 8.30pm

ANNOUNCING...

The new AOR range of hand-helds!



AR 280 (VHF 144-148 MHz)

Special Features:

- Three-channel memory including non-standard split option
 - One-hour fast charging and car direct usage lead
 - 5-watt output
 - Removable battery pack
 - Wall charger
- A\$170 (incl. postage)

AR 180 (Marine)

Special Features:

- Water resistant
 - Exchangeable ni-cad battery pack
 - Optional 50-watt linear amplifier
 - Complete with 73 CHs covering all international maritime frequencies
 - Desk-top charger
- A\$265 (incl. postage)



DELTA COMMUNICATION SERVICES LIMITED

1109 HOUSTON CENTRE, 63 MODY ROAD, TSIMSHATSUI EAST, KOWLOON, HONG KONG.

Phone: 3-699241-6. Telex: HX 38083 APPLE Cables: DELTAENG HONG KONG



Russian amateur satellite in trouble

The Russian amateur satellite, Iskra 2, the first satellite to be launched from a manned spacecraft (reported in this column in the July issue), experienced trouble with its 15m to 10m transponder soon after launch.

Iskra 2 was placed in orbit on May 17th when two cosmonauts, Anotoly Berezovsky and Valentin Lebedev pushed the satellite out of an air lock on their Salyut 7 space station. The satellite carried the first HF to HF transponder ever orbited.

It entered an elliptical orbit, 355 km at apogee, 240 km at perigee, placing it well within the ionosphere. The orbit shrinks at about 1 km a day. About a week

after launch, the transponder was reported to be not functioning.

Transponder problems were put down to either de-sensitisation or feedback as the input and output shared the one antenna. However, the 29.578 MHz beacon is functioning well and has been reported to be heard for as much as an hour after the satellite has passed over the horizon. (Item courtesy Westlink Report.)

AMSAT satellite computer net

Specifications for AMSAT's international computer network, to be called AMICON, are being prepared by Hank Magnuski, K6AM.

The network will operate over a transponder on board the Phase IIIIB satellite now expected to be in orbit in the next month or so. The AMRAD group is also preparing its own recommendation. (From Westlink Report.)

SSB above 300 MHz 'out of the question'?

An article in a recent New Scientist on frequency congestion would have us believe that SSB above 300 MHz is "... out of the question".

There are some amateurs who would disagree. Totally. Like Dick Norman VK2BDN, current holder of the world distance record on 1296 MHz — a contact established using SSB.

The article concerned, 'Why Radio is Running Out of Airwaves', by Barry Fox, discussed various aspects of spectrum congestion in Britain. On SSB and its use on VHF, he says, "At first, engineers could make SSB operate with enough stability only up to 30 MHz. Now,

with modern circuits, the threshold has been raised to 300 MHz, and SSB mobile radio could work in the VHF bands".

"But SSB in the UHF bands ... is still out of the question."

Admittedly, he's probably taking the commercial case where fixed channels are used and the stability requirement is greater than amateurs use. But, out of the question? — hardly.

Amateurs lead the way again.

'Sinadder' from Vicom

Products manufactured by the Helper Instruments Company are now available from Vicom International. These products include the famous 'Sinadder 3'.

The unit features an automatic distortion meter which includes an internal 1 kHz generator or monitor. It measures SINAD sensitivity and gives rapid alignment.


The units ac voltmeter provides nine ranges from 10 mV full scale to 100 volts full scale.

It can be used to check audio circuits from microphone to loud-

speaker levels. An internal audio amplifier and loudspeaker controlled by the range switch and front panel pot maintains proper sound level regardless of input.

It can also be used as an audio signal tracer.

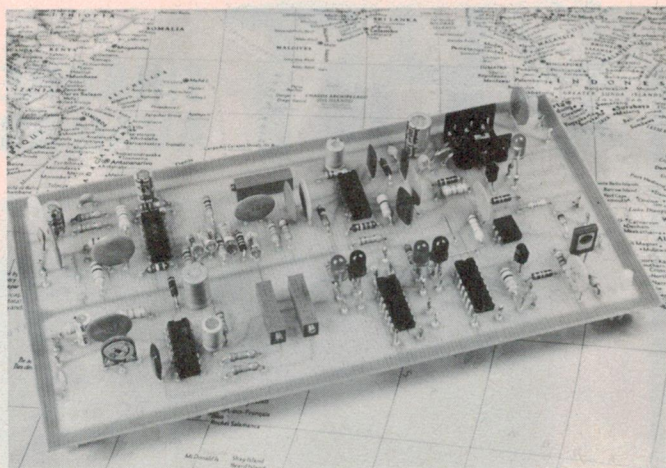Details from Vicom, 57 City Rd, South Melbourne Vic. 3205. (03) 62-6931.



Compact RTTY terminal

Designed for HF and VHF amateur radio and/or commercial use at baud rates of 45 to 50 with a shift of 170 Hz, the MDK-17 RTTY terminal is now available from GFS Electronic Imports.

Other baud rates and shifts may be accommodated but some component changes are necessary.

The MDK-17's design makes for simple hook-up to both transceiver, teletype and/or computer terminal. Its 10 ports provide for all combinations of TTL and high voltage 20-60 mA send-receive systems. An open collector output allows direct keying of HF Transceivers.

State-of-the-art circuitry is used throughout its design, according to the makers, including the XR2211 IC which combines both limiter and active band pass filter in the one package.

The tone generator uses an XR2206 IC which allows for excellent temperature stability, they say. Accurate setting of tone frequencies and demodulator centre frequency

is provided for by using 15-turn trim pots in these critical areas.

Other features include the provision to invert the signal sense in both the send and/or receive modes. LEDs are used to indicate transmitted tone and correct receiver tuning. An auto-start output is available for driving TTL circuitry. Only a single +12 V supply is required as the power source.

The MDK-17 is available fully assembled, aligned and tested for \$145 plus \$5 post or as a complete kit at \$95 plus \$5 post. The kit is supplied with comprehensive, easy to follow assembly instructions. Approximately two hours is required to assemble and test it.

For further information contact GFS Electronic Imports, 15 McKeon Road, Mitcham Vic. 3132.

Miniature X-Y 'scope

Vicom International now represent Vu-Data Corporation of the United States, who have just released a mini X-Y display scope, Model 2010.

The unit can be employed as a stand-alone unit, or mounted in a system panel, and its manufacturers claim that it is ideal for numerous applications previously satisfied only by large and expensive display modules.

This model is claimed to have

excellent trace resolution, CRT brightness, and high frequency capabilities. Vertical axis bandwidth is 10 MHz, while horizontal X-axis bandwidth is 5 MHz, according to the specs.

Contact Vicom, 57 City Rd, South Melbourne Vic. 3205. (03)62-6931.

**NEW STORE
opening October
in Carlingford**


AT CARLINGFORD COURT NEXT TO KENTUCKY FRIED CHICKEN

CAR COMPUTER

HIT

THIS GREAT NEW EA DESIGN IS
AVAILABLE FROM JAYCAR!!!

**FROM
\$109.50**

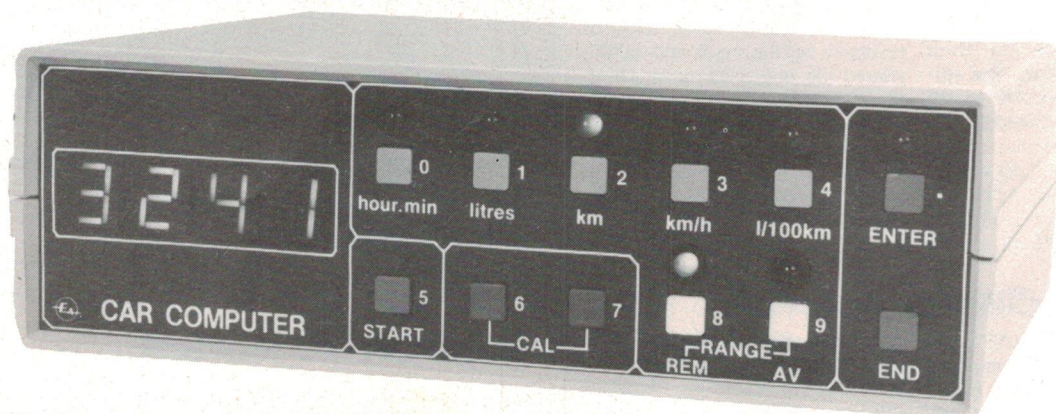

SAVE A FORTUNE ON PETROL BILLS!

—YOU WILL KNOW EXACTLY HOW MUCH FUEL YOU
ARE USING AND THE RATE AT WHICH IT IS
BEING USED!!!

CALCULATES

- FUEL ECONOMY (INSTANTLY AS YOU TRAVEL ALONG) IN LITRES/100KM.
- AVERAGE ECONOMY OVER A TRIP.
- AMOUNT OF FUEL USED SO FAR
- AMOUNT OF FUEL NEEDED (BASED ON AVERAGE USE) TO COMPLETE TRIP. ALSO TIME REMAINING.
- ELAPSED TIME
- SPEED IN K'S/HR. MORE ACCURATE THAN CAR SPEEDO
- DISTANCE TRAVELLED/REMAINING
- HOW FAR YOU CAN GO ON FUEL LEFT

Ref: JULY/AUG 82

**HIGH QUALITY
DOUBLE-SIDED
PLATED THRU
PCB's!
—A MUST!!**

FUEL SENSOR




This is a genuine English 'MORAY' unit that was strongly recommended by EA. Measures fuel from 1-100 litres per hour. Output 20,000 pulses/litre, CMOS/TTL Compatible. A comprehensive data sheet is supplied with each unit.

\$45

speed sensors

Two types available. Both operate with the EA Car Computer and give much the same results. The speed cable unit is handy for front-wheel drive or cars which have no tailshaft. This unit does require the speedo cable (outer sheath) to be cut. It does not affect the operation of the speedometer in any way and can be used with tailshaft cars also. The magnet/coil unit is only really suitable for cars fitted with tailshafts, but the speedo cable is not touched.

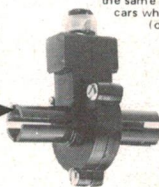

\$19.50

TAIL SHAFT TYPE (COIL/MAGNET)
SPEEDO CABLE TYPE



\$14.50

JAYCAR

125 YORK ST SYDNEY 2000
Ph. 2646688 Telex: 72293
Mail Orders To:
Box K-39 Haymarket 2000

POST AND PACKING CHARGES
\$5-\$9.99 (\$1.20) \$10-\$24.99 (\$2.40)
\$25-\$49.99 (\$3.50) \$50-\$99.99 (\$4.60)
\$100 up (\$6.20)

NEW SHOP HOURS
Mon-Fri 8.30 to 5.30pm
Sat 8.30 to 12.00pm
Thurs night to 8.30pm

YOUR CHANCE TO LEARN ABOUT MICROS WITH THE MICROPROFESSOR FREE!

THAT'S RIGHT, HERE'S YOUR CHANCE TO WIN THE AMAZING MICROPROFESSOR, COMPLETE WITH SPEECH SYNTHESISER AND PRINTER. COMPLIMENTS OF ETI AND EMONA ENTERPRISES WHO MARKET THE MICROPROFESSOR IN AUSTRALIA. TOTAL RETAIL VALUE \$655

The MPF-I Microprofessor features a Z80 microprocessor — the most widely used 8-bit processor, and the basic unit comes as a single board computer complete with 36-key keyboard, a 6-digit display, 2K of RAM, 2K monitor ROM, cassette interface (for storing programs on an ordinary audio cassette tape), 24 input/output lines for expansion (expansion units are available) and a speaker for sound output. It's all powered by a plug pack.

Special manuals are provided aimed at helping you teach yourself by experiment using the Microprofessor.

Amazingly, it sports a tiny BASIC interpreter in a PROM you can plug in. Commands include continue, call, for . . . next, goto, gosub, input, if . . . then, let, list, load, new, print, return, run, save, stop. You get a form of mnemonic readout on the display.

Expansion units include a speech synthesiser and a printer.

The SSB-MPF Speech Synthesiser Board features:

- TI speech synthesis chip.
- 4K EPROM for time-clock program and speech utility.
- Two EPROM sockets for expanding vocabulary.
- Uses keyboard and speaker of MPF-I as input/output device.
- Adjustable voice pitch and volume.
- 9 V, 0.5A adaptor provided.
- Complete accessories including 40-pin, double-headed connector, audio jumper, operation manual, etc.

The PRT-MPF Printer features:

- Compact thermal printer.
- Built-in alphanumeric character patterns
- Built-in MPF-I memory dump utility.
- Built-in MPF-I BASIC program listing utility.
- Built-in Z80-Disassembler listing utility.
- 20 characters/138 dots per line.
- Printing speed 0.8 line per second.
- Printer head life more than 500 000 lines.
- 9 V, 0.6A adaptor provided.



Rules: This contest is open to all persons normally resident in Australia with the exception of members of the staff of Emona Enterprises, Murray Publishers, Offset Alpine, Australian Consolidated Press and/or associated companies. Closing date for the contest is the 31st October 1982. Entries received within seven days of that date will be accepted if postmarked prior to and including 31st October, 1982. The winning entry will be drawn by the editor of Electronics Today International, whose decision will be final. No correspondence can be entered into regarding the decision. Winner will be advised by telegram the same day the result is declared. The name of the winner and the winning answer will be published in the next possible issue of Electronics Today International. Contestants must enter their names and addresses where indicated on each entry form. Photostats or clearly written copies will be accepted but if sending copies you must cut out and include with each entry the month and page number from the bottom of the page of the contest. In other words you can send in multiple entries but you will need extra copies of the magazine so that you send an original page number with each entry. This contest is invalid in states where local laws prohibit entries. Entrants must sign the declaration, accompanying this contest, that they have read the above rules and agree to abide by their conditions.

Just fill in this coupon; attach it to your entry and send it to

ETI "WIN A MICROPROFESSOR" CONTEST 15 Boundary St, Rushcutters Bay NSW 2011.

Name
Address Postcode

In 100 words or less tell us why you want the Microprofessor and what features attract you.

It's that easy, but hurry entries close 31st October 1982.

You're probably solving this sort of problem by pulling out an analysis pad and drawing up a spreadsheet by hand – taking your budget and recalculating every value in a series of columns – then checking them. If you're lucky you have a programmable calculator to help.

Here's what you should be doing: Multiplan running on a personal computer replaces pencils, paper, erasers, calculators and endless manhours in modelling, estimating and planning activities. Like the example here: if your sales tax rate is 17.5%, you simply put that figure at the top of the sales tax column – Multiplan calculates each product's sales tax value. If a price changes or the tax rate changes, you change one number – Multiplan changes the rest. You see all the results on a spreadsheet 63 columns wide, 255 rows deep and pages thick.

Multiplan is a computer program for non-computer people. Multiplan lets you assign names to cells or areas such as 'sales' or 'expenses', then lets you refer to that name in future formulas. On Multiplan you

Mr Howard increases sales tax by 2%.

How does this affect your company's profits?

15 seconds to answer.

can have a formula like:

Profit = Sales – Expenses

On other spreadsheet programs that would look more like:

Profit = R1C3 – R5C12


Multiplan is also the only

spreadsheet program capable of colour operation and there are none of the problems with forward reference handling that can cause other programs to give completely spurious answers. Multiplan lets you access data on other spreadsheets and allows multiple windows on the screen so you can see the effects of new entries on other parts of the sheet.

A friendly system. Multiplan is specifically designed to eliminate the routine and tedious tasks associated with forecasting, modelling and planning. In designing the program, Microsoft, the world's largest producers of personal computer software, aimed to provide users with an easy-to-use tool which maximizes executive thinking time while minimizing the time required to learn and use the system productively.

Multiplan is available right now for use on Apple™ computers, and will soon be available for use on the Osborne 1™ and standard 8" CP/M™ computers. Versions for other computers are under development.

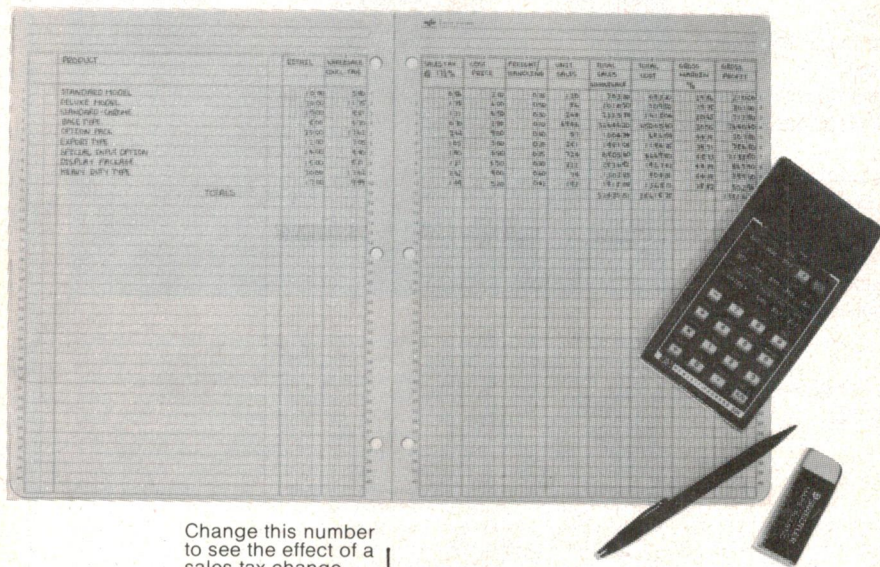Call into your nearest computer store and see Multiplan in action – your next forecast need only take you 15 seconds instead of hours.



Change this number to see the effect of a sales tax change

All dependent variables are automatically calculated to your formula

Simulated screen

PRODUCT	RRP	W SALE	S.TAX	COST	PRY	UNIT	TOTAL	TOTAL	GROSS	PROFIT
	INC	T	17.5%	PRC		SALES	SALES	COST	MARGN	
STO MODEL	10.00	5.00	.86	3.00	.25	1.20	703.20	493.20	29.86	210.00
DELUX MOD	20.00	11.75	1.75	6.00	.50	.86	1010.50	709.50	29.78	301.00
STO-CHROME	15.00	8.81	1.31	4.50	.30	2.64	2325.84	1613.04	30.65	712.80
BASE TYPE	8.00	4.70	.70	2.80	.10	69.46	32646.20	25005.60	30.55	7640.60
OPTION PK	30.00	17.62	2.62	9.00	.60	.57	1004.34	696.54	44.19	307.80
EXPORT TYPE	12.00	7.05	1.05	3.00	.20	2.81	1981.05	1194.25	39.71	786.80
SPEC INPUT	16.00	9.40	1.40	4.80	.25	7.24	6805.60	4669.80	45.73	2175.80
DISPLAY PKG	15.00	8.81	1.31	4.50	.30	3.22	2836.82	1967.42	44.19	869.40
HEAVY DUTY	30.00	17.62	2.62	9.00	.60	.74	1303.88	904.28	44.19	399.60
SPEC DISPL	17.00	9.99	1.49	5.20	.42	1.92	1918.08	1365.12	28.82	552.96
TOTALS							52435.51	38518.75		13816.76

Column widths are individually variable

Multiplan

from **MICROSOFT**

For the name of your nearest Microsoft dealer or more information on Multiplan contact:

Wiser-Microsoft

PO Box 95, Forestville 2087. Ph (02) 451 9445

Apple II version:
\$295
+ tax

Multiplan is expected in stock and the price is correct at time of going to press.

COMPUTING TODAY

Zilog release 'virtual memory' processors

The Z8003 and Z8004 Virtual Memory Processor Units (VMPUs) just released by Zilog, are 16-bit MOS microprocessors offering all the features of their Z8001/2 CPUs, plus integral provisions for operation in a virtual-memory environment.

The Z8003 VMPU generates 23-bit addresses organized into 128 segments of up to 64 Kbytes each. The 8004 VMPU generates 16-bit addresses.

Both are designed to implement a 'virtual memory' environment where programs and data being operated on need not reside simultaneously in main memory.

The benefits of virtual memory are the elimination of main memory size constraints on application programs, with an associated increase in programmer productivity and lower system costs because smaller memory sizes can support large applications.

In such an environment, provision must be made for retrieving parts of the program or data located in 'secondary' storage (e.g. a disk). When the CPU attempts to access such 'non-resident' data, the transaction accessing that data must be interrupted, the state of the CPU saved, the desired data moved to

main memory, the state of the CPU restored, and the interrupted instruction restarted.

The Z8003 has an external abort pin that permits interruption of instruction execution before completion of the instruction.

Ideal for use in shared-memory and multiple-microprocessor systems, the Z8003/4 features an interlock status signal that prevents memory access collisions by arbitrating attempted simultaneous accesses to shared resources, Zilog say.

The Z8003/4 VMPUs are designed to work with present and future Zilog memory management units (MMUs), including the Z8015 Paged MMU, which will be available later. This flexibility allows segmented or paged virtual memory systems to be implemented.

Production quantities will be available in the fourth quarter of 1982, Zilog say.

Motorola to alternate-source Intel bubble memory products

An agreement to cross-license and alternate-source magnetic bubble memory technology has been announced by Motorola Inc and Intel Corporation, of Santa Clara, California.

Under terms of the agreement, the companies will jointly develop two new one-megabit devices based on the architecture of Intel's existing 7110 one-megabit bubble memory.

The new bubble memories will be smaller versions of the present 7110.

The first device will have the same performance as the present 7110, while the second will provide half the access time and twice the data rate (200 kilobits/s).

Intel and Motorola also will jointly adopt a low-height, leaded package for the new memory. The package is

presently under development by Intel and is similar to one currently manufactured at Motorola.

Additionally, to provide complete component-level interchangeability to users, Intel will transfer Motorola design and compatibility data to allow Motorola to produce the peripheral chips necessary to operate the new bubble memories.

These support circuits include Intel's 7220 bubble memory controller, 7230 current pulse generator, and 7242 formatter/sense amplifier. Motorola will manufacture and alter-



X.25 test and development system

The Tekelec TE92 data monitor and test system is capable of handling speeds up to 128 Kbps and operates as either an analyser or simulator in the X.25 environment.

The TE92 monitors traffic and selected data is captured in dynamic RAM (16 Kbytes) or on diskette (80 Kbytes), and presented to the operator as a time-correlated split screen display at the frame and packet level for easy analysis — either in interpreted X.25 mnemonics, in ASCII, EBC Dic, Hex or Binary.

Various data capture triggers are available which allow even specific logical channels within multiplexed traffic to be traced.

As a simulator, the TE92 emulates an X.25 network or a subscriber to that network and correctly handles all X.25 data transfer and error recovery procedures.

Also available is 'Sitrex', an ex-

clusive scenario simulation package, which enables the user to customise applications software, and to introduce deviations from X.25 standards.

The applications of the TE92 are:-

- Network monitoring, maintenance, diagnostic testing, fault detection
- Equipment/software development, testing, certification
- Deviations to X.25 standards, customising protocol
- Protocol analysis, training in X.25 protocol

Tekelec Airtronic is represented in Australia by Paton Electrical Pty Ltd, 90 Victoria Street, Ashfield NSW 2131.

nate-source each of these and any other products required for the two new one-megabit memories.


The cross-licensing agreement also calls for Motorola to provide Intel with a process technology for bubble memory device production.

Customer shipments of the first new bubble memory are expected to begin in the second quarter of 1983, with the higher performance

device available by the end of that year.

The agreement reached by the two leading microprocessor manufacturers is expected to accelerate the growth of the bubble memory market. Users' systems design and production activities will be enhanced by the availability of a standardised bubble memory component architecture.

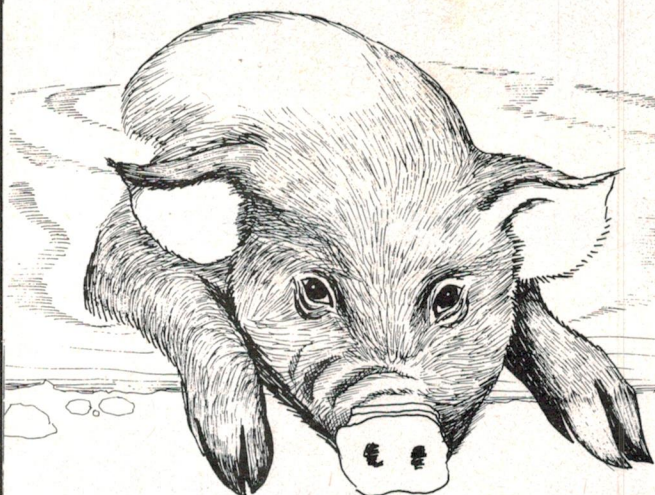magmedia magmedia magmedia magmedia magmedia



THE 100% SOLUTION TO YOUR DIRT PROBLEMS *FREE*

We at Magmedia believe VERBATIM'S New DATALIFE CLEANING DISKETTES are the best in the world. Together with the DATALIFE DISKETTES made in Australia with 7 shielding improvements, 100% tested, 100% certified, 100% warranted we think you'll believe it too.

WE MAKE YOU THIS OFFER:

BUY A BOX OF DATALIFE DISKETTES AT THE NORMAL PRICE AND RECEIVE A FREE VERBATIM DATALIFE CLEANING KIT VALUED AT \$12.42!

SATISFACTION GUARANTEED



magmedia

SYDNEY
(02) 428 1100

MELBOURNE
(03) 699 9688

BRISBANE
(07) 229 1941

CANBERRA
(062) 48 6751

PERTH
(09) 328 3311

MAIL OR PRESENT THIS COUPON TO YOUR NEAREST VERBATIM DEALER LISTED ON THE NEXT PAGE. WITH THE PURCHASE OF ONE BOX OF VERBATIM DISKETTES YOU WILL RECEIVE FREE ONE 8" OR 5 1/4" DATALIFE CLEANING KIT.

OFFER CLOSES 30th SEPTEMBER 1982. BY ORIGINAL COUPON ONLY.

Please supply me with my free Verbatim datalife cleaning kit.

NAME

COMPANY NAME

ADDRESS

..... PHONE No.

TYPE OF SYSTEM

SIGNATURE

SIZE 8" ☐ 5 1/4" ☐

DEALER'S NAME

ADDRESS

TYPE OF DISK PURCHASED
(DEALER TO FILL IN)

Retailers that stock Verbatim Disks where you can obtain the 100% solution to your dirt problems

NSW

COMPUTER CELLAR

MAYFIELD, 136 Maitland St.

COMPUTER CONNECTION

MIRANDA, 629 The Kingsway.

COMPUTER GALERIE

NORTH SYDNEY, 66 Walker St.

COMPUTERLAND

BURWOOD, 31 Burwood Rd.

CHATSWOOD, Chatswood Plaza.

BONDI JUNCTION, 119 Oxford St.

PARRAMATTA, 2/382 Church St.

RYDE, Top Ryde Shopping Centre.

SYDNEY, 31 Market St.

COMPUTER FOCUS

LIVERPOOL, 224 George St.

COMPUTERS GALORE

NEUTRAL BAY, 99 Military Rd.

THE COMPUTER SHOP

STANMORE, 210 Parramatta Rd.

DICK SMITH ELECTRONICS

AUBURN, 145 Parramatta Rd.

BANKSTOWN SQ., T55 Terrace Level.

BLAKEHURST, 613 Princes Highway.

BONDI JUNCTION, 552 Oxford St.

BROADWAY, 818 George St.

BROOKVALE, 531 Pittwater Rd.

CHULLORA, 147 Hume Highway.

GORE HILL, 162 Pacific Hwy.

NORTH RYDE, 396 Lane Cove Rd.

PARRAMATTA, 30 Grose St.

SYDNEY, 125 York St.

TIGHESS HILL, 173 Maitland Rd.

WOLLONGONG, 263 Keira St.

TAMWORTH, Arcade & Kable Ave.

DIRECT COMPUTER SALES

HURSTVILLE, 198 Forest St.

BANKSTOWN, Cnr. Appian & North Terrace

FRANK KINNINMONT BUSINESS SYS.

COFFS HARBOUR, 47 Little St.

NEW GENERATION COMPUTER STORE

LANE COVE, 93 Lonqueville Rd.

PARRYS OFFICE SUPPLIES

LISMORE, 25 Molesworth St.

VIC

ASTRO EDUCATIONAL SUPPLIES

MITCHEM, 483 Whitehorse Rd.

COMPAK COMPUTER SYSTEMS

DANDENONG, 81a Foster Rd.

COMPSOFT

RICHMOND, 235 Swan St.

COMPUTAILOR

MELBOURNE, 430 Little Collins St.

COMPUTER NUMERICAL CONTROL

ASHWOOD, 512 Warrigal Rd.

COMPUTERLAND

MELBOURNE, 123 Lonsdale St.

S. MELBOURNE, 37 Albert St.

HAWTHORN EAST, 399 Riversdale Rd.

COMPUTERWARE

MELBOURNE, 305 Latrobe St.

COMPUTER 2000

FRANKSTON, 14 Young St.

DATA PARTS

SHEPPARTON, 1-3 Naomi St.

DE FOREST SOFT WARE

NUNAWADING, 26 Station St.

DICK SMITH ELECTRONICS

MELBOURNE, 399 Lonsdale St.

COBURG, 260 Sydney Rd.

RICHMOND, 656 Bridge St.

SPRINGVALE, Springvale & Dandenong Rds.

GEELONG, 205 Melbourne Rd.

FRANKSTON, Ross Smith Ave & Nepean Hwy.

GOODMAN & CANNINGTON

SOUTH YARRA, 18 Yarra St.

I.G. SUPPLY CO.

S. MELBOURNE, 113 Moray St.

L & S EDUCATION SUPPLIES

CHELTHENHAM, 99 Argus St.

THE LOGIC SHOP

PRAHRAN, 212 High St.

METROPOLITAN BUSINESS SYSTEMS

COBURG, 338 Sydney Rd.

RAM COMPUTERS

WANGARATTA, 34 Roan St.

ROD IRVING ELECTRONICS

NORTHCOTE, 425 High St.

SEASEN SOFTWARE

MYRTLEFORD, P.O. Box 261.

SYSTEM STATIONARY

GEELONG, 39 Gheringup St.

QLD

A.A.B. EQUIPMENT

CAIRNS, 310 Mulgrave Rd.

A.E.Q.B.

BRISBANE, 466 Upper Edward St.

COMPUTER JOE

TOWNSVILLE, 185 Ingham Rd.

COMPUTERLAND

BRISBANE, 1 Adelaide St.

SOUTHPORT, 126 Scarborough St.

BUDERIM, 6 Paralla St.

DATA COM

BUNDA BERG, S.G.I.O. Arcade.

DICK SMITH ELECTRONICS

BURANDA, 166 Logan Rd.

CHERMSIDE, 842 Gympie Rd.

THE ELECTRONIC CIRCUIT

FORTITUDE VALLEY, 20 Duncan St.

PETER MADDEN & CO.

NEWSTEAD, 2 Byres St.

REX BROCK & CO.

FORTITUDE VALLEY, 621 Wickham St.

S.I. MICROCOMPUTER SYSTEMS

COORPAROO, 226 Old Cleveland Rd.

SHANNON ROBERTSON SYSTEMS

BUDERIM, Middy's Complex, Main St.

TALBOT PRESS

MAYNE, 121 Abbotsford Rd.

TOOWOOMBA COMPUTER CENTRE

TOOWOOMBA, 180b Hume St.

S.A.

COMPUTERLAND

ADELAIDE, 122 Gouger St.

DICK SMITH ELECTRONICS

ADELAIDE, 60 Wright St.

ENFIELD, 435 Main North Rd.

DARLINGTON, Main South & Flagstaff Rds.

W.A.

COMPUTERLAND

PERTH, 5 Mill St.

DICK SMITH ELECTRONICS

ADELAIDE, 60 Wright St.

ENFIELD, 435 Main North Rd.

DARLINGTON, Main South & Flagstaff Rds.

W.A.

COMPUTERLAND

PERTH, 5 Mill St.

DICK SMITH ELECTRONICS

CANNINGTON, Wharf St. & Albany Hwy.

PERTH, 414 William St.

MAGMEDIA

PERTH, 252 Stirling St.

A.C.T.

COMPUTERLAND

PHILLIP, 22-24 Colbee Ct.

DICK SMITH ELECTRONICS

FYSWICK, 96 Gladstone St.

MAGMEDIA

BRADDON, 25 Lonsdale St.

STEVE'S COMMUNICATION CENTRE

FYSWICK, 57 Wollongong St.

TAS

DICK SMITH ELECTRONICS

HOBART, 25 Barrack St.

THE LOGIC SHOP

HOBART, 120 Murray St.

MANAGEMENT TECHNOLOGY


BATTERY POINT, 8 Montpellier Retreat.

SLOW SCAN T.V. FOR RADIO AMATEURS


Construct a fast to slow and slow to fast scan converter in your home as an off campus student.

Full documentation, components and technical assistance available, including assistance in fault finding after instruction.

For further details on off campus studies in Slow Scan T.V. or attending the formal classes held on Wednesday evenings, please contact Mr. John Wilson, Head of Television and Audio Visual Resources on **419 6666**.

**COLLINGWOOD
COLLEGE** 
of Technical
and Further Education

**20 Otter Street,
Collingwood. 3066.**

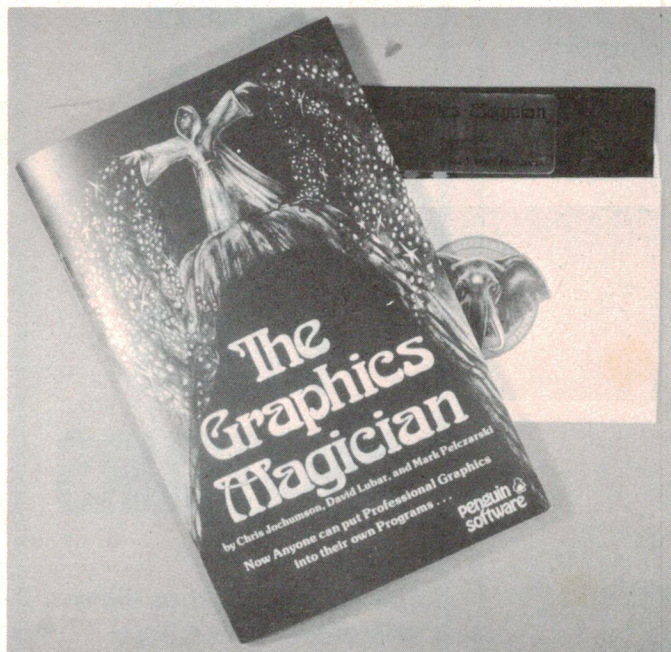

The Graphics Magician

The Graphics Magician is available for Apple II 48K with Applesoft and a disk drive, by Penguin Software; review by Phil Cohen.

The graphics capabilities of the Apple are well known, and it is quite possible to make use of the sophisticated plotting routines directly from BASIC with no additional software.

This is all very well for routine applications, such as the plotting of graphs, histograms, etc, but when it comes to the clever stuff like games animation, it takes quite a bit of effort to make the machine perform.

For example, to make objects on the Apple's screen 'move' you have to get into the machine code 'shape tables' and other mysteries. None of this makes animation very easy.

However, Penguin Software (of Illinois, USA), has produced a series of programs that take all the effort out of animation, and provide a good deal of other nice features, too.

What you get for your money is a plastic bag containing a small 32-page manual and a single 5¼" floppy disk. The floppy contains all the software you need, and (unlike many such packages these days) is not 'copy-protected'.

It has become standard practice for software publishers to 'copy-protect' their disks, making them very difficult to copy — the idea being to cut down on copyright infringement. However, this means that even a bona fide user can't make 'back-up' copies in case of accidents!

This has led to the ludicrous situation of companies producing 'lock-picking' software to get round the 'copy-protection' software of other companies' disks, and selling this 'lock-picking' software to potential buyers of package software — not to enable them to infringe copyright, but just to allow them to make back-up copies for their own security and peace of mind!

However, Penguin Software have (very wisely) chosen not to copy-protect this package — although they have included a strongly-worded warning in the manual against buyers selling unlicensed copies.

Files

The disk contains a large number of files, most of them in 'binary' format. However, the boot-up file (named HELLO, by Apple convention) that is executed when you start the system up with the disk in place, will automatically put onto the screen a full 'menu' of all of the software available — including some very impressive demonstrations.

The package is completely 'menu-driven', so that whenever you are finished with a particular piece of software, exiting will get you back to the menu so that you can choose the next part of the package that you want to use.

The package is in three sections.

The first allows you to create 'shapes' (although not using the Apple shape table concept), 'paths' (which are what the shape will move through), and 'objects' (which are a combination of a shape and a path).


This part of the package will allow you to have the figure of a man running from one side of the screen to the other, with the leg movement included! Each 'shape' is defined in seven 'steps' — each step is actually the same shape slightly altered. As the shape moves across the screen, each of the parts in turn is used automatically, giving the impression that the figure is, for example, 'running'.

The 'path' along which the shape moves is variable, too — you can choose any path you like, and can even have a number of shapes 'chasing' each other along the same path, or one shape moving along different paths under program control.

All sections of the Graphics Magician package give complete control (within the limitations of the machine) over colour.

The second section of the package is for drawing pictures. These might be used as a background for the shapes in the course of the game, for example. The inset on this page shows the standard that can be achieved.

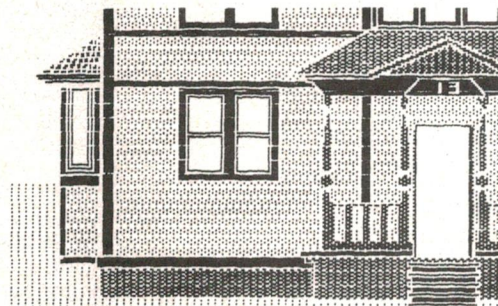A 'brush' can be moved across the screen using the 'paddle' controls (standard with the Apple II). This 'brush' can draw lines, 'paint' in different textures and colours, and even 'fill' areas of the picture automatically — the brush is positioned in an area which is bounded by lines, and a single command causes the area to be filled with a particular colour and texture.



The last section is a sophisticated means of generating Apple 'shape tables', which allow various shapes to be put onto the screen under program control with varying scales, positions and rotations.

... and how is all this used? Well, the whole package is designed so that the results (whether animations, pictures or shape tables) can be

used with stand-alone BASIC or machine code programs developed by the user.

The picture-drawing section has one last trick in this respect — instead of storing the picture as an image of what's on the screen, it is stored in terms of the steps you went through to draw it. What this means is that the picture will take up very much less room, so that literally hundreds of pictures can be stored on one disk.

Manual

One very important part of any such package is the manual that comes with it. The manual for the Graphic Magician is adequate — and when I say 'adequate', please bear in mind that this puts it streets ahead of most of the packages on the market!

Documentation is often thought of as an 'add-on', but in situations like these it becomes almost as important as the software itself. The documentation with this package was enough to allow me to operate it with little effort.

On the whole, I think the package would be invaluable to the adventure freak ('adventure' is a class of computer game that tries to model fantasy situations) — the ability to store all those pictures on one disk is ideal for that (and the manual points this out, too).

Another possible use is for those involved in educational computing. The use of pictures (sophisticated enough to be used as textbook drawings) could allow whole textbooks to be put onto a disk for 'programmed' learning in the true sense.

And then of course there is the indisputable prime use for all domestic computers — for fun. I'm

sure that, even if you had never written a computer game, having this package close at hand would convince you to do so!

The Graphics Magician is distributed by Imagineering, 22 Sir John Young Crescent, Woolloomooloo NSW 2011, and is available through many Apple dealers and computer speciality stores.



16-bit professional microcomputer

A new low cost computer for business has been introduced by Barson Computers Pty Ltd (formerly known as CMC) of Melbourne.

Known as Sirius 1, this personal computer has a 16-bit Intel 8088 microprocessor. Standard memory is 128 Kbytes RAM expandable up to 896 Kbytes.

Two 5¼" (133.35 mm for us) floppy disks give a storage capacity of 2 x 600 Kbytes, formatted, in the single sided version. An optional double-sided, double-density extension brings the storage capacity up to 2 x 1.2 Mbytes.

This multi-language computer accepts BASIC, Fortran, Pascal, PL/1 and PL/M.

Sirius 1 is equipped with one parallel and two serial ports. The parallel port is programmable to be

compatible with most currently available printers. The two serial ports are also programmable to be used in synchronous or asynchronous modes.

Sirius 1 operates under CP/M86 from Digital Research and MS/DOS from Microsoft. Most programs written under CP/M can easily be recompiled to run on Sirius 1.

Sirius 1 can display charts, graphs and half-tone pictures. A voice synthesiser gives Sirius the power of speech.

Barson Computers are at P.O. Box 1675, Nth Sydney NSW 2060. (02)90-7833.

Peripheral input/output device

The Fairchild F3871 Peripheral Input/Output (PIO) device provides two 8-bit I/O ports, external interrupt, and a programmable timer. An 8-bit wide bi-directional data bus transfers I/O data bytes between the F3870 Central Processing Unit and the PIO.

The PIO is used in systems that require the I/O capability and interrupt functions of the F3851 PSU, but do not need the ROM storage of the PSU. The PIO is pin-compatible with the PSU.


The F3871 has the same improved timer and ready strobe output as the F3870 CPU; therefore, for

software compatibility with the F3870, the F3871 PIO should be used in the F8 multichip configurations.


For further information contact Fairchild Australia Pty Ltd, 366 Whitehorse Rd, Nunawading Vic. 3131, (03)877-5444.

Ian R Sinclair Practical Microprocessor Systems

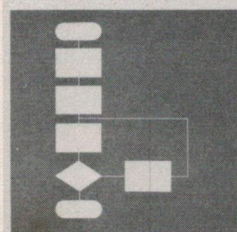**Microprocessors:
Your questions
answered** Alec Wood



Newnes Microcomputer Books

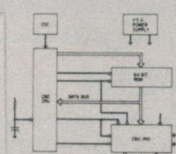

Newnes Microcomputer Books

**ZX81
BASIC BOOK**
Robin Norman



Newnes Microcomputer Books

Microprocessors are cropping up everywhere, and the dream of a computer for everyone is rapidly becoming reality. This collection of books from Butterworths will help you learn more about these fascinating and useful devices.

They cover everything from fundamental principles of microprocessors to assembly language programming. All are recently written by highly respected authors and form the heart of a complete library on microcomputers.

YOUR COMPUTER QUESTIONS ANSWERED

Microprocessors: Your Questions Answered

A brand new book that answers in simple language the many questions that baffle the newcomer to microprocessors. After covering the basics, it describes the hardware and software needed to build a complete microprocessor system. A detailed glossary is included. No. 73084 \$14.95

ZX81 BASIC Book

Get the most from your ZX81 computer. Covers the basic 1K version, the 16K RAM unit and the ZX Printer. Fills in the gaps in the manuals with practical, straightforward information and hints. No. 103177 \$14.95

Practical Microprocessor Systems

Covers complete microprocessor systems - the MPU itself, memory, peripherals and programming. Deals with all aspects through a rudimentary build-it-yourself assessment unit to grasp the practicalities. No. 100946 \$15.00

Interactive Computing in BASIC

An introduction to interactive computing and a practical guide to programming in BASIC. No prior knowledge is assumed. No. 22727 \$16.50

Introduction to Microcomputer Programming

Introduces the concept of the program and the various 'levels' of programming. Then concentrates on programming in BASIC and four assembly languages (8080, 6800, 6502 & Z-80), with plenty of exercises. No. 55601 \$12.50

Personal Computing Questions and Answers

What is a microprocessor? What is hex? How can a personal computer be used in business? Answers the many questions. No. 70434 \$5.95

Available from:

Butterworths

Sydney: The Technical Bookshop.
Melbourne: McGill's Bookshop;
Technical Book & Magazine.

Or directly: 271-273 Lane Cove Road, North Ryde 2113. Phone (02) 887 3444

Please supply the following books:

- | | | |
|--|---|---|
| <input type="checkbox"/> No. 73084 \$14.95 | <input type="checkbox"/> No. 103177 \$14.95 | <input type="checkbox"/> No. 100946 \$15.00 |
| <input type="checkbox"/> No. 22727 \$16.50 | <input type="checkbox"/> No. 55601 \$12.50 | <input type="checkbox"/> No. 70434 \$5.95 |
| <input type="checkbox"/> Cheque/Money order enclosed <input type="checkbox"/> Please debit my credit card | | |
| account as follows: <input type="checkbox"/> Bankcard <input type="checkbox"/> Diners Club <input type="checkbox"/> American Express | | |

Card No: | | | | | | | | | | | | | | | | | | | | | |

Signature Expiry date: / /

Name

Address

Postcode:

Recommended Domestic Retail Prices include postage and are subject to change without notice. This order is subject to acceptance by the Head Office of Butterworths.

Printout

APPLE II 'LOGO' LANGUAGE

Logo started out as a language for large computers, but under the direction of Dr. Seymour Papert, its creator, it was developed into a language for Apple microcomputers, requiring an Apple II or Apple II plus with 64K RAM.

Apple Logo is said to make explicit many of the fundamental ideas of programming, as well as encouraging good programming habits and providing powerful language processing, making word-oriented programs as easy to write as numeric ones. Its commands are not complicated and it doesn't require a knowledge of higher mathematics, making it suitable for computer students of all ages, including young schoolchildren.

Turtle graphics is one of Apple Logo's key features. Simple, literal commands control a 'turtle' cursor that draws on a high-resolution video screen. Apple Logo is interactive, executing commands instantly, and users acquire programming skills by instructing the turtle to generate shapes and designs. For example, the commands 'forward 30 right 90' direct the turtle to draw a line 30 steps long and then make a 90° right turn. By typing the instruction four times, the student programs the computer to draw a box; the series of instructions can then be saved as a single procedure, and the drawing may be quickly incorporated into more complex designs. In this way complex programming is divided, as in many other structured high-level languages, into small, manageable pieces.

Apple Logo is extensible, enabling users to extend the built-in operations of the language by defining and saving new procedures and commands. It also features recursion — which allows a procedure to call itself — as well as list processing and error and file handling. Such features make the Apple II with Logo suitable even for college and university use.

Apple Logo is available now from Electronic Concepts, 55-57 Wentworth Ave, Sydney NSW 2000, Apple Computer Inc's sole authorised Australian distributor. Contact them on (02)212-2833 for further information.

New functions for EXORset

A major redesign has converted the Motorola EXORset from a low-cost software development system to a self-contained combined hardware-software development systems, without any increase in price.

This redesign, the EXORset DS35, now offers an alternative solution to more expensive, complex modular hardware development systems or multi-user timesharing systems, Motorola claim.

A feature of the EXORset DS35 is its ability to operate emulators which connect directly into the user's target system. An opening in the top cover above the card cage allows the appropriate emulation board(s) to be inserted.

Emulators will be available for the MC6805 families of NMOS and CMOS micro-control units. In addition, other compatible EXORbus boards, such as PROM programmers or Micromodules, may be easily inserted into the card cage.

The EXORset DS35 has fully populated 56K RAM, plus an additional card slot.

The EXORset DS35 memory map

is defined by a PROM, allowing the user to reconfigure the architecture of the system. Four EXORciser/Micromodule compatible connectors are available for the disk controller and three additional modules such as input/output or any of the other compatible Motorola modules.

The memory map, EXORbug monitor, and XDOS operating system are compatible with the EXORciser, allowing program portability between different development systems. A configurable RS-422/433 or RS-232C serial interface is provided for interconnection to an external system.

EXORset DS35 is based on the new generation MC6809 8-bit external/16-bit internal micro-processor.

In addition to BASIC-M Pascal is also available for the EXORset DS35 system.

Intel unveils 16-bit 'CPU board on a chip'

Intel Corporation has released a single chip containing a 16-bit CPU and all of the other functions commonly found in a single-board CPU subsystem.

Designated the 80186 it can take the place of 15 to 20 individual ICs and offer a lower-cost, higher-performance solution for cost-sensitive applications such as personal computers, word processors, small business computers and intelligent terminals, Intel say.

Its applications range includes distributed processing nodes and input/output (I/O) subsystems.

Because of its high degree of functional integration, it is less

expensive to design and produce a system using the iAPX 186 than with other 16-bit microprocessors, say Intel.

It takes up less board space, is priced lower than the sum of the parts it replaces, is compatible with all existing 8086 and 8088 software and eliminates the ordering, testing, inserting and inventory costs associated with the replaced chips. It has twice the performance of a standard 5 MHz 8086.

"The 80186 will radically change the economics of building high-volume, 16-bit microcomputer systems," said Jeff Miller, marketing manager of Intel's Microprocessor Operation. "For the first time, all microprocessor designers will be able to afford 16-bit performance."

According to Miller, while the 8086 was introduced at \$115 each for 100-piece quantities in 1978, the 80186, which integrates an enhanced 8086, plus 15 to 20 support chips on one piece of silicon, will be a \$30 product in volume its first year in production.

Designers building new systems can take advantage of advanced CPU features and 10 powerful new instructions. They will also be able to use all of the third-party software now available for the 8086 and 8088. Engineers who want to upgrade existing 8086 or 8088 designs can preserve their software investment and selectively streamline portions of it using the new instructions. Thus, both first-time users and those experienced with the iAPX 86 family will have a lower system cost solution and a much shorter design cycle, say Intel.

Need semis in a hurry? Then just drive into the Applied Technology Semiconductor Centre. No minimum order, no minimum quantity - no wasted time. Just phone before you come in. we'll have your order ready.

(02)439 2963

DRIVE-IN SEMICONDUCTOR CENTRE
35 Dickson Avenue Artarmon NSW
Hours 9-5 Monday to Saturday


What about our range?
How about 193 different 74LS, or 140 4000 series CMOS - over 1500 different semiconductors in stock. Our full range is listed on our exclusive Semiconductor Wall Chart - yours for the asking.

As well as our enormous range of semis, we've got a comprehensive range of resistors, capacitors IC sockets and computer connectors.

AT

APPLIED TECHNOLOGY

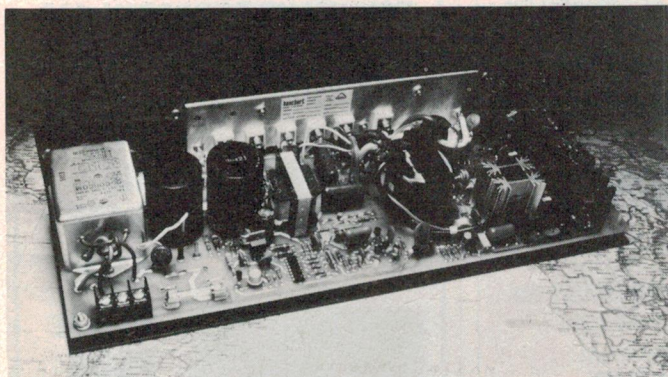Mail orders to:
PO Box 355, Hornsby NSW 2077
Telex APTEC AA72767



Switching supply with VDE certification

Amtex Electronics has released the Boschert XL200-4501 switching power supply which has received the German VDE certification. According to the manufacturer this is the first American-made open frame switcher which has received such certification.

The certification is with respect to safety (VDE 0730) as well as electrical noise (VDE 0871/N12). These VDE specifications are similar to Telecom Australia's requirements, e.g. 3500 V isolation and 6 mm separation for mains tracks on the pcb.

Since the unit is user adjustable for 95 — 132 or 190 — 264 Vac, it is suitable for operation anywhere in the world.

The XL200-4501 is intended for general purpose use in medium power data and office processing systems, e.g. word processors, intelligent terminals, small business computers, microprocessor systems

with CRT displays and peripheral motors for printers and disks. It provides up to 200 W of total power on four outputs: a main rail of 5 V at 20 A, ± 12 V at 4 A each, and -5 V at 3 A.

Price of these units in one-off quantities is \$530 plus sales tax. Delivery is from stock. Also available from stock is the OL152-4001 switching supply designed for the Diablo 1300 series printers. Outputs are $+5$ V at 15 A and ± 12 V at 4 A each.

Enquiries to Amtex, P.O. Box 285, Chatswood NSW 2067. (02) 411-1323.

Intel move

Intel Australia Pty Ltd, a wholly-owned subsidiary of Intel Corporation of the USA, is expanding its operations and has moved to larger premises at the Spectrum Building, 200 Pacific Highway, Crows Nest.

The telephone and telex numbers will remain unchanged, namely (02)436-2744 and AA20097.

The move marks the beginning of Intel's expansion in Australia.

ARCNET local network interface chip to be sold on open market

Datapoint Corporation has announced that the integrated circuits used to interface workstations to a Datapoint ARCNET local network will be made available to the public through Standard Microsystems Corporation of Hauppauge, New York.

Datapoint and Standard Microsystems have signed an agreement under which Standard Microsystems was granted a non-exclusive license to market Datapoint's RIM (Resource Interface Module) chip and the associated ARCNET transceiver chip. Together, the two chips provide the electronics necessary for ARCNET interfacing.

It was announced in September 1981, that the interface chips would be used by Tandy Corporation to interface Radio Shack TRS-80 Model II computers, creating a Radio Shack implementation of the ARCNET local network.

"When we initially made the chip set available to Tandy, we decided to

deal with any other interested vendors on a one-by-one basis," noted Victor D. Poor, Datapoint's Executive Vice President for Research and Development.

"Since the announcement we have received many enquiries from vendors who want information about the chips."

"This agreement with Standard Microsystems will make the chip set publicly available and at the same time relieve Datapoint of having to deal in the semiconductor business — something we don't want to do," Poor said.

Enquiries to Datapoint Corporation Australia, 157 Walker St, North Sydney NSW 2060. (02)922-3100.

Intro to the micro

A new book from the Hayden stable, 'An Introduction to Microprocessors: Experiments in Digital Technology' by Noel T. Smith, landed on the Editor's desk recently and it would seem a good choice for the 'practical' student of digital logic and 6800 microprocessor systems.


The book starts with a swift introduction/revision of solid state devices and integrated circuits, plus some advice on 'breadboarding', as the book encourages the reader to actually try out the circuits and techniques illustrated.

Chapters two to six then cover logic gates, synchronising circuits, clocked logic, data manipulation and display and data processing — the latter covering the basics of microprocessing, built around the Motorola MC14500B. Experiments are given all along the way, reinforcing the learning process by practice.

CMOS and TTL logic are covered.

Chapter seven covers multibit microprocessors, specifically the 6802 and system components — PIA, ACIA and memory. The rear of the book contains a useful array of data sheets and device pinouts. In general, the treatment is thorough, well organised and clearly written — a book well worth a close look if you're just getting into digital logic and microprocessing. 178 pages, 278 x 217 mm, soft cover. Available from Butterworths, P.O. Box 345, North Ryde NSW 2113. (02)887-3444.

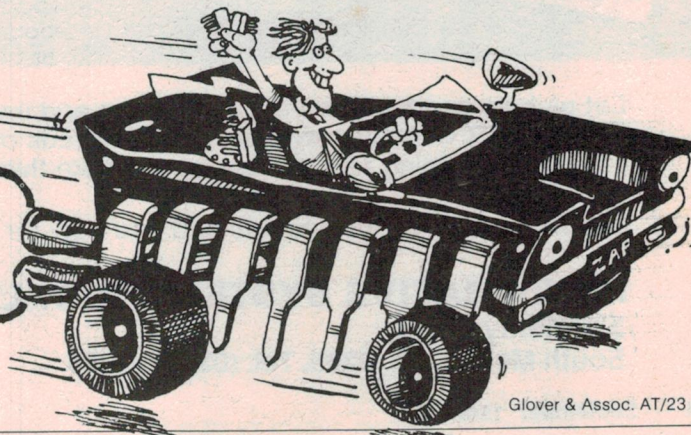**Drive in
Semiconductor
Centre,
1500 lines and
instant pickup**



Glover & Assoc. AT/23

**Software
Source Pty Ltd.**

89 OXFORD ST.,
BONDI JUNCTION
PH: (02) 389 6388 P.O. BOX 364,
EDGECLIFF 2027

SOFTWARE AND PERIPHERALS FOR THE SORCERER

WRITE FOR
FREE
CATALOGUE

AT LAST!!!

A stand alone 2716/2732/
2532 E-PROM
PROGRAMMER, controlled by
Z-80 CPU at 2 mHz, that
requires only single 5V!



Read, verify, compare or even
key up your E-PROM.
Burn two 2716 E-PROMS into
one 2732 or vice versa.

Available only from
**PHILITRONIC
COMPONENTS &
SERVICES**

...\$320 S/T included.

Also available—switching
power supply that is very
compact yet gives out 5 amp at
+5 V; 1 amp at +12 V; -12 V;
as well as -5 V.

Dealer enquiries welcome.


Contact Philip Lui on
(03) 842-5303.




THE COMPUTERIST



TOP VALUE PERFORMANCE FOR INSTRUMENTATION AND CONTROL

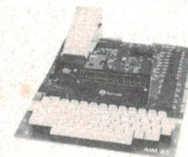

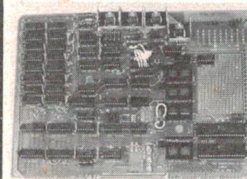**AIM 65
1K
\$478
PLUS
DRAM
PLUS
32K
\$369**



A65-010 ASSEMBLER \$39.38
A65-020 MICROSOFT BASIC \$65.00
A65-030 PL65 \$125.00
A65-040 MATHS PACK (Links to FORTH) \$39.38
A65-050 FORTH \$73.12
A65-060 PASCAL (5x4K ROM) \$112.50



P.O. BOX 6502,
GOODNA, 4300.
AUSTRALIA.
PH: (07) 288 2757
Prices for prepaid
orders

You get **EXPANDABILITY** with the

Cromemco Business System



START UP PACKAGE:

The Cromemco System One
Computer.
Powerful terminal.
High speed Printer.
Debtors and invoicing system.
Installation with 12 months free
maintenance.
System training.
Price: **\$9995** (inc. tax)

Let us help computerise your accounting and invoicing with our **Cromemco**
BIZMASTER Computer system. With hundreds of installations, easy to use programs, and
our unique training techniques you can take this big step safely with us.

Call us now for further details and see how far **Cromemco** will go.

INFORMATIVE SYSTEMS PTY. LTD.

337 Moray Street,
South Melbourne, 3205. Tel. (03)690 2899

82 Pacific Highway,
St. Leonards, 2065.

Independent Apple software

Eight new, independently-developed software programs are being offered by Apple computer.

Independently developed software programs are selected for publication by Apple's software evaluation group. The new selections comply with Apple's requirements for user-friendly, quality programs.

Comm-pac is a data communications program that enables an Apple II to communicate with other computers, time-sharing systems, networks, newswires, and other subscription services.

Parallax is a collection of graphics utilities which lets the user develop and manipulate high-resolution shapes for Applesoft BASIC programs.

Designer's Toolkit is a program for the Apple II that computerises the drafting table. Emulating pen, pencil, and brush on paper, Designer's Toolkit and the Apple Graphics Tablet let the user generate graphics for mapping, architecture, and drafting.

Magic Spells is a learning game that transforms the memorisation of spelling lists into an adventure

complete with castles, treasures, demons, and a sage wizard.


Math Strategy and Spelling Strategy are two innovative programs that teach youngsters how to use the mind's eye to sharpen math and spelling skills.

Moptown is a collection of entertaining and interesting logic games for children. Self-paced learning of reasoning skills is reinforced through the use of sound and colorful 'Moppet' characters.

Speed reader is a complete reading development course designed to double and even triple reading speed while increasing comprehension.

These and other independently developed software programs published by Apple are listed in the 1982 Special Delivery Software (SDS) catalogue.

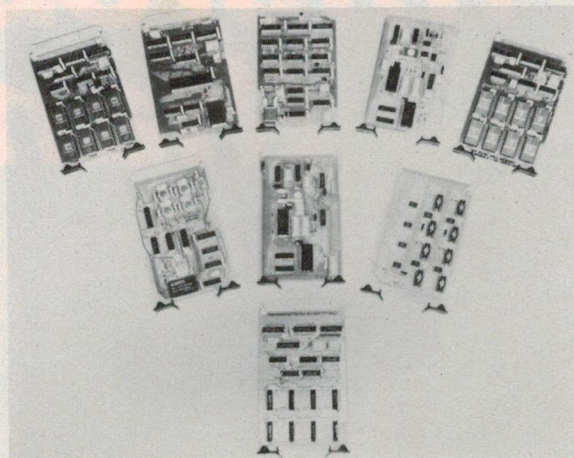To submit programs for evaluation by Apple, write to Software Evaluation, 2025 Mariani Ave, Cupertino CA 95014.



Thorn-EMI Eurocards

Thorn-EMI has appointed Rank Electronics as its Australian distributor of the Thorn-EMI Eurocard range of microprocessor modules.

Looking to expand their available range of application hardware, Rank Electronics seized the opportunity to distribute the South Australian designed and manufactured product. The Thorn-EMI Eurocard offers users low cost, high reliability and compatibility with a number of


independent vendor supplied rack-ing and packaging systems.

For further information contact your local Rank Electronics sales office, or Rank Electronics, 19 Trent Street, Burwood Vic. 3125. (03) 29-3724.

RADIO DESPATCH SERVICE

869 George Street,
Sydney. 2000.
(Near Harris Street)
Telephone:
(02) 211 0191 (02) 211 0816
Open: Mon-Fri 8.15 am to
5.30 pm. Thursday night late
shopping till 8.30 pm. Sat
8 am to 11.45 am.


TEXAS INSTRUMENTS CALCULATORS

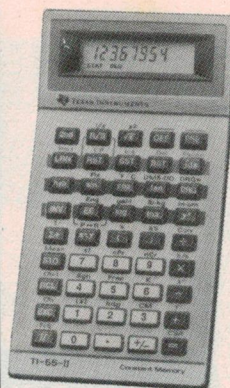

TI-55-II
suggested retail
\$59.95

OUR PRICE
\$55.45
Including tax

\$49.29
Tax Exempt

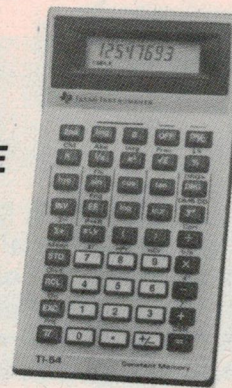

TI-54
suggested retail
\$45.00

OUR PRICE
\$41.65
Including Tax

\$37.00
Tax Exempt

	Tax Ex.	Incl. S/Tax
TI-1750 III	15.62	17.57
TI-1760 DATACARD	20.70	23.95
TI-1790 DATACHRON	35.23	39.95
TI-5025	80.36	90.44
TI-5100	35.00	39.38
BA II Executive	41.12	46.26
MBA	64.55	72.62
PROGRAMMER II	61.67	69.38
TI-30 II	17.26	19.42

TI-35 II

TI-40

TI-54

TI-55 II


TI-58c

TI-59

PC-100C

	Tax Ex.	Incl. S/Tax
TI-35 II	22.20	24.98
TI-40	32.86	36.97
TI-54	37.00	41.63
TI-55 II	49.29	55.45
TI-58c	107.00	120.26
TI-59	224.00	254.73
PC-100C	205.00	231.60

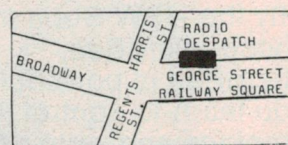**Calculator Accessories
and Spare Parts Plus
Educational Aids.**




COME AND SEE US NOW!

MAIL ORDERS TO:
MAIL ORDER DEPT E.T.


Radio Despatch Services, 869 George St., Sydney 2000 Ph: (02) 211 0191 211 0816

microbee, more than you ever


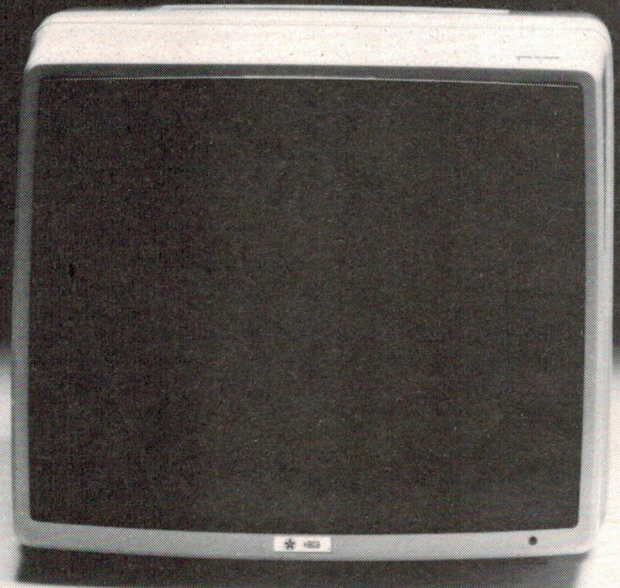


With one giant step, Australia's MicroBee brings the power of the personal computer within your reach. MicroBee is now ready built with a superb new case. Yet incredibly it costs no more. The no compromise computer you can afford. MicroBee is a complete learning package. Explore and master programming with the BASIC manuals, and inbuilt 16K ROM BASIC. Find out why the NSW Department of Education chose MicroBee.

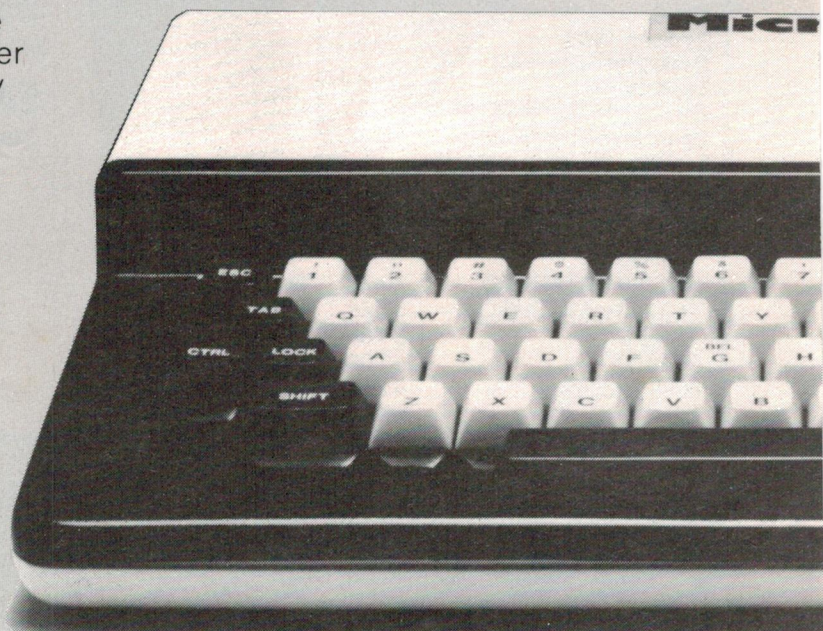MicroBee is powerful and "friendly". You learn to control the built in sound, graphics and write and correct programs more easily with MicroBee. Printers, modems and cassette storage plug straight in. The optional parallel and Z80



expansion power thought possible

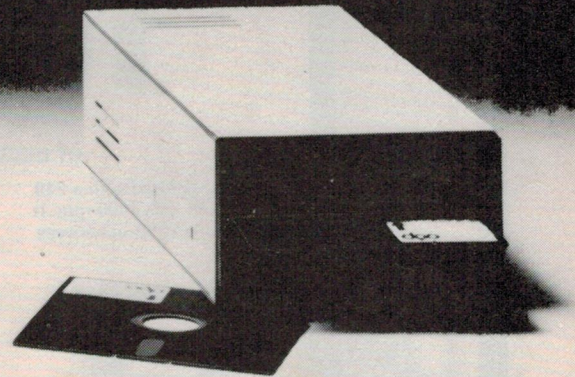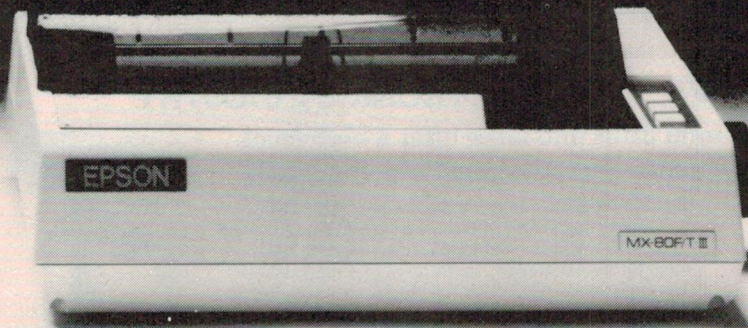

port let you connect joysticks or use the world standard S100 bus. MicroBee grows with you. Inexpensively. Add disc drives, colour graphics and EPROM programmers. Write programs in Z80 code. Or upgrade to disc drives and CP/M with the new 64K memory card. MicroBee, your first class ticket into computing.

To order MicroBee
phone (02)487 2711
or mail order:
PO Box 311 Hornsby
NSW 2077

\$399⁰⁰
16K
Fully built & tested

microbee



Goods in stock and prices correct at time of going to press.

APPLIED TECHNOLOGY


1A Pattison Ave Waitara NSW 2077

Hours: 9-5 Monday to Saturday

Phone (02)487 2711 Telex APPTEC AA72767

Glover & Assoc. AT/18

32K BYTES FOR THE ZX81

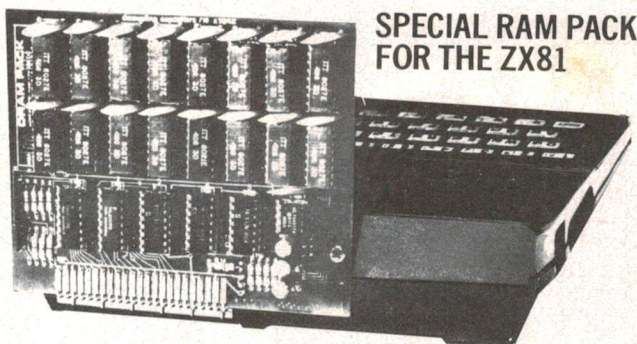

**SPECIAL RAM PACK
FOR THE ZX81**

**PRICE FOR 32K RAM PACK (RP32)
ONLY: \$165.00 incl. p&p (Australia)**

VEN 0057

This board uses Dynamic RAM chips for lower cost and lower power consumption.


Simply plugs into the ZX81 expansion port offering 32K bytes for Basic programs and data handling. No extra PSU required. AMAZING!!!

Extra memory to help you build up your ZX81 into a powerful microprocessor system at an affordable price. Compare the price with other RAM PACKS available on the market!!!

SEND ORDER TO:

VENDALE PTY. LTD., Dept. T7, P.O. Box 456, Glen Waverley,
VICTORIA 3150.
36 Plymouth St.,
Glen Waverley
(03) 232 0444.

VENDALE

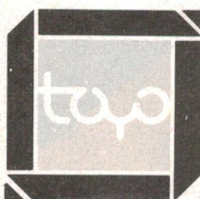


TOYO

**PRECISION EQUIPMENT FOR THE
ELECTRONICS INDUSTRY**

The TOYO mini drills and lathe offer a high level of accuracy comparable with larger machine tools.

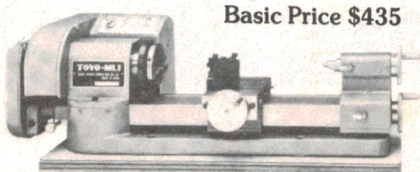The MINI LATHE (as illus) is fitted with a 240 volt motor, speed range from 250-3000 rpm. It has a swing of 100mm and is 250mm between centres. Weighs 15kg.



Basic Price \$435

Accessories available
*Prices & Tax

The MINI DRILL comes in two models, MINI DRILL I, a standard speed drill offering 6 speeds from 850-3100 rpm, with a 6.5mm drilling capacity. Weight 5.4kg, ideal for model makers, instrument and repairers, etc. The high speed MINI DRILL IH has 2 speeds 8,000 + 12,000 rpm with a drilling capacity from No. 80 to 6.5mm and weighs 5.4kg, is suited for drilling printed circuit boards etc.

A machine vice is included with both models.

Mini Drill I \$165

Mini Drill IH \$165




For brochures, prices and information contact

MELBOURNE MACHINERY CO. (SALES) PTY LTD
51 Queensbridge St, South Melbourne, Vic (03) 61 2911.

PP28 Portable EPROM programmer.

The Stag Electronic Designs Ltd PP28 Portable EPROM/EEPROM Programmer provides versatile programming facilities for 24 and 28 pin devices within a case which easily fits into any briefcase. The PP28 has extremely powerful error-free editing commands including relocate, compliment clear, auto-fill, split and shuffle. LED's indicate failure to program, verify error and also provide simultaneous display of address, RAM and PROM data. For safety the PP28 has overcurrent and short circuit protection on all the EPROM pins and tests for part reversal. Checksum and cyclic redundancy checks are also performed to ensure complete programming integrity. The in house capability of your MDS can also be improved by down loading to the PP28 at up to 9600 Baud, using your MDS and other standard formats.

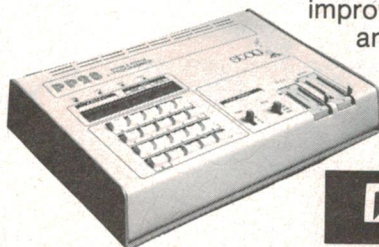

For more information on the PP28 and other Stag Products contact:—

Digitec.

Digitec Australia Pty. Ltd.
3rd Floor, 3 Chester St., Oakleigh, Vic. 3166.
Phone (03) 568 6922

stag



Versatile speech synthesiser

This speech synthesiser, originally designed for the Tasman Turtle robot (see ETI, April/May/June '82), is an extremely versatile unit with functions and features offered in no other speech synthesiser system. Applications range from a talking doorbell, to a communications aid for the handicapped, from a self-learning tool to an industrial equipment voice indicator. Or whatever you dream up.

Allan Branch

Flexible Systems, Hobart, Tasmania


THERE ARE MANY speech synthesisers about now. In the last few years a number of companies have produced specialised integrated circuits or IC sets designed to produce speech, electronically, in various ways. The result is a maze of talking electronics — clocks, cars, ovens, calculators, alarms and learning aids to name a few. Just what led up to this modern electronic wonder?

For some time, psychologists and artificial intelligence researchers have been developing a careful understanding of the human speech communication mechanism. The ultimate aim, as could be expected, is to develop machines that can listen, understand, answer back or ask questions and then carry out an appropriate task.

The problem has always been the enormous amount of data or information stored in even very short utterances. Electronic memory has not yet reached the stage where unlimited 'words' can be stored and recalled at will.

That is not to say that the data cannot be recorded at all. Mankind has been coding verbal speech in various ways and storing the coded information, so that it is available for decoding relatively easily, for thousands of years! Some of these techniques are not usually realised for what they are since they are a part of every day life and a major activity in communication.

The types of encoding and decoding used so that the speech data can be stored varies in these old techniques. The most common is the use of written symbols such as hieroglyphics, alphabet characters, shorthand symbols or pictures. Speech synthesis in this case goes under the common name of 'reading'. The trouble is that man is still the instrument needed to do the coding (writing) and then the decoding (reading).

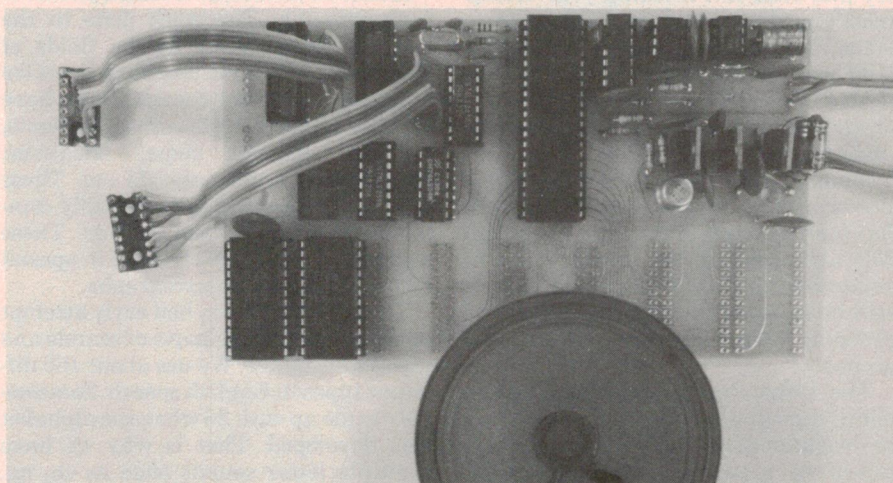

The speech synthesiser uses National Semiconductor's Digitalker chip set on a board just 155 x 90 mm.

Recording or storage

The first cylinder recording and playback machines were the start of the electronic version of speech coding and eventual synthesis. The speech data were stored, and still are, as a code of displacement values from a reference line on a physical medium such as plastic or metal. A machine does the coding (disc-cutting lathe) and a machine (record player) does the synthesis on decoding. The playing back can be done when and in what order the user requires. It is normally done by a human who selects the record, the track and the time of playback (synthesis) although it can be done by machine (a jukebox). Tape recordings are another example.

The ease with which these types of equipment work and their abundance in western society obscure a very important fact. The information content or number of bits of information stored is colossal. A lay person would tend to think of a unit of information as being a sentence or a word or a letter. This is not so.

Sampling

Sampling theory dictates that a sampling rate of at least twice the maximum frequency to be reproduced is necessary to record and playback an analogue signal by taking 'samples' of that signal. Imagine a voice with a highest frequency of 1000 Hz (normal female speech). A sample rate of at least 2000 Hz is required. For an analogue device such as a microphone or record stylus, this means the physical equipment has to have a response of at least 2000 Hz (i.e. be able to vibrate that quickly).

Now each single sample bit (analogue) has a particular value, say between 1 and 256. A binary number having eight bits would be necessary to represent each value. Therefore one second of speech would require the equivalent of approximately two kilobytes of memory or storage information. This is about half a track at the start of an LP record or a couple of 2114 memory IC chips.

A total of 20 minutes of speech, therefore, occupies some 20 x 60 x 2000 bytes ►

Project 647

or 2.4 megabytes of memory, the equivalent of some 36 microcomputers having 64K of RAM!

Alternatively, this occupies one side of a normal LP record, and LP records have frequencies greater than 1000 Hz.

Not yet convinced? Twenty minutes of speech is recorded in about 20 pages of a paperback book, so a 200 page book, which is not a large book, holds ten times as much again — 24 megabytes!

Redundancy

Language, written or spoken, is a remarkable thing. Despite its apparent efficiency in storage capacity, it contains a considerable amount of redundant information. Try this as an example: get a friend to write out a sentence in pencil on a single line. Then have them rub out the bottom half of the sentence. Now you try and read it. Providing your 'friend' hasn't used some strange Gaelic expressions or something similar, you'll find that you can decipher the sentence — with a little difficulty perhaps. This is a crude example because both essential and redundant information is removed but you can see that you *can* synthesise the original sentence *even though 50% has been removed*. If the right redundant bits are removed, the sentence can be reduced even further than that and yet still be restored through synthesis, and probably with greater speed and accuracy.

The same can be done with speech using digital electronics. By removing the redundancies and with appropriate sampling, speech patterns can be 'compressed' and stored for later synthesis into what we recognise as speech.

There are three techniques currently used to achieve this extraction or compression of data and they are based on different ways of looking at the speech waveform.

If one looks at a speech waveform on an instrument such as an oscilloscope then a waveform like the one below is seen:

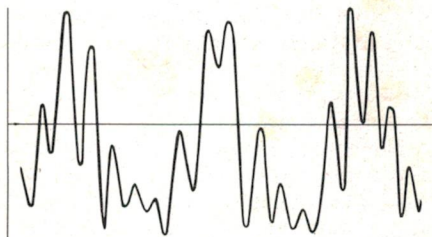


Figure 1. Typical waveform.

If the amplitude of the waveform is recorded for consecutive periods of time then the speech data has been *coded* and if the code is read back so that the original amplitude variation can be regenerated, then the speech is *syn-*

thesised. The technique is called *waveform digitisation*.

A second technique is called *phoneme reconstruction*. The work done in the last 50 years or so in the fields of linguistics and acoustics have revealed 'subunits' of human speech. These have various names like phonemes, formants, glottals, nasals, stops, fricatives, morphemes, trills, laterals etc. These can be put together in reasonably complicated ways to form sounds. These parts or subunits can be seen in special recordings called spectrographs.

The alphabet was a bad early attempt to distinguish these parts of sounds and give them names. We use about 160 different types in English speech. Someone only came up with 26 when the alphabet was developed. That is why we have multiple letter sounds such as ch, ng, ough, ea, oo, sh, etc.

It is possible to get by with only 40 if you don't mind 'mechanical' speech. A piece of speech written with this sort of data should look something like:

" ʒə 'lɪŋgwɪst 'sɔ: ʒə pɛlɪkən# "

Figure 2.

It becomes relatively easy to synthesise speech from these subunits since only a small number of sound subunits have to be stored and each word can be generated by recalling which phonemes to use and what order to use them in. This uses less memory than the waveform digitising mentioned earlier. A data rate of about 400 bits per second will suffice. The problem is what symbols to use when specifying various phonemes. A conventional typewriter or computer keyboard runs out after 26.

A more sophisticated (but not yet more satisfying) method approaches the problem from a completely different viewpoint. In fact, this method was one of the earliest attempted in the young days of acoustics. It models the human vocal tract and is called (by some people)

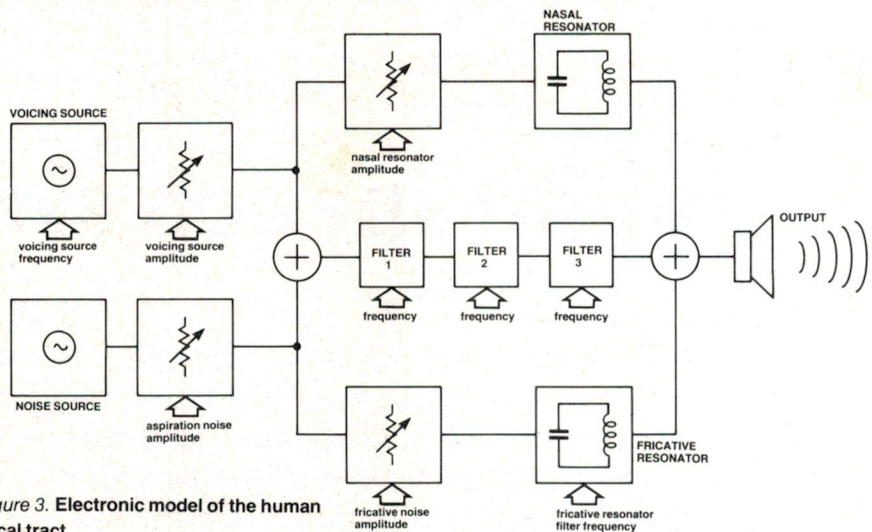


Figure 3. Electronic model of the human vocal tract.

linear predictive coding. A 'noise' generator, either mechanical (tubes and wind pump) or electronic (an oscillator or oscillators), is used and various things are done to the noise to copy the things that we do when we cause speech to occur.

An electronic model of the vocal tract is shown in Figure 3. When we speak we do various things at different times with different parts of the vocal tract. These variables include things like alter the diameter of the pharynx at set places, block the nasal cavity, raise or lower the tongue, oppose lips and teeth, stretch vocal cords, close the glottis, etc.

With synthesis, the variables are identified for each sound to be coded and only information about these actions are stored in memory. When recalled, these variables tell the mechanical or electronic equipment what to do as it generates noise. With luck, the noise sounds like speech. The memory requirements are about five times that of the phoneme reconstruction technique.

The three major techniques of speech synthesis — waveform digitisation, phoneme reconstruction and linear predictive coding, are employed in digital electronic speech synthesisers produced by specialist IC manufacturers. Each produces a chip or chip set capable of producing clearly recognisable words, sounds and phrases. There are limitations in the 'vocabulary' each produces and the quality of the sound generated, but having heard the result one cannot help being amazed. The companies involved are National Semiconductor, Texas Instruments and Votrax. The technique employed and chips or chip set are as follows:

Waveform digitisation

National's DT1050 Digitalker

Phoneme reconstruction

Votrax's SC-01

Linear predictive coding

TI's TMS-5100 'speak 'n spell'

ETI-647 'TURTLE TALK' SPEECH SYNTHESISER BOARD

- Mounts in 'Tasman Turtle Robot' (ETI-645 — April/May/June '82)
- Can be used as 'stand-alone' speech synthesiser
- Can interface to almost any computer
- Produces fixed words using simple program
- Can say alphabet and numbers
- 109-word minimum vocabulary, plus prefixes, suffixes, tones
- Vocabulary expandable to about 600 words (up to 8 ROMs)
- Words can be spelled
- Different languages available (mixture permitted)
- Different voices (male, female, child) possible
- Sounds other than speech can be used
- Phrases, sentences easily programmed
- World exclusive 'mute' facility to create other words, etc
- Clock oscillator on-board
- Audio amp. on-board
- Voltage regulators on-board
- ROM power saver circuit

An excellent discussion on the three techniques, well worth reading, was published in the November 1981 issue of *Practical Computing* (p. 112-114).

Turtle Talk

Inevitably, a speech synthesiser system must be a conglomeration of compromises between storage capacity, data rate, speech quality and cost. The higher the data rate, the better the speech quality. When setting out to select a system to add speech to the Tasman Turtle Robot (see ETI, April/May/June '82) we looked for a system that gave compromise between data rate and speech quality. The National Digitaltalker system was selected. It applies a series of data compression techniques to remove as much as possible of the data not absolutely necessary. Word and sound reconstruction is done by a complex algorithm, but the Digitaltalker, we thought, provided the best quality available and still required only modest memory space.

A number of extra functions, plus interfacing, were designed into the Turtle Talk Board using the Digitaltalker so that an extremely powerful speech synthesis board results. The extra functions include a 'ROM power saving' circuit and a 'mute' facility that permits other words to be constructed from the standard vocabulary words. This feature is a *world first* and the subject of a patent application. The features of the ETI-647 'Turtle Talk' Speech Synthesiser are summarised in the accompanying panel.

The design

An overall block diagram of the speech synthesiser board is shown in Figure 4. From this you can see that the system is virtually self-contained. The only necessary external inputs required to produce speech are 13.8 Vdc power (or 12 Vdc) and data in. The latter can be provided from a set of switches, from discrete logic or from a microprocessor or microcomputer. All necessary interfacing and decoding is done on-board as well as power regulation and audio filtering and processing.

In all, 12 ICs are incorporated, although not all of them may be required, depending on the way you interface the synthesiser to the 'outside world'. Up to eight 'speech' ROMs can be included on-board, although only the 'basic' two will be provided with kits. These provide a total of 144 'words'. This includes 109 'real' words, the 26 letters of the alphabet (ay, bee, see, dee...), the numbers one to twenty plus 'thirty', 'forty', 'fifty', 'sixty', 'seventy', 'eighty', 'ninety', 'hundred', 'thousand', 'million' and 'zero'. Also included are the word prefixes 'centi', 'milli' and 're', as well as the suffix 'ss' for making plurals. Two tones and five 'silence' periods make up the remaining 'words'.

More speech ROMs can be added if a larger vocabulary or a foreign language is required.

A block diagram of the National Semiconductor speech processor chip used in this project is shown in Figure 5. This IC, designated MM54104, uses the waveform digitisation technique discussed earlier.

Word selection input (SW1 — 8) is held in a register. This is multiplexed with data from the speech ROMs (DATA 1 — 8). From this, two digital control signals emerge — a 'control word address' and a 'phoneme address'. These are held in two registers and multiplexed onto the speech ROM address buss (ADR 0 - 13). 'Control words' from the ROM (via the ROM data input) are held in a 'control word register', passing to the 'control logic' which accepts 'chip select' (CS), 'com-

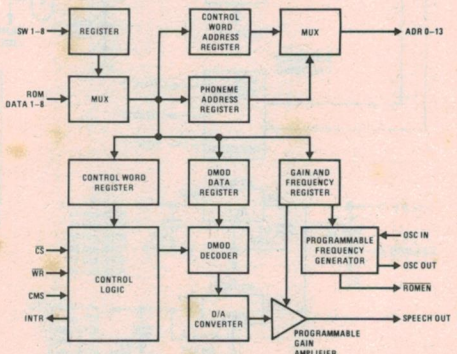


Figure 5. Internal block diagram of the Digitaltalker speech processor chip.

mand select' (CMS) and 'write' (WR) inputs for overall control of the IC, and also puts out an 'interrupt' (INTR) signal for communication back to the equipment sending input to the chip.

The frequency and amplitude information of speech phonemes (word sub-units) are reassembled by the speech processor chip from binary data fetched from the ROMs at the appropriate time. The encoded amplitude information is passed to 'deltamodulation decoder' (the DMOD DECODER block) which drives a digital-to-analogue converter (the D/A CONVERTER block). This changes the digital amplitude information to partial amplitude information which passes through a programmable gain amplifier. The encoded gain and frequency information is held in a 'gain and frequency register'. This selects frequency information from the programmable frequency generator and sets the gain of the programmable amplifier. The resultant is speech or whatever sound is programmed. ►


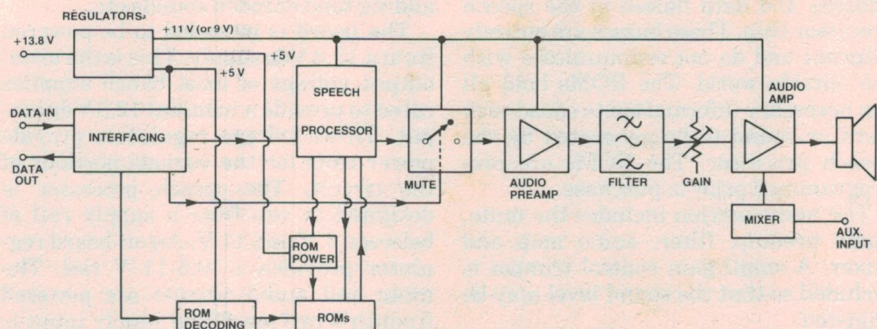



Figure 4. Block diagram of the 'Turtle Talk' speech synthesiser project.

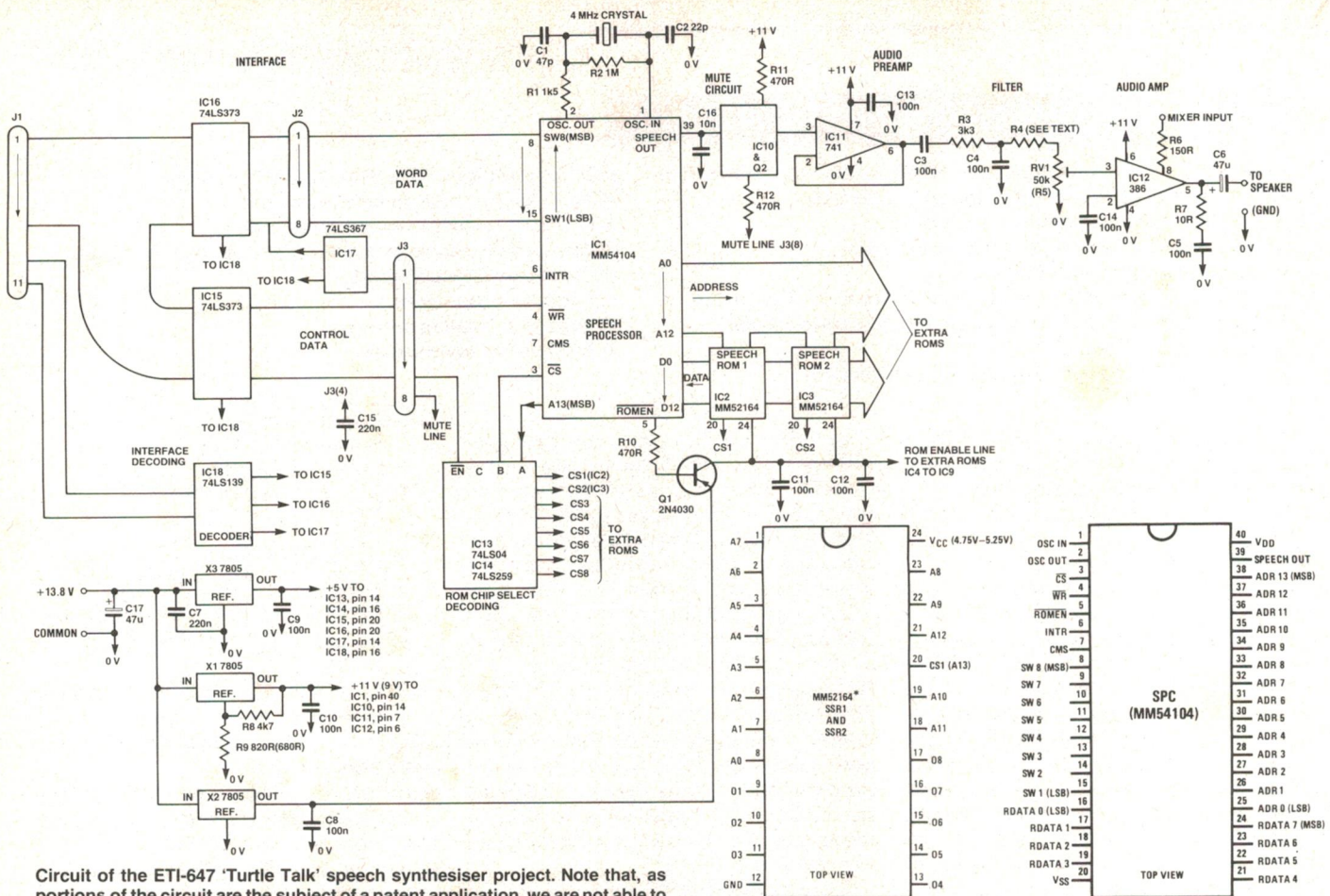

Circuit of the ETI-647 'Turtle Talk' speech synthesiser project. Note that, as portions of the circuit are the subject of a patent application, we are not able to give a pin-for-pin circuit but this is sufficient for seeing how it functions and fault-finding.

Note: 'Turtle Talk' is a trademark of Flexible Systems.

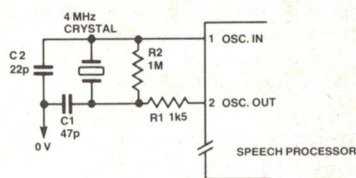The MM54104 IC has facility for a crystal oscillator or can accept an external 'clock' input. This facility provides all the required clock facilities for the chip and provides a frequency reference from which speech frequency information is derived. A 4.000 MHz crystal is employed in this project, the 'osc. in' and 'osc. out' pins of the IC being used to form an oscillator.



Each speech ROM is connected to the address and data busses of the speech processor chip. These busses are entirely internal and do not communicate with the outside world. The ROMs hold all the necessary information to cause each word or sound to be generated by the speech processor. The ROMs are pre-programmed prior to purchase.

The audio section includes the mute, audio preamp, filter, audio amp and mixer. A small gain control trimpot is included so that the sound level may be adjusted.

The mute is an exclusive feature of this design, adding extensive sound

handling capabilities to the conventional Digitalker. It nulls the audio output to the speaker without resetting the processor.

The filter is designed to give an optimal frequency response to the stepped analogue data emanating from the speech processor chip. The filter provides a lower cutoff at 200 Hz and a roll off at the high end at around 8 kHz. The speech signal is smoothed and residual sampling frequency noise is removed. An LM386 low voltage audio power amplifier chip provides drive to an external loudspeaker.

The mixer is primarily designed to take the horn input from the Tasman Turtle but could be adopted for other uses, perhaps microphone over-talk, adding tone encoded sounds etc.

The board is intended to be powered from a 13.8 Vdc supply. This is the usual output voltage of most bench supplies rated to provide a nominal 12.5 Vdc output. Three voltage regulators provide power rails for the various portions of the circuit. The speech processor is designed to run from a supply rail of between 7 V and 11 V. An on-board regulator provides a 10.5-11 V rail. The mute and audio circuits are powered from this rail too. If the supply input is likely to fall below 13.2 V, or the supply input is 12-12.6 V, then this rail should

be set at around 9 V. This is simply done by changing the value of one resistor.


There are two other regulators, each providing a +5 V rail. One supplies the interface and decoding circuitry, the other is used to supply the speech ROMs. As these only need to have the supply voltage present when being accessed, power consumption can be reduced by only turning on the supply to them as required. Accordingly, a 'power saver' circuit is incorporated to effect this.

If a separate source of power is available, the on-board regulators can be dispensed with.

Construction

A double-sided circuit board with plated-through holes is employed. Sockets are used to mount all the ICs. All the other components are soldered directly to the board. We recommend you use a temperature-controlled soldering iron with a small 'wedge' or 'chisel' point as the tracks and pads on the pc board are quite fine. All soldering is done from the rear side (i.e. non-component side) of the pc board. Use 20g or 22g resin-cored solder. The pc board tracks are solder plated to aid assembly and help prevent poor joints.

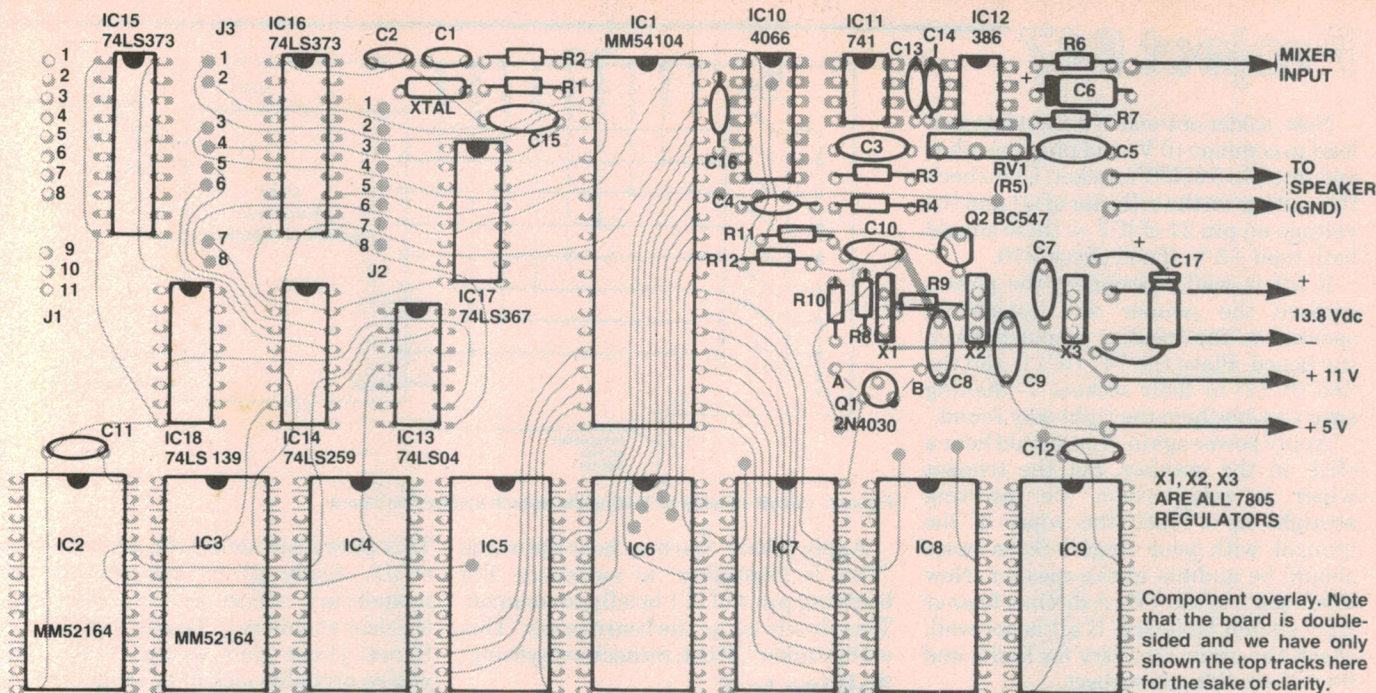Examine the overlay diagram and identify which way up and which way



around the board goes. Commence construction by soldering all the IC sockets in place. Note that they are all orientated in the same direction. If you have your board facing the same way as our overlay shows, pin 1 of all IC sockets is at the top left hand corner.

Solder all the resistors in place next. Note that a link is used in place of R4. A resistor is only used here if the synthesiser is to drive a subsequent audio amplifier. The function of R4 is to reduce the level out of the audio amp, IC12 (the 386), while still permitting a reasonable setting range for the gain control trimpot. If contemplating this, a good value to start at would be 10k. Don't solder in the trimpot yet.

If you intend powering the unit from a supply having an output less than 13.2 V, then use a 680 ohm resistor for R9 instead of the 820 ohm value specified, otherwise regulator X1 will not function as the $V_{in} - V_{out}$ voltage may fall below the regulator dropout voltage of 2 V, causing a malfunction of your synthesiser.

Solder all the capacitors in place next. Start with the ceramic capacitors, then solder the greencap (C16) in place and finish with C6. Leave C17 off for the present. Ensure the polarity of C6 corresponds to the overlay.

Now solder in the gain control trimpot — RV1(R5). The trimpot pins may be a tight fit in the holes, but a little gentle pressure will seat them home. Make sure the pads are well heated before applying solder. You might lightly tin the pins of the trimpot before mounting it, also.

The three voltage regulators can now be soldered in place, unless you have provision for off-board power supply rails and don't intend running the board

from a 12 V or 13.8 V supply. Make sure you orient them correctly. The overlay shows a thick line on that part of the regulators which have the metal mounting tab, i.e: the tabs of all the regulators face toward the right side of the board, where the dc supply input connects.

Solder the two transistors in next. Make sure these, too, are the right way round. Don't seat Q1 right down on the board. Insert it such that its bottom flange is about 5 — 6 mm off the board. Solder the 4 MHz crystal in place next. Do it quickly so that excessive heat cannot damage the quartz crystal inside the can.

Now solder in place a length of figure-8 flex for the dc supply input. Use a type that has one lead marked (i.e: 'speaker' flex), so that you can identify which is the positive and which is the common lead. Having done that, C17 can be soldered in place. Make sure you get it the right way round.

Now you're ready for an initial test. **DON'T PUT ANY ICs IN THEIR SOCKETS YET.**

First checks

Make a complete physical check of your work *first*. See that there are no poor joints, no unsoldered leads and no solder 'dags' lying about or solder 'bridges' between tracks or pads. Check that all components are correctly placed. When you're satisfied, you can apply power.

Check voltages at the following points (all with respect to common):

- Input pin of X3 — +13.8 V (or +12 V)
- Output pin of X3 — +5 V
- Output pin of X2 — +5 V
- Output pin of X1 — +11 V (or +9 V)
- Collector of Q1 (case) — 0 V

PARTS LIST — ETI-647

Resistors

R1	all 1/2W, 5% unless noted
R2	1k5
R3	1M
R4	3k3
R5	(link)
R6	(see RV1)
R7	150R
R8	10R
R9	4k7
R10	820R
R11	470R
R12	15k
RV1	10k min. vert. trimpot

Capacitors

C1	47p ceramic
C2	22p ceramic
C3, 4, 5, 8, 9, 10, 11	
12, 13, 14	100n disc ceramic
C7, C15	220n ceramic
C6, C17	47u/16 V electro.
C16	10n greencap

Semiconductors

IC1	MM54104 SPC
IC2, 3, 4, 5, 6	
7, 8, 9	MM52164 SSR
IC10	4066
IC11	741
IC12	386
IC13	74LS04
IC14	74LS259
IC15, 16	74LS373
IC17	74LS367
IC18	74LS139
X1, 2, 3	7805, LM340T5
Q1	2N4030
Q2	BC547

Miscellaneous

ETI-647 pc board (TTB-A) — this board is copyright to Flexible Systems who are the sole supplier; 4 MHz HC18/u crystal; IC sockets — 1 x 40 pin, 2 x 24 pin (or 8 x), 2 x 20 pin, 3 x 16 pin, 2 x 14 pin, 2 x 8 pin; ribbon cable and DIP headers or plugs to suit connection to computer; loudspeaker to suit; figure-8 cable, etc.

Price estimate \$240 — \$250

- Pin 40 of IC1 — +11 V (or +9 V)
- Pin 14 of IC10 — +11 V (or +9 V)
- Pin 20 of IC15 — +5 V
- Pin 24 of IC2 — 0 V

Project 647

Now, solder one end of a short 'jumper' lead to common (0 V) and plug the other end into pin 5 of IC1's socket. Now check the voltage on the collector of Q1 and the voltage on pin 24 of IC2 — these should both read +5 V. If not, check R10.

If all is well, disconnect the power, remove the jumper and connect a speaker to the speaker output pads on the board. Place the 741 (IC11) and the 386 (IC12) in their sockets — making sure you get them the right way round.

Apply power again. You should hear a click in the speaker. Set the trimpot wiper to mid-position (i.e. pointing straight up). Touch the wiper of the trimpot with your finger. Some noise should be audible in the speaker. Now touch pin 3 of the 741. A distinct buzz or hum should be heard. If all is not well, check the audio circuitry for faults and fix it if anything is suspect.

Turn off the power and put IC10, the 4066, in its socket. Apply power again. Touching pin 1 should cause a slight noise to be heard in the speaker, touching pin 2 should do the same. Temporarily jumper pin 8 of J3 to the +5 V aux. supply input. Now touch pin 2 of the 4066. No noise should be heard in the speaker. If not, check that R12 is correct and the Q2 is OK and correctly oriented. Remove power. Put all the other (LS-TTL) ICs in their sockets. Apply power and check that +5 V appears on the upper right hand pin of each. Remove power.

Now you can insert IC1 in its socket. Note that it is a MOS chip and should be supplied in conductive foam or other conductive package. Use the usual MOS-handling precautions when inserting it in its socket. Make sure you don't bend any leads under the chip package. Apply power once again and check that you get +11 V (or +9 V) on pin 40. If you have a CRO, check pins 1 and 2 for signs of oscillation — you should get a 4 MHz sinewave here. The amplitudes on the two pins will differ. (Pin 1 will have the greater amplitude signal — you may need a x10 probe to avoid 'loading' of the circuit causing it to cease oscillation). Alternatively a receiver covering this frequency could be used. You should find a strong signal on 4 MHz. If no sign of oscillation can be found, remove power and check the circuit and components around the crystal.

If all is well, remove power and insert the two speech ROMs, IC2 and IC3. These, like IC1, are also MOS devices so take care of them. One of these is marked SSR1 — this is IC2. The one marked SSR2 is IC3. Above all, make sure you insert them the right way round. See that no pins get bent under the package when inserting them into the sockets.

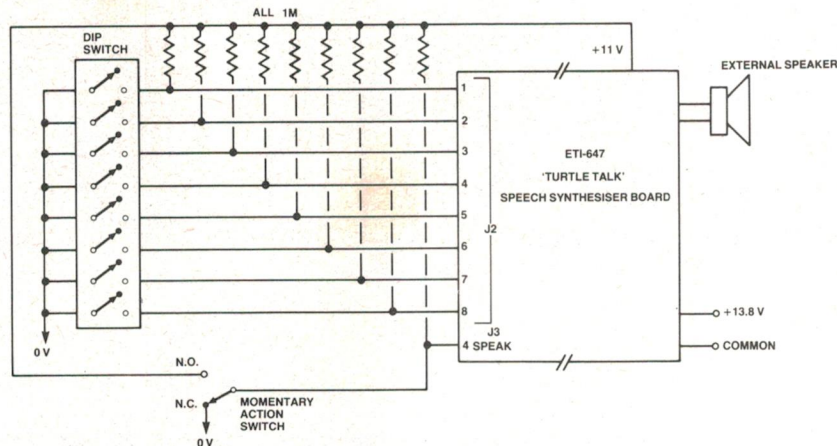


Figure 6. Circuit suitable for testing the speech synthesiser board.

Apply power. You may hear the words "This is Digitalker" at switch-on. Try bridging pin 4 of IC1 briefly to common. This should cause the board to say "This is Digitalker". If not, recheck everything.

Talking test

For this you will need an 8-way DIP switch, nine 1M resistors, a momentary action SPDT switch and either some ribbon cable or a host of hookup wire. Wire up the circuit shown in Figure 6. (Note that 0 V goes to COMMON on the pc board.) Set all the DIP switches ON.

This puts a low on all the address lines of J2. Apply power and operate the momentary action switch. Your synthesiser should say "This is Digitalker". If not, check your wiring. If it's OK, you're probably sick of hearing "This is Digitalker" so set up another address on the DIP switch by consulting the accompanying table. Upon operating the momentary action switch you should hear the word set-up. Try a few others. All OK? Well, you're ready to 'Turtle Talk'!


(... to be continued).

TABLE I. DT1050 MASTER WORD LIST

Word	8-Bit Binary Address			8-Bit Binary Address			8-Bit Binary Address	
	SW8	SW1		SW8	SW1		SW8	SW1
THIS IS DIGITALKER	00000000	1	Q	00110000	1	IS	01100000	1
ONE	00000001	1	R	00110001	1	IT	01100001	1
TWO	00000010	1	S	00110010	1	KILO	01100010	1
THREE	00000011	1	T	00110011	1	LEFT	01100011	1
FOUR	00000100	1	U	00110100	1	LESS	01100100	1
FIVE	00000101	1	V	00110101	1	LESSER	01100101	1
SIX	00000110	1	W	00110110	1	LIMIT	01100110	1
SEVEN	00000111	1	X	00110111	1	LOW	01100111	1
EIGHT	00001000	1	Y	00111000	1	LOWER	01101000	1
NINE	00001001	1	Z	00111001	1	MARK	01101001	1
TEN	00001010	1	AGAIN	00111010	1	METER	01101010	1
ELEVEN	00001011	1	AMPERE	00111011	1	MILE	01101011	1
TWELVE	00001100	1	AND	00111100	1	MILLI	01101100	1
THIRTEEN	00001101	1	AT	00111101	1	MINUS	01101101	1
FOURTEEN	00001110	1	CANCEL	00111110	1	MINUTE	01101110	1
FIFTEEN	00001111	1	CASE	00111111	1	NEAR	01101111	1
SIXTEEN	00010000	1	CENT	01000000	1	NUMBER	01110000	1
SEVENTEEN	00010001	1	400HERTZ TONE	01000001	1	OF	01110001	1
EIGHTEEN	00010010	1	80HERTZ TONE	01000010	1	OFF	01110010	1
NINETEEN	00010011	1	20MS SILENCE	01000011	1	ON	01110011	1
TWENTY	00010100	1	40MS SILENCE	01000100	1	OUT	01110100	1
THIRTY	00010101	1	80MS SILENCE	01000101	1	OVER	01110101	1
FORTY	00010110	1	160MS SILENCE	01000110	1	PARENTHESIS	01110110	1
FIFTY	00010111	1	320MS SILENCE	01000111	1	PERCENT	01110111	1
SIXTY	00011000	1	CENTI	01001000	1	PLEASE	01111000	1
SEVENTY	00011001	1	CHECK	01001001	1	PLUS	01111001	1
EIGHTY	00011010	1	COMMA	01001010	1	POINT	01111010	1
NINETY	00011011	1	CONTROL	01001011	1	POUND	01111011	1
HUNDRED	00011100	1	DANGER	01001100	1	PULSES	01111100	1
THOUSAND	00011101	1	DEGREE	01001101	1	RATE	01111101	1
MILLION	00011110	1	DOLLAR	01001110	1	RE	01111110	1
ZERO	00011111	1	DOWN	01001111	1	READY	01111111	1
A	00100000	1	EQUAL	01010000	1	RIGHT	10000000	1
B	00100001	1	ERROR	01010001	1	SS (Note 1)	10000001	1
C	00100010	1	FEET	01010010	1	SECOND	10000010	1
D	00100011	1	FLOW	01010011	1	SET	10000011	1
E	00100100	1	FUEL	01010100	1	SPACE	10000100	1
F	00100101	1	GALLON	01010101	1	SPEED	10000101	1
G	00100110	1	GO	01010110	1	STAR	10000110	1
H	00100111	1	GRAM	01010111	1	START	10001111	1
I	00101000	1	GREAT	01011000	1	STOP	10001000	1
J	00101001	1	GREATER	01011001	1	THAN	10001001	1
K	00101010	1	HAVE	01011010	1	THE	10001010	1
L	00101011	1	HIGH	01011011	1	TIME	10001011	1
M	00101100	1	HIGHER	01011100	1	TRY	10001100	1
N	00101101	1	HOURL	01011101	1	UP	10001101	1
O	00101110	1	IN	01011110	1	VOLT	10001110	1
P	00101111	1	INCHES	01011111	1	WEIGHT (Note 2)	10001111	1


Note 1: "SS" makes any singular word plural

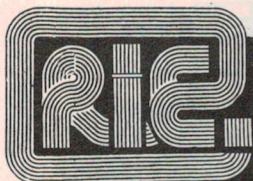Note 2: Address 143 is the last legal address in this particular word list. Exceeding address 143 will produce pieces of unintelligible invalid speech data.



C. Itoh PRINTERS

FROM ROD IRVING ELECTRONICS

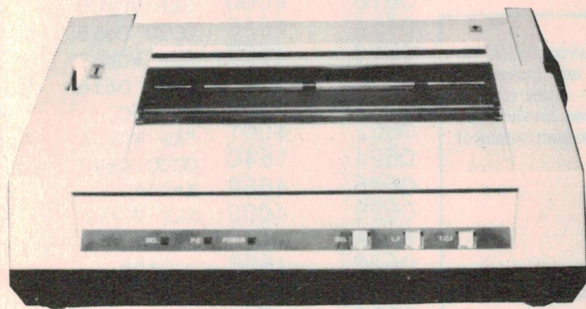

Pro/Writer Printer 8510

Print Features: Number of columns—136 col. max. Print Speed—120 CPS. Print Direction—Single-directional and Bidirectional, Switch Selectable. Throughput Speed—From 44 to 152 lpm. Character spacing (max. number of columns per line)—Pica 10 CPI (80), Double Width 5 CPI (40), Compressed Font 17 CPI (136), Double Width 8.5 CPI (68), Elite 12 CPI (96), Double Width 6 CPI (48), Proportional Double Width Proportional. Line Spacing—Variable to 1/144". Print Width—203 mm (8") max.

Forms Type: Fan Fold Roll or Cut Sheet: Width—113 mm to 254 mm (4.5" to 10.0"). Total Thickness—0.05 to 0.28 mm (0.002" to 0.011"). Number of Copies—Original + 3 copies nominal.


Form Feed: Method—Tractor or Friction. Form Loading—Either rear or top.

Interface—Serial: Method—EIA RS232-C and 20mA (40 & 60mA switchable option) Current Loop Serial Interface. Baud Rate (BPS)—110, 300, 600, 1200, 2400, 4800, 9600. Transmitting Method—Half Duplex. Synchronization—Asynchronous.

Interface—Parallel: Method—TTL compatible, 7-bit, parallel interface. Control Signals—ACK, BUSY, SELECT, DATA STB, INPUT PRIME FAULT, INPUT BUSY, PAPER EMPTY. Instruction Codes—(ASCII): CR, LF, VT, FF, CAN, SO, SI, DEL, DC1, DC2, DC3, DC4, GS, RS, US, FS, EM; GRAPHIC SYMBOLS: BIT GRAPHICS.

Error Detection: (1) Parity (VRC)—Odd, Even, No-parity. Switch selectable. (2) Framing Error—Stop bit check. (3) Overrun Error—Error is detected when data are received before the previous data have been processed.

Physical dimensions: 398 mm W x 120 mm H x 285 mm D (15.7" W x 4.7" H x 11.2" D). **Weight:** 8.5 kg (18 lbs., 12 oz.)

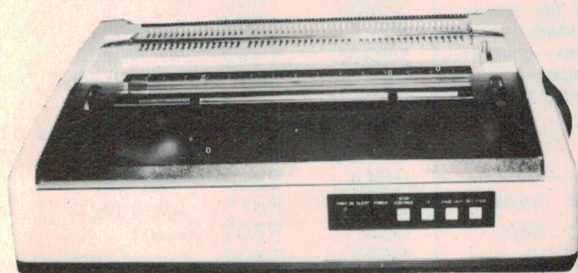


Model 1550

The Model 1550 is a compact desk-top dot matrix serial impact printer used for data communication terminals, hardcopy of CRT displays, peripheral terminals for minicomputers and microcomputers, and small-sized business systems.

The character format is a dot matrix of 7(H) x 9(V), or 8(H) x 8(V).

Print speed is 120 characters/second. Up to 136 characters can be printed per line at 10 CPI.

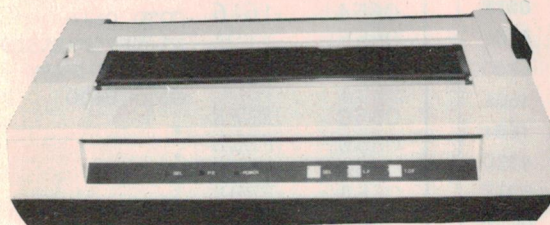Its main features are: • Compact desk-top dot matrix printer • 136-column print • Lightweight • Low power-consumption • High-quality print • Bit image graphics • Graphic Symbols • Prints in six different languages • High reliability • Low cost.



F-10 Printmaster Daisy Wheel Printer

Print Speed: 40 CPS. **Print Method:** Static Print Impact. **Number of Printable Columns:** 136, 163, Variable. **Character Spacing:** 1/120 Inch (minimum). **Line Spacing:** 1/48.

Return Time: 900 msec. **Line Feed Time:** 40 msec. **Paper Width:** 406 mm (maximum).

Print Characters: 96. **Printwheel:** Industry Standard 96 Character Wheel. **Interface:** Industry Standard 8-bit Parallel, RS232-C Compatible, X-ON, X-OFF, 12-bit Qume and Diablo Compatible. **Dimensions:** 574 mm W x 405 mm d x 153.5 mm H (22.5" W x 15.9" D x 6" H). **Weight:** 14 kg (30.8 lbs.) with cover and power supply. **Noise:** Less than 65 Db (1M from Platen, A Scale).

RITRONICS WHOLESALE

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. (03) 489-8131.

TO ORDER: Heavy items sent Comet Freight on Mail Order Phone 481-1436. Wholesale Customers Phone: 489-7099. Mail Orders to RITRONICS WHOLESALE, P.O. Box 235, Northcote 3070. Minimum P&P \$2. Add extra for heavy items, registration and certified mail. Prices and specifications subject to change without notice.

Turn to Page 96 for our Big Board Specials

Bankcard mail orders welcome
ORDER FORM
 Please Debit my Bankcard
 No.
 Expiry Date
 Name
 Signature

ET 19/82/6

This month we have two programs for you, both contributed by readers. The first program, Dice, has the instructions listed in the way we have done with most programs to date, so you can see how it works and get ideas for using in your own programs. The second, Greeblie Catcher, is listed in a 'compact' form, showing the program code only. We will be publishing more programs in this fashion in the future, leaving it to you to disassemble them. However, the author of Greeblie Catcher has included notes on the structure and workings of his program so you can see what's going on.

DICE

Adrian Ollerenshaw
O'Sullivan Beach, S.A.

This program 'throws' any number of dice up to six at a time and displays a row of real dice patterns. At the start of the program the screen is blank. Pressing any key from 0 to 6 causes that number of dice to be thrown and displayed (0 gives no throw). For another throw, simply press any key to erase the screen and then the key corresponding to the number of dice to be thrown.

Much better than boring old plastic dice that roll off the table when you least want them to, eh?!

GREEBLIE CATCHER

Robert Atkinson
Jamberoo, NSW

This is a games program which consists of a moveable 'catcher' and two 'greeblies' which you attempt to catch as they move down the screen. Each greeblie caught is stored at the left hand side of the screen for later stewing in galah fat, or as a score, or whatever tickles your imagination.

The greeblies appear randomly and move down and across the screen in a random manner. You have to position your catcher underneath them before they hit the bottom. Five misses and the game ends!

You can move your catcher quickly or slowly left or right to catch a greeblie. Here are the key functions:

- 0 . . . fast left
- 1 . . . slow left
- 5 . . . slow right
- 6 . . . fast right

The program contains three sets of subroutines which are called by the program mainline. Initialisation, or program setup, is from 0600 to 061F. The program

mainline runs from 0620 to 0670. It proceeds in the following steps: undraw catcher — add movement variables — check end of travel? — draw catcher — do greeblie subroutines — set movement variables — check if end of game? — go back to start. A total of eleven variables are used:


- A, B catcher
- 4, 5, 6, 7 greeblies
- 8, 9 store
- 1 misses
- E randomiser
- C movement variable

The greeblie subroutines are at 0670 to 069F (greeblie A) and 06A0 to 06AF (greeblie B). There is a further subroutine at 06D0 to 07FF, for storing the greeblies.

The greeblie subroutines follow the following sequence: undraw — random movement — check end of travel? — check if missed — draw — check if hit catcher? — if yes, go to store — return — (end of travel) add 1 to misses — start at random location at top of screen — return.

Go get them greeblies!

0600	A6E8	6A02	6B2C	DAB3	0678	85E4	CE02	7EFF	84E4
0608	C42F	6500	A6E8	D452	0680	4530	1698	4400	6402
0610	C62F	6700	A6EB	D672	0688	442F	642E	D452	4F00
0618	6832	6900	6100	6D00	0690	163A	26D0	D452	169A
0620	A6E8	DAB3	8AC4	4A2F	0698	7101	C42F	6500	1684
0628	6A2E	4A30	6A2E	4A00	06A0	A6EB	D672	CE02	7EFF
0630	6A02	4A01	6A02	DAB3	06A8	86E4	CE02	87E4	66FF
0638	1670	16A0	00FF	00FF	06B0	4730	16C8	4600	6602
0640	00FF	00FF	6C00	00FF	06B8	462F	662E	D672	4F00
0648	6E00	EEA1	6CFE	6E01	06C0	163C	26D0	D672	16CA
0650	EEA1	6CFF	6E05	EEA1	06C8	7101	C62F	6700	16B4
0658	6C01	6E06	EEA1	6C02	06D0	FA18	00FF	00FF	4530
0660	A6E8	3105	1620	0000	06D8	00EE	D892	7804	383E
0668	00FF	00FF	00FF	00FF	06E0	00EE	6832	7904	00EE
0670	A6EE	D452	CE01	7E01	06E8	8181	FF20	5000	5020

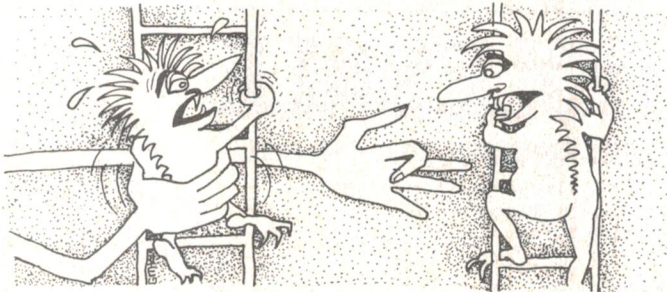


```

0600      6A00      set VA=00
0602      6B00      set VB=00
0604      F10A      V1=KEY PRESSED
0606      4100      SKF V1=00
0608      1604      GOTO 0604
060A      62F9      SET V2=F9
060C      8214      V2=V2+V4
060E      3F01      SKF VF=01
0610      1616      GOTO 0616
0612      6F00      VF=00
0614      1604      GOTO 0604
0616      CC07      VC=RND AND 00
0618      4C00      SKF VC#00
061A      1616      GOTO 0616
061C      4C07      SKF VC#07
061E      1616      GOTO 0616
0620      A65C      I=065C
0622      4C01      SKF VC#01
0624      1640      GOTO 0640
0626      A662      I=0662
0628      4C02      SKF VC#02
062A      1640      GOTO 0640
062C      A668      I=0668
062E      4C03      SKF VC#03
0630      1640      GOTO 0640
0632      A66E      I=066E
0634      4C04      SKF VC#04
0636      1640      GOTO 0640
0638      A674      I=0674
063A      4C05      SKF VC#05
063C      1640      GOTO 0640
063E      A67A      I=067A
0640      DAB7      SHOW 7 BYTES AT
0642      6E0A      VE=OA      VA,VB
0644      FE18      TONE=VE
0646      FE15      TIMER=VE
0648      FEO7      VE=07
064A      3E00      SKF VE=00
064C      1648      GOTO 0648
064E      7A08      VA=VA+08
0650      71FF      V1=V1+FF
0652      3100      SKF V1=00
0654      1616      GOTO 0616
0656      F10A      V1=KEY PRESSED
0658      00E0      CLEAR SCREEN
065A      1600      GOTO 0600
065C      FEFE      .
065E      FEFE      .
0660      FEFE      .
0662      FEFE      .
0664      FEFE      dice patterns
0666      FEFE      .
0668      FEFE      .
066A      FEFE      .
066C      FEFE      .
066E      FEFE      .
0670      FEFE      .
0672      FEFE      .
0674      FEFE      .
0676      FEFE      .
0678      FEFE      .
067A      FEFE      .
067C      FEFE      .
067E      FEFE      .
0680      FEFE      .


```


K-NAR COMPUTER CARDS


S100 Z80 SYSTEM CARD SPECIALISTS

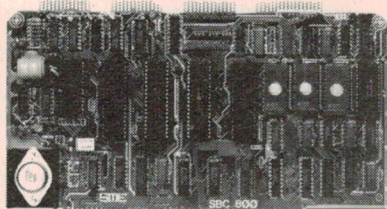

SBC-800

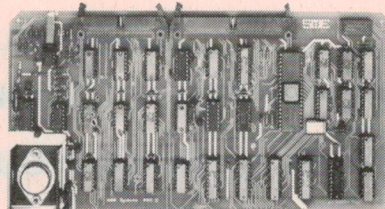

FDC-II

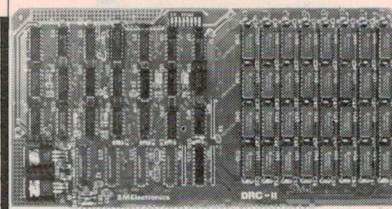

DRC-II

You know the SME Systems boards as the most powerful and technically up-to-the-minute manufactured in Australia today.

Using K-NAR's mail order system can save you dollars. Compare our prices on these high performance cards.

SBC-800

4Mhz Z-80 CPU, two serial RS232 ports, software programmable Baud rate gen., Centronics parallel port, 22 prog. I/O lines, real time clock (battery backed), 2K CMOS RAM, power on reset/power fail detect, battery backed as standard, etc. List Price \$495. Our Price \$395.

SBC-400

4Mhz Z-80 CPU, 1K Static Ram, RS232 I/O with Sync/Async, Centronics interface, 4Ch. counter/timer, Soft. Prog. Baud rate generator, 2K CP/M BIOS EPROM option. List Price \$395. Our Price \$315.

FDC-II

Enhanced floppy disk controller, IBM 3740 compatible, operates 5 & 8" and single/d. density drives, handles up to 4 drives, runs multi-density CP/M2.2 & MP/M 2. Vectored interrupt operation optional. List Price \$465. Our Price \$370.

DRC-II


The board for multi-user installations. 64/256K dynamic RAM card, bank select, fast 4Mhz operation, on-board memory prom, dip-switch selectable boundaries, bank mode allows up to 8 boards on bus, hidden refresh, phantom disable. List Price \$600. Our Price \$475.

CRC-48


Fool-proof memory system. State-of-the-art CMOS memory card with memory protection. on board battery back-up, compatible with DRC-II, write protection enable/disable, can be used as complete EPROM card or any combination of EPROM or CMOS ram. List Price \$525. Our Price \$420.

VDC-8024

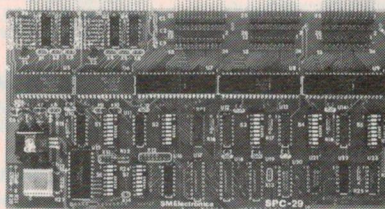
The low cost alternative to stand-alone terminal. Flexible 80x24 memory mapped video display board with full ASCII, semi graphics, Inverse & half intensity video, flicker free screen updating. Battery backed option offers diagnosis of system shut downs. List Price \$325. Our Price \$265.




SPC-29

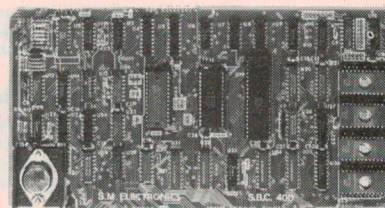


SBC-400

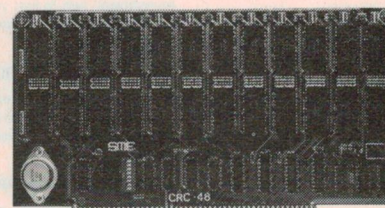

CRC-48

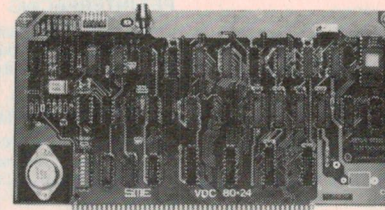

VDC-8024

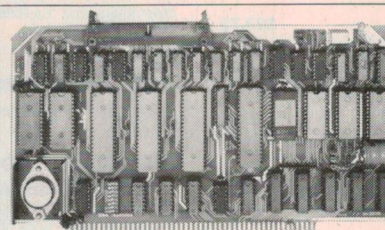

MPC-6 DARTBAUD

MPC-6 DARTBAUD

For Multi-user systems. Multi-channel RS232 Intelligent I/O card with full I/O buffering and high level input/output drivers. 6 channels, on-board Z80 processor, software programmable baudrates, 6K buffer memory (battery backed). User programmable features for system tailoring. List Price \$725. Our Price \$575.

SPC-29

High performance dual serial & 9 parallel port I/O CARD, with full I/O address decoding. Switch selectable baud rates. Link patch area, programmable modes for strobed/latched I/O. List Price \$295. Our Price \$235.

PACKAGE SPECIAL

Try this for value

SBC-800 • FDC-II • DRC-II

& 5-slot motherboard with mini-cage. Monitor/BIOS EPROM.

Special package price \$1425*



PO Box 412, Dandenong, 3175 Phone (03) 795 5858
Authorised distributor of SME Systems products.

* Prices subject to change without notice. All prices excluding tax. For retail prices add 17.5%.
All boards fully assembled and tested and backed by 90-day guarantee.

To K-NAR Computer Cards

Please send me product data sheets.
(I enclose 4 stamps).

I wish to order
My cheque/order form is enclosed
Please debit my Bankcard No.

Name
Address

Signature

Please include me on your new product mailing list. I am mainly interested in systems for ☐ Hobby, ☐ Industrial use ☐ Education ☐ Business ☐ Process control ☐ Other



A Computer is Almost Human

— except that it never blames other computers for its mistakes —
and it doesn't mind how many books you refer to . . .

CP/M PRIMER

A complete one-stop course on CP/M, the very popular operating system for 8080, 8085 and Z80-based microcomputers. Complete terminology, hardware and software concepts, start-up of a CP/M system, and a complete list of CP/M-compatible software.

21791 \$21.95

APPLE MACHINE LANGUAGE

This straightforward book teaches machine language programming through BASIC, the transition being made step-by-step. Many sketches of video displays are provided, as well as exercises with answers.

90230-7 \$21.95

EXPLORE COMPUTING WITH THE TRS-80 (AND COMMON SENSE)

This introduction to microcomputers and the BASIC language is suitable for novices and users of the TRS-80. Among the topics covered are creating tables, arts and graphics, games and simulation.

96137-7 \$17.95

TELEMATIC SOCIETY

An extensive update of 'The Wired Society', this book demonstrates how developments in telecommunications will affect the way we live.

02460-3 \$17.50

Z8000 CPU USER'S REFERENCE MANUAL

A technical manual from Zilog, this book discusses all aspects of the Z8000 package, including instruction sets, data types, addressing modes, systems inputs, timing, memory address space, registers, bit manipulation instructions, external interface devices, etc.

83890-2 \$20.75

PROGRAMMING IN BASIC FOR PERSONAL COMPUTERS

Simple instructions show how to give BASIC commands and statements a wide range of applications, from programming video games to developing business or scientific programs.

30739-X \$11.75

APPLE BASIC

This book gives the beginner a thorough introduction to BASIC programming on an Apple computer, and covers all areas of programming, including graphics, games, mathematical programs, and a great deal more.

39099-2 \$19.25

TRS-80 ASSEMBLY LANGUAGE SUBROUTINES

A wide spectrum of applications is discussed in this book, which provides easy-to-use routines that can be used as they stand or modified.

31188-2 \$19.25

THE UCSD PASCAL HANDBOOK

Language descriptions organized in a quick and easy reference are given in this book for readers with no prior experience of Pascal programming.

35536-7 \$23.75

BASIC FOR BUSINESS FOR THE TRS-80

This book covers the application of BASIC language to business uses on the TRS-80 models II and III.

90352-4 \$22.25

STARTING FORTH

A clear and complete guide to FORTH, this book covers fundamental principles and then a full set of high-level FORTH commands. It concludes with advanced techniques and style.

42922-7 \$23.75

PROGRAMMING WITH ADA

This sourcebook features a thorough coverage of ADA language and stresses topics unique to ADA, such as packages, tasks, and order mechanisms for concurrent programming and multi-tasking. This text is best used by programmers with some experience in other high-level languages.

30697-0 \$23.75

THE 68000: PRINCIPLES AND PROGRAMMING

An easy-to-read, systematic approach to the 68000 advanced 16-bit microprocessor. The book guides you through the complex architecture, instruction set, pinouts and interfacing techniques. Written for design engineers, programmers and students.

21853 \$22.00

PET GAMES AND RECREATIONS

Presenting an interesting mixture of diversions guaranteed to entertain and educate. Ideal for beginners, yet also challenging to computer veterans, the book features progressive levels of difficulty and five different types of games.

95529-X \$21.00

THE PET PERSONAL COMPUTER FOR BEGINNERS

This handy guide is written for use with all varieties of PET computer, from the original 2001 to the new 8032 Super PET. It is suited to novices with no practical experience and provides advice and practical examples.

61827-8 \$23.00

PASCAL PROGRAMMING FOR THE APPLE

This book teaches UCSD Pascal on the Apple II. Many examples, programs for financial applications, graphics, file structures and sound reproduction are supplied.

95454-4 \$19.75

APPLESOFT LANGUAGE

Written for Apple II micros that use the Microsoft language, this introduction covers each aspect of programming in non-technical language, from elementary concepts to advanced techniques.

21811 \$15.50

TRS-80 ASSEMBLY LANGUAGE MADE SIMPLE

If you have an understanding of BASIC programming, this book will help you learn to plan, write and hand-assemble your own assembly language programs in memory, using the T-bug and Level II BASIC ROM subroutines.

21851 \$19.25

MOSTLY BASIC: APPLICATIONS FOR YOUR TRS-80 — BOOK 1

28 ready-to-use BASIC programs which have been completely tested and debugged. Programs include a telephone dialler, digital stop-watch, spelling test, house buying guide, gas mileage calculator, and others. Complete with explanations of each program, sample runs, and complete program listing.

21788 \$19.25

MOSTLY BASIC: APPLICATIONS FOR YOUR TRS-80 — BOOK 2

32 ready-to-run BASIC programs, including two to test your ability in history and maths, a Dungeon of Danger that's strictly for fun, eleven household programs, seven on money and investment, two to test your ESP level, and more. Complete with explanations, sample run and listing for each program.

21865 \$19.25

INTERMEDIATE PROGRAMMING FOR THE TRS-80 MODEL I

Step-by-step instructions for the TRS-80 user who wants to progress from BASIC to machine and assembly language programming with the TRS-80 Model I system. A complete how-to guide with numerous examples.

21809 \$14.95

CIRCUIT DESIGN PROGRAMS FOR THE TRS-80

A number of programs written to aid you in using your TRS-80 and Level II BASIC for the design and analysis of many electronic circuits. The programs analyse information on ms values, periodic waveforms, integrated circuit timers and bipolar transistor circuits.

21741 \$21.75

PET INTERFACING

Demonstrates how to build numerous interfacing devices for PET hardware. BASIC language programs are used throughout, and the book includes a discussion of the microprocessor's internal architecture and general hardware/software interfacing.

21795 \$25.25

TRS-80 — MORE THAN BASIC

Learn to program in Z80 mnemonics by using the book's error-tolerant interactive monitor program. Over 26 commands available, with total documentation that helps you change the commands to meet specific applications.

21813 \$15.95

SMALL BUSINESS COMPUTERS: A GUIDE TO EVALUATION AND SELECTION

Ideal for the inexperienced user, this text emphasises management considerations in determining the feasibility, economics, evaluation, selection, contracts and practicality of installing a computer.

81134-6 \$14.95

BASIC FOR EVERYONE


349 pages of BASIC information for all purposes.

61481-5 \$22.00

INTRODUCTION TO PASCAL

The second edition of this popular book has been updated to conform to the new international standard of Pascal. The contents illustrate the design and construction of Pascal programs, involving a wide range of basic computer algorithms in a practical context.

91522-4 \$22.00

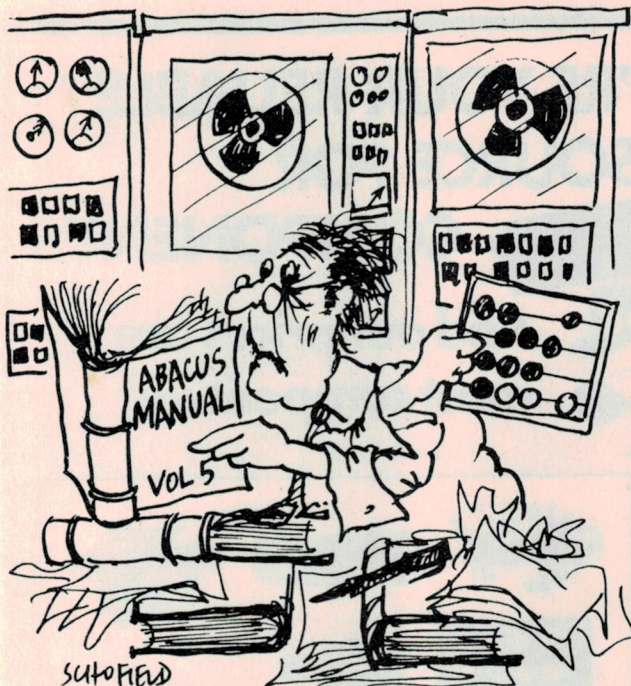

INTERFACE PROJECTS FOR THE APPLE II

A series of interface projects that are easily built and enable the user to realise the computer's potential through project construction. Projects are primarily hardware-orientated, with some software supporting the hardware.

69387-6 \$15.95

ATARI GAMES AND RECREATIONS

Beginners and advanced users can use the preprogrammed games in this book to improve their skill. Charts, flash cards, an error dictionary and graph paper designs are among the features.

90242-0 \$19.25

THE ATARI ASSEMBLER

This practical book gives detailed instructions for using the Atari Assembler cartridge for novices with some knowledge of BASIC programming. Fundamental information on programming in assembly language is given.

90236-6 \$19.25

INTERFACE PROJECTS FOR THE TRS-80

This book provides the TRS-80 user with a series of interface projects that are easily built and enable the user to discover the computer's capabilities through project construction. Projects are primarily hardware-orientated, but some supporting software is included.

69429-5 \$19.25

Z80 USER'S MANUAL

An all-in-one guide to Z80 pin definitions, CPU control signals, support chips, interfacing peripherals and much more.

99516-X \$15.95

PET/CBM BASIC

This book provides a thorough introduction to BASIC programming on a PET computer, explaining programming concepts for graphics, including three-dimensional letters, bar graphs and the use of sound effects in PET programs.

61751-4 \$19.25

PET BASIC 1

For users of the PET computer, this book covers such topics as creative graphics, humour and interesting small programs.

95524-9 \$19.25

VIC BASIC

Simple VIC BASIC programs are provided, with full explanations of how to effectively combine colour, sound and graphics on the Commodore VIC.

98377-3 \$19.25

PROGRAMMING THE TRS-80 POCKET COMPUTER

This book explains all aspects of problem-solving in BASIC, and covers cassette machine interfacing and how to make the best use of the system's keyboard and display.

30531-1 \$13.25

Z80 MICROCOMPUTER HANDBOOK

This thorough handbook covers hardware, software and microcomputers built around the Z80.

21500 \$17.50

Z80 MICROCOMPUTER DESIGN PROJECTS

This book provides a complete look at the internal architecture of the Z80, the heart of many microcomputers, and even shows how to build a microcomputer, the EX80, using this powerful chip.

21682 \$20.75

APPLE INTERFACING

Using this book, you will be able to perform useful experiments which will provide a much clearer understanding of the fundamentals of computer interfacing and computer electronics. A better understanding of interactions between hardware and software will enable you to communicate more effectively with your Apple.

21862 \$15.95

THE S100 AND OTHER MICRO BUSES

The key to successful computer expansion is a complete understanding of the bus system, through which the computer communicates with peripherals. This book will give you that understanding.

21810 \$13.25

EXPERIMENTS IN ARTIFICIAL INTELLIGENCE FOR SMALL COMPUTERS

Artificial intelligence is the capability of a device to perform functions normally associated with human intelligence, such as game playing, problem solving, reasoning, creativity and verbal communications. With this book, a small computer with extended BASIC and some knowledge of BASIC language, you can conduct interesting and exciting experiments in artificial intelligence.

21785 \$13.25

MICROCOMPUTER DESIGN AND TROUBLESHOOTING

Tells you how to design microcomputer systems and make them work without an expensive commercial development system or the need for costly test instrumentation. The author also provides a complete description of two popular microprocessors — the 8085 and the 6502.

21819 \$26.75

INTRODUCTION TO FORTH

The most complete book available on the MMS FORTH version of FORTH, but also a fundamental approach to programming in all versions of FORTH. Many programming examples are provided, with direct comparisons to the Microsoft Level II BASIC version of these programs.

21842 \$14.95

6809 MICROCOMPUTER PROGRAMMING AND INTERFACING, WITH EXPERIMENTS

Gives a solid understanding of how to program and interface the high-performance 6809 microprocessor. The author completely explores internal structure, addressing modes, data movement instructions, registers, arithmetic logic and test instructions for the 6809.

21798 \$21.95

COMPUTER GRAPHICS PRIMER

Almost every page has a colour drawing, photograph, picture or a schematic to help you learn computer graphics quickly and easily. Programming concepts apply to all microcomputers, and examples are given in BASIC for the Apple II.

21650 \$21.95

CIRCUIT DESIGN PROGRAMS FOR THE APPLE II

A series of ready-to-run Apple II programs ideal for electronics design engineers and others faced with solving problems related to plotting and verification of experimental data. The programs may be used as subroutines in larger programs, and many can be translated to run on other microcomputer systems.

21863 \$21.50

ORDER FORM

Send to ETI Book Sales, 4th Floor, 15 Boundary St, Rushcutters Bay NSW 2011.

Please allow 4-5 weeks for delivery.

Post & Handling: \$2.20 per book.

Please forward

No.	Qty.				
		42922-7	...	21795	...
		30697-0	...	21813	...
21791	...	21853	...	81134-6	...
90230-7	...	95529-X	...	61481-5	...
96137-7	...	61827-8	...	91522-4	...
02460-3	...	95454-4	...	69387-6	...
83890-2	...	21811	...	90242-0	...
30739-X	...	21851	...	90236-6	...
39099-2	...	21865	...	69429-5	...
31188-2	...	21788	...	99516-X	...
35536-7	...	21809	...	61751-4	...
90352-4	...	21741	...	95524-9	...
				21863	...

I enclose \$ inc. p&h

Name

Address

..... Postcode

Please debit my ☐ Bankcard ☐ American Express card Expiry Date

Number:

Signature




WE'RE YOUR RELIABLE SOURCE FOR COMPONENTS

And our prices are
most competitive!

Whenever you're
looking for quality components
— capacitors, switches, connectors, ICs, resistors,
speakers, volume controls, and displays — we offer you your best selec-
tion, your best quality, and your lowest prices. And we keep large
stocks on hand to ensure prompt delivery.

Delsound

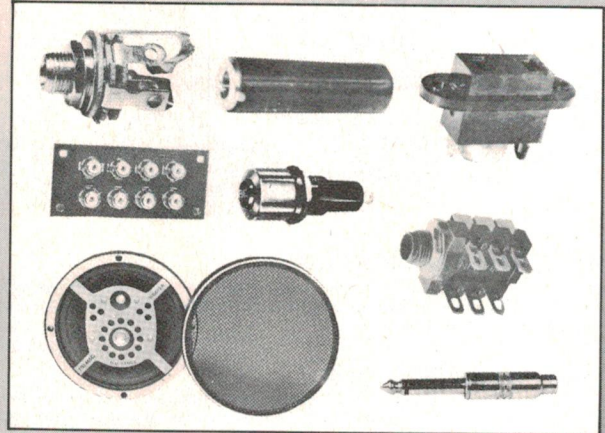1 WICKHAM TERRACE, BRISBANE 4000 — PH (07) 229 6155 TELEX AA44442
QLD. DISTRIBUTORS OF
• SWANN (MCMURDO) PRODUCTS • SWITCHES & ELECTRONIC HARDWARE
• AUDITEC AUDIO MODULES • CLIFF KNOBS, PLUGS & SOCKETS • R.C.A.
SEMICONDUCTORS • NATIONAL SEMICONDUCTORS.



12" GREEN MONITOR KG-12N Display Monitor




\$249.00

Designed to fit Telereader equipment and computers with composite video output, the 12" (31cm) CRT displays up to 2000 characters, using an implosion-proof green phosphor. Dependable 14-transistor circuitry with DC restoration for raster prevention.

Input Signals	Composite Video Signal, Negative SYNC.
CRT Size	1.0 +0.5 Vp-p, 75 ohm
Phosphor	31cm diag. (12 inches diag)
Semiconductors	P31 (Green)
Video Amp	IC 1
Bandwidth	Transistors 14
Display Area	Diodes 15
Display Format	18MHz
Scanning	Horizontal 21cm (46uS)
Frequency	X Vertical 15 cm (18.23mS)
Power Input	2000 Characters max.
Power Consumption	(80 char. X 25 lines)
Dimensions	Horizontal 15.75KHz, 60Hz
Weight	Model KG-12NU AC120V 60Hz
	Model KG-12NE AC220V 50Hz
	Model KG-12NB AC240V 50Hz
	Model KG-12NA AC240V 50Hz

DOT MATRIX PRINTER Model 8510/8510P

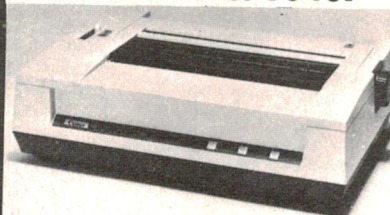

8510 Dot Matrix Printer

This compact desk top dot matrix serial impact printer is ideal for hard-copying CRT displays, and for data communications and peripheral minicomputer terminals. Features include variable fonts, dot graphics, 4-copy capability, print speed of 100 characters per second, 136 characters per line.


\$930.00

8510P Dot Matrix Printer

Identical to the 8510 model, with additional Centronix — compatible parallel interface for compatibility with the Telereader equipment. • Power source: AC 100/115/220/240V • Dimensions: 15 1/4" W x 11 1/4" D x 4 1/4" H (398mm W x 285mm D x 121mm H) • Weight 8.5kg (18.7lb)

\$799.00

POWER SUPPLY HP-315

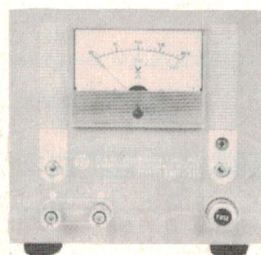

Stabilised DC power supply suitable for 100W class power ampl. used at the based station. 13.8V output at 15A (20A peak) stability 2% or better.


\$165

EMTRONICS

649 George St., Sydney NSW 2000
Ph: (02) 211 0531 P.O. Box K21
Haymarket NSW 2000.

The refined Turtle

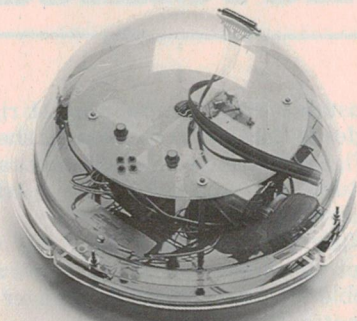Assembling the turtle produced a few problems for Stephen Thomas. So after a period of teeth-gnashing and hair-tearing he has made some mechanical and electronic modifications. He now has a refined pet, better trained than the original rascal.



Stephen Thomas

Mechanical modifications

I assembled the turtle as described (April, May and June issues of ETI) and found that the pen solenoid plunger not only touched the base plate, but was pushed in by about 4 mm. I thought that if I glued the grommet under the plunger, as was suggested, the plunger would have even less space in which to move.

So I figured out that the top plate could move up by 12.7 mm (that's half an inch) and would still fit comfortably under the dome. This led to the revised mounting arrangements shown in Figure 1(b).

A side effect of this method is that the pc board can be secured before the long bolts are installed, so that less juggling is required to get the top plate screwed down. This has benefits when you come to mount further pc boards in the Turtle at a later date.

And I found another problem with the solenoid. The bolts holding down the plate, which stops the plunger from twisting, made it difficult to mount the speaker. This situation was made even worse by using Silastic which, although it is an excellent sealant, is a somewhat dubious glue. So I made a little widget out of masonite to go between the solenoid and the speaker (with a cutout for the bolt head) and stuck them all together with epoxy as shown in Figure 2.

I had a problem with the pen alignment and could not persuade the confounded animal to produce coherent graphics. The main problem was at corners, where the pen would describe a sort of random small arc before setting off on a straight line again. Wobble in the solenoid plunger was part of the problem. I could not adequately adjust the centering of the pen either. I altered the pen assembly as shown in Figure 2. I cut and bent up a four-fingered 'claw' from sheet metal and attached it to the

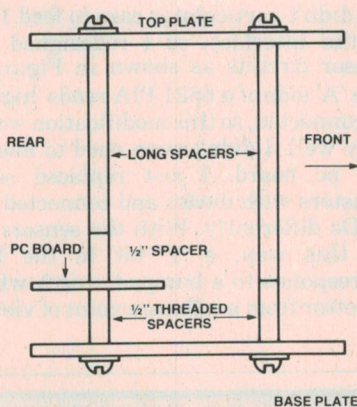


Figure 1(a). Original mounting arrangements.

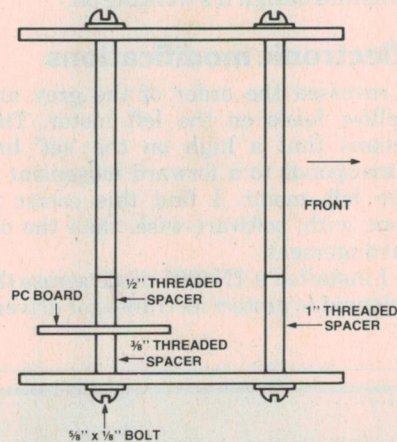


Figure 1(b). Better arrangement for mounting top plate to base plate.

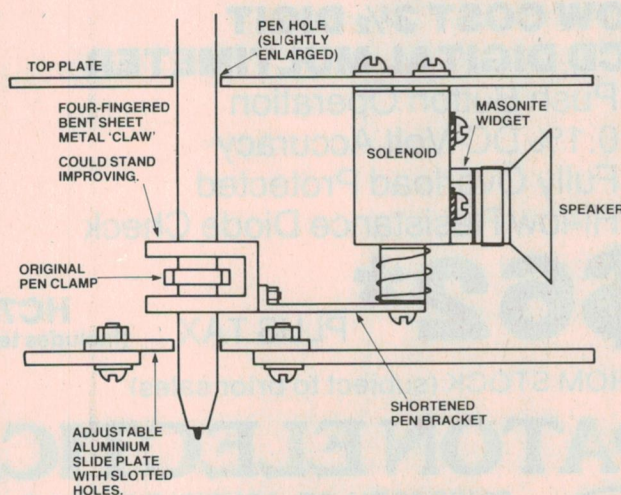


Figure 2. Modifications with aluminium slide plate and widget.

original pen bracket. The pen is held loosely in this claw with the original pen clamp permitting limited up-down movement. The bracket also permits an amount of horizontal movement. To pos-

ition the pen, I made an adjustable 'slidey' plate from aluminium and bolted this over the original pen hole in the base which I had enlarged. I cut slots in the base and corresponding slots in the

The refined Turtle

adjustable plate, but running at right angles to the slots in the base, as shown in Figure 3. This permits a considerable latitude of adjustment for perfect centering of the pen.

With the pen set up this way the graphics improve out of sight and any wobble in the solenoid plunger is immaterial.

If I can lay my hands on another wooden 'foot', I am going to put it on the back of the turtle. I have a rather long, heavy control cable and I find that the foolish reptile will occasionally lurch backwards, completely ruining the graphics design it's working on.

Electronic modifications

I reversed the order of the grey and yellow leads on the left motor. This means that a high on the 'set' line corresponds to a forward movement of the left motor. I find this easier to cope with, software-wise, than the old arrangement.

I installed a 1N4007 diode across the solenoid to protect its transistor driver.

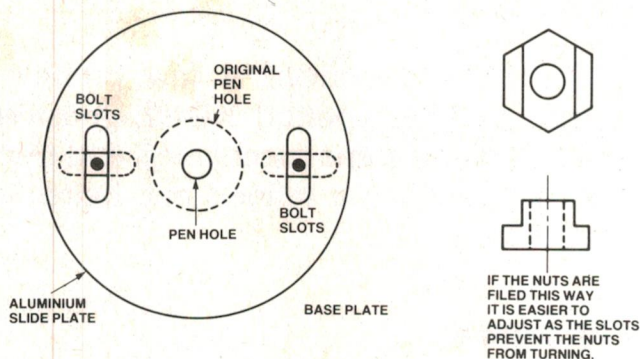


Figure 3.

I didn't particularly care to feed 12 V to the interface, so I redesigned the sensor circuits as shown in Figure 4. The 'A' side of a 6821 PIA reads 'high' if unconnected, so this modification works very well. I didn't even need to modify the pc board. I just replaced some resistors with diodes and connected the LEDs differently. With the sensors set up this way, a '1' bit in the PIA corresponds to a bumped switch which is better from a software point of view. ●

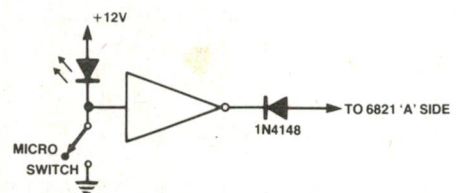


Figure 4. Redesigned sensor circuits.



HUNG CHANG

**LOW COST 3½ DIGIT
LCD DIGITAL MULTIMETER**


- ★ Push Button Operation
- ★ 0.1% DC-Volt Accuracy
- ★ Fully Overload Protected
- ★ Hi-low Resistance Diode Check

\$62*

PLUS TAX

HC703
(Includes test leads)

*FROM STOCK (subject to prior sales)

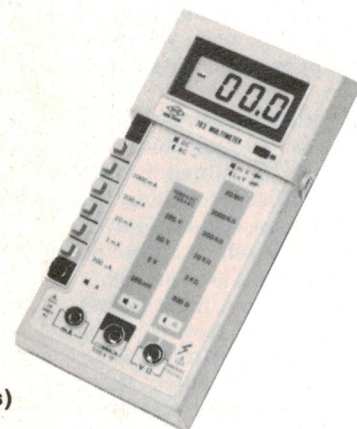

BANKCARD WELCOME

PATON ELECTRICAL PTY. LTD.

90 VICTORIA ST, ASHFIELD NSW 2131. TEL: (02) 797 9222
136 UNION RD, ASCOT VALE VIC. 3032. TEL: (03) 370 5994

AGENTS:

NSW: Newcastle (049) 61 5628 Wollongong (042) 71 3844 ACT: (062) 80 4654 PNG: Lae 43 2277 NZ: (04) 68 3589 QLD (S): (07) 52 5231 QLD (N): (070) 51 2404 WA: (09) 381 4477
SA: (08) 268 2300 TAS: (002) 34 5978 (003) 31 9868.

TASMAN TURTLE ROBOT KIT

EXCLUSIVE TO ETI READERS

Special Offer Price:

\$349.00

(tax exempt: \$297.00)

**plus \$6 post and handling
(inc. registration).**

This product has never previously been offered as a kit and would normally retail for around \$600.

OFFER CLOSES SEPTEMBER 30

Here is a not-to-be-missed opportunity to get started in robotics. For minimum cost this kit will provide you with the basic equipment to construct a robot which can be driven by remote control, electronic hand control or under computer control. Called the 'Minimum Turtle Kit', it has been put together by Flexible Systems of Hobart, Tasmania, manufacturers of the Tasman Turtle (see Printout, page 82, February ETI). Using this kit as a start you can develop a sophisticated robot capable of a huge variety of tasks.

The complete Minimum Turtle Kit comes ready for assembly according to the construction description published in ETI, packed in a box which has been designed so that the Turtle may be housed or stored in it after assembly.

HOW TO PURCHASE A MINIMUM TURTLE KIT

Fill out the coupon here and include a cheque or money order for a total of \$355. Make out the cheque or money order to 'Flexible Systems, Turtle Kit Offer', and post it, together with the coupon, to:

ETI/Turtle Robot Kit Offer
ETI Magazine
15 Boundary St
Rushcutters Bay NSW 2011

The orders will be processed by ETI and, on clearance of the cheque or money order by Flexible Systems, the kit will be despatched directly to you via registered post.


Tax exemption: For schools, TAFEs, etc. this kit can be purchased at the tax exempt price **only** if the coupon is accompanied by a signed order and a tax exemption declaration.

LAST CHANCE!

OFFER CLOSES SEPTEMBER 30

NOTE: This offer is made by Flexible Systems in co-operation with ETI Magazine. ETI is acting as a clearing agent for orders. All mail orders will be despatched by registered post. Please allow four to six weeks for delivery.

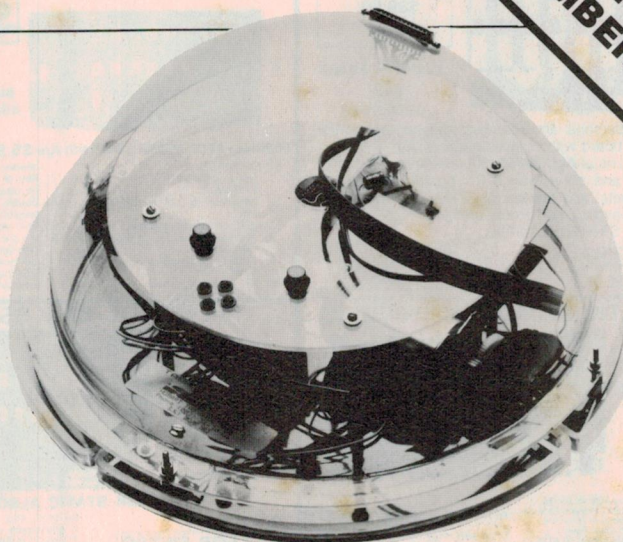**SPECIAL OFFER
OFFER EXTENDED
TO SEPTEMBER 30**



DEMONSTRATIONS: see the Turtle — live!

NOTE: Turtle kits are now supplied with a clear plastic base and modified and improved motor mounting components. The modifications remove the need for adjustment of the wheels once the unit is assembled and the clear base allows viewing of the graphics while the Turtle is drawing.

WHAT YOU CAN DO WITH IT

You can use your Minimum Turtle to experiment with many aspects of robotics by interfacing it with a computer: draw figures under program command, solve mazes, make measurements, identify objects, etc. It can be driven via a cable or a remote control. The Minimum Turtle has been designed so that a wide variety of add-on projects may be included to increase the sophistication as you desire.

THE MINIMUM TURTLE KIT CONTAINS:

- All hardware (base, nuts and bolts, perspex dome, 'touch' ring, pen solenoid, speaker, etc)
- All mechanical parts (wheels, gears, axles, two stepper motors, etc)
- 'Standard Turtle' electronic control pc board and components
- All wire and cable for internal wiring
- A 25-pin plug for bidirectional data buss, control lines and power supply connections
- Comprehensive instruction manual

*Tasman Turtle is a registered trademark of Flexible Systems.

COUPON

Please supply Minimum Turtle Kit(s)

I enclose \$ plus \$6 each postage (inc. registration).

TOTAL \$

Name

Address

. Postcode

Cheque or Money Order No

Signature

(please allow four to six weeks for delivery)


64K S100 STATIC NOW AVAILABLE \$399 + TAX

DON'T FORGET TO CHECK WITH US BEFORE YOU BUY A COMPUTER OR OTHER PRODUCTS

ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE, VICTORIA

16K EPROM CARD-S 100 BUSS

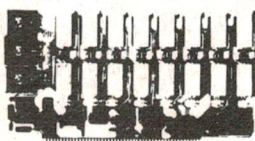

**\$89.50
KIT**

**BLANK PC BOARD
\$49**

USES 2708's!

Thousands of personal and business systems around the world use this board with complete satisfaction. Puts 16K of software on line at **ALL TIMES!** Kit features a top quality soldermasked and silk-screened PC board and first run parts and sockets. Any number of EPROM locations may be disabled to avoid any memory conflicts. Fully buffered and has WAIT STATE capabilities.


OUR 450 NS 2708'S
ARE \$5.90EA. WITH
PURCHASE OF KIT

**ASSEMBLED
AND FULLY TESTED
ADD \$36**

S100 COMPUTER PRODUCTS

32K S-100 EPROM CARD

NEW!

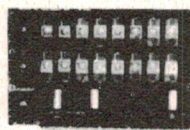

\$99.95

**KIT
USES 2716's
Blank PC Board - \$59
ASSEMBLED & TESTED
ADD \$30**

SPECIAL: 2716 EPROM's (450 NS) Are \$5.90 EA. With Above Kit.

KIT FEATURES

1. Uses +5V only 2716 (2Kx8) EPROM's
2. Allows up to 32K of software on line!
3. IEEE S-100 Compatible
4. Addressable as two independent 16K blocks
5. Cromemco extended or Northstar bank select
6. On board wait state circuitry if needed
7. Any of all EPROM locations can be disabled
8. Double sided PC board, solder-masked, silk-screened
9. Gold plated contact fingers
10. Unselected EPROM's automatically powered down for low power
11. Fully buffered and bypassed
12. Easy and quick to assemble

*** * * AVAILABLE AGAIN * * ***



- 16K Dynamic RAM Board
- Fully Expandable to 64K
- Assembled, tested and guaranteed
- S100 Compatible

16K Dynamic RAM Board assembled and tested: Special \$269 plus tax (4mHz) \$299 plus tax (4mHz) This must be the best offer available on quality tested dynamic RAM boards.

32K Assembled and tested \$289 plus tax (4mHz)
48K Assembled and tested \$309 plus tax (4mHz)
64K Assembled and tested \$329 plus tax (4mHz)

16K STATIC RAM KIT-S 100 BUSS

**KIT \$179
A&T \$199**



KIT FEATURES

1. Addressable as four separate 4K Blocks
2. ON BOARD BANK SELECT circuitry (Cromemco Standard Allows up to 512K on line)
3. Uses 2114 (450NS) 4K Static Rams
4. ON BOARD SELECTABLE WAIT STATES
5. Double sided PC Board with solder mask and silk screened layout. Gold plated contact fingers
6. All address and data lines fully buffered
7. Kit includes ALL parts and sockets
8. PHANTOM is jumpered to PIN 67
9. LOW POWER under 1.5 amps. TYPICAL from the +8 Volt Bus
10. Blank PC Board can be populated as any multiple of 4K

BLANK PC BOARD W DATA \$55

LOW PROFILE SOCKET SET \$22

SUPPORT IC'S & CAPS \$29

ASSEMBLED & TESTED-ADD \$30


**OUR #1 SELLING
RAM BOARD!**

16K STATIC RAM SS-50 BUSS

PRICE CUT!

**\$199 KIT
A&T \$219**

**FULLY STATIC
AT DYNAMIC
PRICES**

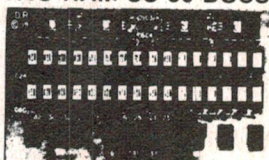

32K STATIC ALSO AVAILABLE

KIT FEATURES

1. Addressable on 16K Boundaries
2. Uses 2114 Static Ram
3. Runs at Full Speed
4. Double sided PC Board Solder mask and silk screened layout Gold fingers
5. All Parts and Sockets included
6. Low Power Under 1.5 Amps Typical


**FOR SWTPC
6800 BUSS!**

BLANK PC BOARD - \$49 COMPLETE SOCKET SET - \$22 SUPPORT IC'S AND CAPS - \$45

ETI 660 THE \$99 COMPUTER!

FEATURES INCLUDE:

Colour capability, operates from optional 9 V plugpack; 1K memory expandable to 3K on-board; single-board construction; cassette interface; audio output; simple to program (uses Chip-8)
Expansion projects coming up include ASCII keyboard, light pen, games software, etc.
Starter Kit (1K RAM, 88W Video) \$99.00
9 V, 1 amp plug pack to suit \$12.50
Colour video option \$13.50
RAM Expansion (add to PCB) \$16.00

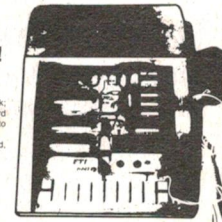

ETI636 7 SLOT MOTHERBOARD WITH ACTIVE TERMINATION

Kit of Parts \$89.00. Assembled and tested \$115.00, inc tax.
RITRON COMPUTER GRADE POWER SUPPLY: +5V Reg. 10A, ± 16V Unreg. Kit of parts \$89.90 inc tax A&T \$109.00 inc tax
Write for list of other power supplies. Tax free prices also available.

SINGLE BOARD COMPUTER KIT NOW ONLY \$499

Including tax (\$435 tax exempt)

Also available: Blank PCB's with Roms \$275 + Tax.
Assembled & Tested \$559 + Tax.

THE FERGUSON PROJECT: Three years in the works, and maybe too good to be true. A tribute to hard headed, no compromise, high performance, American engineering! The Big Board gives you all the most needed computing features on one board at a very reasonable cost. The Big Board was designed from scratch to run the latest version of CP/M*. Just imagine all the off-the-shelf software that can be run on the Big Board without any modifications needed! Take a Big Board, add a couple of 8 inch disc drives, power supply, and an enclosure, and you have a total Business System for about 1/3 the cost you might expect to pay.

FEATURES: (Remember, all this on one board!)

64K RAM

Uses industry standard 4116 RAM'S. All 64K is available to the user, our VIDEO and EPROM sections do not make holes in system RAM. Also, very special care was taken in the RAM array PC layout to eliminate potential noise and glitches.

Z-80 CPU

Running at 2.5 MHZ. Handles all 4116 RAM refresh and supports Mode 2 INTERRUPTS. Fully buffered and runs 8080 software

SERIAL I/O (OPTIONAL)

Full 2 channels using the Z80 SIO and the SMC 8116 Baud Rate Generator. FULL RS232! For synchronous or asynchronous communication. In synchronous mode, the clocks can be transmitted or received by a modem. Both channels can be set up for either data-communication or data-terminals. Supports mode 2 Int. Price for all parts and connectors: **\$65**

BASIC I/O

Consists of a separate parallel port (Z80 PIO) for use with an ASCII encoded keyboard for input. Output would be on the 80 x 24 Video Display.

REAL TIME CLOCK (OPTIONAL)

Uses Z-80 CTC. Can be configured as a Counter on Real Time Clock. Set of all parts: **\$19**

24 x 80 CHARACTER VIDEO

With a crisp, flicker-free display that looks extremely sharp even on small monitors. Hardware scroll and full cursor control. Composite video or split video and sync. Character set is supplied on a 2716 style ROM, making customized fonts easy. Sync pulses can be any desired length or polarity. Video may be inverted or true.

FLOPPY DISC CONTROLLER

Uses WD1771 controller chip with a TTL Data Separator for enhanced reliability. IBM 3740 compatible. Supports up to four 8 inch disc drives. Directly compatible with standard Shugart drives such as the SA800 or SA801. Drives can be configured for remote AC off-on. Runs CP/M* 2.2.

FOUR PORT PARALLEL I/O (OPTIONAL)

Uses Z-80 PIO. Full 16 bits, fully buffered, bi-directional. User/selectable hand shake polarity. Set of all parts and connectors for parallel I/O. **\$29**

PFM 3.0 2K SYSTEM MONITOR

The real power of the Big Board lies in its PFM 3.0 on board monitor. PFM commands include: Dump Memory, Boot CP/M*, Copy, Examine, Fill Memory, Test Memory, Go To, Read and Write I/O Ports, Disc Read (Drive, Track, Sector), and Search. PFM occupies one of the four 2716 EPROM locations provided. It does not occupy any of the 64K of system RAM!

Bankcard
Mail Order
Welcome

ETI 9/82/4

Please debit my Bankcard.
Bankcard No. _____
Expiry Date _____
Name _____
Signature _____

General enquiries (03) 489-8131. Mail order enquiries (03) 481-1436. Ritronics Wholesale (03) 489-7099. (Tax Exempt Enquiries)

Prices subject to change without notice. Send 60¢ and SAE for free Price lists. MAIL ORDERS PO BOX 235, NORTHCOTE, Vic. 3070. Minimum pack and post \$5.00. Telex AA38897.

PLEASE WRITE OR RING FOR THE BEST POSSIBLE PRICES ON DISC DRIVES, PRINTERS AND OTHER COMPUTER COMPONENTS.

ETI 8/82/4

MPI Hi-D Mini Drives

freedom
of choice

Our
way..

.. or theirs

Professional, push-button disk eject, or industry standard flip-front... Either way, MPI builds the quality in. Head load for media protection, 5mSec track-to-track and a choice between 48, 96 and 100TPI, single or double sided 5¼" Floppy Drives.

TRUE FREEDOM OF CHOICE

Authorised Dealers:

Sydney: (02) E&M Electronics 51 5880. Applied Technology 487 2711. QT Computers 29 5599. Micro Repair 747 1061. Computer Components 868 3614. **Wollongong:** (042) Macelec 29 1455. **Brisbane:** (07) Baltec 36 5183. **A.C.T.:** (062) Ortex 80 5283. Boulevard 48 5411. **Perth:** (09) Micro Controls 445 2544. Electronic Systems 335 7313. **Adelaide:** (08) DC Electronics 223 6946. Micro '80 211 7244. **Melbourne:** (03) Stewart Electronics 543 3733. Ellistronics 602 3282. Ritronics 489 8131. Pennywise Peripherals 82 2389. Deforest Software 877 6946. Comp Soft 428 5269. **Tasmania:** Coastal Computers (004) 31 3259.

daneva australia pty ltd.

66 Bay Road, Sandringham, Vic., 3191. Ph: 598 5622. Telex: AA34439


SAWTRON KG103 SERIES

VHF & UHF HANDY
TRANSCEIVERS

THE SAWTRON KG 103
SERIES FEATURES:-

- THE LATEST THICK FILM HYBRID I.C. TECHNOLOGY.
- MODULAR CONSTRUCTION TECHNIQUES.
- EXCELLENT SENSITIVITY, SELECTIVITY AND BLOCKING.
- RUGGED CONSTRUCTION.

PERFORMANCE AT A
REALISTIC PRICE.

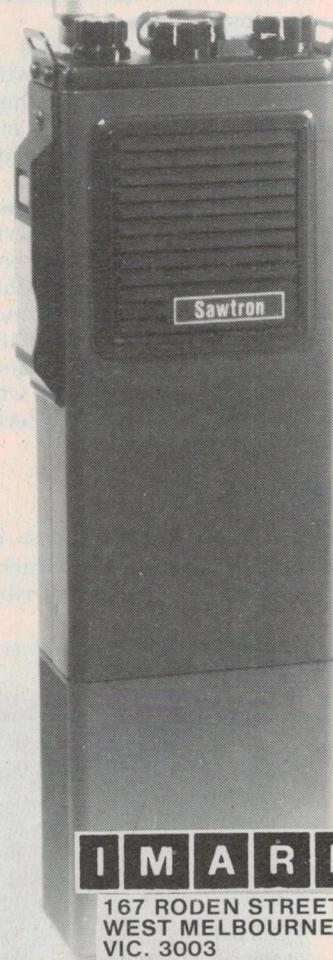

I M A R K

167 RODEN STREET,
WEST MELBOURNE.
VIC. 3003
PHONE (03) 329 5433.
TELEX AA37753

RS232 serial interface troubleshooter

Making a 'standard' RS232 interface work can be a nightmare. 'Standards' notwithstanding, you can regain lost sleep with this troubleshooting unit.

Graham Wideman

IN LAST MONTH'S ETI we explained how computer serial interfaces of the RS232 type are supposed to work, and why they frequently won't. This month we present the design and construction details of a test unit which solves most of these problems. You may wish to build it as described here, or simply borrow the principles to troubleshoot interfaces using other instruments.

The troubleshooter provides the capability to patch together any wiring arrangement, and to monitor what is happening on each wire. In this much it parallels the better commercially-available RS232 'problem solvers'.

However, it also includes an apparatus for determining exactly which interface wires are outputs, inputs, not connected, or shorted, thereby making possible a complete picture of a totally unknown interface. This is extremely useful if the equipment in question has no manual, or as is more likely, has a manual which leaves the subject of the RS232 interface completely ambiguous.

Patching board

The heart of the troubleshooter is a breadboard patching block which is wired permanently to a pair of ribbon

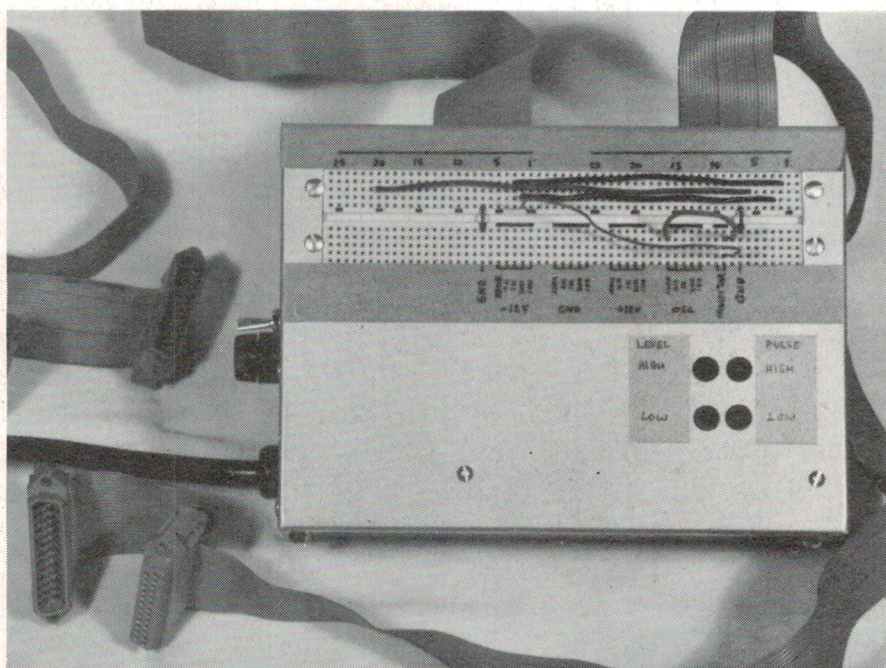


Figure 1. The RS232 troubleshooter.

cables, each cable having attached to it both male and female DB25 connectors of the 'insulation displacement' squashed-on variety. After peeling the adhesive plastic backing off the breadboard block

(and cleaning it up a bit), the individual conductors of the ribbon cable are soldered to the *underside* of the rows of contacts in the breadboard, as shown in the photo of Figure 2, and detailed in the diagram of Figure 3.

This simple device already gives two capabilities, as shown in Figure 4. First, both cables can be attached, one to each of the pieces of equipment which are to be interfaced together. Having both a male and female connector on each cable ensures that plugging in will be no problem. Then the particular pin-to-pin wiring can quickly be tried out using jumper wires on the tester's breadboard patching area, before a permanent cable is made up.

The second way to use the device as so far described, is for 'tapping into' an existing interface arrangement which is now perhaps malfunctioning. Suppose

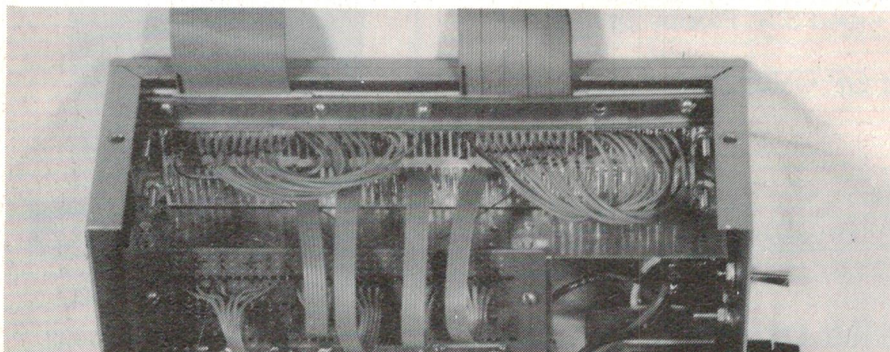


Figure 2. Closer view of breadboard area used for patching the troubleshooter's two DB25-equipped ribbon cables, and for connection to the unit's signal monitor and test signals.

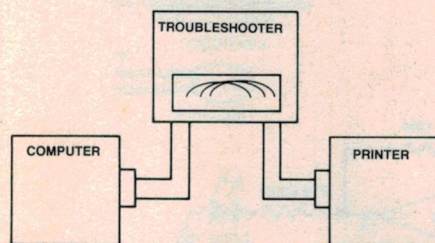


Figure 4a. Using the troubleshooter's patching area to rig new trial cable before making permanent version.

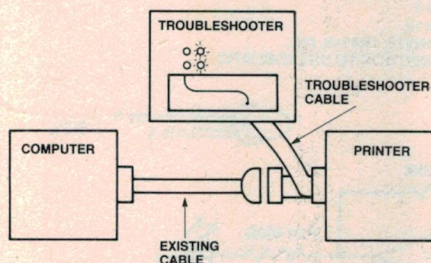


Figure 4b. Using just one ribbon cable, the troubleshooter provides a convenient way to tap into and monitor the signals on a 'supposed to be working' RS232 hookup.

the 'existing system' is a computer talking to a printer. Simply unplug one end of the computer-to-printer cable (let's say the printer end), and plug it into one of the two connectors (male or female as appropriate) on one of the troubleshooter's ribbons. Plug the remaining connector on the *same* ribbon into the receptacle on the printer. Now the short length of ribbon between male and female DB25s carries the connection from computer to printer, and in addition this ribbon brings out all 25 lines to the breadboard where they may be conveniently monitored.

Signal monitor

In order to monitor the signals on an RS232 line it is possible to get away with simply a LED with a resistor in series. However this loads the line, possibly changing the conditions you were trying to monitor. Additionally, you would not see any quick pulses of activity which may be important.

Consequently the monitor incorporated in this tester has been designed to address these two problems. Four LED are used, two to indicate a steady high or low level, while the other two flash on for about a half second in response to a positive or negative pulse. The level LEDs respond only to valid high or low signals; a voltage in the middle (around zero), or an open line will cause neither LED to illuminate. The LEDs are powered from a built-in mains power supply, and the RS232 line is monitored via high impedance buffers, so as not to disturb it.

(It should be remembered here that the RS232 line levels are -3 V to -12 V for a 'low' representing a data '1', and +3 V to +12 V for a 'high' representing a 'zero'. With no data the line sits at low.)

The monitor input is soldered to the underside of a contact strip on the breadboard (actually two strips, in case of wear), and thus may be patched to any other contact as desired for observation of the signals there. ►

Test Signals		Ribbon		From DB25s	
		00000	00000	DB25	
		00000	00000	24	25 DB25 Cable A
		00000	00000	22	24
		00000	00000	20	23
		00000	00000	18	22
		00000	00000	16	21
		00000	00000	14	20
		00000	00000	12	19
		00000	00000	10	18
		00000	00000	8	17
		00000	00000	6	16
		00000	00000	4	15
		00000	00000	2	14
		00000	00000	25	13
		00000	00000	23	12
		00000	00000	21	11
		00000	00000	19	10
		00000	00000	17	9
		00000	00000	15	8
Ground		00000	00000	13	7
		00000	00000	11	6
-12V	100k	00000	00000	9	5
"	4k	00000	00000	7	4
"	1k	00000	00000	5	3
"	300	00000	00000	3	2
"	100	00000	00000	1	1 DB25 Cable A
		00000	00000		
Ground	100k	00000	00000		
"	4k	00000	00000		
"	1k	00000	00000		
"	300	00000	00000		
"	100	00000	00000		
		00000	00000	24	25 DB25 Cable B
		00000	00000	22	24
+12V	100k	00000	00000	20	23
"	4k	00000	00000	18	22
"	1k	00000	00000	16	21
"	300	00000	00000	14	20
"	100	00000	00000	12	19
		00000	00000	10	18
		00000	00000	8	17
Osc.	100k	00000	00000	6	16
"	4k	00000	00000	4	15
"	1k	00000	00000	2	14
"	300	00000	00000	25	13
"	100	00000	00000	23	12
		00000	00000	21	11
Monitor		00000	00000	19	10
"		00000	00000	17	9
		00000	00000	15	8
Ground		00000	00000	13	7
		00000	00000	11	6
		00000	00000	9	5
		00000	00000	7	4
		00000	00000	5	3
		00000	00000	3	2
		00000	00000	1	1 DB25 Cable B
		00000	00000		

Figure 3. Diagram showing one possible arrangement for the breadboard connection area. Note that the DB25 ribbon cables occupy one 'side' of the board, and the test monitor and signals occupy the other. Opposite each ribbon's pin number 7 is a ground connection, across which would normally be installed a small inductor.

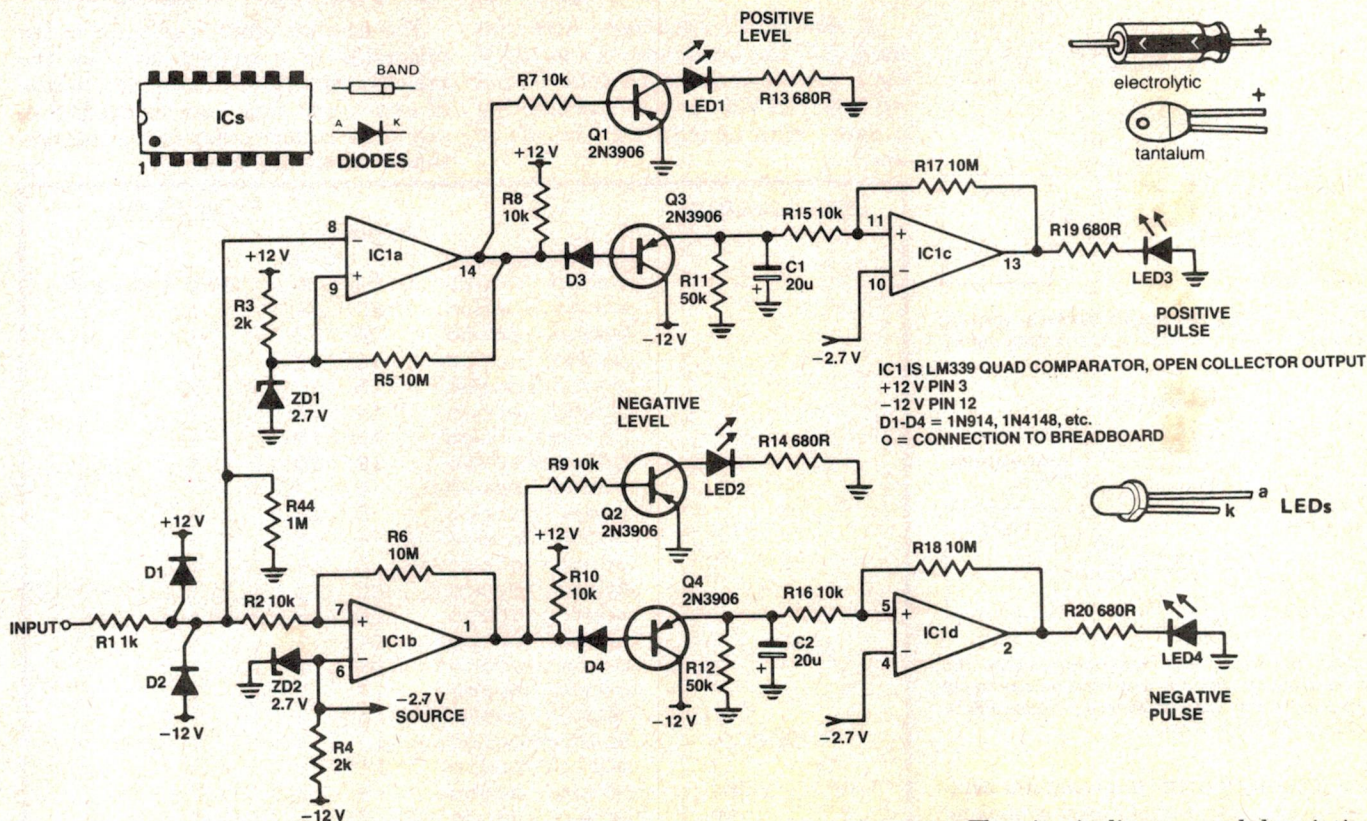


Figure 5. Circuit diagram of monitor section.

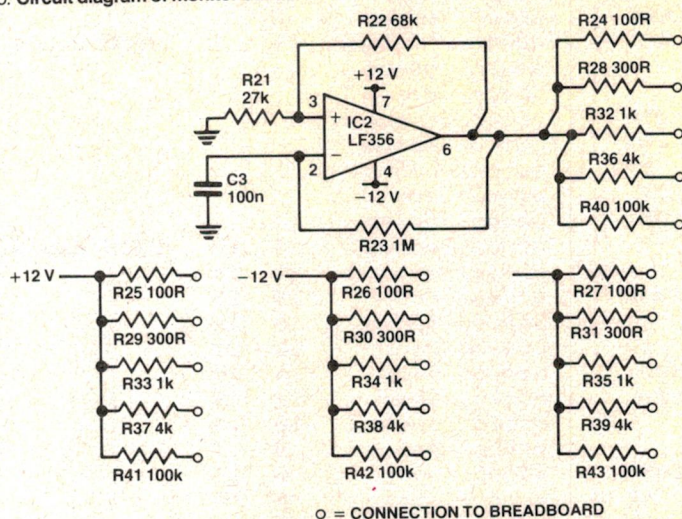


Figure 6. Circuit of test oscillator, and other test levels.

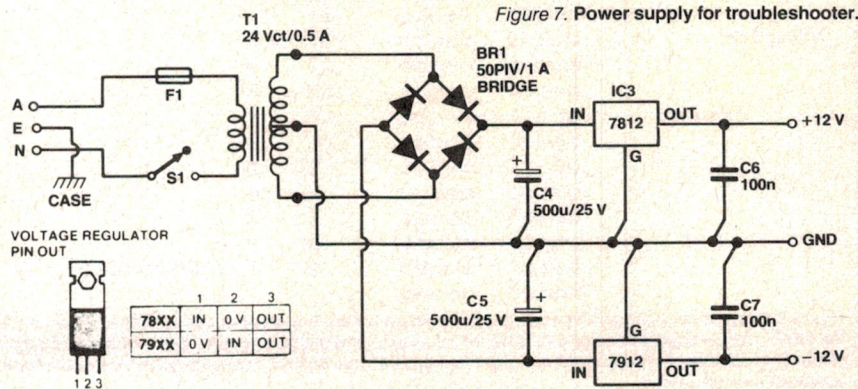


Figure 7. Power supply for troubleshooter.

The circuit diagram and description for the monitor, the test oscillator to be described, along with the power supply, are to be found in Figures 5 to 7.

Generated signals

Of immediately obvious use are the 'high' and 'low' signals provided. These may be used to apply 'halt' or 'go' signals to handshaking lines. Additionally there is built-in a square-wave generator which continuously oscillates between high and low conditions at a rate of approximately five times per second.

Each of these signals, along with ground, is supplied to contacts on the breadboard via a selection of resistors, from 100 ohms to 100k ohms. The usefulness of this arrangement may not be immediately apparent, and for explanation I must describe the electronic circuits which transmit or receive on an RS232 line.

How it works

The monitor

The schematics for the troubleshooter's main monitor, test oscillator and power supply are to be seen in Figures 5 to 7.

Components R1-D1-D2 prevent the input signal from causing damage should it happen to exceed the troubleshooter's power rail limits. From there the input signal is routed to two very similar 'channels', one concerned with 'high' levels and pulses, the other with 'low' levels and pulses.

Looking then at the positive channel, the input signal arrives at the negative input of comparator IC1a, where it is compared to a reference of about 2V7 (which is set by ZD1 at the positive input of IC1a). Supposing that the input signal exceeds 2V7, then IC1a's output is low, turning on Q1 via R7, and illuminating LED1 to indicate a 'high level'.

At the same time, the low level (about -10 V) at the output of IC1a turns on Q3, quickly charging C1 'down' to about -9 V. IC1c sees this voltage and compares it to -2V7, sees that it is lower and lowers its own output illuminating LED3 to indicate a 'high pulse'.

If the monitor input now drops below 2V7, IC1a's output will go high, turning off Q1 and the 'high-level' LED1, and also Q3. However the 'high pulse' LED3 will remain on for a short while (about a half second) as C1 is charged up past the 2V7 point by R11. Notice that this delayed LED3 action would have occurred even if LED1 had been on for only an

invisibly short length of time. Hence LED3 makes visible short pulses which cannot be seen by simply watching the level, whether on the troubleshooter's level LEDs, or even with an oscilloscope.

The negative channel works similarly, the only change being to swap the positive and negative inputs of the input comparator.

Test oscillator

As we shall see, IC2's output must sit in either high (about +10 V) or low (about -10 V) states. Let us assume it is initially low, and that C3 starts out uncharged, so that there is 0 V at the op-amp's negative input.

Since the op-amp output is at say -10 V, the positive input will be at approximately -3 V, established by the R21-R22 voltage divider. Remembering that we assumed the negative input to be at 0 V, the 'low' output will remain temporarily unchanged.

However, the low output will charge C3 via R23 downwards. After a while the op-amp negative input will be less than its positive input (at -3 V), and thus the output will change states to +10 V. When this happens the voltage at the positive input changes, of course, to +3 V, maintaining this state of affairs.

Again we must wait for C3 to be charged via R23, this time up to +3 V. You should be able to see that this oscillating action will continue, and that the period is the time taken for C3 to charge from -3 V to +3 V, then back down to -3 V, when R23 is pulled up to +10 V and then down to -10 V respectively.

The values given provide a frequency of about 5 Hz, quite suitable for this testing purpose.

The oscillator output is delivered to the breadboard area via various values of resistor, as described in the text.

Of drivers and receivers

For various reasons, special purpose buffers are used to send signals and

receive signals on an RS232 line. These are called 'drivers' and 'receivers', and are exemplified by the National LM1488 and 1489 respectively. Figures 8 and 9 show a simplified view of how the driver output and receiver input look electrically.

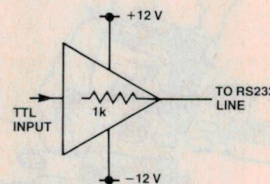


Figure 8. Simplified view of an RS232 'driver' output.

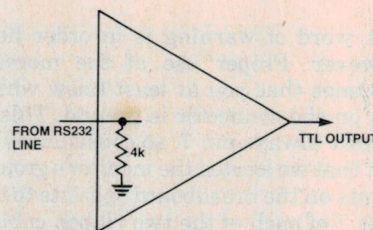


Figure 9. An RS232 'receiver' looks like this electrically.

The points to notice are that a receiver input looks like a (approximately) 4k resistor to ground. An operating driver output looks like a (approximately) 500 ohm resistor pulling up to 12 V (nominally), or pulling down to -12 V, according to its state.

Knowing these facts it is apparent that if a high or low signal is applied through a resistor to a receiver input or driver output, the resulting signal on the line (which can be monitored) will be high, low or in-between depending upon the value of resistor used.

Therefore, when looking at an unknown line, by applying the test oscillator's output via each resistor in turn, it is quickly possible to tell what that line does. The chart in Figure 10 details this.

Parts List

Resistors

R1	1k
R2	10k
R3, 4	2k
R5, 6, 17, 18	10M
R7, 8, 9, 10, 15, 16	10k
R11, 12	50k
R13, 14, 19, 20	680
R21	27k
R22	68k
R23	1M
R24, 25, 26, 27	100
R28, 29, 30, 31	300
R32, 33, 34, 35	1k
R36, 37, 38, 39	4k
R40, 41, 42, 43	100k
R44	1M

Capacitors

C1, 2	20u/20 V electrolytic
C3, 6, 7	0u1 tantalum s
C4, 5	500u/25 V electrolytic

Diodes

D1, 2, 3, 4	1N914 or 1N4148 etc
ZD1, 2	2V7 small zener diode
BR1	Bridge rectifier, 50 PIV/1 A
LED1, 2, 3, 4	LEDs of your choice of colour

Transistors

Q1, 2, 3, 4	2N3906
-------------	--------

Integrated circuits

IC1	LM339
IC2	LF356A
IC3	7812
IC4	7912

Transformer

T1	240 V primary, 12-0-12/500 mA secondary
----	---

Miscellaneous

Breadboard, case, fuse and holder, switch for power, power lead and plug etc.

Oscillator Signal via Resistor (ohms)

Condition	100k	4k	1k	300	100
Open	HL	HL	HL	HL	HL
Receiver Input	None	HL	HL	HL	HL
Driver Out-Low	L	L	L	FL/HL	HL
Driver Out-High	H	H	H	FH/HL	HL
Short to Ground	None	None	None	None	None
Short to +12 V	H	H	H	H	H
Short to -12 V	L	L	L	L	L

Charts shows the Level LEDs (not 'pulse' LEDs) activated in various cases.

H = High; L = Low; None = neither LED on; HL = alternating H and L; FL = Flashing Low; FH = Flashing High

Figure 10. Chart showing how to test an unknown RS232 line, and the monitor's indications under various conditions.



A word of warning is in order here however. Proper use of the monitor assumes that you at least know which pin on the connector is ground. This is almost always pin 7, so consistently in fact that we located the monitor's ground points on the breadboard opposite to the pins 7 of each of the two ribbon cables, and permanently left a small jumper installed at these two locations (see Figure 3). However, there are lurking about some units which don't abide by this standard. The only thing you can do about this (if you are documentationless and suspect this problem) is to open the case and actually trace the unit's circuit-board ground and see what DB25 pin it goes to.

Construction notes

The construction is not too critical. As can be seen the prototype version was built using Veroboard. One plan which is extremely useful to follow is to make a simple frame assembly like the one shown in Figure 11, which serves two purposes.

First it includes a flat clamp to grip the two ribbon cables (liberal use of double-sided wall-tile sponge adhesive tape also helps). Secondly, it keeps together the circuit board and the breadboard. In both these respects it makes wiring to the breadboard easier, and virtually eliminates any problems of wire breakage when the various parts are moved about during construction or testing of the project. As the photos show, the entire guts of the prototype can be removed in one piece, connected to the case only by the leads to the PSU.

Another hint: **DON'T FORGET** when soldering the ribbons to the breadboard

that the numbering of the DB25 pins is *not* the same sequence as the ribbon cable conductors. This is shown in Figure 3.

Improvements

Although our troubleshooter has proved tremendously useful, I cannot claim that our prototype is the last word. In fact, I feel that if done again we would add several extra LEDs as simple on-off high-low indicators along with the existing level plus pulse monitor, so as to keep an eye on several lines at once. You may wish to adopt this idea in your unit.


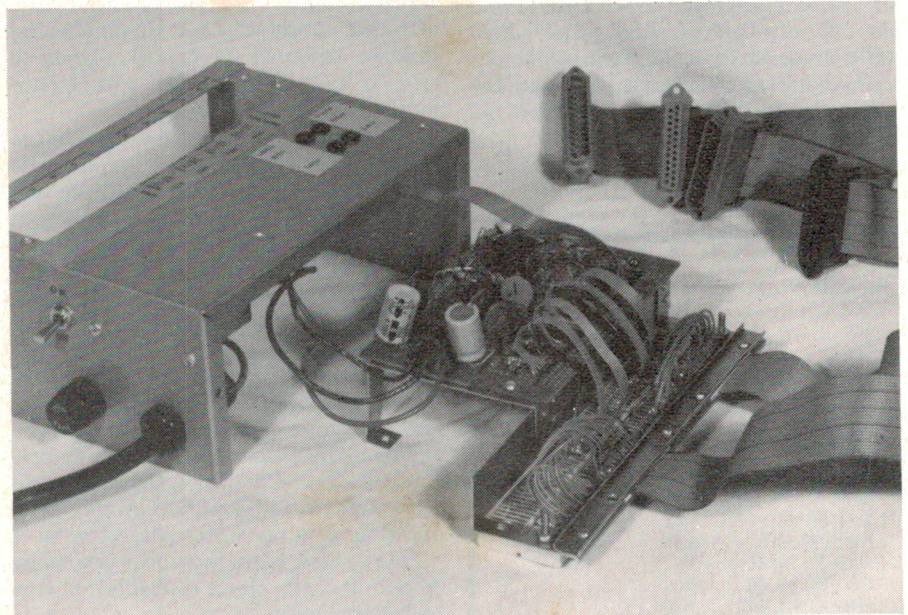


Figure 11. When constructing a unit such as this, where there are a lot of wires hanging around, it's helpful to use brackets and cable clamps like the ones in this photo. They prevent undue strain on soldered connections, improving reliability, and enable the circuitry to come out of the box in one piece, more or less, for testing purposes during construction, or later if the unit needs repair.

NEED A PROTOTYPE?

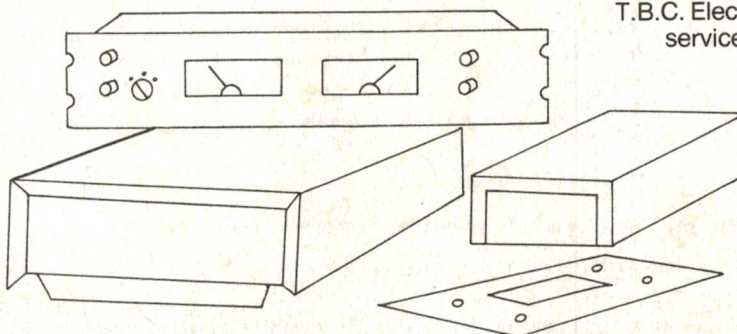


T.B.C. Electronic Metal Fabricators can offer you a complete service sheet metal fabrication. Fitting and turning, PCB assembly and wiring.

We can provide a fast efficient service for prototypes and or small production runs at a realistic cost. Contact us and discuss your requirements. Write to:

T.B.C. ELECTRONIC METAL FABRICATORS

P.O. Box 193 Hornsby NSW. Phone: (02) 848 8777

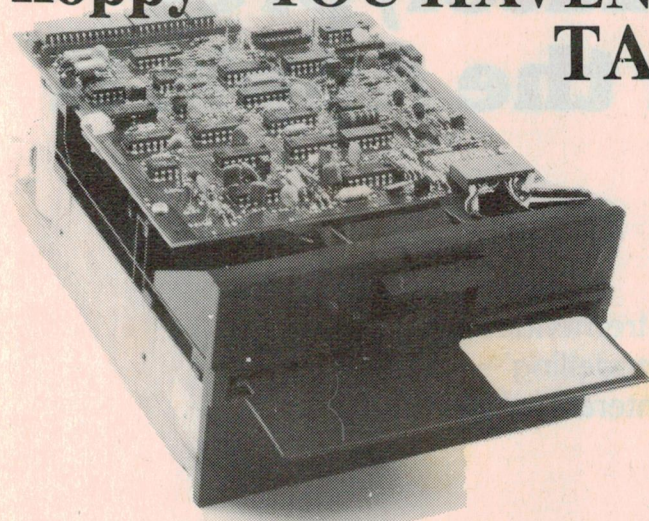If you're still looking for the best 5¼" floppy—YOU HAVEN'T FOUND US YET!! TANDON TM100—S.



Australian Representative

AE ADAPTIVE
ELECTRONICS P/L

418 St. Kilda Road, Melbourne, 3004.
Ph: (03) 267 6800 (4 lines).
Telex: AA32565

Tandon's TM-100 family of mini-floppies offer the absolute highest storage capabilities of any 5¼" high-speed, random access disk drive available in two single head and two double head models, single and double density.

Unsurpassed Storage Capacity - Up to an incredible 1000K bytes information on 160 tracks. Recording density is 5877 BPI.

Advanced Dual-Head Design - Tandom Magnetics has for years been the leading designer and supplier of read/write heads to most major disk drive manufacturers.

Increased Throughput - Tandon's TM-100 have a track-to-track access time of only 5 milliseconds (an incredible 3 milliseconds double track density.)

Proven Reliability - Designed for total reliability, as demonstrated by more than 50,000 production models in operation.

MICROBASE (09) 328-9308
CISA (02) 29-1599
COMPAK (03) 592-6285
TOOWOOMBA (076) 32-7542

RADIO REMOTE CONTROL

CUSTOM MADE HIGH
SECURITY LOW POWER
RADIO CONTROL UNITS

IDEAL FOR RADIO REMOTE
SWITCHING OF A MYRIAD OF
MECHANICAL DEVICES
INCLUDING:

- ☆ DOORS AND GATES
- ☆ LIGHTS ☆ CAMERAS
- ☆ SLIPWAYS ☆ VEHICLES

A FULL DIGITAL SYSTEM,
BINARY CODED FOR
MAXIMUM SECURITY WITH
SWITCH SELECTABLE
CODING.

FOR DETAILS CONTACT:

Silverstone

ELECTRONICS

6/2 SCHOFIELD ST., RIVERWOOD
NSW 2210. PH: (02) 533 3517

APPLE ADD ONS FROM PROMETHEUS

VERSACARD \$236

VERSABOX \$300

AUTO DOC \$146

16K RAM \$120

128K RAM \$609

PARALLEL CARD

C/W GRAPHICS \$146

PARALLEL CARD \$98

PLUS TAX IF APPLICABLE

We have many more in stock
write or call for further
information.

Dealer enquiries welcome.
Australian Distributor.

COMPUTER CITY

600 OLD CLEVELAND RD.,
CAMP HILL 4152 BRISBANE
TELEPHONE: (07) 398 6759
(07) 398 6571

**Techni Parts is under
new management and
a new name!
Now we stock more.**

**SPECIAL —
INTERSIL ICL 7106 D.V.M. KIT
ONLY \$28**

FAIRCHILD - SEMI CONDUCTORS
INTERSIL - SEMI CONDUCTORS
SIEMENS - SEMI CONDUCTORS
HITACHI - OSCILLOSCOPES
ARLEC - TRANSFORMERS & OTHER
ELECTRICAL PRODUCTS


See our range of:
MULTI METERS - CROs - HANDTOOLS
SOLDERING EQUIPMENT
A WIDE RANGE OF COMPONENTS FOR
THE ENTHUSIAST
HELPFUL ADVICE & RANGE OF DATA BOOKS

SHOP 3.
DRIVE-IN SHOPPING CENTRE
95 LATROBE TERRACE
P.O. BOX 287
PADDINGTON QLD. 4064
TEL: 369 1474



HOURS 8.30-5.00
LATE NIGHT THURSDAY
& SATURDAY MORNING.

STUDENT DISCOUNTS
MAIL ORDERS
\$2.50 POST & PACKING

 **eco technics**

'Prey' — A predator/prey simulation for the Apple II

by Phil Cohen

The plotting capabilities of the Apple II are tremendous. Phil Cohen has used them for a bit of 'modelling' — simulating the way that different species interact when one is eating the other!

SIMULATION IS ONE of the most interesting abilities of the computer. Using just a machine and a little bit of imagination, you can 'create' whole worlds.

The program that I've developed makes use of the high-resolution graphics capabilities of the Apple — but I'm sure that anyone enthusiastic enough can modify it to run on almost any machine.

What it does is to build a 'model' of a little piece of territory. On this territory, there are two species of animal. They are called 'predator' and 'prey', and it is the delight of the predator species to catch and eat the prey.

Now the prey eats grass — and this grass grows in the territory with a particular yield per unit area (i.e. for any given square meter of territory, a certain number of kilograms of grass will grow each year). . . and so on.


What the program does (and I'll explain its operation in detail) is to build up a set of equations which tell the computer what the relationship between, say, the amount of grass and the birth rate of the prey is. So the computer can then tell you the answer to questions like 'What will happen if the grass yield per unit metre falls by half?' (this could be caused by blight or drought).

What the computer does is to produce a graph which shows, over a ten year period, what the population level of both the prey and the predators (shown as a dotted line) will be. The program allows you to alter a number of things at the start of the run, and will also allow you to put in a 'crisis' — a sudden change in one of the variables — at any time during the ten years. ▶



AUSTRALIAN AMP

LOW-PROFILE DIP SOCKETS

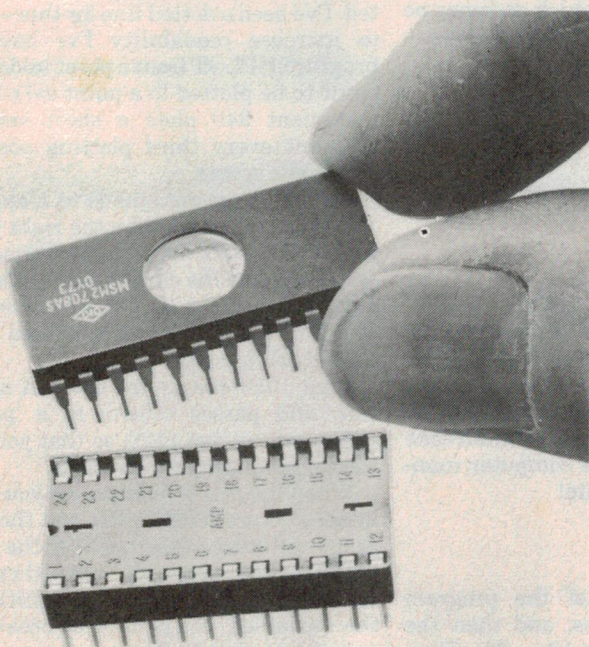

DIPLOMATE

Features

- Low Profile
- Dual wiping contacts
- Large target area, with tapered lead-in ramps
- Designed for automatic machine insertion—
- Tin or gold plated phosphor bronze or beryllium copper contacts
- Closed bottom
- Visual polarization
- Designed to meet EIA RS-415
- Stackable end-to-end and side-to-side for high board density.

Technical information available on request.

SOANAR

Soanar Electronics Pty Ltd

30-32 Lexton Road, Box Hill, Vic., 3128, Australia.

VICTORIA: 840 1222

QUEENSLAND: 52 1131

N.S.W. 789 6733

WEST. AUST. 381 9522

STH. AUST. 42 8918

TASMANIA: 31 6533



IMAGINEERING

"your software professionals"

Presents

Screenwriter II

A complete word processing system for Apple II Computer

Screenwriter II offers you a 70 column screen, Upper/Lower case, software based keyboard buffer and print spooling — which allows you to do your editing while printing. All this with no additional hardware required. Screenwriter II runs on any 48k Apple II with Dos 3.3.

FEATURES

- Global Search & Replace
- Insert & Image Modes
- Macro Capabilities
- Proportional Spacing
- Text Move
- Supports Additional Disk Drives
- Hyphenation
- Form Letter Capabilities
- Complete Editing & Printing Functions
- Generation of Indices

ALL THIS FOR ONLY \$152.00 (recommended retail). Fully compatible with Digitek Expander Cards and the General Manager database program.

ON RELEASE NOW

Available from your local Apple Dealer and our
dealer of the month: Computer Programs Machines
Paul Campbell: (08) 21-2666
Imagineering: (02) 358-3011

The model

There are a number of variables set up at the start of the run.

Territory size

This is the amount of land on which both the predators and the prey live. Program variable: TR.

Prey population

The total number of prey on the territory. Program variable: P1.

Predator population

The total number of predators. Program variable: P2.

Food yield per unit area

This is the amount of grass (prey food) grown per square metre of the territory. Program variable: YD.

Prey natural life span

This is the number of years that one of the prey species will live if it doesn't get eaten. Program variable: L1.

Predator natural life span

This is the life span of each member of the predator species. Program variable: L2.

Prey cull losses

Basically, this is a measure of how many of the prey are killed by man. Program variable: CU.

Of these variables, only the predator and prey population levels will be changed by the program in the normal course of events. (Any of them can be changed by using the 'crisis' input — but I'll come to that later.)

The program, given this information, will go on to calculate the state of play at the end of each period (one period representing roughly two weeks). It does this by applying a number of equations — I'll go through these one by one.

Number of kills

This is the number of prey that is killed and eaten by the predators. The program calculates this by calculating the probability that one of each species will be at the same spot at the same time. So the number of kills is equal to the predator population times the prey population divided by the territory size. The mathematicians amongst you will notice that this is not actually the probability, and the naturalists will notice that there are a few other factors to be considered — but this is only a rough model.

Food available

The program multiplies the territory size by the yield and comes up with a total amount of grass grown in the period. No attempt has been made to properly quantify any of the variables in this model.

Number of prey births

This is calculated by taking the amount of grass, dividing by the number of prey, and then limiting it to 25% of the original population.

Number of predator births

Similarly, the number of predator births is proportional to the amount of food for that species (in their case, the number of prey killed) — and again, it is limited to 25% of the original population.

Number of natural deaths

The number of births is subtracted from the total population (which assumes no infant mortality) and the whole thing is divided by the life span.

Predator and prey populations

Each of the factors (births, deaths, etc) are either added to or subtracted from the original population to give the new populations.

Having finished doing all of the calculations, the program will simply plot the predator and prey populations on the screen, and then start all over again, giving a total of 240 steps in 10 years. To do this sort of thing by hand would take some weeks — but the computer manages it in about a minute!

How it works

The first few lines of the program initialise the variables, and then the screen is cleared (lines 10 — 60). Then the program prints out the current state of all of the variables, and asks whether you want to alter any of them before the run (lines 70 — 360).

You can alter any or all of them at this stage, and the program will print out the current state each time. If you enter a '9', the program takes this as a signal that you are satisfied with the initial state of the variables, and goes on to the next part.

This asks you for the 'crisis' input — that is, a sudden change in one of the variables at a particular point in the run. So for example, you can cause the prey population to drop to half its usual value at year 5 (this could be due to disease, etc).

Line 410 translates the 'crisis' year into a position across the screen.

Line 470 sets the machine into HGR mode — that is, with most of the screen in high-resolution graphics mode, and with a small 'text window' at the bottom, for displaying messages.

The next few lines (490 — 530) put the base line onto the graph. This represents zero population in either species, and has breaks in it to show the years (10 in all).

Then the calculations start in earnest, as I listed above, at lines 580 — 830.

By the time the program reaches line 850, the values for P1 (prey population) and P2 (predator population) have been worked out, and are ready for plotting.

The next section to line 900 plots the prey population as a solid line. The variable OY holds the last value plotted, and HPLLOT is used to ensure that the line really is solid — if I had just put the point onto the screen, then sudden changes would cause a break in the plot. This way, it's solid all the way.

Then the predator population is plotted. I've used a dotted line for this — and to increase readability I've had the program HPLLOT from a point under the point to be plotted to a point over it. So statement 940 plots a short vertical segment every third plotting position across the screen.

Now all that remains is to make the 'crisis' change if we're in the right year. Line 960 checks the year, and lines 980 — 1070 make the change, and print the fact on the screen (in the text window). The previous value of the altered variable is printed too.

Line 1080 checks for the end of the run, and passes control to a 'pause' statement at line 1120, so that you can have a good look at the results.

When the plot is finished, all you have to do is to press RETURN and the program will start again, but with the variables set the way they were when the run finished. If you want to re-initialise the variables, you'll have to break the program and re-RUN it.

Sample runs


Figure 1 shows a sample run. I left the variables set up the way they were initialised, and put in a change in predator population at year 3. In year 3, the predator population changed from 75 to 150. This could be due, for example, to problems in other areas forcing an influx of predators all of a sudden.

```
1 SIZE OF TERRITORY          500
2 PREY POPULATION            100
3 PREDATOR POPULATION        75
4 FOOD YIELD PER UNIT AREA   15
5 PREY NATURAL LIFE SPAN     10
6 PREDATOR NATURAL LIFE SPAN 20
7 PREY CULL LOSSES            1

WHICH WOULD YOU LIKE
TO ALTER (9 = FINISHED) ? 9

YEAR FOR CHANGE (0 - 10) ? 3
WHICH VARIABLE TO CHANGE (1 - 7) ? 3
VALUE TO BE SET AT YEAR 3 ? 150
```


Figure 1(a). Sample run. Change in predator population at year 3.

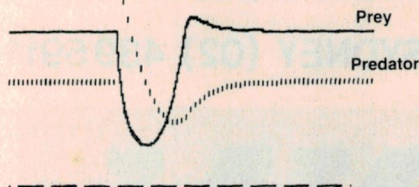

YEAR 3 PRED 75 -> 150

Figure 1(b). Doubling the predator population causes a fast drop in the prey population.

The plot shows the prey population (solid line) and the predator population (dotted line). The change doubles the predator population, which causes a fast drop in the prey population due to increased number of kills. However, as soon as the number of prey starts to drop, starvation of the predators makes their population drop too. In fact, it will drop (at the end of year 5) to below its normal value. This drop in the predator population will cause the prey population to go back up, but its overshoot is limited by food availability, and so it quickly settles down. By the end of the 10 year period of the run, things are back to normal again.

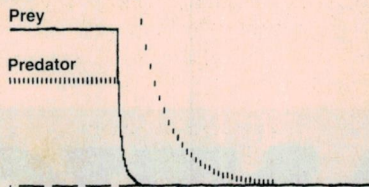


YEAR 3 PRED 75 -> 250

Figure 2. Predator population increased even further.

However, interesting things start to happen when you increase that 'crisis' blow. In Figure 2 I've increased the predator population even further. So far, in fact, that there are enough predators to completely kill out the prey population. Naturally, when there are no prey, the predators die out too.

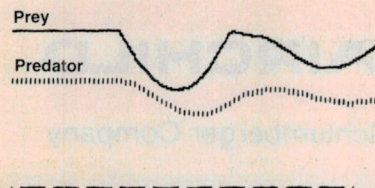An interesting thing happens if you put in a proportion of 'cull' (i.e. killing of the prey at a constant rate, by humans, say). Figure 3 shows this. If the intention of the cull was to reduce the prey population (perhaps to reduce crop losses), then the cullers would be surprised to see that three years after the cull started, the prey population was



YEAR 3 CULL 1 -> 7

Figure 3. Prey population culled.

slightly more than its initial value, due to the dynamic effects of the predator population!

Suggestions for further work

The possibilities of this sort of thing are endless. Naturally, the model I've used here could be extended (one rather obvious extension would be to put names to the two species, and to try to model a real system).

But there are other directions in which the thing can move — what about introducing seasonal variations in birth rate, food yield, hunting capabilities, etc?

There's even the possibility of making the whole thing two-dimensional. Break the territory up into a number of areas, and see what happens when a change is introduced into one area.

'PREY' — SIMULATION FOR THE APPLE II

```

10 REM FIRST, INITIALISE THE VARIABLES TO THEIR STARTING VALUES
20 TR = 300:P1 = 100:P2 = 75:YD = 15
30 L1 = 10:L2 = 20:CU = 1
40 TEXT
50 REM NOW CLEAR THE SCREEN (THE HARD WAY, TO CATER FOR ALL TERMINALS)
60 FOR I = 1 TO 30:PRINT:NEXT I
70 PRINT "1 SIZE OF TERRITORY";TAB(30);TR
80 PRINT
90 PRINT "2 PREY POPULATION";TAB(30);INT(P1)
100 PRINT
110 PRINT "3 PREDATOR POPULATION";TAB(30);INT(P2)
120 PRINT
130 PRINT "4 FOOD YIELD PER UNIT AREA";TAB(30);YD
140 PRINT
150 PRINT "5 PREY NATURAL LIFE SPAN";TAB(30);L1
160 PRINT
170 PRINT "6 PREDATOR NATURAL LIFE SPAN";TAB(30);L2
180 PRINT
190 PRINT "7 PREY CULL LOSSES";TAB(30);CU
200 PRINT:PRINT
210 REM THE NEXT PART OF THE PROGRAM ALLOWS YOU TO CHANGE THE STARTING
220 REM CONDITIONS BY ALTERING ANY OR ALL OF THE VARIABLES
230 PRINT "WHICH WOULD YOU LIKE"
240 INPUT "TO ALTER (9 = FINISHED) ? ";A
250 PRINT
260 ON A GOTO 300,310,320,330,340,350,360,370
270 REM I DIDN'T USE A STRING ARRAY HERE BECAUSE IT WOULD HAVE MADE THE
280 REM REST OF THE PROGRAM DIFFICULT TO READ - ALL OF THE EQUATIONS
290 REM WOULD HAVE BEEN IN TERMS OF ARRAY ELEMENTS
300 INPUT "TERRITORY SIZE ? ";TR:GOTO 60
310 INPUT "PREY POPULATION ? ";P1:GOTO 60
320 INPUT "PREDATOR POPULATION ? ";P2:GOTO 60
330 INPUT "FOOD YIELD PER UNIT AREA ? ";YD:GOTO 60
340 INPUT "PREY NATURAL LIFE SPAN ? ";L1:GOTO 60
350 INPUT "PREDATOR NATURAL LIFE SPAN ? ";L2:GOTO 60
360 INPUT "PREY CULL LOSSES ? ";CU:GOTO 60
370 REM THE NEXT PART OF THE PROGRAM ALLOWS YOU TO 'INJECT' A CHANGE IN
380 REM ANY OF THE VARIABLES AT ANY POINT IN THE RUN
390 INPUT "YEAR FOR CHANGE (0 - 10) ? ";YR
400 REM YX IS THE POSITION ON THE SCREEN WHICH CORRESPONDS TO THAT YEAR
410 YX = INT(24.2 * YR)
420 INPUT "WHICH VARIABLE TO CHANGE (1 - 7) ? ";V%
430 IF V% > 7 OR V% < 1 THEN GOTO 420
440 PRINT "VALUE TO BE SET AT YEAR ";YR;" ";
450 INPUT VL
460 PRINT:PRINT:PRINT
470 HGR
480 REM PUT THE BASE LINE ONTO THE SCREEN (WITH A GAP FOR EACH YEAR)
490 HPLLOT 0,159
500 FOR I = 3 TO 242 STEP 22
510 HPLLOT I - 3,159
520 HPLLOT I + 3,159
530 NEXT I
540 REM X IS THE CURRENT POSITION ACROSS THE SCREEN
550 X = 0
560 REM START GRAPH
570 REM KL IS THE NUMBER OF KILLS MADE BY THE PREDATORS

```

```

580 KL = (P1 * P2) / TR
590 REM FD IS THE AMOUNT OF FOOD AVAILABLE TO THE PREY
600 FD = TR * YD
610 REM THE NEXT STATEMENT ENSURES THAT THERE WILL BE NO BIRTHS IF
620 REM THERE IS NO POPULATION!
630 IF P1 = 0 THEN B1 = 0:GOTO 670
640 B1 = FD / P1
650 REM THE NEXT STATEMENT LIMITS THE BIRTH RATE TO A PERCENTAGE OF THE
660 REM CURRENT POPULATION
670 IF B1 > P1 / 4 THEN B1 = P1 / 4
680 REM THE PREDATOR BIRTH RATE IS PROPORTIONAL TO THE NUMBER OF KILLS
690 B2 = 10 * KL / P2
700 IF B2 > P2 / 4 THEN B2 = P2 / 4
710 REM M1 AND M2 ARE THE NATURAL MORTALITY RATES FOR THE TWO SPECIES
720 M1 = (P1 - B1) / L1
730 M2 = (P2 - B2) / L2
740 REM THE NEW PREY POPULATION IS THE OLD ONE MINUS THE NUMBER OF
750 REM NATURAL DEATHS, MINUS THE NUMBER OF PREDATOR KILLS, PLUS
760 REM THE NUMBER OF BIRTHS, AND MINUS THE AMOUNT OF 'CULL' BY HUMANS
770 P1 = P1 - M1 - KL + B1 - CU
780 REM THE NEW PREDATOR POPULATION IS THE OLD ONE MINUS NATURAL DEATHS
790 REM PLUS BIRTHS
800 P2 = P2 - M2 + B2
810 REM NOW MAKE SURE BOTH FIGURES ARE SENSIBLE
820 IF P1 < 0 THEN P1 = 0
830 IF P2 < 0 THEN P2 = 0
840 REM NOW WORK OUT THE VERTICAL POSITION FOR THE PREY POPULATION PLOT
850 Y = 159 - (.5 * P1)
860 IF Y < 0 THEN Y = 0:IF Y > 159 THEN Y = 159
870 IF X = 0 THEN GOTO 900
880 REM HPLLOT FROM THE LAST POSITION TO THIS ONE
890 HPLLOT X - 1,OY:HPLLOT TO X,Y
900 OY = Y
910 REM NOW DO THE SAME FOR THE PREDATORS
920 Y = 159 - (.8 * P2)
930 REM THE NEXT STATEMENT WILL GIVE A DOTTED LINE FOR THE PREDATORS
940 IF Y > 1 AND Y < 158 AND INT(X / 3) = X / 3 THEN HPLLOT X,Y - 1:HPLLOT
TO X,Y + 1
950 X = X + 1
960 IF X < > YX THEN GOTO 1000
970 REM NOW DO THE CHANGE THAT WAS REQUESTED
980 PRINT "YEAR ";YR;" ";
990 ON V% GOTO 1000,1010,1020,1030,1040,1050,1060
1000 PRINT "TERR";TR:TR = VL:GOTO 1070
1010 PRINT "PREY";INT(P1):P1 = VL:GOTO 1070
1020 PRINT "PRED";INT(P2):P2 = VL:GOTO 1070
1030 PRINT "YIELD";YD:YD = VL:GOTO 1070
1040 PRINT "PREY SPAN";L1:L1 = VL:GOTO 1070
1050 PRINT "PRED SPAN";L2:L2 = VL:GOTO 1070
1060 PRINT "CULL";CU:CU = VL
1070 PRINT "-> ";VL;" ";
1080 IF X < 242 THEN GOTO 560
1090 REM THE NEXT STATEMENT INPUTS A 'DUMMY' VARIABLE TO KEEP THE
1100 REM CURSOR ON THE SCREEN SO THAT YOU CAN VIEW THE FINAL PLOT
1110 REM BEFORE STARTING AGAIN
1120 INPUT " ";A#
1130 GOTO 40

```


FAIRCHILD


A Schlumberger Company

MELBOURNE (03) 877 5444

SYDNEY (02) 439 5911

OPERATIONAL AMPLIFIERS

DEVICE	DESCRIPTION	DEVICE	DESCRIPTION	DEVICE	DESCRIPTION
μ AF771	Single BIFET Operational Amplifier	μ A301A	General-Purpose Operational Amplifier	μ A748	Operational Amplifier
μ AF772	Dual BIFET Operational Amplifier	μ A308	Super Beta Operational Amplifier	μ A749	Dual Audio Operational Amplifier/ Preamplifier
μ AF774	Quad BIFET Operational Amplifier	μ A308A	Super Beta Operational Amplifier	μ A759	Power Operational Amplifier
μ A101	General-Purpose Operational Amplifier	μ A318	High-Speed Operational Amplifier	μ A776	Multi-Purpose Programmable Operational Amplifier
μ A101A	General-Purpose Operational Amplifier	μ A324	Quad Operational Amplifier	μ A791	Power Operational Amplifier
μ A102	Voltage Follower Operational Amplifier	μ A348	Quad Operational Amplifier	μ A798	Dual Operational Amplifier
μ A107	General-Purpose Operational Amplifier	μ A702	Wideband DC Amplifier	μ A1458	Dual Internally-Compensated Operational Amplifier
μ A108	Super Beta Operational Amplifier	μ A709	High-Performance Operational Amplifier	μ A1458C	Dual Internally-Compensated Operational Amplifier
μ A108A	Super Beta Operational Amplifier	μ A741	Precision Operational Amplifier	μ A1558	Dual Internally-Compensated Operational Amplifier
μ A110	Voltage Follower Operational Amplifier	μ A715	High-Speed Operational Amplifier	μ A2902	Quad Operational Amplifier
μ A124	Quad Operational Amplifier	μ A725	Instrumentation Operational Amplifier	μ A3303	Quad Operational Amplifier
μ A148	Quad Operational Amplifier	μ A739	Dual Low-Noise Audio Preamplifier/ Operational Amplifier	μ A3403	Quad Operational Amplifier
μ A201	General-Purpose Operational Amplifier	μ A740	FET Input Operational Amplifier	μ A4136	Quad Operational Amplifier
μ A201A	General-Purpose Operational Amplifier	μ A741	Frequency-Compensated Operational Amplifier		
μ A208	Super Beta Operational Amplifier	μ A747	Dual Frequency-Compensated Operational Amplifier		
μ A208A	Super Beta Operational Amplifier				
μ A224	Quad Operational Amplifier				
μ A248	Quad Operational Amplifier				

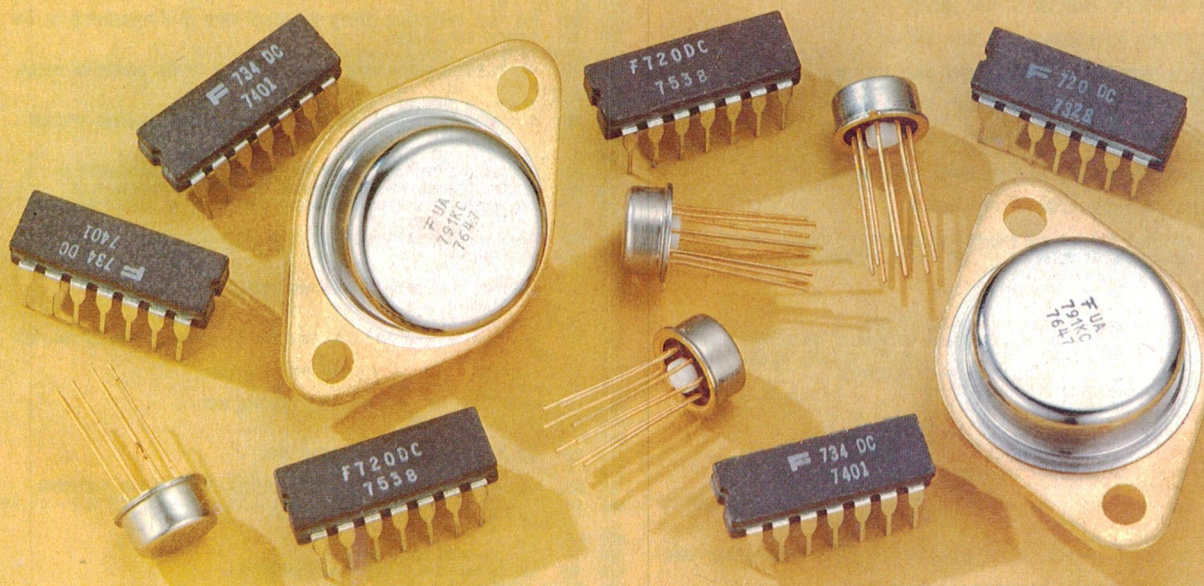

AVAILABLE FROM



PROUDLY AUSTRALIAN

The George Brown Electronics Group.

N.S.W.: George Brown & Co. Pty. Ltd.
 A.C.T.: George Brown & Co. Pty. Ltd.
 VIC.: Browntronic Pty. Ltd.
 S.A.: Protronics Pty. Ltd.
 WA.: Protronics Pty. Ltd.

Ph. 519 5855 Telex AA21732
 Ph. 80 4355 Telex AA62128
 Ph. 419 3355 Telex AA35886
 Ph. 212 3111 Telex AA88261
 Ph. 362 1044 Telex AA93883

The ZX PRINTER
— designed for use
with ZX81 and ZX80
with 8K BASIC ROM.
Alpha-umerics! Graphics!

\$190
incl. Sales Tax

sinclair ZX81

PERSONAL COMPUTER

\$199
COMPLETE

* excluding mains adaptor

sinclair

COMPLETE WITH BASIC MANUAL, LEADS, ONLY \$199

**16K-BYTE
RAM PACK \$150**

**Higher specification,
lower price — how's it done?**

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

The ZX81 comes complete with all leads to connect to your TV (colour or black and white) and cassette recorder.

New, improved specification

- Z80 a microprocessor — new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.

- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function — useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.

- Able to drive the new Sinclair printer (not available yet — but coming soon!)
- Advanced 4-chip design, microprocessor, ROM, RAM, plus master chip — unique, custom-built chip replacing 18 ZX80 chips.

ZX Software Cassettes

Send for free catalogue of Games, Business, Educational, Junior Education. Encl. S.A.E.

FREE New Basic ZX81 Manual

ORDER FORM: SINCLAIR EQUIPMENT (A'SIA) P/L

86-88 Nicholson St., Abbotsford, Vic. 3067. Ph. (03) 419 3033.

QUANTITY	ITEM	ITEM PRICE	TOTAL
	Ready assembled ZX81 Sinclair Personal Computer including leads, BASIC manual, excluding mains adaptor.	\$199	
	16K-BYTE RAM pack (optional extra)	\$150	
	1.2 Amp Adaptor	\$ 17.50	
	ZX Printer	\$190	

I enclose cheque/Bankcard/Diners Club/Amex

Total _____

□□□□□□□□□□□□□□

Name _____

Address _____ P'code _____

Signature _____

ETI

N.S.W.: ACORN ELECTRONICS, A.E.D. MICROCOMPUTER PRODUCTS, B.B.J. COMPUTER SHOP PTY. LTD., GISA MICROCOMPUTERS PTY. LTD., COMPUTER FACTORY, COMPUTER GALLERY, COMPUTERLAND CHATSWOOD, COMPUTERLAND EAST SYDNEY, COMPUTERS GALORE, COMPUTER WAVE PTY. LTD., DAVID REID ELECTRONICS PTY. LTD., DICK SMITH ELECTRONICS, DIRECT COMPUTER SALES, L. & B. TELEVISION SERVICES PTY. LTD., THE LOGIC SHOP, L.S.T. ELECTRONICS, MICLA SALES AND SERVICE, MINIT COMPUTER SERVICE, PAUL DEREZ RADIO T.V. SERVICES, IRINITY COMPUTING, **A.C.T.:** COMPUTER WORLD, DICK SMITH ELECTRONICS, STEVE'S COMMUNICATION CENTRE, **TASMANIA:** BIRCHALLS, THE LOGIC SHOP, QUANTUM COMPUTERS, J. WALSH & SONS PTY. LTD. **N.T.:** ASCOM ELECTRONICS, EYLES COMPUTER SERVICES, **VICTORIA:** B.B.J. COMPUTER SHOP PTY. LTD., C. & G. COMPUTERS PTY. LTD., COMPUTERLAND OF MELBOURNE, COMPUTERLAND, CAMBERWELL, DICK SMITH ELECTRONICS, LOGIC SHOP, LOGIC SHOP, MIND BENDERS OF CROYDON, MINIT COMPUTER SERVICE, MYER MELBOURNE STORES, RADIO PARTS GROUP, ROD IRVING ELECTRONICS, STRACHAN OFFICE SUPPLIERS, **S.A.:** ACUIS AUSTR. PTY. LTD., DICK SMITH ELECTRONICS, MYER S.A. STORES, OMNI COMPUTING, **QUEENSLAND:** ALLIANCE COMPUTER PRODUCTS, COMPUTER CITY, CUSTOM COMPUTER SERVICE, DATACOM, DICK SMITH ELECTRONICS, MYER QLD., THE LOGIC SHOP, PURELY ELECTRONICS PTY. LTD., SCOTT'S AUDIO-OPTICAL, SOFTWARE 80, TEC ELECTRONIC IMPORTS. **W.A.:** DICK SMITH ELECTRONICS, MICROBASE.

Use your Motorola 6800 D2 kit to program 2716 EPROMs

If you have been waiting for cheap, easy to program and easy to use EPROMs before incorporating non-volatile memory into your microcomputer system or building dedicated microprocessor projects, then you need wait no longer. With the 2716-type EPROMs now available and this very simple interface you can program EPROMs very quickly and cheaply using a Motorola 6800 D2 kit.

David L. Craig.

OVER THE PAST couple of years there has been a remarkable development in the EPROMs available for use in microprocessor systems. After the difficult-to-program 1702 EPROMs with 512 x 8 storage, we saw the 2708 EPROM arrive with twice the storage capacity (1024 x 8 bits) and considerably simpler programming requirements. The 2708 has become relatively cheap, but many hobbyists have probably been put off using this device because it requires three power supply voltages (+12 V, +5 V, -5 V) when the rest of the microprocessor system probably only uses one (+5 V); it also requires a programmer capable of switching a +26 V programming supply, and it requires each location to be programmed about 100 times in a loop, making programming of individual locations difficult.

Now we have the 2716, which makes EPROMs much more attractive to hobbyists. It contains 2K x 8 bits of storage, uses only a single +5 V power supply, requires a static +25 V programming supply, with each location being programmed with a single 50 ms TTL-level pulse, and allows programming of any number from 1 to 2048 locations at a time. And best of all is the price — around \$5 each in one-off quantities from some sources. This represents far better value than the 2708 ever did.

2716 EPROMs can be programmed using a Motorola 6800 D2 kit and the very simple and low-cost interface circuit shown in Figure 1. The programmer interface connects to the user PIA (Peripheral Interface Adaptor) of the D2 kit. A programming power supply of

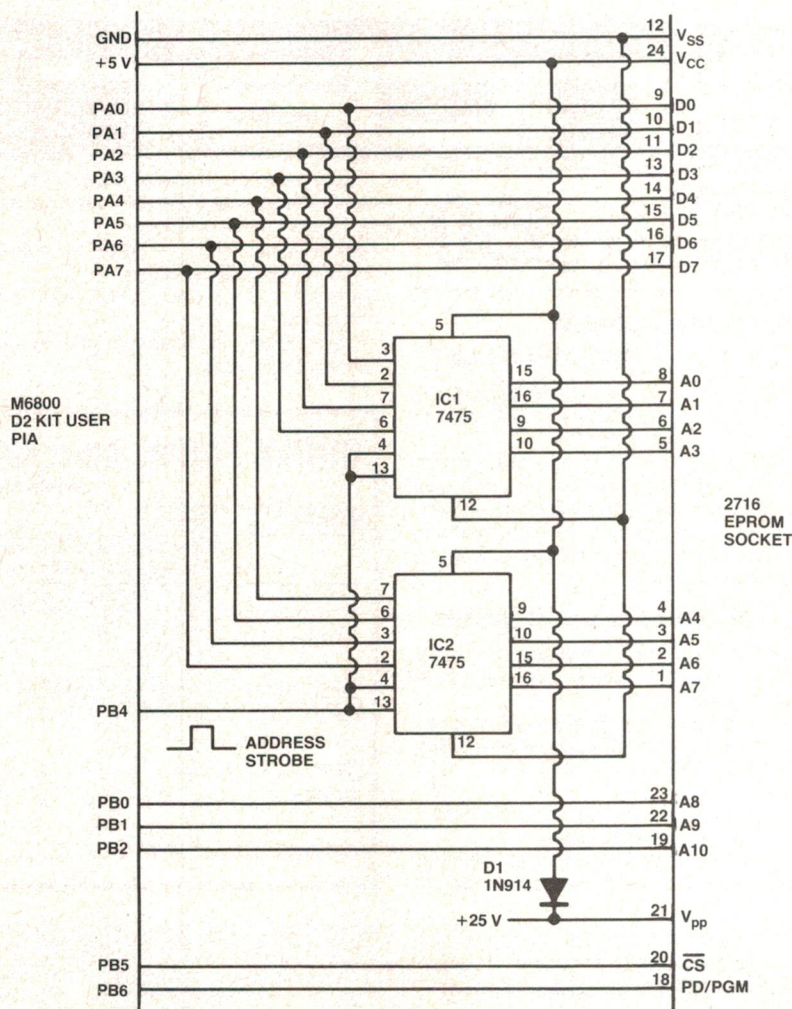


Figure 1. 2716 EPROM programmer interface circuit.

+24 V to +26 V is also required. The interface circuit simply uses two 7475 quad latch ICs to latch the address information from the PIA, and one diode to feed +5 V to the Vpp pin of the 2716 with the +25 V programming supply turned off. No pc board layout is given since the circuit is so simple and the method of construction will depend on the system with which the interface is to be used.

All the signal generation and timing required are handled by a software routine called 'PG2716', for which a full listing is given. The routine latches the address of the location to be programmed into the 7475s, then reads the contents of that location, checking that it is erased (i.e. \$FF), programs the location and then again reads the contents to verify the programmed data. Each address of the EPROM is programmed in turn in this way. The waveforms required by the 2716 for this sequence are shown in Figure 2. Using these waveforms and the comments in the listing the operation of the routine should be fairly easily followed. The routine occupies only 170 bytes of memory, and while the listing shows it assembled beginning at location \$1E00, it is relocatable without changes. The only fixed locations used are \$A002-A005 and \$A042-A043, which are in the D2 kit stack RAM.

The principle of operation of the programmer is that the data to be stored in the EPROM is first loaded into RAM and then copied as a block into the EPROM. The only restriction on loading the data into RAM is that the eleven low-order address bits (A0-A10) of the data in RAM must correspond to the address in the EPROM at which that data byte is to be stored; i.e. a 2K x 8 block of data in the D2 kit RAM maps directly to the 2716 EPROM.

The sequence of steps to be followed in using the programmer is:

- connect the interface circuit to the D2 kit
- insert the EPROM into the interface socket
- power up the D2 kit
- load the programmer program and the data to be programmed into the D2 kit memory
- power up the +25 V programming supply
- enter the beginning address of the data in the D2 kit memory into \$A002-3, and the end address into \$A004-5 via the D2 kit keyboard (note that any number of data bytes from 1 to 2048 can be specified.)
- start the programmer by entering \$1E00 G via the D2

kit keyboard

- if the EPROM is programmed successfully, the JBUG prompt ' ' will appear on the D2 kit display after approximately 100 seconds
- power down +25 V programming supply
- power down D2 kit

The EPROM is then programmed ready for use.

In the event of an error, a software interrupt of the programming routine will occur.

- if the SWI occurs at \$1E33, the EPROM was not correctly erased
- if the SWI occurs at \$1E34, programming did not occur correctly

In either case, after the SWI, X = location at which failure occurred, A = data expected at failed location, B = data in EPROM at failed location.

2758 (1K x 8 bit) EPROMs can also be programmed with this programmer. 2758 EPROMs are 2716 EPROMs with only the lower or upper half working. To program a 2758, load the data to be programmed into the appropriate half of a 2K x 8 block in the D2 kit RAM so that the 1K x 8 data maps directly into the working half of the 2K x 8 locations

in the 2758.

One note of warning should be given for purchasers of 2716-type EPROMs. Some manufacturers, e.g. Texas Instruments, have designated a three power supply 2K x 8 EPROM with the 2716 code (e.g. TMS 2716). Be careful to purchase the single power supply version — from Texas this is the TMS 2516.

A place suitable for using 2716 EPROMs, though it is not mentioned in the manual, is in the two sockets on the main D2 kit board provided for optional PROMs. The straps on the board necessary for 2716 use are E0-E4, E1-E2, E3-E7 and E5-E9. All other connections on the pc board are correct. Wherever it is that you use 2716 EPROMs, one thing is certain — you will never go back to 2708s.

The principle of using a programmable input-output port with a single interface to program 2716 EPROMs could easily be applied to microprocessor systems using other processors, e.g. Z80, 8080, etc. It can also be applied to programming other EPROM types, and the author has built such an interface for Intersil IM6654 512 x 8 bit CMOS EPROMs.

(Ref. 'An Ultra-Low-Cost Programmer for CMOS EPROMs', *Electronic Engineering* (UK), Jan. 1981, pp 23-25.)

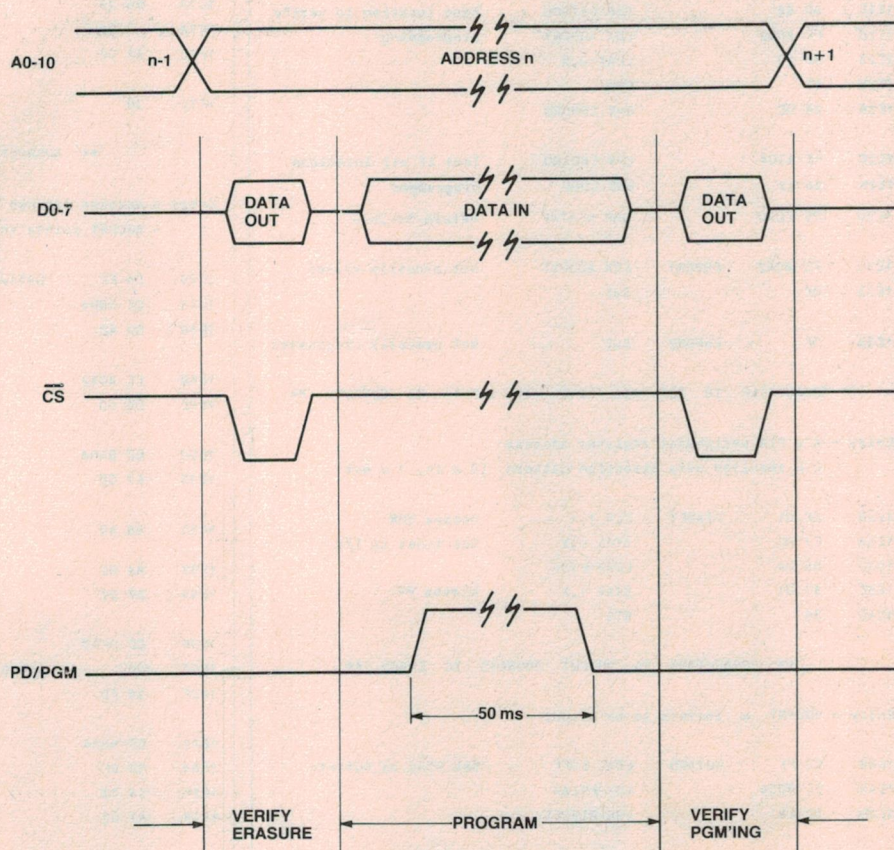


Figure 2. 2716 EPROM programmer waveforms.

Program Listing

** 2716 EPROM PROGRAMMER PROGRAM **

```

8004      PIAA      EQU $8004      User PIA
8005      PIACRA    EQU $8005
8006      PIAB      EQU $8006
8007      PIACRB    EQU $8007

A002      BEGADD    RMB2           From begin address
A004      ENDADD    RMB2           From end address

A042      ADOPNT    RMB2           Pointer at address to be
                                   read or programmed

1E00      C6 FF      PG2716      LDAB #$FF      Set PIAB as outputs
1E02      CE 8006      LDX #PIAB
1E05      8D 31      BSR PIASET
1E07      C6 20      LDAB = $20      Initialize PIAB
1E09      E7 00      STAB 0,X

1E08      FE A002      LDX BEGADD      Initialize ADOPNT
1E0E      09          DEX
1E0F      08          LOOP      INX
1E10      FF A042      STX ADOPNT      Update pointer

1E13      8D 33      BSR OUTADD      Output address

1E15      8D 53      BSR DATARD      Read data and
1E17      86 FF      LDAA #$FF
1E19      11          CBA          verify EPROM
1E1A      26 14      BNE ERROR1      location erasure

1E1C      8D 66      BSR DATAWR      Program EPROM location

1E1E      8D 4A      BSR DATARD      Read location to verify
1E20      FE A042      LDX ADOPNT      programming
1E23      A6 00      LDAA 0,X
1E25      11          CBA
1E26      26 0C      BNE ERROR2

1E28      BC A004      CPX ENDADD      Test if all locations
1E28      26 E2      BNE LOOP      programmed
1E2D      7E E08D      JMP RESTAR      Return to JBUG

1E30      FE A042      ERROR1      LDX ADOPNT      Not properly erased
1E33      3F          SWI
1E34      3F          ERROR2      SWI          Not properly programmed

** SUBROUTINE TO SET PIA LINES AS INPUTS OR OUTPUTS **

Entry - X = PIA peripheral register address
      B = required data direction pattern (0 = in, 1 = out)

1E38      6F 01      PIASET      CLR 1,X      Access DDR
1E3A      E7 00      STAB 0,X      Set lines as I/O
1E3C      86 04      LDAA #$04
1E3E      A7 01      STAA 1,X      Access PR
1E40      39          RTS

** SUBROUTINE TO OUTPUT ADDRESS TO EPROM **

Entry - ADOPNT = address to be output

1E48      C6 FF      OUTADD      LDAB #$FF      Set PIAA as outputs
1E4A      CE 8004      LDX #PIAA
1E4D      8D E9      BSR PIASET
1E4F      B6 A043      LDAA ADOPNT+1      Output low byte

```

```

1E52      A7 00      STAA 0,X      to PIAA
1E54      B6 A042      LDAA ADOPNT
1E57      84 07      ANDA #$07      Mask off high 5 bits
                                   of high byte

1E59      8A 10      ORAA #$10
1E5B      E6 02      LDAB 2,X      Output high 3 bits
1E5D      C4 E0      ANDB #$E0      of address to PIAB
1E5F      18          ABA          and output low
1E60      A7 02      STAA 2,X      byte into latches by
                                   setting address strobe
                                   high

1E62      86 EF      LDAA #$EF      Set address strobe low
1E64      A4 02      ANDA 2,X      to latch address

1E66      A7 02      STAA 2,X
1E68      39          RTS

```

** SUBROUTINE TO READ DATA FROM EPROM **

Entry - address latched
Exit - data in B

```

1E6A      5F          DATARD      CLR      Set PIAA as inputs
1E6B      CE 8004      LDX #PIAA
1E6E      8D C8      BSR PIASET

1E70      86 DF      LDAA #$DF      Set PB5 low to read
1E72      A4 02      ANDA 2,X      data
1E74      A7 02      STAA 2,X

1E76      E6 00      LDAB 0,X      Read data

1E78      86 20      LDAA #$20      Set PB5 high to end
1E7A      AA 02      ORAA 2,X      data read
1E7C      A7 02      STAA 2,X

1E7E      39          RTS

```

** SUBROUTINE TO WRITE DATA TO EPROM **

Entry - address latched
- ADOPNT points to data

```

1E84      C6 FF      DATAWR      LDAB #$FF      Set PIAA as outputs
1E86      CE 8004      LDX #PIAA
1E89      8D AD      BSR PIASET

1E8B      FE A042      LDX ADOPNT      Point to data
1E8E      E6 00      LDAB 0,X      Fetch data

1E90      CE 8004      LDX #PIAA
1E93      E7 00      STAB 0,X      Output data

1E95      86 40      LDAA #$40      Set PB6 high for
1E97      AA 02      ORAA 2,X      50ms to program
1E99      A7 02      STAA 2,X      EPROM location

1E9B      CE 0F00      LDX #$0F00      50ms delay
1E9E      09          DLY50      DEX
1E9F      26 FD      BNE DLY50

1EA1      CE 8004      LDX #PIAA      Set PB6 low to end
1EA4      86 BF      LDAA #$BF      programming pulse
1EA6      A4 02      ANDA 2,X
1EA8      A7 02      STAA 2,X

1EAA      39          RTS

```


Once weekly for a good looking body.

Every car, like a new born baby, starts off with a beautiful body. But the trick is keeping it that way, so the good news is Wash-n-Wax and Glo-Wash from The Kitten System.

Now you can buy a beautiful body off the shelf, and keep your car in showroom condition.

Glo-Wash is made especially for cleaning your valuable investment.

Whereas ordinary detergent and water may only clean the surface, Glo-Wash removes stubborn road grime that would otherwise become ingrained and cause your paintwork to rapidly deteriorate.

And if you want to give your car extra special protection, The Kitten System brings you Wash-n-Wax. Wash-n-Wax is the blend of specially developed high quality cleaning agents and waxes that protects as it waxes your car's body.

But the beauty of both Wash-n-Wax and Glo-Wash is their wash-on/hose-off simplicity; there's no need to chamois anymore. And a good looking body won't cost you an arm and a leg: a bottle of Wash-n-Wax or Glo-Wash will wash the average car at least 17 times.

So for a good looking body, use Glo-Wash or Wash-n-Wax from The Kitten System at least once a week.



THE KITTEN SYSTEM.

THE CREAM OF CAR CARE

Exclusive to Marantz. Very sophisticated. Very superior. Very expensive.



Very high fi indeed.

These Marantz Gold components represent the world's most advanced, most inspired, most stringently tested and sophisticatedly engineered audio equipment.

For the wealthy — exclusive toys.
For the connoisseur — the finest hi-fi money can buy.

The Marantz TT1000 (around \$2500), with its precision-made high density glass and golden aluminium sandwich structure, is justifiably described as one of the most beautiful turntables ever.

'Playing a series of direct-recorded discs, warped discs, discs with nasty low frequency content and discs requiring unusual trackability performance, showed clearly that this system borders on the superlative in areas where even most good turntables only provide good to above average performance.'

'...the resonance characteristics of the TT1000 are the lowest we have yet seen from any turntable irrespective of its selling price.'

'This is top-of-the-line equipment for people who rate hi-fi as their greatest pleasure in life'.
— Louis Challis, *Electronics Today International*, April 1981.

Similarly, the Marantz SM1000 Stereo Amplifier (around \$5000) is designed to be the ultimate in luxury and performance.


When it was bench-tested by ETI Magazine in an exhaustive lab study, Louis Challis stated 'The Marantz SM1000 Amplifier has the capability to provide superlative performance at home, in a laboratory, in a studio, or in a rock band with the ease and panache of a professional.'

'The power output claims are modest for the unit is readily capable of producing 625 watts into an 8 ohm load with both channels driven...'

And when the Marantz ST8 FM/AM Tuner (around \$700) was

put through its paces so technically surprising was its performance that a second series of tests was devised to check the first results.

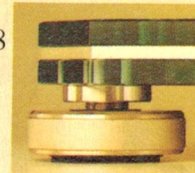'As a result... the Marantz ST8... far ahead of any tuner we have ever measured and better than any tuner we have ever seen reviewed in any other magazine, either local or overseas.' — Paul de Noskowski, *Electronics Australia*, April 1981.



The TT1000's adjustable, high-absorption air suspension audio insulator feet.

Marantz Gold. The New Audio Standard.



ST8


Detailed specifications of these exclusive Marantz Gold components are available on request by writing to:

Marantz (Australia) Pty. Limited,
19 Chard Road, Brookvale, NSW 2100
Phone (02) 939 1900 Telex AA24121
Melbourne (03) 544 2011
Brisbane (07) 44 6477
Adelaide (08) 223 2699
Perth (09) 276 3706
Townsville (077) 72 2011

marantz®



ELECTRONIC LIFESTYLE

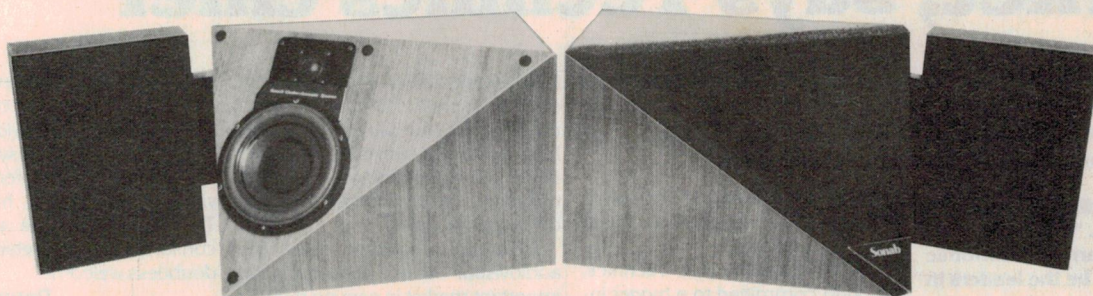

Sonab is back!

It's true. Not a word of a lie. Holders of the Sonab name in Australia, Concept Audio, have 'resurrected' the name with the release of a new Stig Carlsson product.

Sonab of Sweden Pty Ltd was established in 1972 to market in Australia the now-famous Carlsson loudspeakers plus Sonab-branded amplifiers, turntables and cassette decks.

In 1977, due more to politics than to economics, the Swedish-based parent company closed down. Service on all Sonab products however was maintained and has been to this day by Concept Audio Pty Ltd.

Concept have delightedly announced that Stig Carlsson has designed a new product to be known as the OA.51 Ortho-Acoustic Loudspeaker System. This system is now available throughout Australia under the Sonab name through a limited number of specialist hi-fi outlets.

The speaker is designed to be

wall-mounted or to stand on a bookshelf and has a recommended retail price of \$1100. The sound quality is superb — typically Sonab inasmuch as it offers a very open, clean and detailed sound, according to Concept.

Details from Concept Audio, 22 Wattle Rd, Brookvale NSW 2100. (02)938-3700.

Going the National 'Way'

National have just released what they claim is 'the world's smallest, lightest, highest performance, easiest to operate' stereo cassette recorder, called the 'Way'.

The player measures 75 mm wide by 108 mm high by 28 mm deep and weighs only 223 grams without batteries.

The Way's compact dimensions arise from the use of a specially-fabricated flexible printed circuit board, a Matsushita engineering development. This fits neatly over the tape transport system which features a high-torque rare-earth magnet coreless dc motor, high quality drive belt, and an anti-rolling mechanism to assure rotational stability when listening on the move. (Matsushita is National's parent company.)

The head is secured by stainless steel support, assuring excellent tape-to-head contact and optimum alignment. For fast-forward and rewind, a special assembly moves forward around the tape to push the pressure pad away from the tape, thereby avoiding abrasion of the head or tape. A hyperbolic head is employed to further improve tape-to-head contact while reducing the contour effect and improving low-range reproduction, National say.



The Way is produced in three styles, though all have the same features. Play and stop buttons are located on top and require only a gentle tap to activate. Large, lockable fast-forward and rewind buttons are located on the cassette lid;

switching is accomplished via the reel table spindles, so the buttons are flat and do not protrude.

Even when the unit is in its supplied belt holder, the user can change cassettes and operate all controls with one hand. A three-position tape eq/tone selector gives the user a choice of response characteristics for normal and metal cassette reproduction.

The open-air stereo headphones supplied with the player have the cord attached to only one side. Built into the cord is a remote pause button which, in locked position, also turns the power off to reduce battery drain. Two stereo headphone jacks are incorporated.

Other features include LED battery indicator, auto-stop, dc-in jack, and external battery adaptor.

Quoted frequency response is 30 Hz to 14 kHz on normal tape, 30 Hz to 15 kHz on metal tape. Fast-forward and rewind time is given as 120 seconds with C60 tape. The unit is powered from two 1.5 V cells. Type AA cells fit within the unit, but for longer playing times, a separate battery pack taking D-size cells is included.

The unit was due for release in August and should be generally available in September. Further details from National Panasonic, 95-99 Epping Rd, North Ryde NSW 2113.

Beyer dynamic microphone

Beyer have released their new M300N(C) microphone, similar in design to the widely used model M400.

Rank Electronics claim that the M300 is a good quality microphone with a stainless steel basket and is intended to stand up to the rigours of road use.

It is a pressure gradient microphone with a very low feedback and its capsule suspension significantly reduces body noises. The M300 has

a cardioid pattern and a wide frequency response of 50-15 000 Hz. It is supplied with a 7.5 m Switchcraft cable and clamp.

For further information please contact Rank Electronics, 16 Suakin St, Pymble NSW 2073. (02)449-5666.

Bring sanity back to hi-fi market, says Technics chief

In Japan late in June, Technics Marketing chief Peter Lee, told a dealer/editorial seminar that hi-fi sales would remain depressed for a while, but despite price cutting and dumping, Technics were committed to bringing sanity back to the marketplace.

"The immediate future is grim," Lee said. "But those who survive the current economic depression will be the leaders in the future."

He said that consumer dollars are going into video, and that the situation for the hi-fi industry is made worse by high interest rates that make it difficult for dealers to commit to stock. High home loan interest rates were also taking money out of the consumer market that would otherwise be spent on hi-fi.

This has created problems in the hi-fi industry and manufacturers have been dumping stock since last October. This has put new low price points on hi-fi and in an attempt to

meet these new low prices points the industry is being forced from hi-fi down into low-fi.

Lee told dealers that Technics, although committed to a bigger involvement in the market place, was pledged to try and bring sanity back to hi-fi retailing. Technics plans to attack the market in the next two years on a number of fronts.

At the June Technics dealer/audio conference the areas of attack were mapped out.

The main thrust will be in 'new wave' audio. This is compact hi-fi and portable hi-fi for outdoor music, plus component, system, audio visual, and deck-receivers for indoors.

This 'new audio' is breaking into,

and is expected to eventually take over, the music centre and system markets. The portable hi-fi will be large portables, while the compact hi-fi is the Walkman type hip stereo using headphones. 'Stereo to go', as come people call it.

Although Technics sees the audiovisual area becoming an important market in coming months

it doesn't anticipate entering this market for some time, other than to supply tuners and video control centres for hi-fi/video systems.

There are no plans for a Technics video recorder or high quality TV monitor, a move which many consumers and retailers would doubtless welcome.

Dennis Lingane

More from Milty

Concept Audio, the importers and distributors of Milty Products in Australia, have announced some new additions to their record-care range.

Firstly, following hot on the heels of the now-famous Permostat anti-static record treatment, is a product to be known as Permoclean. This is a fluid cleaner and the claim by the manufacturer is that it will clean a record as effectively as any professional record cleaning machine.

It is said to remove both organic and inorganic matters from the surface of a record together with the removal of micro-dust particles from the inner groove of the record.


A new pad has been developed, known as the Duo Pad. This will be used in both Permoclean and Permostat kits in future and is a double-sided buffing device.

The unique feature of the Duo Pad is that as surfaces become old

and worn, replacement cartridges will become available — therefore allowing the Duo Pad to be used on a continuing basis at a very economical price.

The final new product to come into the Milty Products line-up is a rubber work mat. This mat, which comprises 55 000 tiny rubber tentacles, will hold a record firmly in position whilst Permostat and Permoclean are being applied. The mat can also be used when applying other record cleaning and treatment processes.

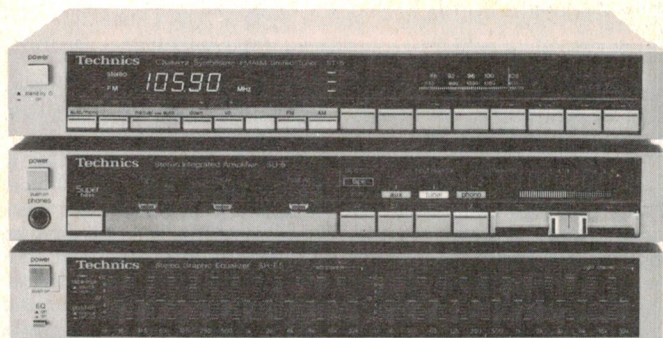All products are expected to be at hi-fi shops and record bars in October. Enquiries to Concept Audio Pty Ltd, 22 Wattle Rd, Brookvale NSW 2100. (02)938-3700.



This three-component range from Technics comprises an integrated amplifier, tuner and graphic equaliser measuring only 315 mm wide which 'plug in' to each other — no more cables. These are to be released into the 'new audio' area, where compactness, versatility and value for money are important.

Matsushita and Ampex get together on video tape

Matsushita Electric Industrial Co of Japan recently announced that their 'M-format' half-inch video recording format for broadcast use had been adopted and developed by Ampex, a leading manufacturer of broadcasting video equipment.

The M-format professional video system employs a VHS half-inch video cassette and enables a single-unit configuration of camera/VTR combination for electronic news gathering (ENG) and electronic field production (EEP).

M-format is said to have superior picture quality and better portability

over conventional three-quarter-inch formats, and two Japanese broadcasting equipment manufacturers, Hitachi Denshi and Ikegami, have already announced that they will be adopting the M-format system. They exhibited the systems at this year's National Association of Broadcasters' convention.

Fostex monitor

Fostex recently released the Model 6301 self-powered personal monitor.


This unit can be used to monitor signals from tape recorders to electric guitars, from synthesizers to amplifiers.

The use of the 6301's 10 watt amplifier is available when no other power service exists.

The compact size: 188 x 120 x 118 mm and its weight of only 3.2 kg make this unit very versatile.

Frequency response is quoted as 80 Hz to 13 kHz, distortion at 0.05% at one watt output.

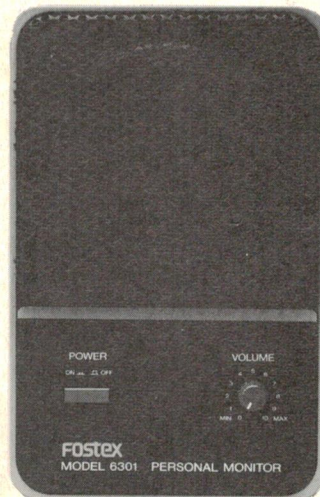Suggested price is \$198 each. Distributed in Australia by Trade-power International Pty Ltd, 115 Whiteman Street, South Melbourne Vic. 3205. (03)690-6873.





“ICS helped take me from fish and chips to silicon chips.”

— A true ICS student story.

It's a long way from the counter of a take away food bar to an electronic technician's work bench. But that's what George Raftou achieved in under three years with ICS training. This is his story.

“I wanted a career, but I'd left school early, so I didn't have much hope. I couldn't afford to go on apprentices wages. And because of my education they wouldn't even have me at tech.”

That was three years ago, about the time George saw the International Correspondence Schools coupon in a magazine.

“I don't know why I picked electronics. I just figured with all the stereos and TV's around there seemed to be a lot of opportunities.”

Study on full wages.

“The best thing about ICS was that I could study when it suited me and earn good money at the same time.”

ICS guided study helped George progress quickly. Systemised lessons, study notes and the guidance of a tutor make ICS programs one of the most personalised methods of learning. You learn at your own pace, taking time over difficult areas, rushing through subjects known to you.

After just one year, George passed his first PMG exam. This enabled him to join an electronics school that normally wouldn't take anyone who had left school so early.

“I joined halfway through the year, but was right up with the class,” George told us.

Today, George Raftou works with a leading electronics company servicing

calculators. He hopes the next promotion will see him in the company's computer division. All that achieved in less than three years.

Turn your hobby into a career.

Like George Raftou you can use ICS training to enter the world's fastest growing industry.

Check the ICS electronics courses listed below then nominate a specific course in the coupon. We'll send you information without cost or obligation.

1. Basic Electronics.
2. Electronics Technician. Approved by TETIA.
3. Electronic Instrumentation and Control Systems.

4. Electronic Technology.
5. Electronics Maintenance.
6. Radio-Electronic Telemetry: electrical and electronic aspects of telemetering.
7. Amateur Radio Operator's Certificate of Proficiency.
8. Digital Electronics.
9. Data Processing.
10. TV Servicing. Approved by TETIA.
11. TV Principles.
12. Electrical Engineering Technician.
13. Electrical and Electronic Drafting.
14. Automobile Electrician.
15. Industrial Electrician.
16. Electrical Mechanic.

International Correspondence Schools
(A'sia) Pty Ltd. 400 Pacific Highway,
Crows Nest, N.S.W. 2065
Tel: (02) 43 2121.

I am interested in the following course/s (please specify.)

Mr/Mrs/Miss.....

Please Print

Address.....

Postcode.....

Occupation.....

Age.....

Phone.....

Tick here if currently full time student. ☐

Write to your nearest ICS city: **International Correspondence Schools.**

Sydney: 400 Pacific Highway, Crows Nest, N.S.W. 2065 Tel: (02) 43 2121.

Melbourne: 18-20 Collins Street, Melbourne, VIC. 300 Tel: (03) 656 1950.

Brisbane: 131 Elizabeth Street, Brisbane, QLD. 4000 Tel: (07) 221 0178.

Adelaide: 28 Grenfell Street, Adelaide, S.A. 5000 Tel: (08) 219 4154.

Perth: P.O. Box D157, Perth, W.A. 6001 Tel: (09) 321 8530.

New Zealand: 45 Courtenay Place, Wellington 1, N.Z.

0376



Bankcard



ICS 074 M&W

Not Just Speaker Wire



Conventional speaker wire limits the performance of your sound system by decreasing power output, restricting dynamic range, and reducing clarity and definition. You can significantly improve the performance of your audio system by switching from your present speaker wire to Monster Cable.

Constructed of over 500 strands of high purity copper in a unique configuration, Monster Cable is specifically engineered for low resistance, low capacitance, and low inductance. The Results?

Deeper, tighter bass.

Maximum power transfer.

Increased clarity and definition.

Wider dynamic range.

Even low-powered systems show a remarkable improvement. Recommended by leading audio manufacturers, Monster Cable is safe to use with all amplifiers and receivers, regardless of design.

Don't be deceived by imitations. If it doesn't say Monster Cable you're not getting all the performance you paid for.


MONSTER CABLE

DISTRIBUTED BY CONVOY SYDNEY (02) 358 2088

Available from: NSW—AUTO ACOUSTICS Sydney * ABSOLUTE SOUND Sans Souci * BING LEE DISCOUNTS Fairfield * CAMPBELL-TOWN HI FI Campbelltown * DUTY FREE TRAVELLERS SUPPLIES Sydney * FUTURE AUDIO North Sydney * THE HI FI SHOP Hurstville * LEISURE SOUND Sydney, Artarmon, Parramatta * LEN WALLIS AUDIO Lane Cove * MIRANDA HI FI Miranda, Parramatta, Roselands, Bondi Junction * PARK HI FI Summer Hill, Sydney * RUSSIN HI FI Ashfield * WARRINGAH HI FI Mona Vale * WOOLLAHRA ELECTRONICS Woollahra * CLASSIC CAR SOUND Adamstown * EASTERN HI FI Newcastle West * HUNTER VALLEY ELECTRONICS Maitland * NEWCASTLE HI FI Newcastle * PITMAN'S RADIO & TV SERVICE Wagga Wagga * SOUND COMPONENTS Tamworth * WARDELLS SIGHT & SOUND Broadmeadows * WOLLONGONG HI FI Wollongong A.C.T.—GURATONE Philip VICTORIA—TIVOLI HI FI Hawthorn * NATIONSOUND Melbourne * EAST COAST AUDIO Albert Park * SOUND BUFF * STEVEN BENNETT AUDIO Geelong * PROUD'S AUDIO WORLD Bendigo * SHEPPARTON HI FI Shepparton QLD.—STEREO SUPPLIES Brisbane * REG MILLS STEREO Buranda * HANDO'S HI FI Toowoomba * DOWNTOWN HI FI Brisbane * LIVING SOUND CENTRE Ashgrove * QLD. ENTERTAINMENT COMPANY Eight Mile Plains * GOLD COAST HI FI & STEREO SOUND Southport * HIGHWAY SOUND CENTRE Mt. Isa * STEREO WORLD Cairns * GEOFF BRADFORD HI FI Toowoomba * DISCO STEREO SUPPLIES Townsville * CUSTOM SOUND CENTRE Nambour STH. AUST.—BLACKWOOD SOUND Blackwood * THE SOUND CRAFTSMEN Hawthorn * TRACK HI FI Adelaide * GREENFELL PLAZA HI FI Adelaide * ASLIN HI FI Mount Gambier * WHYALLA TV & RADIO Whyalla W.A.—AUDIO DISTRIBUTORS Moornan Park * THE AUDIO CENTRE West Perth * JAPAN HI FI Victoria Park * ALBERT'S TV & HI FI CENTRE Perth * ESPERANCE ELECTRONICS Esperance * NORTH WEST AUDIO Karratha TAS.—UNITED ELECTRONICS Launceston * BEL CANTO Hobart * QUANTUM SOUND CENTRE Hobart.

B&W DM12

THE UNOBTRUSIVE REVOLUTIONARY

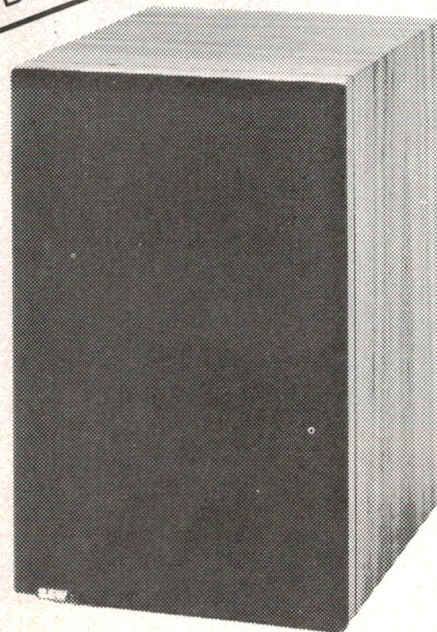

We could have built something smaller, but we were determined to build a miniature speaker that rises way above the limitations hitherto imposed by a small enclosure. In particular, we wanted to achieve wider response and more realistic sound levels in the low frequency range. We also wanted safe power-handling capacity. Thanks to our unique resources in computer and laser technology and the sheer creativity of our design team, DM12 achieves all this and more.

It's certainly small.

Just 355mm (14 in) high x 220mm (8¾ in) wide x 270mm (10½ in) deep.

106dB.

That's the surprising peak sound pressure level DM12 produces from its 12 litre enclosure.

Monitor standard.

Frequency linearity + 2 dB 85 Hz to 20kHz.


APOC-protected.

B & W's exclusive audio-powered overload circuit protects against accidental damage or overload.

For further information see your B & W dealer or contact
Convoy International Pty Ltd
4 Dowling Street Woolloomooloo NSW 2011
Telephone (02) 3582088

B&W

LOUDSPEAKERS

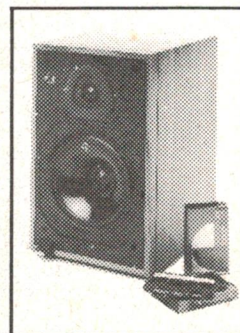

LIFESTYLE NEWS

New Audiogramme loudspeakers

Latest in the range from Australian speaker maker, Audiogramme, is the 'Series Two' AG model lineup.

There are four models in the range, designated AG 25, AG 45, AG 65 and AG 85. The cabinet measures 790 x 330 x 330 mm.

The AG 25 is a compact two-way bass reflex system with a 215 mm bextrene cone bass-mid driver and a 25 mm soft-dome tweeter. Crossover is at 2.5 kHz and response is quoted as 50 Hz to 20 kHz. Impedance is 8 ohms and it measures 530 x 295 x 295 mm.

The AG 45 is a three-way bass reflex model measuring 700 x 295 x 295 mm. It uses the same bass-mid driver and tweeter as the AG 25 with the addition of a 19 mm soft mylar dome super tweeter. Crossovers are at 2.5 kHz and 10 kHz. Response is quoted as 45 Hz to 25 kHz and nett enclosure volume is 40 litres.

The AG 65 is an acoustic suspension type, unlike the rest. It is a three-way system employing the same drivers as the AG 45. Crossover frequencies are located at 2 kHz and 10 kHz. Response is quoted as 38 Hz to 25 kHz. Enclosure volume is

58 litres and impedance 6.5 ohms. The cabinet measures 790 x 330 x 330 mm.

'Flagship' of the range is the AG 85. This is a bass reflex enclosure measuring 760 x 355 x 355 mm employing a four-way system. Bass driver is a 265 mm bextrene cone unit, mid-range is a 60 mm soft polymer dome unit, while the tweeter and super tweeter are the same as employed in the other models. Crossover frequencies are located at 1.2 kHz, 3 kHz and 10 kHz. Response is given as 35 Hz to 25 kHz and the impedance as 8 ohms. This unit includes stands, whereas stands are optional on the others.

The speakers have input power ratings of 80 W, 100 W, 120 W and 150 W for the AG 25, AG 45, AG 65 and AG 85 respectively.

Further information from Audiogramme Loudspeakers, P.O. Box 24, Indooroopilly Qld 4068. (07) 369-9670.



Convoy get Systemdek

Just as we went to press, Convoy International were crossing their eyes and dotting the tees on an agreement to handle the Systemdek turntable in Australia.

Convoy will release the Systemdek II here this month. This unit features a 24-pole precision synchronous motor mounted on an anti-vibration assembly within the cylindrical housing that stands on three levelling legs.

The platter is belt driven and is quoted to start up in two seconds for audible stabilisation. Two speed operation requires manual change between 33 and 45 rpm.

The platter is a 1.73 kg 10 mm

thick glass slab and the record mat is made of high density lambs wool. Wow and flutter is quoted as 0.09% DIN (peak, weighted), rumble as 78/77 dB (DIN B weighted) and hum as -72 dB (DIN B weighted).

It is expected to sell here for \$399. A spirit level for setting it up can be obtained for \$3.99 too. Details from Convoy International, 4 Dowling St, Woolloomooloo NSW 2011. (02) 358-2088.

When the sound has to be right, trust Shure



When sound is your business you can't afford equipment that's second best. When it comes to microphones there's one name you know you can trust - Shure.

We are in the business of setting standards. Our new SM85 sets new standards for hand held microphones. While it is a condenser microphone of studio quality, the SM85's tough, lightweight case and capsule cushion make it ready for the roughest use. And distortion figures are superior to some very expensive 'studio only' condenser mikes. Contact Audio Engineers for expert advice on the microphones you know you can trust.

Audio Engineers P/L

342 Kent St., Sydney Phone (02)29 6731
Victoria (03)44 3295 Queensland
(07)369 9670 W.A. Athol M Hill (09)325 7811



SHURE

LIFESTYLE NEWS

Mini stereo

Sanyo's M-G10 is a rugged and light portable cassette player with positive, simple controls.

Weighing only 310 gms and 3.2 cm thick, M-G10 comes complete with a shoulder strap and carry case. A set of comfortable, foam-cushioned headphones lets you listen anywhere.

Tape heads are designed to give excellent stereo performance from all tapes, including metal. The unit has locking controls for fast-wind of the tape in either forward or reverse, and the automatic stop mechanism disengages the tape at the end of play.

Sanyo's M-G10 operates on three 'AA' size batteries or ac power with an optional adaptor. Suggested retail price is \$78.



For further information, contact Mr. W. Fabiszewski, Sanyo Australia Pty Ltd, 225 Miller Street, North Sydney NSW 2060. (02)436-1122.

'Off the rack' stereo

Within a year or so we could be buying our hi-fi components off a rack packaged in a plastic bubble card.

The concept might appear ridiculous now, but after seeing what Technics has in store for us this coming year that possibility is not so ridiculous.

Technics plan to release a new midi hi-fi system this month in which all the components simply plug into each other. It does away with the need for RCA leads and a rat's nest of wiring in the rear of the components.

You simply buy an amplifier, then a tuner and plug the tuner into the top of the amplifier, each having specially located connection sockets.

The cassette deck, and any other hi-fi component like an equaliser, plugs in the same way. It takes all the hassle out of installation.

In the initial release the components will all still carry their own power transformers and power cords and so will still need to have a Kambrook type power board.

But the next step could be to do away with the transformers in all the add-on components. One would need only a power transformer in the amplifier. The power supply for

components would then be taken from the amp via the interconnecting 'bus' sockets.

This would make them very light, much cheaper to produce, and could eventually lead to a self service supermarket type shop.

You simply select your hi-fi system in components and then plug one into the other for both power and audio. No wiring and no fuss installation.

The Technics 'midi system' is expected to sell under \$1000 and is being described by Technics as "personal audio" because it will appeal mostly to teenagers looking for a sound system for the bedroom, or a young couple wanting a sound system for a flat in which space is at a premium.

The systems will have a minimum of 25 watts although consumers will eventually be able to select different amplifiers with different power performance.

Technics expect this personal audio to take around 30 per cent of the audio market quite quickly.

New Mordaunt-Short speakers

Further to the successful launch of the Mordaunt-Short Series 3 loudspeakers, Concept Audio, their Australian importer and distributor, has announced a new addition to the range.

This is to be known as the Ms-20 and will comprise identical components to the Carnival Series 3. However it will be housed in a conventional wooden box and finished in a black stain.

This new two-way loudspeaker system will have a recommended retail price of \$398. Enquiries to Concept Audio, 22 Wattle Rd, Brookvale NSW 2100. (02)938-3700.


Complete Disco System



for only \$2950

including

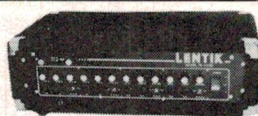- LENTIK PDM 1000 MIXER
- TWO TECHNICS SLB 202 TURNTABLES
- LENTIK 150W RMS POWER AMP
- TWO LENTIK 112 HT 3 WAY ENCLOSURES (rated at 150W RMS EA.)
- MICROPHONE HEADPHONES AND ALL NECESSARY LEADS
- MUSICOLOR IV
- FOUR PAR 38 LIGHT BOXES (four globes in box)
- ONE YEAR PARTS AND LABOUR WARRANTY



LENTIK PA 4200

- 150W RMS
- 4 CHANNEL
- BUILT IN REVERB
- BASS AND TREBLE CONTROL ON EACH CHANNEL
- MASTER VOLUME AND MASTER REVERB

\$565

Without carpeted box

\$515



LENTIK SLAVE AMPS

- 75W MONO \$299
- 75 + 75 STEREO \$390
- 150W MONO \$350
- 150 + 150W STEREO \$495
- 350W MONO \$450

MANUFACTURED IN QUEENSLAND BY:

UNITED SOUND SYSTEMS

Corner Ann and Warner Streets, Fortitude Valley 4006. Phone 52 2899, 52 7538
SERVING QUEENSLAND AND NORTHERN NEW SOUTH WALES

UNITED SOUND SYSTEMS QLD. AGENT FOR ETONE

Models available ex stock

611 12"	300 mm	30W RMS	\$34.90
616 12"	300 mm	Twin Cone	\$42.60
511 12"	300 mm	40W RMS	\$45.10
516 12"	300 mm	Twin Cone	\$60.20
231 12"	300 mm	60W RMS	\$66.20
236 12"	300 mm	Twin Cone	\$79.20
241 12"	300 mm	80W RMS	\$82.95
246 12"	300 mm	Twin Cone	\$88.20
451 12"	380 mm	100W RMS	\$140.50
484 12"	380 mm	200W RMS	\$220.40
801 15"	380 mm	200W RMS	\$242.20
805 15"	380 mm	250W RMS	\$247.30



BACKGROUND MUSIC TOO EXPENSIVE
NOT WITH A LENTIK AM/FM AUTO REV

CASSETTE RADIO

- AM/FM Radio
- Auto Reverse
- Cassette Deck
- Built in 20 watt Amplifier
- line out socket

Only requires speakers

\$399

All prices include freight to Qld. Coastal Cities.
Trade inquiries welcomed.

The range of Hi-Fi equipment you thought was beyond your means is now within your grasp.

RECEIVERS

SEPARATE AMPS

CASSETTE DECKS

The Yamaha separate amplifier series is designed specifically for the truly sound-conscious audiophile who will accept nothing but the ultimate in reproduction purity and accuracy. Yamaha separate amps also offer a wide range of features, permitting you to tailor your system to your own requirements.

Cassette decks employ an original "low-impedance" head design. The special head windings are used, as compared to conventional windings, to give the deck a more rapid response to transients, especially in the bass range.

INTEGRATED AMPS
TUNERS
CASSETTE DECKS
TURNTABLES
RECEIVERS
SEPARATE AMPS
SPEAKERS
CARTRIDGES
HEADPHONES
SYSTEM COMPONENTS

A Hundred Years of Musical Experience

YAMAHA HI-FI



Please send me the latest
Yamaha Hi-Fi catalogue.

Name _____

Address _____

Postcode _____




Yamaha Hi-Fi Division, Rose Music Pty. Ltd.,
17-33 Market St., South Melbourne, Victoria. 3205.

MCR/RM 3861 E

It's at home



C3

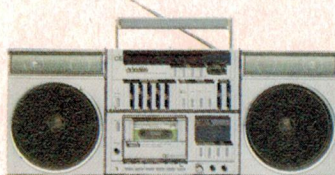

C5



C7



C9


Up till now, about the only place you could hear great sound outdoors was at a rock concert.

SANYO
That's Life!


But now Sanyo has answered that problem beautifully, with a new range of portable Stereo Radio/Cassette Recorders, with detachable speakers. The quality of sound is, in a word, amazing.

So now, enjoying great sounds in the great outdoors, or anywhere else for that matter, is as easy as picking up one of these new Sanyos.

anywhere.

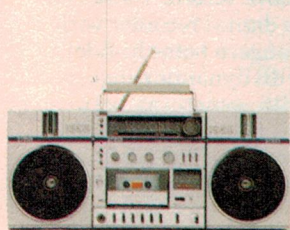

PH420K

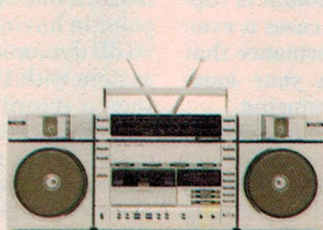

PH460K



PH480K



PH492K

In addition, Sanyo are now distributors in Australia for Fisher Equipment, and we are pleased to announce their new range of portable Stereo Radio/Cassette Recorders, with detachable speakers.


Obviously, there's not enough room here to go into details, so we'd like to suggest you see your nearest Fisher retailer.

As they say, hearing is believing.
But, that's life.



FISHER

Distributed by Sanyo Australia Pty Ltd

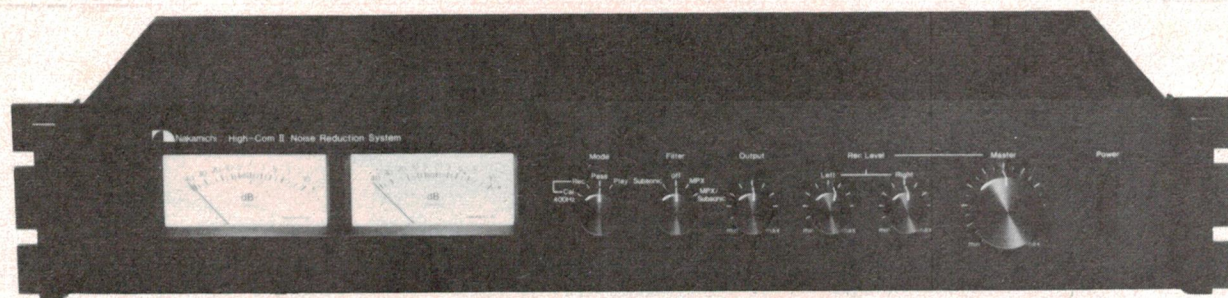

Nakamichi High-Com II noise reduction system

Is this the noise reduction system '... for all seasons? Very probably, for, apart from providing 20 dB of noise reduction and improved dynamic range for tape recorders of all sorts, the High-Com II can probably achieve adequate decoding for CX-encoded discs!

Louis Challis

IN THE LAST three weeks I have reviewed a number of excellent original half-speed mastered recordings from Mobile Fidelity in the States. Two of the most exciting of these are Earl Klugh's 'Finger Paintings' (MFSL1-025) and Respighi's 'The Festeromane — The Pines of Rome', starring the Cleveland Orchestra and Lorin Maazel (MSSL1-507). These records are typical of the latest generation of half-speed mastered microgroove records with imported pressings and superlative plating being produced in Germany, America and Japan. The real advantage of these records is not just the loving care and attention given to the original musical production, but more importantly the technological loving care given to their mastering, and most particularly to their pressing.

With all this attention, the maximum dynamic range that can currently be achieved on a conventional microgroove record, even with half-speed mastering recording in the studio and lots and lots of good luck, is about 65-68 dB. Obviously, with digital recorders capable of producing 96 dB of dynamic range, this falls somewhat short of the

NAKAMICHI HIGH-COM II NOISE REDUCTION SYSTEM

Dimensions: 482 mm wide x 82 mm high x 270 mm deep
Weight: 5 kg
Manufactured: by Nakamichi Corporation, Tokyo, Japan
Price: \$400
Distributor:

real dynamics that the medium is capable of producing. In most cases it even falls short of the best performance that your amplifier, and even your loudspeakers, are capable of producing.

Early in the 1970s or thereabouts, a little known band of entrepreneurs in America, under the banner of Sheffield Laboratories, commenced recording and marketing direct-on-disk records whose technical excellence and music quality were just the sort of thing people like you and I were looking for to show off the *real* capabilities of our high fidelity systems. Obviously, direct-on-disk is very nice, but it is also very difficult to execute, relatively expensive and unusually complex for the musicians, who found, like Dame Nellie Melba back in the years of the pre-electronic recording, that if you were

wrong, you were wrong, and had to start recording again from scratch.


The development of digital recording has not really solved those problems, it has only exacerbated the difference between the best that the laboratory and studio technology can produce, compared with the modest yet reasonable dynamic range capabilities of the modern microgroove record. There is no point in having a digital recorder with a 96 dB dynamic range, a home hi-fidelity system with 100 dB dynamic range, and then a record with something between 50 and 68 dB of dynamic range, depending on which record you happen to buy, how clean it happens to be and a variety of equally significant other little factors which add up to a big difference in total performance.

Noise reduction systems

We have previously written about the Dolby A, B and the new Dolby C noise reduction systems, and also dbx, which have all played exciting and important roles in the development of tape recorders with superior signal-to-noise performance.


That's all very nice, of course, but by and large, with the exception of direct-on-disk and the best of the digitally encoded recordings, nobody has done very much about the microgroove recordings. (The possible exceptions, of course, are dbx with their specially encoded records, and AEG Telefunken of West Germany and Nakamichi, who together developed the High-Com system based on the Telcom C4D system).

The C4D system was developed for broadcast stations and recording studios, and was intended to provide the best features of dbx and, I suspect, some of the best features of the Dolby system as well. The High-Com system was developed some three or four years ago and the High-Com II is a more recent development which reached the Australian market in 1981. Surprisingly, more recently another equally important noise reduction system specifically developed for records has been released in America and is being pushed very solidly under the banner of the CX format. When I looked more closely at the CX concept and the High-Com II concept, I was amazed at the similarity of their encode/decode or compress/expand characteristics. These are both essentially based on the use of a 2:1 expansion and 1:2 compression ratio for signals normally falling within the -20 dB to +10 dB range.

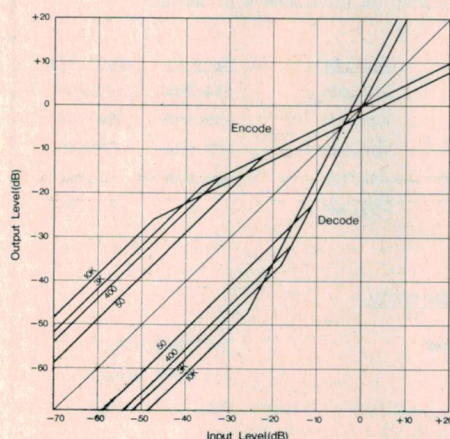

Encoding-decoding characteristics of the Nakamichi High-Com II system. (From Nakamichi information brochure.)

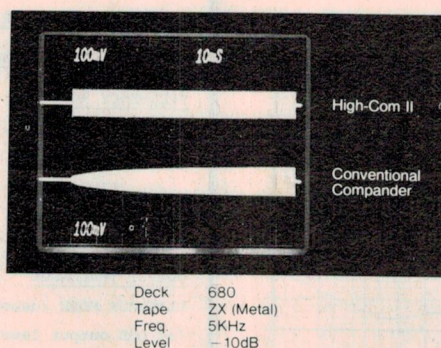The significant difference really between the High-Com II and the CX compression/expansion system is that the High-Com divides the audible spectrum up into two bands, with different threshold points for changing encoded to normal amplification threshold. Thus signals above 10 kHz



Transient response of the Nakamichi High-Com II compared to a conventional compander. (From Nakamichi information brochure.)

have a 0.5 compression ratio which starts at -25 dB, the signals between 10 kHz and 3 kHz start at -18 dB, the signals down to 400 Hz start at -16 dB, whilst signals below 50 Hz start at -12 dB. This selective compression and expansion threshold point is designed to make best use of the dynamic range excursion characteristics, which can conveniently be encoded on either a tape recorder or on a conventional microgroove record. The major attribute claimed for the system is that it provides a genuine 20 dB improvement in signal-to-noise ratio, compared with either tape format or normal microgroove record format. More importantly, there is little penalty in terms of loss of compatibility with normal format, and the signal-to-noise improvement extends for the full frequency range of the recorded material, unlike with Dolby B or Dolby C. One could argue that this is a variation on the basic theme of the dbx system, but as it takes place over a somewhat more limited range, it maintains a basic similarity and compatibility with both tape recorder and conventional record formats.

Design and appearance

The High-Com II typifies the Nakamichi concept of design and appearance. The unit is really primarily intended for rack mounting as a sub-element associated with a tape recorder/amplifier system and, as Nakamichi will tell you, preferably with a Nakamichi cassette recorder. However, don't be misled; it can work with anybody's brand of recorder and with any type of tape recorder, i.e. reel-to-reel, compact cassette, micro-cassette or cartridge.

The front panel is finished in black with white engraving. On the left hand side are two VU meters, each reading

from +10 to -40 VU and featuring rear illumination. In the centre of the front panel is a mode switch with four settings: 'record', which is the position used for encoding; 'pass', which allows signals to pass through the unit without encoding or decoding; 'playback', which is the decode mode for tape recorders; and 'disk', which is the decode mode for playback from a High-Com-encoded disk (or, as it transpires, is also most probably equally suitable for a CX-encoded disk).





Adjacent to the mode switch is the filter tone switch, which also has four positions, respectively: 'subsonic', which provides -10 dB of attenuation at 20 Hz and -40 dB of attenuation at 11 Hz; 'off'; a 'multiplex' position, which provides 35 dB of attenuation at 19 kHz; and a '400 test tone' position for provision of the internal level calibration and system alignment signal for use with either tape recorder or record player.

On the right hand side of the deck are two recording level controls for setting the record level and calibration level for left and right channels of tape recorders or High-Com or CX-encoded disks.

On the extreme right hand side of the front panel is a master volume control, which provides similar functions to the two adjacent recording level controls but within one single potentiometer. Adjacent to it is an illuminated power on/off switch.

The rear panel contains four sets of coaxial line sockets, with four pairs of sockets for line in and line out and four pairs for connecting to a recorder. Adjacent to each of the recorder in and out sockets is a rotary calibration control for setting the correct operating point for the record and/or playback decode modes when using the internal calibration signal. All that is required to operate the system correctly is to patch it up with four pairs of coaxial leads to your amplifier, or amplifier and tape recorder, to achieve the full capabilities of its encode and decode capability.

The inside of the unit features four large-scale socket-mounted 24-pin integrated circuits, twelve 8-pin integrated circuits and eleven transistors. These are mounted on one medium-sized printed circuit board, which encompasses approximately two-thirds of the chassis area. Only the transformer, the two VU meters and a few other components at the rear panel and on the front panel are separately wired through to the board. In typical

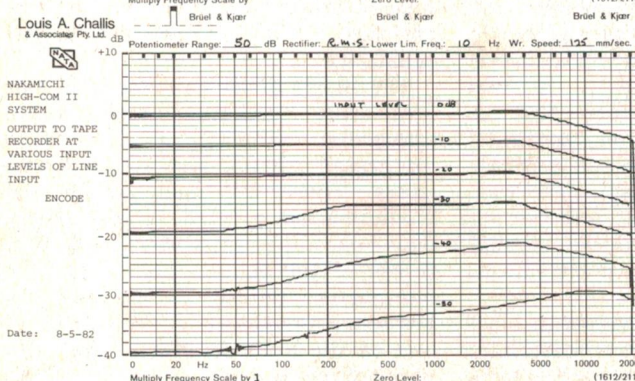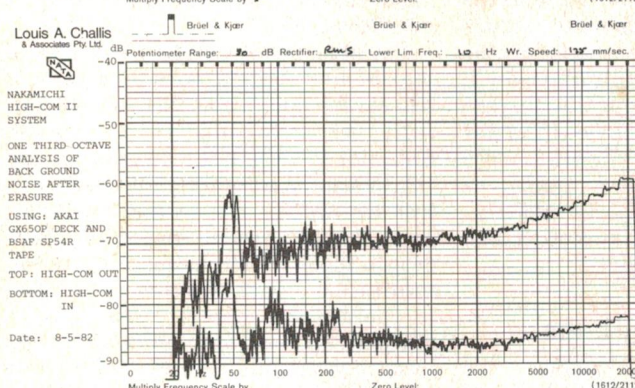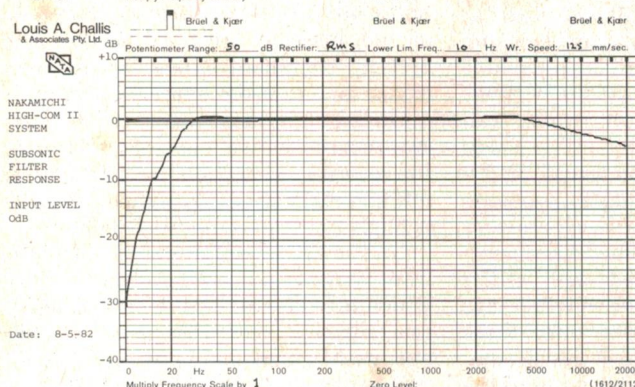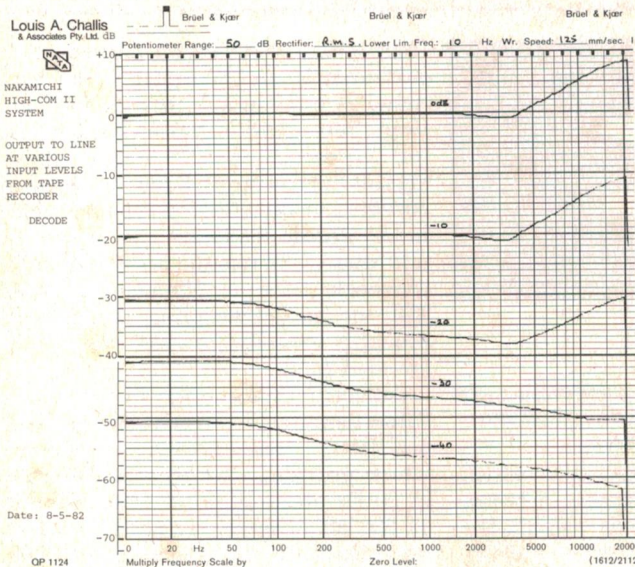

MEASURED PERFORMANCE OF NAKAMICHI HIGH-COM II SYSTEM

SERIAL NO. 03142

FREQUENCY RESPONSE

20-20000Hz ± 1 dB

INPUT IMPEDANCE

LINE

LEFT RIGHT

32k ohms

33k ohms

PLAYBACK

33k ohms

33k ohms

OUTPUT IMPEDANCE

LEFT

RIGHT

PLAYBACK MODE (decode)

(at 0dB output level)

	63Hz	1kHz	6.3kHz	10kHz
2nd	-54.0	-56.2	-54.1	-53.8 dB
3rd	-64.4	-65.7	-63.5	- dB
4th	-70.9	-85.7	-75.6	- dB
5th	-80.2	-80.6	-	- dB
THD	0.21	0.16	0.21	0.20 %

(at +6dB output level)

	63Hz	1kHz	6.3kHz	10kHz
2nd	-52.8	-54.0	-57.6	-51.0 dB
3rd	-58.7	-60.4	-58.4	- dB
4th	-66.2	-82.5	-76.4	- dB
5th	-78.1	-77.9	-	- dB
THD	0.26	0.22	0.29	0.28%

INTERMODULATION DISTORTION

$f_1 = 330\text{Hz}$ and $f_2 = \text{kHz}$ mixed 4:1

DISTORTION component near 8kHz

COMBINED LEVEL AS INDICATED ON HIGH-COMM V.U. METRE.

LEVEL	$f_2 = 2f_1$	$f_2 - f_1$	$f_2 + f_1$	$f_2 + 2f_1$
+5dB	-49.3dB	-47.4dB	-54.5dB	-48.7dB
+3dB	-51.5dB	-48.3dB	-55.8dB	-50.5dB
0dB	-56.1dB	-50.6dB	-58.8dB	-55.5dB
-5.0dB	-62.9dB	-53.1dB	-64.1dB	-61.7dB
-10 dB	-65.0dB	-55.7dB	-	-67.2dB

COMPRESSION / EXPANSION RATIO

COMPRESSION

1:2 (see graphs)

EXPANSION

2:1 (see graphs)

SIGNAL TO NOISE IMPROVEMENT (see curves)

AKAI	GX650P deck	17dB (Lin)	19dB (A)
SONY	TC-FX6C	18dB (Lin)	20dB (A)

Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.

Nakamichi thoroughness the printed circuit layout from the underside of the card is clearly printed on the front, as are all the component designations to simplify troubleshooting if and when servicing has to be performed.

Two things are clear: firstly that the special integrated circuits providing the High-Com function have been specially fabricated for this particular module, and secondly that the extent of the circuitry involved in the High-Com II system is more complex and more demanding in terms of its overall performance capabilities than the comparable CX circuit encoder/decoders (which are single-band rather than two-band devices). The main features the High-Com system offers are the two-band frequency selective encoding/decoding, and the ability to reduce the low frequency modulation of high frequency components during transients which are part of normal programme content. This is obviously more critical when recording onto cassette decks, where high frequency pre-emphasis and hiss problems are far more important than they are in the case of a record.

One obvious question that could be asked is, "To what extent is the High-Com system more useful than Dolby B or Dolby C?" In the case of Dolby B this is very easy to answer, as the High-Com circuit is capable of producing at least 12 dB more effective signal-to-noise ratio than is achievable on a Dolby B recorder. If one takes into account the greater headroom and top-end dynamic range of the High-Com system, then this figure can be increased to almost 18 dB.

On test

The objective testing of the High-Com II system was straightforward. The first set of results we produced was a set of level recordings showing the record mode or what might otherwise be called the encoding process for the High-Com. These show clearly how the primary compression in the mid-band region extends from typically 10 Hz through to 4 kHz, above which point a gliding increasing level of de-emphasis takes place to further reduce the amount of high frequency signal on the tape. In the range 30 dB to 40 dB a modified low frequency de-emphasis is introduced, so that the likelihood of low frequency modulation interacting with mid-frequency components above 100 Hz is reduced.

It is in this region that the 'anti-

pumping' capabilities are provided, which are the means by which the tonal and frequency level balance for both singing and music is maintained.

The non-linearity of the curves is matched by a directly comparable inverse function in the playback or decode mode, which is shown on the expanded-range level recordings. The degree of expansion over the range -30 dB to 0 dB, together with the high frequency pre-emphasis, becomes quite pronounced for signals above 20-25 dB, whilst a consequent de-emphasis takes place for signals in the -30 dB range down to the lower-level signals.

Tape hiss (as well as record surface noise) is dramatically reduced, so that overall dynamic range is increased by more than 20 dB. To prove this more effectively, I decided to use a conventional reel-to-reel recorder in the form of an Akai GX650D, which is not equipped with any internal noise reduction system. I would have preferred to be able to record from input to output and output back to input on the High-Com system, but without a second unit this is not feasible. I found that the dynamic range for the A-weighted signal-to-noise ratio relative to 0 VU was expanded from a normal 55 dB up to a very much more desirable 74 dB, whilst the true total dynamic range was expanded to 85 dB relative to the 3% third harmonic distortion. An 85 dB dynamic range is not to be scoffed at, and I was very impressed.

I repeated this exercise on a Sony TCFX6C and was even more surprised to find that the enhancement took the form of an effective reduction in the level of mains frequency signal, so that the unweighted noise level improvement relative to 0 VU was 18 dB and the A-weighted improvement 20 dB.

An equally important factor that required assessment was of course what the distortion characteristics would be during either decode or playback mode at say, 0 dB or +6 dB relative to normal output. I was pleased to find that the highest level of distortion measured at 0 dB was 0.21%, whilst at +6 dB it was still only 0.29%. These are excellent figures, so my next concern was whether a similar performance would be achieved for intermodulation distortion, which in a device of this type, with so many changes or non-linearities of frequency response, might well prove to be troublesome. This test was performed at levels of +5, +3, 0, -5 and -10 dB. The highest level of an intermodulation distortion product that I could measure

was -47.4 dB at the f_2-f_1 frequency at +5 dB, and -55.7 dB at -10 dB. Over the range +5 to -10 VU there was a slow but small improvement in intermodulation distortion, but the level of the intermodulation distortion products was nonetheless excellent and generally less than 0.4%, becoming almost immeasurable at most of the intermodulation frequencies below -10 VU.

All the other parameters proved to be within the manufacturer's specification and therefore no cause for concern.

Subjectively

The acid test of any system in the end is the listening test. I continued the testing of the High-Com system with a series of cassette recorders, tape recorders and most particularly with the Nakamichi demonstration test record. This is pre-encoded with the High-Com II record characteristics, so that on playback a dynamic range in excess of 86 dB is theoretically possible. The demonstration record has been made in America, not Japan, and the choice of music is excellent. I spent more than an hour of rapturous listening and re-listening to the record to convince myself that I was listening to a record and not to a digital tape. That record convinced me that the High-Com II system really does work, does almost everything claimed for it, and that in most respects offers an unquestionably superior performance (at a significant price penalty) when compared with Dolby B, Dolby C and even the best of the dbx systems.

This system, of course, is designed to be used principally with tape format, whilst the CX system that CBS has just started marketing is designed to be used only with records.

Summary

The High-Com II system really works. It does its job better than I would have expected, the only disadvantage being that we have another noise reduction format to add to five existing formats, with a sixth, the CX system, soon to be added. The one grace-saving feature here is that I suspect the High-Com system will be almost fully compatible with the CBS CX system, and if this proves to be so, then by purchasing this unit you may well save yourself the cost of a CX decoder, whilst at the same time being able to produce your own High-Com-encoded tapes. ●

MINI-MART

Where readers can advertise — For Sale/Wanted/Swap/Join.

● We'll publish up to 24 words (maximum) totally free of charge for you, your club or your association. Copy must be with us by the 1st of the month preceding the month of issue. Please — please — print or type adverts clearly, otherwise it may not turn out as you intended! Every effort will be made to publish all adverts received; however, no responsibility for so doing is accepted or implied. Private adverts only will be accepted. We reserve the right to refuse adverts considered unsuitable.

● **Conditions:** Name and address plus phone number (if required) must be included within the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Adverts must relate to electronics, audio, communications, computing etc — general adverts cannot be accepted. Send your advert to:

ETI Mini-Mart,
4th Floor, 15 Boundary St,
Rushcutters Bay NSW 2011.

AUDIO

AMPLIFIER — Davred 8+8 with Rank-Arena speakers. Cost \$140, sell \$70. Auto turntables, without base, suits amp — \$20. (02)419-2568 after 7 pm.

AUDIO SPECTRUM ANALYSER — stereo, 20 Hz to 20 kHz. Merguro-Mat 140. Ideal testing amplifiers, mics, tape decks etc. Mint condition, \$990 ono. (02)46-5451.

SPEAKERS — ABC monitors used by ABC recording studios, large 15" woofers, midrange and tweeters. New speakers in each. Superb sound, \$550 ono. (02)46-5451.

REALISTIC TM102 stereo tuner with outdoor antenna. Both only 5 mths old. Together cost over \$120, sacrifice both for \$60. (08)251-1649.

DBX 117 dynamic range expander, \$150. Glenn Stewart (02)387-3801 or write 7/290 Birrell St, Bondi NSW 2026.

TUBE AMPLIFIERS: Quad 22 pre-power amp, Leak 60 pre-power amp. Spare Mullard tubes, mint condition, from \$150. (02)46-5451.

SPEAKERS: Richard Allen 15-inch woofers in large four-way cabinets. Superb sound. \$400 ono. (02)46-5451.

MISCELLANEOUS

ELECTRONIC 12-tune doorbells, fully built and tested, total of 75. Would sell for \$34.95 ea, the lot only \$900. Phone Bert, ah, (03)758-4086.

MATERIAL TO MANUFACTURE 500 'TK 101' electronic ignition units. 2000 24 x 18 glossy posters. If you have the knowledge and time you can gross \$30 000. I will sacrifice for \$3000. Phone Bert, ah, (03)758-4086.

FOR SALE: TV test gear. 1: All functions, Unaohm, type EP685 pattern generator. 2: B&K 467 CRT restorer/analyser. \$750. Carl, (066)55-6632.

CRT WANTED: Any model. Write to P. Dickson, 7 Wendover Walk, Glengowrie SA 5044. Include model and price.

FOR SALE: Electronic data manuals and reference books at fraction of original cost. (02)20545 ext. 340 (bh.)

OSI 32K RAM board + 40 pin connector, \$320. AM/FM cassette radio, \$20. Cassette recorder, \$10. Software, etc. Send SAE for list. J. Burns, 6 Banksia St, Townsville Qld. 4814. (077)73-1896.

FOR SALE: Printed circuit board Circuitape system autops etching tank processing unit, incl. exposure unit and gold plating gear, plus chemicals. \$300 ono. (02)666-7969.

STORAGE OSCILLOSCOPE, BWD 845, dc — 30 MHz, dual trace, dual timebase with delay, auto storage x-y, alt, chop, add. Tube OK. Probes and manual. \$1700. S. Leonard, (03)419-5111 bh.

CRT — B/W, 53 cm, from AWA K130 chassis. Deflection coils included. May not work. \$20. Phone Michael (Jnr), (03)481-6062 a.h.

SORCERER Mk1, 32K c/w monitor, \$800. Sony TC-755 tape deck with 10½" reels, \$400. Sansui AU-555A amplifier, \$50. (004)25-2324.

WANTED: two copies "Acoustics" by L.L. Beranek, Pub: McGraw Hill. J. Verrenkamp, 4 Commercial Rd, Highett Vic. 3190. (03)555-4766 b.h.

COMMUNICATIONS

WANTED — TELEPRINTER. Teletype Model 15 or Siemens Model 100. Details to Frank Rees, 27 King St, Boort Vic. 3537.

PARABOLIC DISH antenna, 4 metre diameter. Easily transported sections. With stand. Rigid construction, \$1500 ono. David (03)481-4237.

COMPUTERS

SELL: ZX80, 8K ROM, 16K RAM, power supply, manuals, etc, and software. Ex. cond, \$400 inc post. A. Birbara, 10 Wade Ave, Leeton NSW 2075. (069)53-3240.

HUNTER USERS' GROUP: All microcomputers. Meets on the second Wednesday of every month, Room 308, Building W, Newcastle University, 7.45 pm. Members are mainly hobbyists with Apples, etc. Interested persons contact the Secretary, P.O. Box 39, Broadmeadow NSW 2298.

ZX81 WITH 16K RAM pack, never used, \$295. N.R. Chambers, 36 Teneriffe Drive, Brisbane Qld. 4005. (07)358-4258.

FOR SALE: SPACER, a self relocating m/i utility which adds spaces to a BASIC listing, making it easy to read & debug, plus COMPRESS, which removes spaces. \$13.50 (TRS80 L2 or DISC). Dennis Bareis, 286 Lennox St, Maryborough Qld. 4650.

SALE: ETI/DG640 VDU (4 MHz), \$100. ETI-685 S100 2650 (½ MHz with 4K RAM, monitor and software), \$180. Both cards, \$250 (worth over \$400). K. Walsh, (02)642-6339 after 4 pm.

SELL: HP 41-CV. The ultimate in alphanumeric programmable calculators. As new, complete with manuals, etc, \$370. Peter Cooper, 7 Olinda Rd, Windsor Gardens SA 5087. (08)261-5586.

FOR SALE: PET Commodore, 32K with cassette unit, tractor feed printer, ample software and full documentation. Excellent condition, \$1500. (02)872-3221.

SHARP PC1211 pocket computer plus cassette interface and 150 program applications manual, \$200 ono. Phil Mawson, 75 Green Pt Rd, Oyster Bay NSW. (02)528-5572.

FOR SALE: TRS-80 computer, level 2, 16K, green screen, monitor, plus software and books. Best reasonable offer. Ring Darrin, (02)969-3850, after 4 pm.

QUEENSLAND SUPER 80 USERS GROUP, contact Garry Gattfield, 165 Frasers Road, Mitchelton, for membership enquiries (regular monthly meeting and newsletter).

TELETYPE 38 15" tractor/friction feed, ASCII encoded, serial I/O plus 110 pulse gen plus neg. volt supply plus paper (box). \$500 ono. (062)-81-6107.

SELL: Sharp PC-1211 with cassette interface. \$180. System-80 with Syspand-80. \$745. Maclean, Formartin State School, Bowenville Qld. 4404. (076)92-4231 ah.

WANTED: Group of computer enthusiasts need low-cost hardware/software for club activities, will consider all offers. Sinclair Sydney Radio Computer Club, P.O. Box 323, Coogee NSW 2034.

SELL: Semcon 32K static RAM card, as new, Motorola Exorciser buss, IC sockets throughout, suit 6800 D2 kit upgrade. \$400 ono. Phone (03)818-7898 ah.

APPLE II unlimited vocab. speech synth. Plugs into peripheral slot. Complete with speaker and instructions. \$150 ono. (060)24-4540.

\$100 CARDS — DGZ80 CPU (with PIC), \$100; DGZ80 BASIC assembler tape, \$20; DG640 VDU, \$45; TCT 16K RAM, \$110; four LOGOS 8K RAM, \$50 each; two 32K ROM (2708/2726), \$50 each. (03)543-5451 a.h.

OSI CHALLENGER 1P in good cond. with 8K RAM, RS232 interface, software accessories and plenty of advice. \$460 neg. Paul Webster. (02)663-4932.

ZX80 plus 16K RAM, improved full size keyboard plus case and books, programs. Over \$450-worth. Sell \$360. (03)489-5863 after 6 pm.

OSI C1PMF 32K and disk, only \$1395. Single-key disk BASIC/assembler/editor and extended monitor. 9600 baud printer port. With disks and TV monitor. David (062)318-864.

TRS80 Model 1 level 2 16K permanent lower case, stabilised inverse video, huge amount of software, magazines. \$690. (047)36-4136 a.h.

SWTP 6800 computer, dual serial and parallel ports, operating manual, tape and disk software, \$500. PR40 printer, \$85. Disk driver 5" and 8", \$145. (051)56-8291.

FOR SALE: Microace 4K ROM, 16K RAM plus leads, power supply and book of programs, \$250. Phone (02)639-3115 a.h.

TANDY MODEL 1, 48K, expansion interface, three disk drives, Centronics printer with CP/M, sell \$2500 ono. (02)428-5866.

PRINTER: Dick Smith GP-80. Cost \$495, sell \$350. (02)419-2568; after 7 p.m.



Electronics Today International is published by Murray Publishers Pty Ltd, 15 Boundary St, Rushcutters Bay NSW 2011. It is printed (in 1982) by Offset Alpine, cnr. Wetherill and Derby Sts, Silverwater NSW, and distributed by Network Distribution Company, a division of Australian Consolidated Press Ltd, incorporated in NSW.

Editor

Roger Harrison VK2ZTB

Technical Editor

David Tilbrook VK2YMI

Assistant Editor

Jennifer Whyte B. App. Sc.

Advertising Production

John Gerrie

Editorial Staff

J.B. Scott B.Sc./B.E. (Hons)

VK2YBN

Jan Vernon B.A.

David Currie

Geoff Nicholls B.Sc./B.E.

Layout

Bill Crump

Githa Pilbrow

Typesetting

Julie Hewlett

Reader Services

Paula Maloney

Managing Editor

Collyn Rivers

Acoustical Consultants

Louis Challis & Associates

Mail enquiries: There is no charge for replies, but a foolscap-sized, stamped, addressed envelope must be enclosed. Queries relating to projects can only be answered if related to the item as published. We cannot advise on modifications to projects, other than errata or addenda, nor if a project has been modified or if components are other than specified. We try to answer letters as soon as possible. Difficult questions may take time to answer.

Phone enquiries: We can only answer readers' technical enquiries by telephone after 4.30 pm. The number to ring is: **(02)33-5669**. In enquiring by telephone about back issues or photostats, please ring **(02)268-9015**.

Editorial and Sales Office:

4th Floor, 15 Boundary St, Rushcutters Bay NSW 2011. Ph: (02)268-9811; Tlx: 27243

Sales Manager: John Whalen
(address as above)

Melbourne: Virginia Salmon, 150 Lonsdale St, Melbourne Vic 3000. Ph: 662-1222; Tlx AA34340

Adelaide: Admedia Group, 24 Kensington Rd, Rose Park SA 5067. Ph: 332-8144; Tlx AA82182.

Brisbane: Geoff Horne Agencies, 16 Bellbowrie Centre, Bellbowrie Qld 4070. Ph: 202-6813.

Perth: C. Thomas, Adrep Advertising Representatives, 62 Wickham St, East Perth WA 6000.

New Zealand: Frank Hargreaves, Circulation Marketing Manager, c/- ACP, 4th Floor, Sun Alliance House, 42-44 Shortland St, Auckland. Ph: (9)30311.

United Kingdom: Australian Consolidated Press, Ludgate House, 107 Fleet St, London EC4A 2AL. Ph: 353-1040; Tlx: 267163.

Japan: Genzo Uchida, Bancho Media Services, 15 Sanyocho, Shinjuku-Ku, Tokyo 160. Ph: 359-8866; Cable: Elbanchorito; Tlx: BMSINC J25472 Tokyo.

USA: Australian Consolidated Press, 21 East 40th Street (Floor 23), New York NY 10016. Phone: (212) 685-9570.

The publisher accepts no responsibility for unsolicited manuscripts, illustrations or photographic material.

ORDER FORM

I enclose \$ for (tick appropriate box/es). All prices include postage.

Send orders to: ETI, 4th Floor, 15 Boundary St, Rushcutters Bay NSW 2011. Phone: (02)33-4282.

☐

Subscriptions

\$25.75 per year within Australia

\$

\$39.00 overseas (surface mail)

\$

Airmail rates on application

☐

Back issues

\$2.50, available from November 1978.

☐

or photocopies

\$2.50 per article per issue

Project No. Month Year \$

Project No. Month Year \$

Project No. Month Year \$

Project No. Month Year \$

Please attach a list if more than four required.

☐

Binders

No. @ \$6.10 in NSW

\$

No. @ \$7.50 in other states

\$

NAME (Please print)

ADDRESS

Please debit my ☐ Bankcard

☐ American Express card

Number:

Signature

DREGS


IT CAN BE AMUSING to ponder the 'what if's' of this life. Take for example, a situation involving the inventor of the principle behind our 'photophone' project this month (ETI-918, page 25). To save you whipping through the pages, I'll tell you who it was — none other than Alexander Graham Bell, better known for his invention of the telephone. And probably one of the most-cursed men in history, the telephone being both a beast and a blessing. Anyway, ponder a moment on this 'what if?'

If the Saxes (that Germanic race of people, also called Saxons, who once conquered Britain) ... yes, what if the Saxes had beaten Alexander Graham Bell to his invention? Would we all be using Saxephones instead of telephones?

Twisted that a bit, didn't I. Well, Bell gave his name to the unit of loudness — the Bel. The most convenient form we know as the decibel. Now, what if the Saxes ... etc? Would we be using decisaxes instead of decibels?

Let's try somebody else. Mr Heinrich Hertz for example. The man who proved Maxwell's electromagnetic theory was worth more than the paper it was printed on. He gave his name (... though posthumously) to the unit of frequency.

But what if a gentleman by the name of Pound had proved Maxwell's electromagnetic theory? Today we'd probably be talking about a hi-fi amp's frequency response extending from 20 Pounds to 20 kilopounds! Oh, Mother. That would have really stuffed the Metric Conversion Board (now defunct) right up! At least they didn't put Hertz's name to the unit of frequency so they would have, at least, had someone to blame.

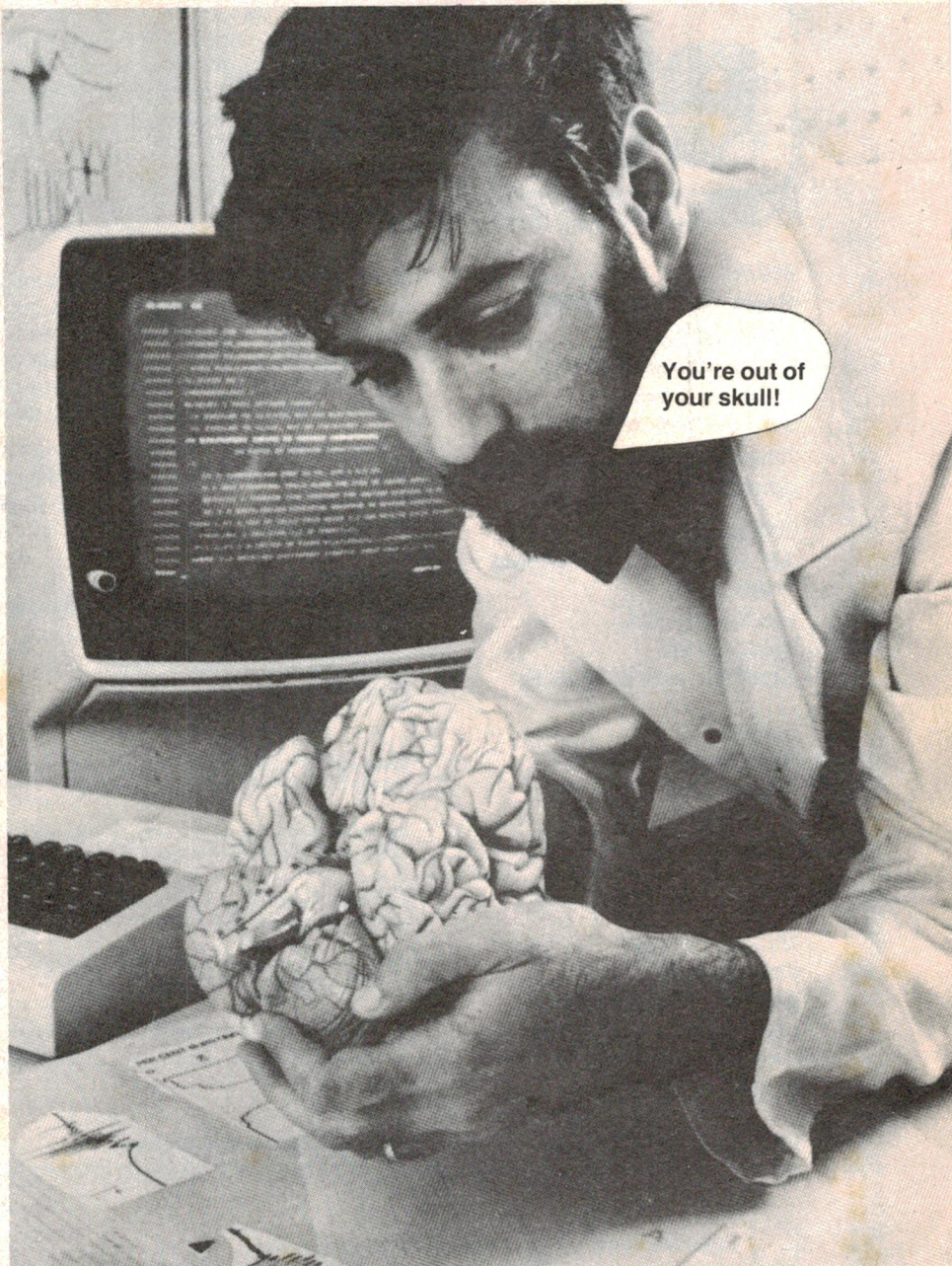

Consider Georg Ohm. Wonderful fellow. Persistent, he was, in experimenting with the electrical resistance of wires of differing composition under the most arduous of circumstances in his draughty lodgings. But what if his name was Throssell? How would you feel walking into the local electronics store and asking for "a 39 kilothrossell resistor, please"? It hardly bears thinking about. Except in Dregs, of course.

Take that famous team who invented

the transistor: Shockley, Bardeen and Brattain. No doubt many of you have had to regurgitate the names of that trio in an examination at some time or another. But, what if their names were Martin, Barton and Fargo? How would you cope with the all-too-common mental block in an examination when asked to name the team who invented the transistor and you could recall the first two names but only that the last started with F.?



What is your turntable's "warp factor"?

You may not realize it but every record has some degree of warp. And no matter how slight, it can give your turntable fits.

Warp, along with off-centring, were the reasons why Sony invented Biotracer.

The continuously correcting action of the electronic Biotracer tonearm perfectly suspends the stylus in the record grooves with no tension resulting from the forces of gravity or lateral pressure.

Biotracer is featured on Sony's PS-X600 and X500 with the advantages of stifling low frequency resonance, expanding dynamic range and maximizing performance from any cartridge you use. Biotracer also suppresses peak tonearm resonance electronically within a range of 3dB.

The sole object of its design was to neutralize the effects of record warp and off-centring through microcomputer precision. Which Sony does with aplomb.



PS-X600

SONY
THE ONE AND ONLY



Ken Middleton writes our accounting systems. He'll see you to tailor the right one for your business.

The biggest problem with most computer accounting packages is just that - they're packages. Designed to suit 'The Average Business'. Which probably isn't your business.

The MiniMicro Accounting Package is unique. It has all the power and features of other accounting packages, but without the restrictions. You don't have to fit your accounts into our system - we fit our system around you. So that you can get the information you need to keep your business running.

That's why Ken Middleton of MiniMicro Supermart, the man who designed the MiniMicro Accounting Package, is the man you'll deal with. Each installation is fully custom

written around the framework of a powerful, easy to use accounting system. And it's not like other 'custom' software that takes months to write and costs "about \$???". Full implementation of the MiniMicro Accounting Package takes two to three weeks and costs \$1500. That's it.

And because you're dealing with the man who'll write your package, there are no communications breakdowns. The MiniMicro Accounting Package is a completely menu driven General Ledger/Debtors system with provision for Creditors as part of the Chart of Accounts. It will run on most CP/M based microcomputers. A large range of suitable hardware is available from MiniMicro Supermart.

And good news for accountants. The MiniMicro Accounting Package is designed for easy implementation in an accountant's practice.

So if you need to computerise your accounting, but you're not impressed with the capabilities or price of systems you've seen, give us a call. Let Ken show you how the MiniMicro Accounting Package can help solve your accounting problems - instead of giving you new ones.

**MINIMICRO
SUPERMART**
Pty Limited

Showroom:
33-35 Atchison Street,
St Leonards NSW 2065
Phone: (02) 439 1628

Dealer enquiries to:
John F. Rose Computer Services Pty Ltd
33-35 Atchison Street, St Leonards, NSW 2065
Phone (02) 439 1220 Telex AA27901